

IMPORTANT: Besides your calculator and the sheets you use for calculations you are only allowed to have an A4 sized “copy sheet” during this exam. Notes, problems and alike are not permitted. Please submit your “copy sheet” along with your solutions. You may get your “copy sheet” back after your solutions have been graded. **Do not forget to write down units!**

## ELE222E INTRODUCTION TO ELECTRONICS (21618)

Midterm Exam #1 ✍ 21 March 2005 ⌚ 10.00-12.00

İnci ÇİLESİZ, PhD, Özgür ATEŞ, BSE


- What is a semi-conductor? What are similarities and differences between conductors and semi-conductors? Explain within a maximum of 4 to 5 sentences. (10 points)
- Assume you are to create a diode using n- and p-typed doped silicon with the following possible doping parameters:  $N_D : 10^{15} \text{ 1/cm}^3$ ,  $10^{17} \text{ 1/cm}^3$ , and  $N_A : 10^{16} \text{ 1/cm}^3$ ,  $10^{18} \text{ 1/cm}^3$ . Study the four possible pn junction combinations, find barrier voltages and saturation currents for let's say a junction area of  $1 \text{ mm}^2$ .

- Which unbiased pn junction ( $N_D = ?$ ,  $N_A = ?$ ) has the lowest barrier potential? Why? (10 points)
- Which unbiased pn junction ( $N_D = ?$ ,  $N_A = ?$ ) has the smallest saturation current? Why? (10 points)
- Which unbiased pn junction ( $N_D = ?$ ,  $N_A = ?$ ) has the largest depletion capacitance? Why? (10 points)

NOTE:  $L_n = 10 \text{ }\mu\text{m}$ ,  $L_p = 5 \text{ }\mu\text{m}$ ,  
 $\mu_n = 1350 \text{ cm}^2/\text{Vs}$ ,  $\mu_p = 480 \text{ cm}^2/\text{Vs}$ .  
 $n_i = 1.5 \cdot 10^{10} \text{ 1/cm}^3$ ,  
 $q = 1.602 \cdot 10^{-19} \text{ C}$ ,  $\epsilon_r = 12$ ,  
 $\epsilon_o = 8.85 \cdot 10^{-12} \text{ F/m}$ ,  $V_T = 25 \text{ mV}$ .

- Study the 3-stage amplifier circuit on the right at DC. For  $h_{FE} = 100$ ,  $V_T = 25 \text{ mV}$ ,  $|V_{BE}| = 0,6 \text{ V}$ ,

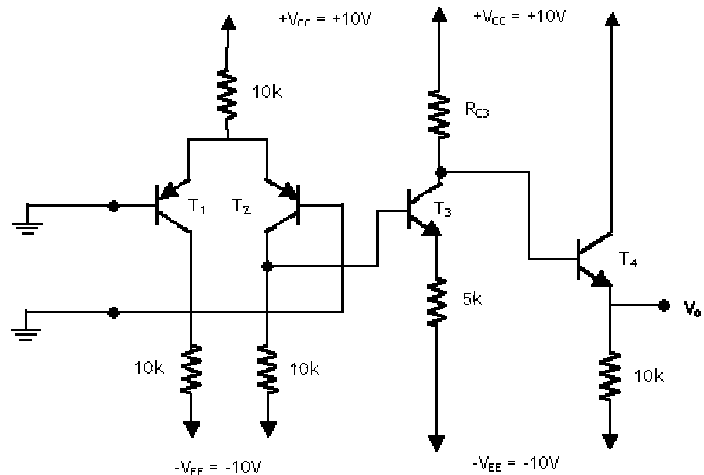
- Find the collector currents of all 4 transistors and value of  $R_{C3}$  such that  $V_0 = 0\text{V}$ . (30 points)



- design a BJT based current mirror that will provide the current provided by the  $10\text{k}$  resistor connected to the common emitters of the differential stage. (10 points)

- For the circuit shown on the left sketch  $V_{out}$  as a function of  $V_{in}$  for  $V_{in}$ :  $-10 \text{ V}$  to  $+10 \text{ V}$  assuming all three resistors are  $10\text{k}$  and the voltage drop across conducting diodes are constant at  $0,6 \text{ V}$ . (20 points)

 HINT: Analyze the circuit first at  $V_{in} = 0\text{V}$ ; then at  $+10 \text{ V}$  and  $-10 \text{ V}$ , and finally at values in between.



GOOD LUCK!

## SOLUTIONS TO PROBLEMS OF MIDTERM EXAM ON 21 MARCH 2005

1.

CONDUCTORS		SEMI-CONDUCTORS
Charged carriers conduct current.	similarity	Charged carriers conduct current.
Charged carriers are electrons ONLY.	difference	Charged carriers are electrons AND holes.
Electron density is $\sim 10^{23}/\text{cm}^3$ .	difference	Electron or hole density in intrinsic semiconductor silicon is about $10^{10}/\text{cm}^3$ .
Electron density is the same all the time.	difference	Electron/hole density may be increased by doping the intrinsic semiconductor.
...	...	...

For more information consult your textbooks.

2. From Einstein Relation,  $D_{p/n} = V_T \cdot \mu_{p/n}$ , one can calculate  $D_p = 12 \text{ cm}^2/\text{s}$  and  $D_n = 33.8 \text{ cm}^2/\text{s}$ .

Using the formulae  $V_B = -V_T \cdot \ln\left(\frac{n_i^2}{N_A \cdot N_D}\right)$ ,  $I_o = A \cdot q \cdot n_i^2 \cdot \left[\frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A}\right]$ ,

$w = \sqrt{\frac{2 \cdot \epsilon_o \cdot \epsilon_r \cdot V_B}{q \cdot \left[\frac{1}{N_A} + \frac{1}{N_D}\right]}}$ , and  $C = \epsilon_o \cdot \epsilon_r \frac{A}{w}$ , we can say that

- The unbiased pn junction A has the lowest barrier potential because barrier potential is proportional to doping ratios, and junction A has the lowest doping ratios  $N_D$  and  $N_A$ .
- The unbiased pn junction D has the smallest saturation current because saturation current is inversely proportional to doping ratios, and junction D has the highest doping ratios  $N_D$  and  $N_A$ .
- The unbiased pn junction D has the largest depletion capacitance because it has the smallest depletion width which is inversely proportional to the sum of doping ratios  $N_D$  and  $N_A$ .

The table below shows it in figures:

	A	B	C	D
$N_D [1/\text{cm}^3]$	$10^{15}$	$10^{15}$	$10^{17}$	$10^{17}$
$N_A [1/\text{cm}^3]$	$10^{16}$	$10^{18}$	$10^{16}$	$10^{18}$
$V_B [\text{mV}]$	613	728	728	843
$I_o [\text{fA}]$	987	866	2500	9,9
$w_{\text{depletion}} [\text{nm}]$	945	983	326	111
$C_{\text{depletion}} [\text{pF}]$	112	108	326	958

3. The first stage of the 3-stage amplifier is a differential stage. Since both transistors are ideal, their collector currents are the same and equal to

$$I_{C1} = I_{C2} = \frac{V_{CC} - V_{BE1}}{2R_E} = \frac{10V + V_{BE1}}{20k} = \frac{10V - 0,6V}{20k} = \frac{9,4V}{20k} = 0,47mA$$

Now, following the blue loop

$$-(I_{C2} - I_{B3})10k + V_{BE3} + (h_{FE} + 1)I_{B3}5k = 0$$

$$I_{C3} = h_{FE} \frac{10k * I_{C2} - V_{BE3}}{(h_{FE} + 1)5k + 10k} = 0,8mA$$

We are told that  $V_0 = 0V$ . Thus

$$I_{E4} = \frac{0V - (-V_{EE})}{10k} \text{ or}$$

$$(h_{FE4} + 1)I_{B4}10k = 10V$$

$$\Rightarrow I_{C4} = h_{FE4}I_{B4} = 0,99mA$$

Also,

$$V_{B4} = +V_{CC} - R_{C3} * (I_{C3} + I_{B4}) = +10V - R_{C3} * (0,91mA + 9,9\mu A) =$$

$$\text{Therefore, } R_{C3} = \frac{10V - 0,6V}{0,8mA + 9,9\mu A} = 11k6$$

BJT based current mirror design:



$$I_{ref} = 2I_{C1} = 2I_{C2} = 0,94mA.$$

On the right is my design. NOTE that the collector of  $T_6$  is connected to the common emitters of the differential stage. At DC  $V_{E1} = V_{E2} = 0,6V$ , that means,  $V_{C6} = 0,6V$ . This voltage should keep  $T_6$  in active mode! Does it?

$V_{B6} = 9,4V$ . For BC junction to be reverse biased,


$V_{C6} \leq V_{B6} - 0,6V$  that is  $V_{C6} \leq 8,8V$ .

 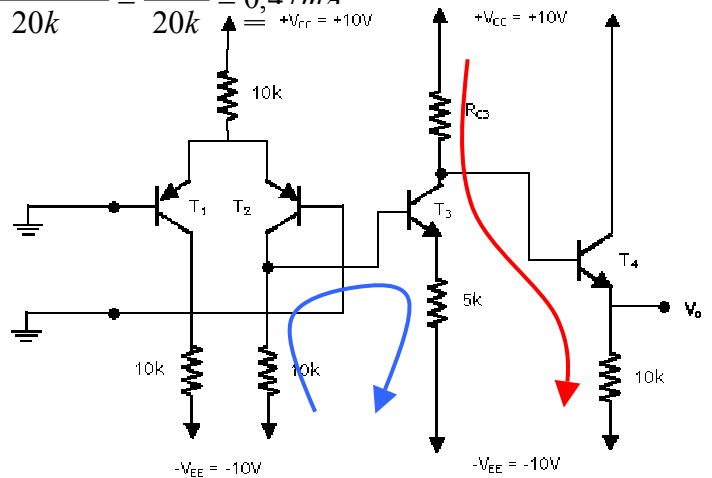$V_{C6} = 0,6V < 8,8V$  and THUS this condition is satisfied.



 4. Assume there is no  $V_{in}$ .  $V_{out} = 0V$  because of the symmetry of the circuit, and because all diodes are conducting. This is the same as  $V_{in} = 0V$ .

Now assume  $V_{in} = 10V$ . We can easily see that  $D_1$  and  $D_3$  are reverse biased because most of the voltage drop from  $+10V$  to  $-10V$  is over the resistors  $R_1$  and  $R_2$ . In other words, the anode of  $D_1$  is much less than  $+10V$  whereas the cathode is at  $+10V$  (reverse bias). Also,  $D_4$  is conducting, thus, the cathode of  $D_3$  is at  $9,4V$  whereas the anode of  $D_3$  is much less than  $+9,4V$ . That means current flows (a) from  $+10V$  over  $R_1$ ,  $D_2$ , and  $R_3$  to ground (follow blue line), and (b) from  $V_{in}$  over  $D_4$  and  $R_4$  to  $-10V$ . Since only  $0,6V$  drops on the conducting diodes  $9,4V$  drops over the two resistors  $R_1$  and  $R_3$ . Since  $R_1$  and  $R_3$  have equal values, we divide the voltage drop by 2 and this



is  $V_{out} = 4.7V$ .

Now assume  $V_{in} = -10V$ . Similar to the observations above,  $D_4$  and  $D_2$  are reverse biased because most of the voltage drop from  $+10V$  to  $-10V$  is again over the resistors  $R_1$  and  $R_2$ .

In other words, the cathode of  $D_4$  is much higher than  $-10V$  whereas the anode is at  $-10V$  (reverse bias again). Also,  $D_1$  is conducting, thus, the anode of  $D_2$  is at  $-9.4V$  whereas the cathode of  $D_2$  is much higher than  $-9.4V$ . That means current flows (a) from the ground over  $R_3$ ,  $D_3$ , and  $R_2$  to  $-10V$  (follow red line), and (b) from  $+10V$  over  $R_1$  and  $D_1$  to  $V_{in}$ . Since only  $0.6V$  drops on the conducting diodes  $9.4V$  drops over the two resistors  $R_2$  and  $R_3$ . Since  $R_2$  and  $R_3$  have equal values, we divide the voltage drop by 2 and this is  $V_{out} = 4.7V$ .

Finally, we need to consider the output for  $0V \geq V_{in} \geq -10V$  and  $0V \leq V_{in} \leq +10V$ . One sees easily that when all the 4 diodes are conducting, the output  $V_{out}$  follows the input  $V_{in}$  because the circuit is symmetrical. When do all the 4 diodes conduct? See the sketch below....Capito????

