



ELCT 508: Communication Microelectronics


Lecture 07:
Differential Amplifiers

Dr. Hany Ayad Bastawrous

Department of Electronics and Electrical Engineering

hany.bastawrous@guc.edu.eg

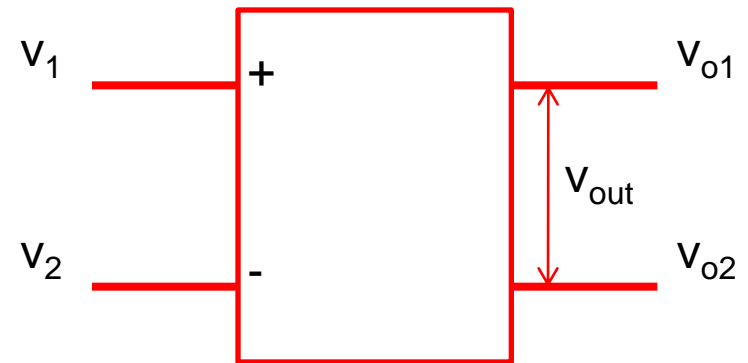A differential amplifier is one that responds to the difference between the two signals applied at its input and ideally rejects signals that are common to the two inputs



$$v_1 = v_{Icm} - \frac{v_{Id}}{2}$$


$$v_2 = v_{Icm} + \frac{v_{Id}}{2}$$

Possible configurations

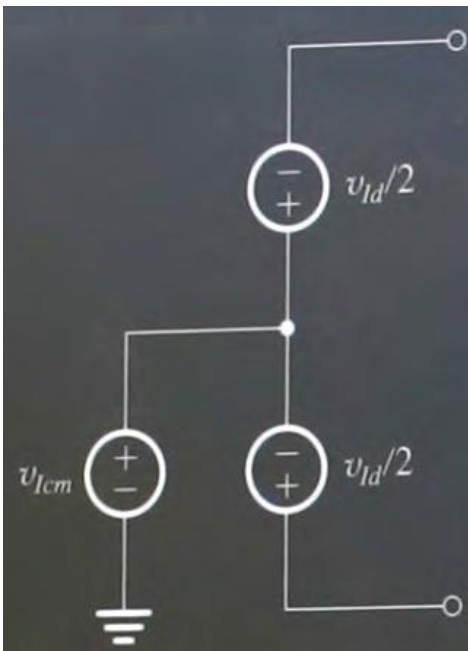1. Dual-input balanced-output
2. Dual-input unbalanced-output
3. Single-input balanced-output
4. Single-input unbalanced-output

$$v_{out} = A_d v_{Id} + A_{cm} v_{Icm}$$

Differential-mode gain **Common-mode gain**



Common-mode rejection ratio (CMRR)

A quantity that measures the degree of rejection of common-mode signals in preference to differential signals

$$\text{CMRR} = 20 \log \frac{|A_d|}{|A_{cm}|}$$

Output offset voltage

The voltage that appears at the output of the differential amplifier when the input terminals are connected together ($V_{id}=0$).

Input offset voltage


Equals to the output offset voltage divided by the differential voltage gain

Control parameters:

v_{B1} and v_{B2}


Outputs:

v_{C1} and v_{C2}

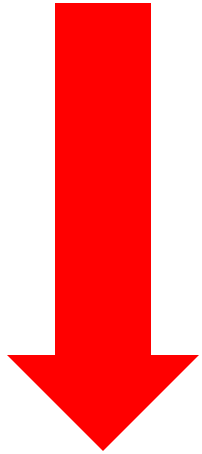


- 1) Large-signal analysis
- 2) Small-signal analysis

BJT differential pair

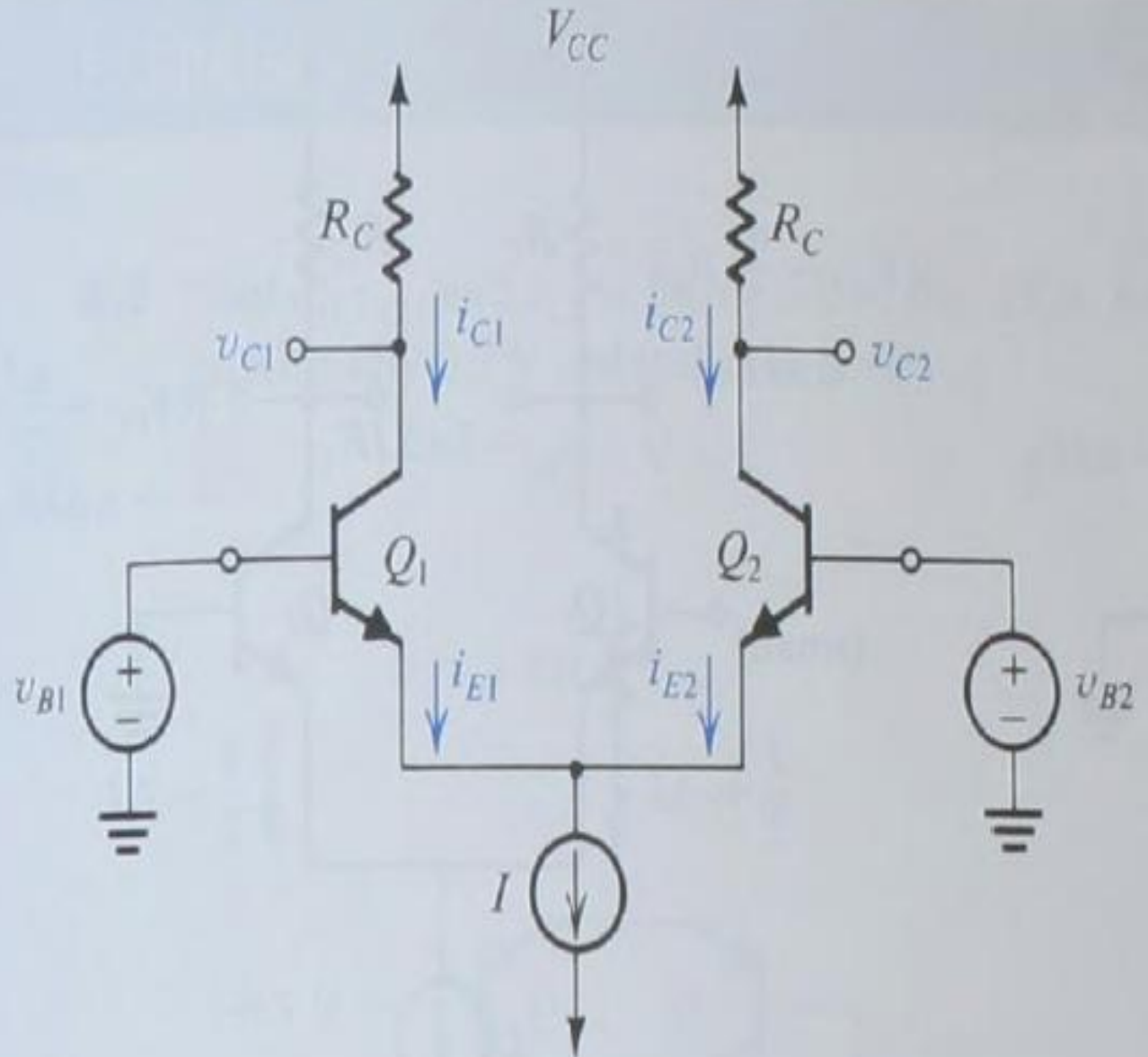


Large-signal analysis


Case 1: $v_{B1}=v_{B2}=v_{CM}$

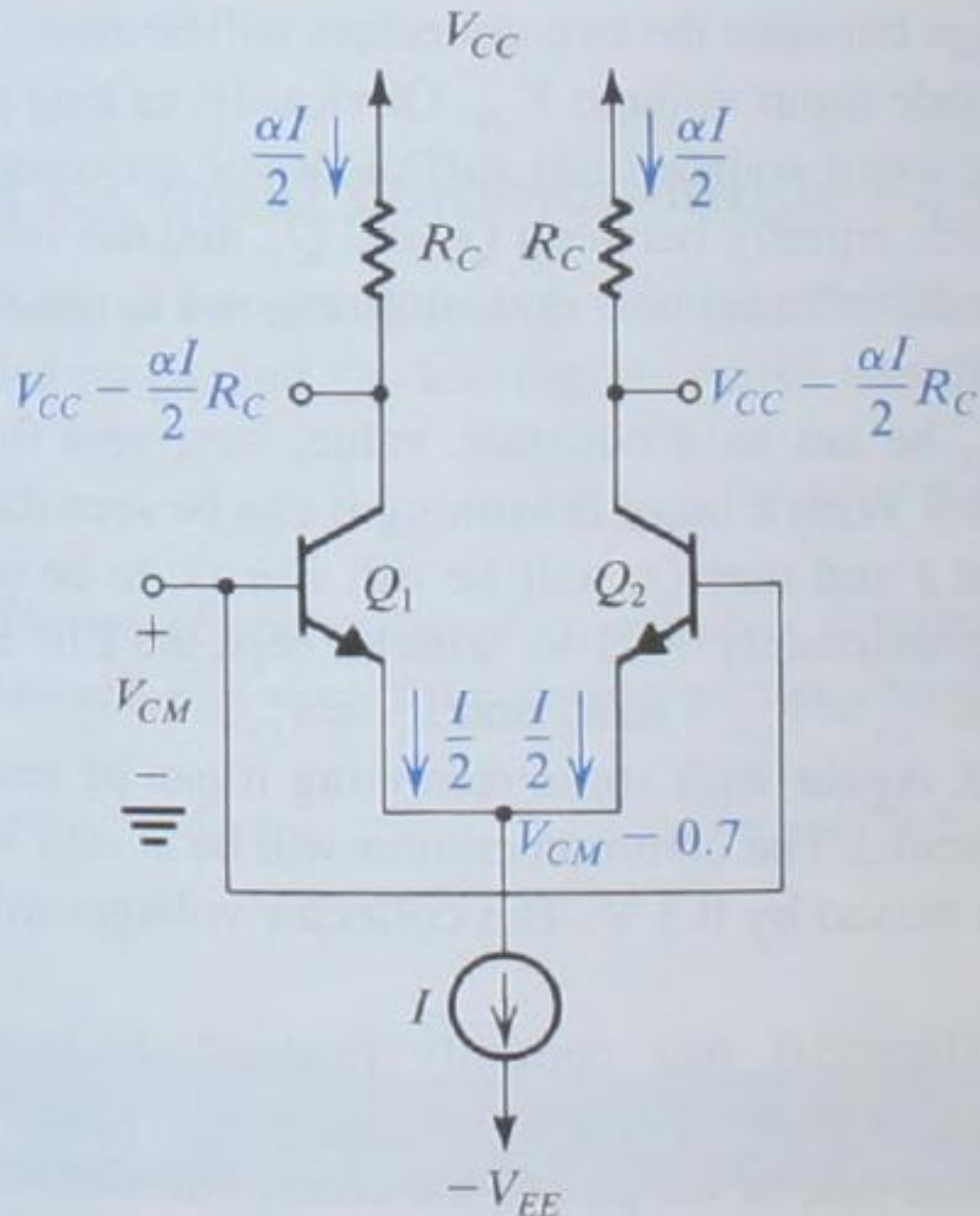

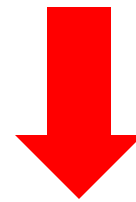Q_1 and Q_2 are matched transistors and operating in the active mode




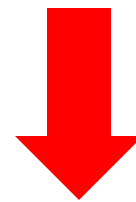Only common-mode output is available and differential-mode output is zero




$$v_{O1} = v_{O2} = V_{CC} - \frac{\alpha I}{2} R_C$$


Case 2: $v_{B1} = 1V$ & $v_{B2} = 0V$

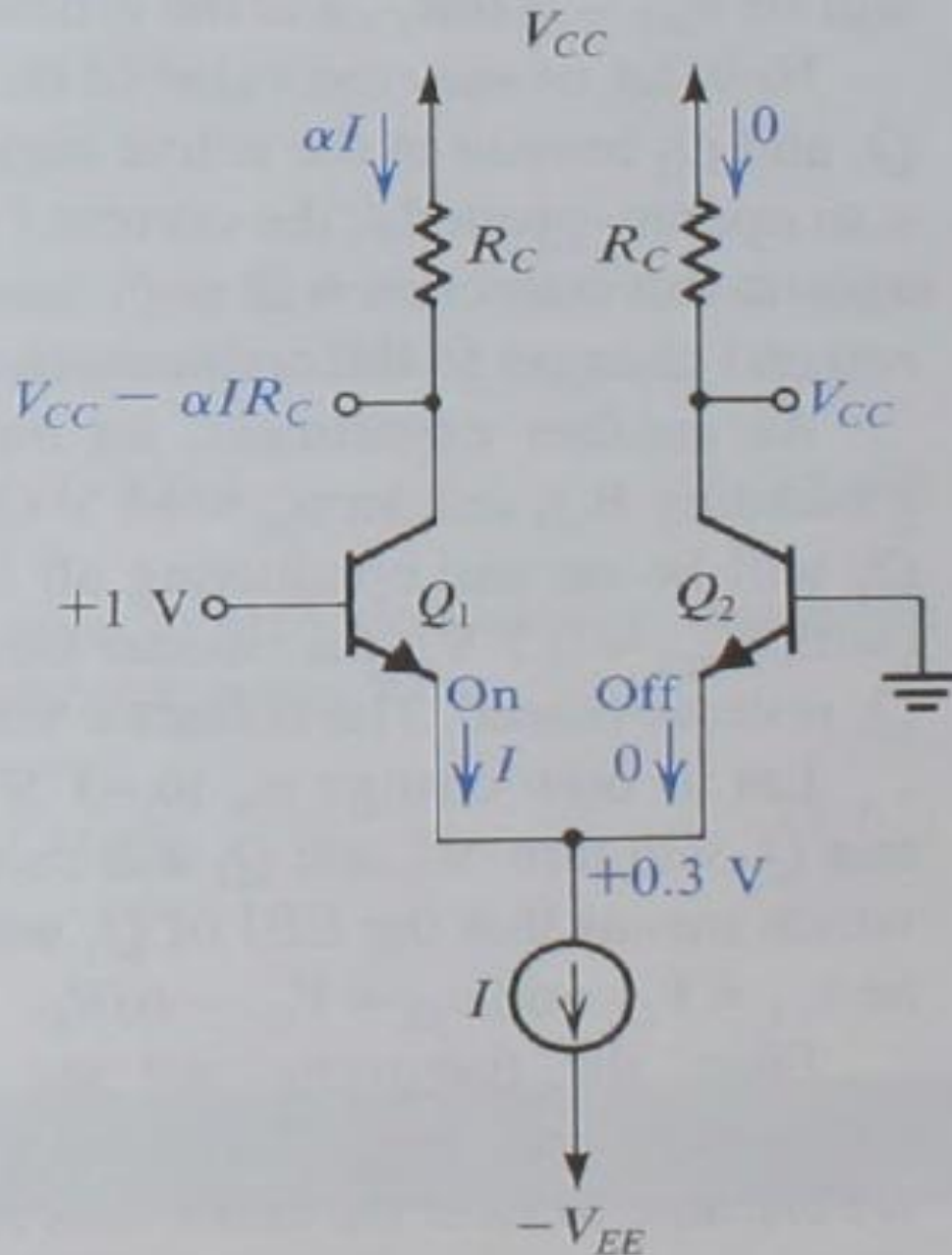

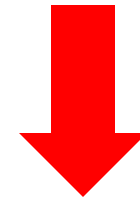Q_1 is ON and operating in the active region while Q_2 is OFF




Differential-mode output is not zero

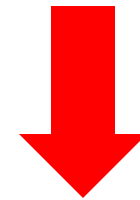


$$v_{O1} = V_{CC} - \alpha I R_C$$

$$v_{O2} = V_{CC}$$


Case 3: $v_{B1} = -1V$ & $v_{B2} = 0V$

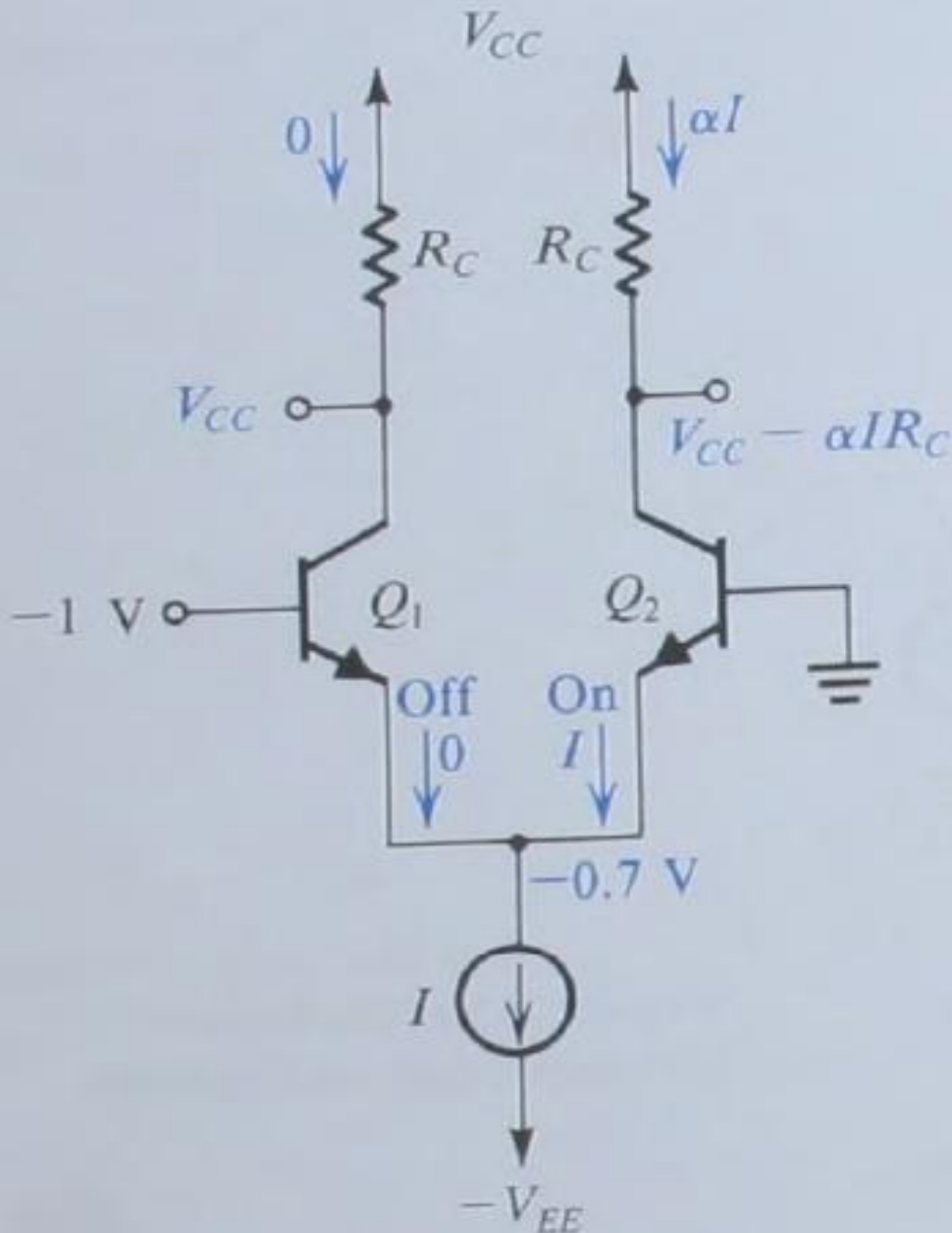

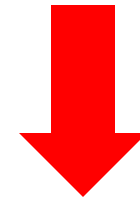Q_1 is OFF while Q_2 is ON
and operating in the
active region



Differential-mode
output is not zero

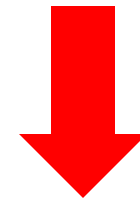

$$v_{O1} = V_{CC}$$

$$v_{O2} = V_{CC} - \alpha I R_C$$

Large-signal operation of BJT differential pair

Q_1 and Q_2 are 2 matched BJTs

$$\therefore \beta_1 = \beta_2 = \beta$$


and $I_{S1} = I_{S2} = I_S$

$$I_{C1} = I_S e^{\frac{V_{BE1}}{V_T}}$$

$$I_{C2} = I_S e^{\frac{V_{BE2}}{V_T}}$$

$$V_{BE1} = V_T \ln\left(\frac{I_{C1}}{I_S}\right)$$
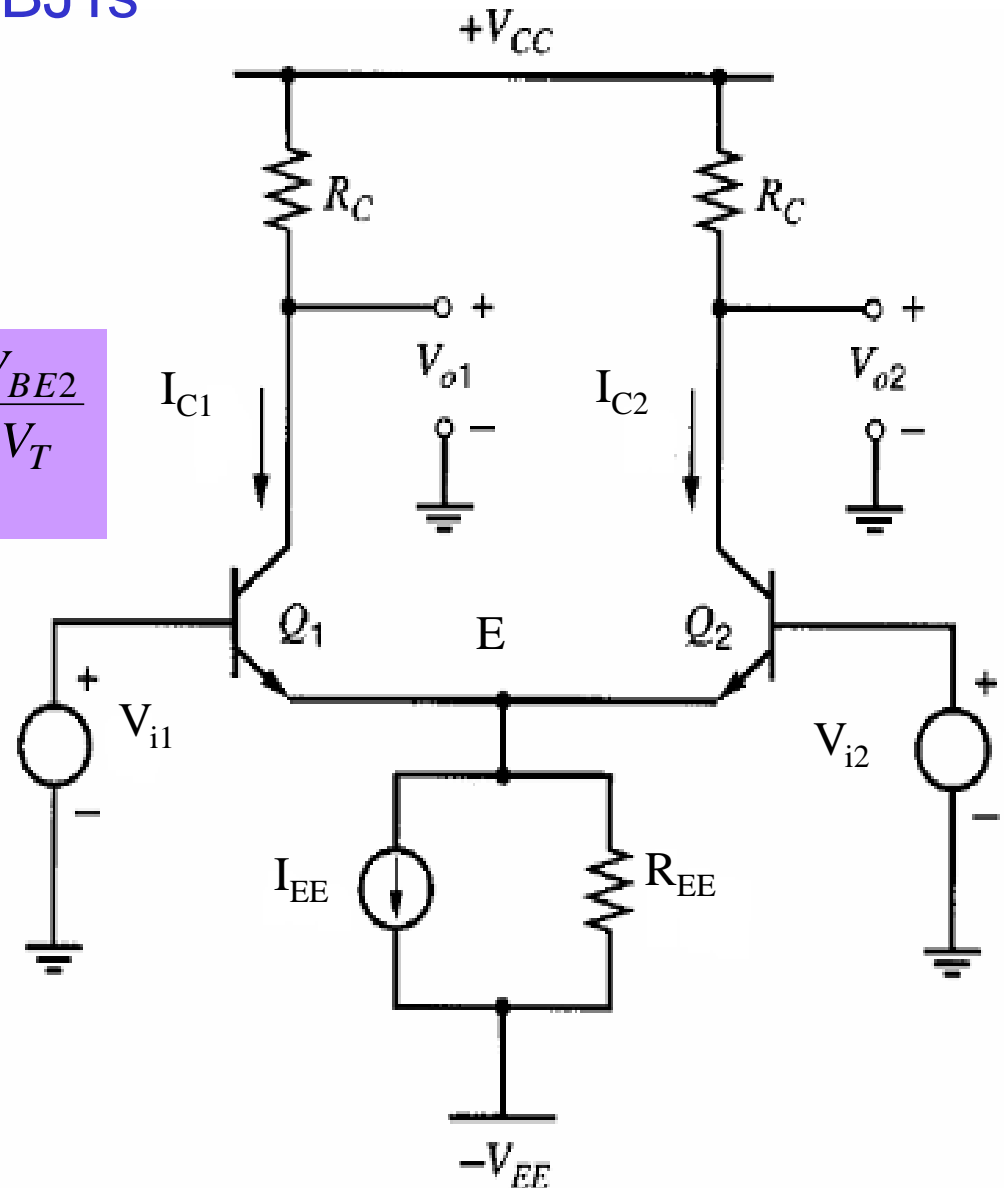
$$V_{BE2} = V_T \ln\left(\frac{I_{C2}}{I_S}\right)$$



$$V_E = V_{i1} - V_{BE1} = V_{i2} - V_{BE2}$$

$$V_{i1} - V_{i2} = V_{id} = V_T \ln\left(\frac{I_{C1}}{I_S}\right) - V_T \ln\left(\frac{I_{C2}}{I_S}\right)$$

$$\therefore V_{id} = V_T \ln\left(\frac{I_{C1}}{I_{C2}}\right)$$

$$\Rightarrow \frac{I_{C1}}{I_{C2}} = e^{\frac{V_{id}}{V_T}}$$


Assume that $R_{EE} \sim \infty$ and $\beta \approx \infty$

$$\Rightarrow I_{C1} + I_{C2} = I_{EE}$$

$$\therefore I_{C1} = \frac{I_{EE}}{1 + e^{-\frac{V_{id}}{V_T}}}$$

and
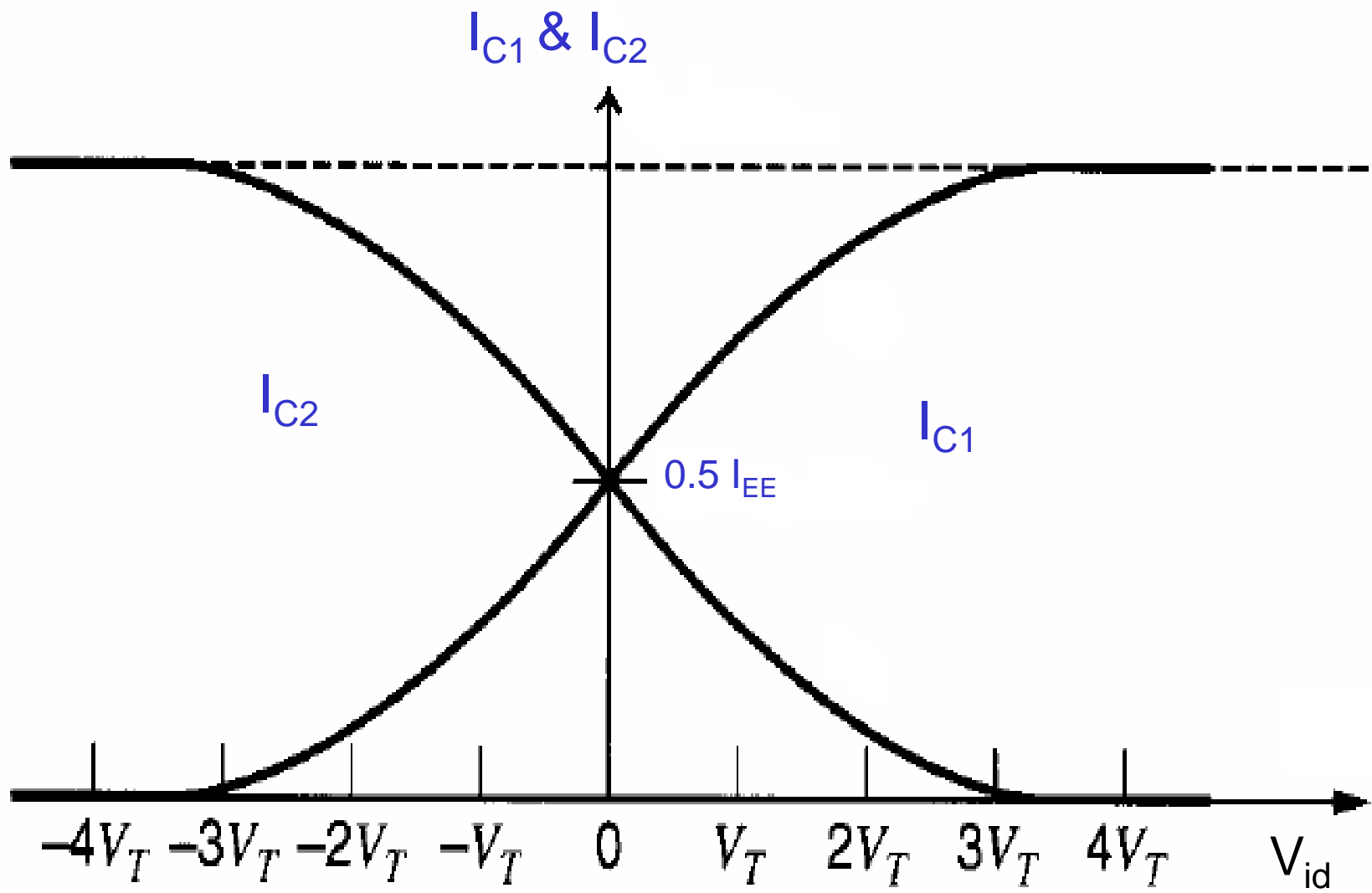
$$I_{C2} = \frac{I_{EE}}{1 + e^{\frac{V_{id}}{V_T}}}$$




$$I_{C1} - I_{C2} = I_{EE} \tanh\left(\frac{V_{id}}{2V_T}\right)$$

$$V_{od} = V_{o1} - V_{o2} = -(I_{C1} - I_{C2})R_C = -I_{EE}R_C \tanh\left(\frac{V_{id}}{2V_T}\right)$$

$$\therefore V_{od} = -I_{EE}R_C \tanh\left(\frac{V_{id}}{2V_T}\right)$$
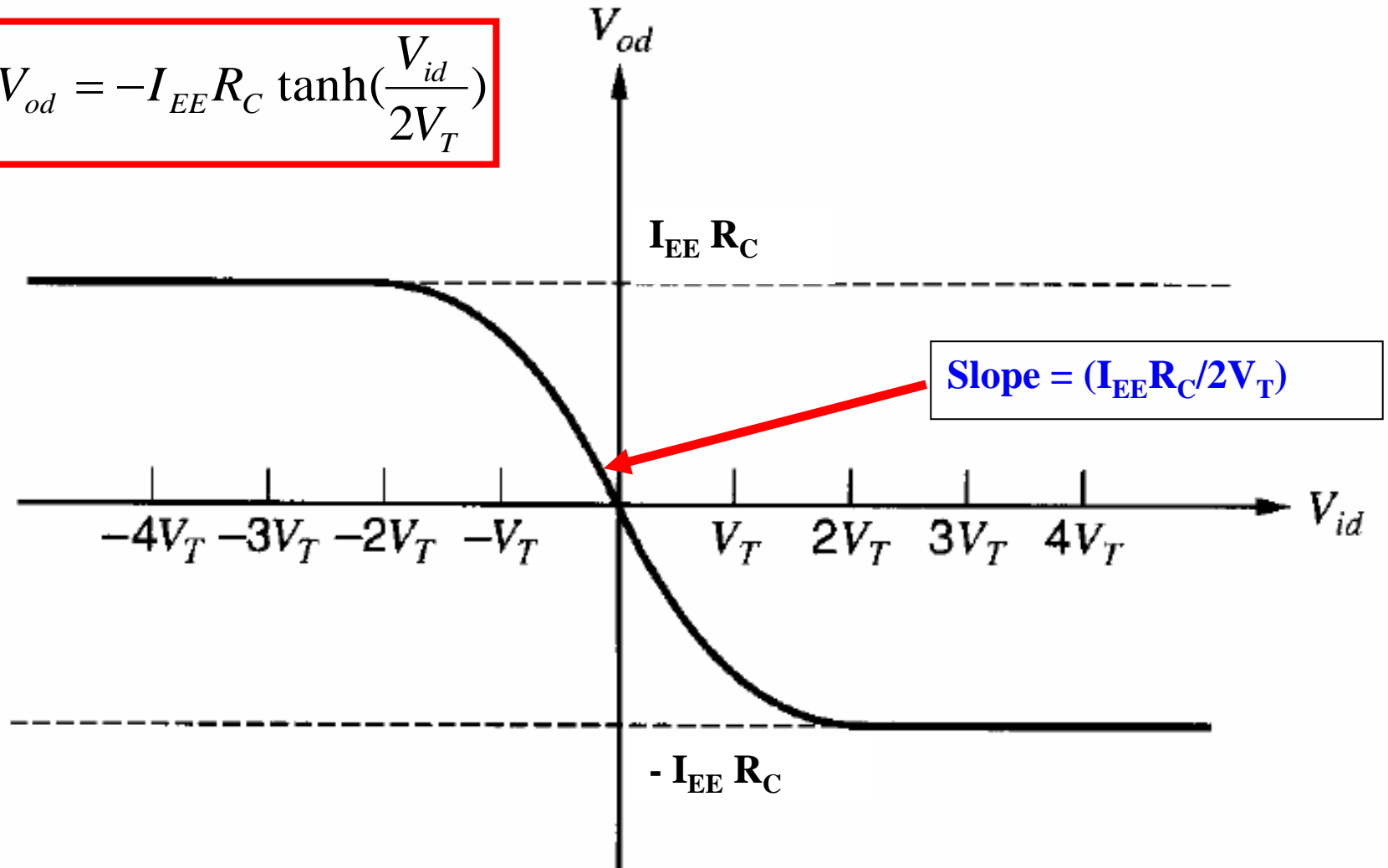
$$V_{od} = -I_{EE}R_C \tanh\left(\frac{V_{id}}{2V_T}\right)$$



Note:

$$V_{od} \cong \left(\frac{I_{EE}R_C}{2V_T}\right)V_{id}$$


For

$$|V_{id}| \ll V_T$$

Small-signal analysis

Small-signal operation of BJT differential pair

(a) Using small-signal model

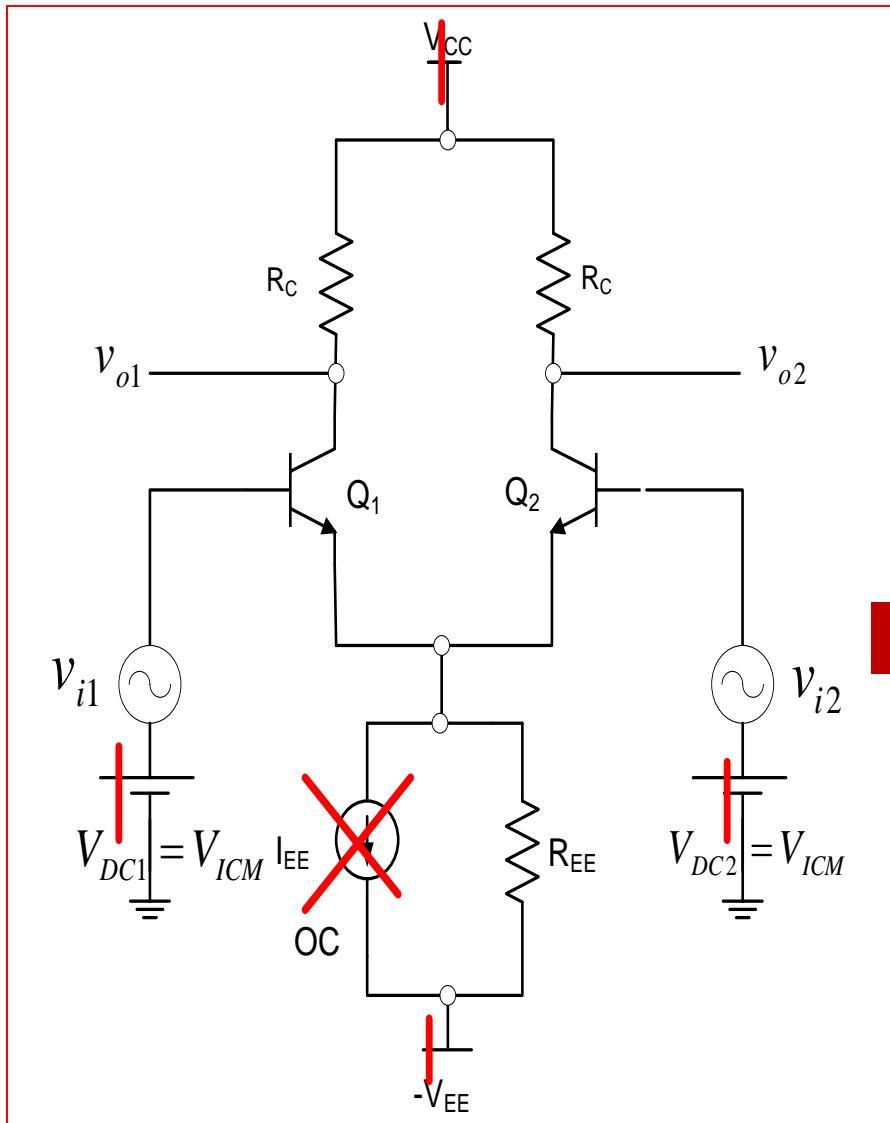

$$v_{i1} = v_{ic} - \frac{v_{id}}{2}$$


$$v_{i2} = v_{ic} + \frac{v_{id}}{2}$$

Case 1: $v_{id} = 0 \Rightarrow v_{i1} = v_{i2} = v_{ic}$ (Common-mode)

$$\because v_{i1} = v_{i2} \Rightarrow \therefore i_{B1} = i_{B2} = i_B$$

$$v_{R_{EE}} = 2R_{EE}(\beta + 1)i_B$$
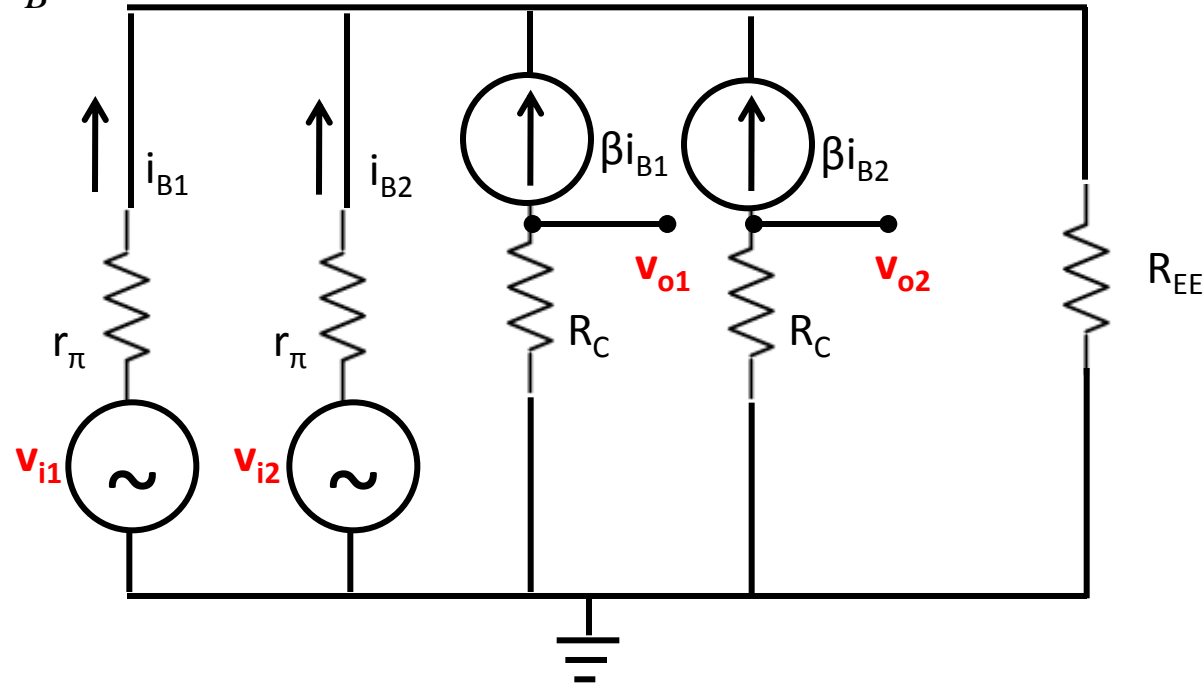
$$i_B = \frac{v_{ic}}{2(\beta + 1)R_{EE} + r_\pi}$$



$$\therefore \frac{v_{o1}}{v_{ic}} = \frac{v_{o2}}{v_{ic}} = \frac{\beta R_C}{2(\beta + 1)R_{EE} + r_\pi} \approx \frac{g_m R_C}{1 + 2g_m R_{EE}}$$


$$A_{CM} \equiv \frac{v_{o1}}{v_{ic}} \approx \frac{g_m R_C}{1 + 2g_m R_{EE}}$$

Case 2: $v_{ic} = 0 \Rightarrow v_{i1} = -v_{i2} = v_{id}/2$ (Differential-mode)

$$\because v_{i1} = -v_{i2} \Rightarrow \therefore i_{B1} = -i_{B2}$$

$$\therefore v_{R_{EE}} = 0$$

$$i_{B1} = \frac{v_{id} / 2}{r_{\pi}}$$

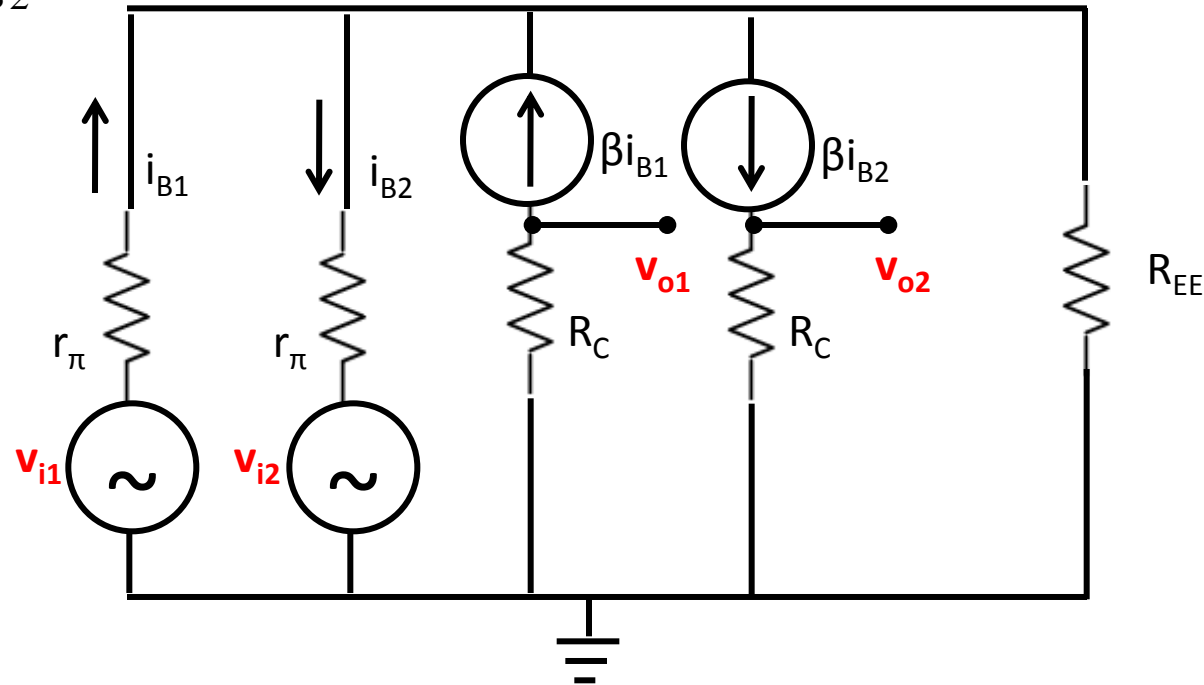


$$\therefore \frac{v_{o1}}{v_{id} / 2} = -\frac{v_{o2}}{v_{id} / 2} = -g_m R_C$$




$$A_{DM} \equiv \frac{v_{o2} - v_{o1}}{v_{id}} = g_m R_C$$

$$CMRR \equiv \frac{A_{DM}}{A_{CM}} = 1 + 2g_m R_{EE}$$


(b) Using half-circuit concept

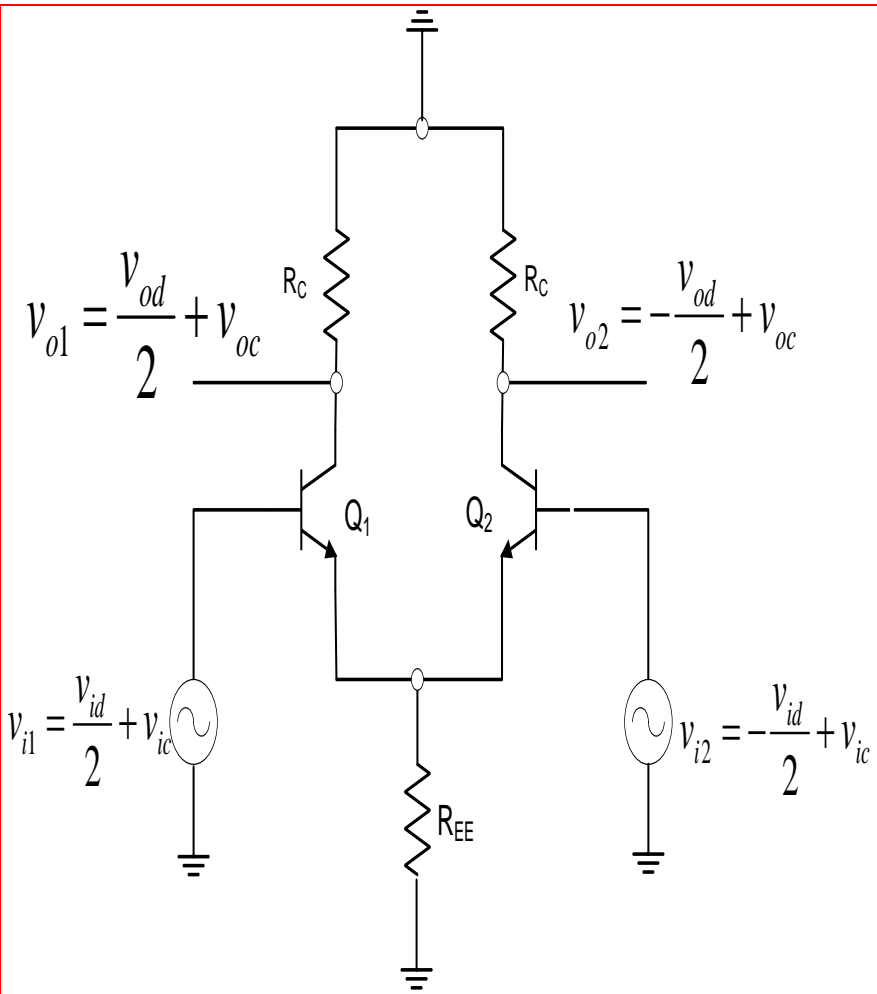


Differential-mode

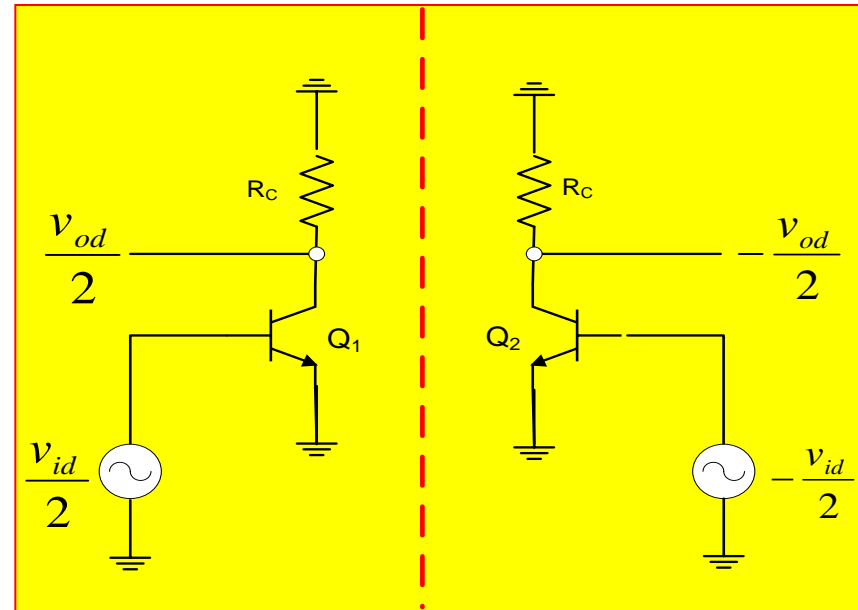

Common-mode

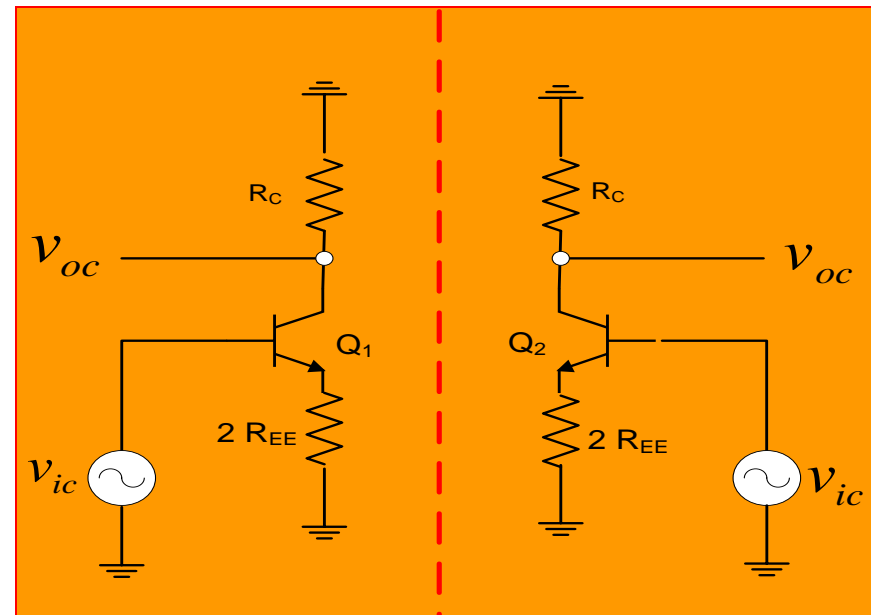


a- Differential-mode

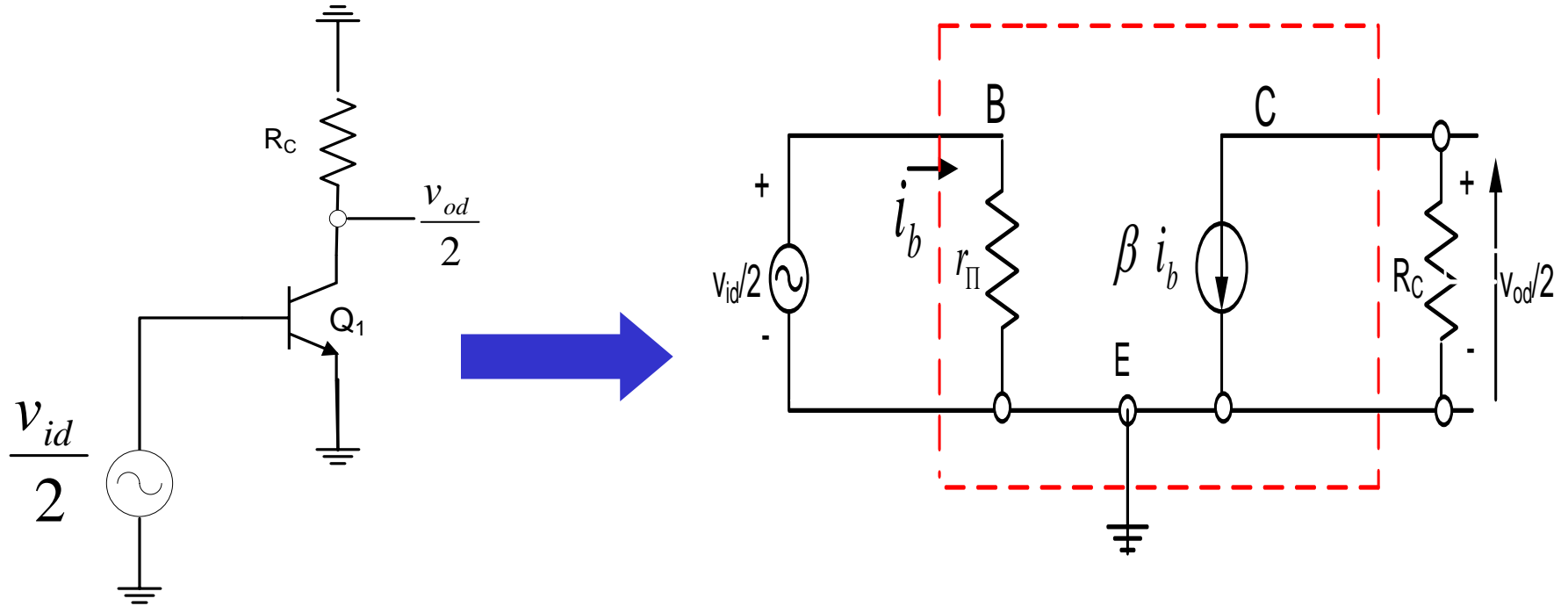

$$A_{DM} = \frac{v_{od}}{v_{id}} = -\frac{\beta R_C}{r_{\pi}} = -g_m R_C$$

b- (Common-mode)

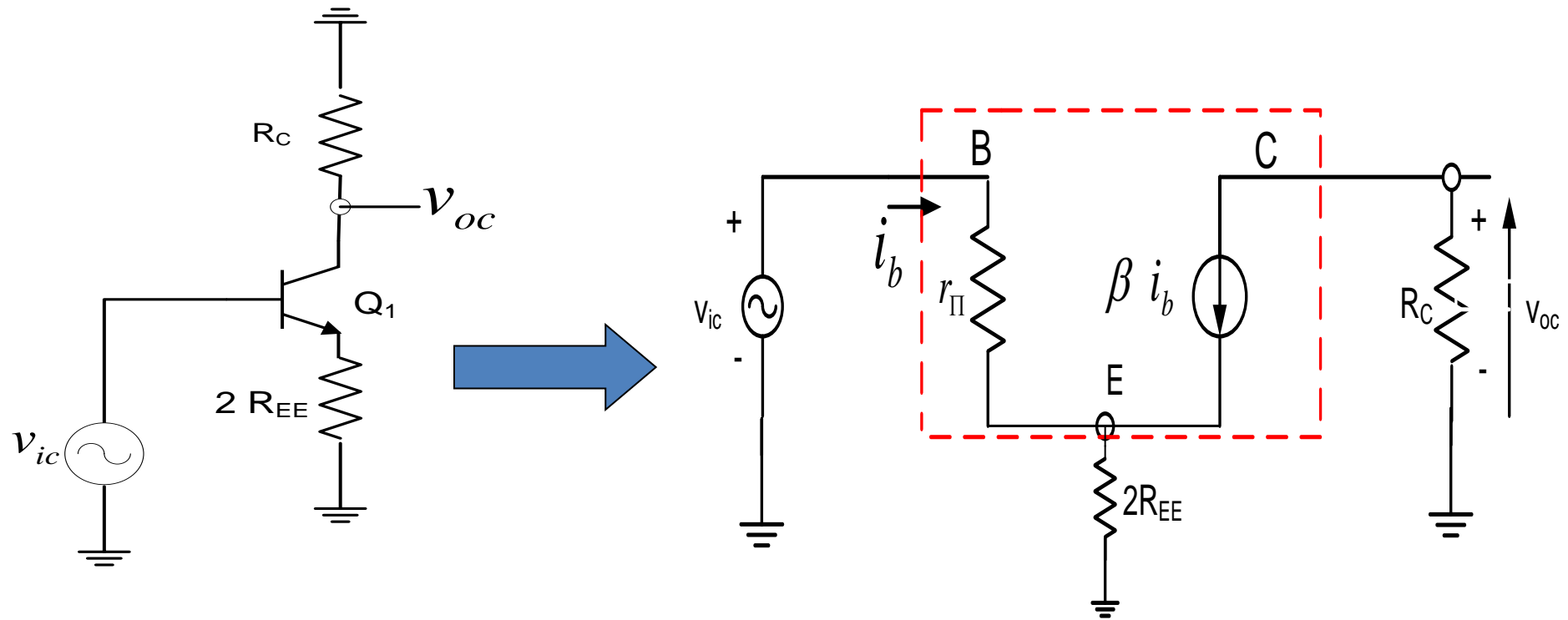

$$A_{CM} = \frac{v_{oc}}{v_{ic}} = - \frac{\beta R_C}{r_{\pi} + 2(1 + \beta)R_{EE}} \cong - \frac{g_m R_C}{1 + 2g_m R_{EE}}$$


$$\therefore CMRR \equiv \frac{A_{DM}}{A_{CM}} = 1 + 2g_m R_{EE}$$

Simple current source (Current mirror)

For Q_3 and Q_4 are matched transistors, Q_3 is acting as a diode (in the active-mode)

$$V_{BE3} = V_{BE4} \Rightarrow I_{B3} = I_{B4}$$


$$\therefore I_{C3} = I_{C4} = I_{EE}$$

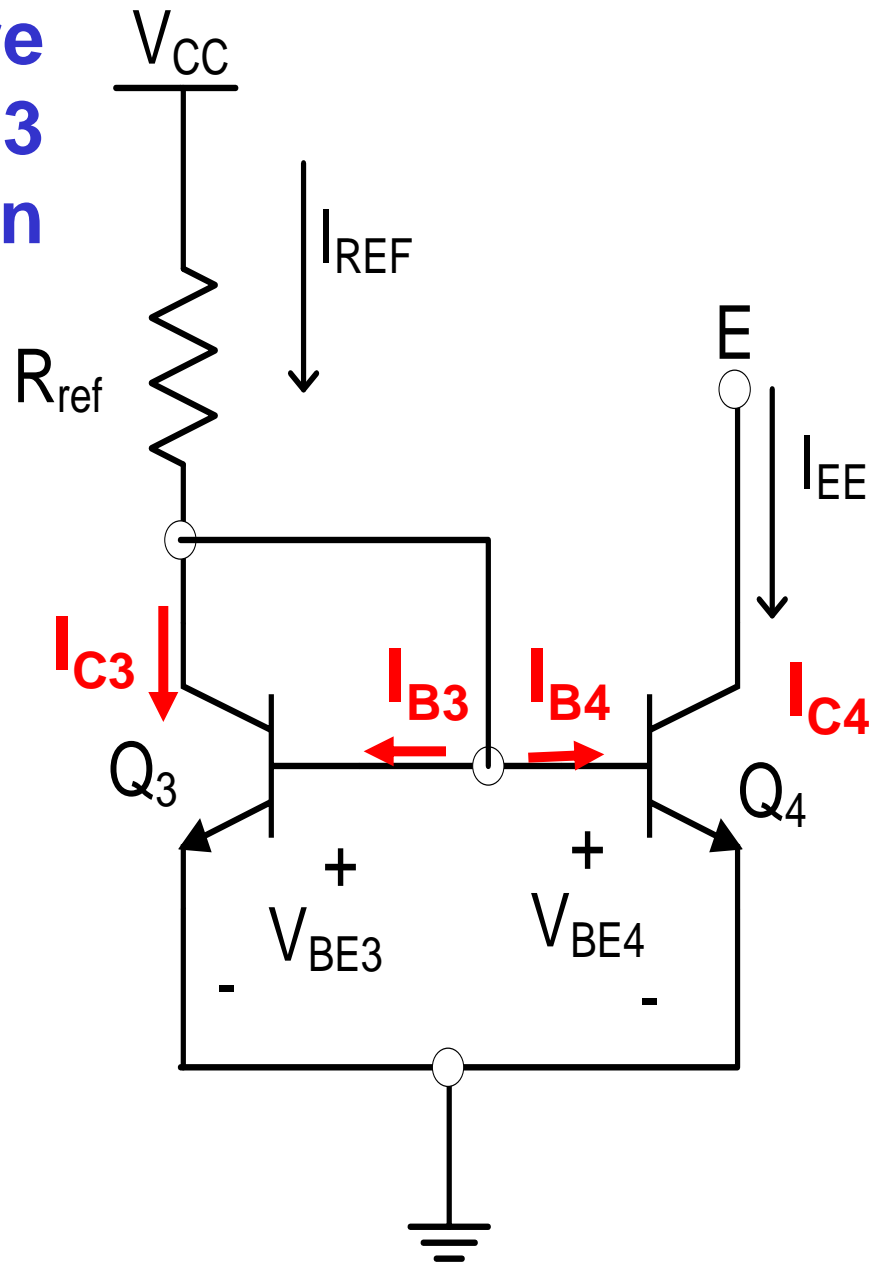

$$I_{REF} = I_{EE} + \frac{2I_{EE}}{\beta}$$

$$I_{EE} = \frac{I_{REF}}{\left(1 + \frac{2}{\beta}\right)}$$
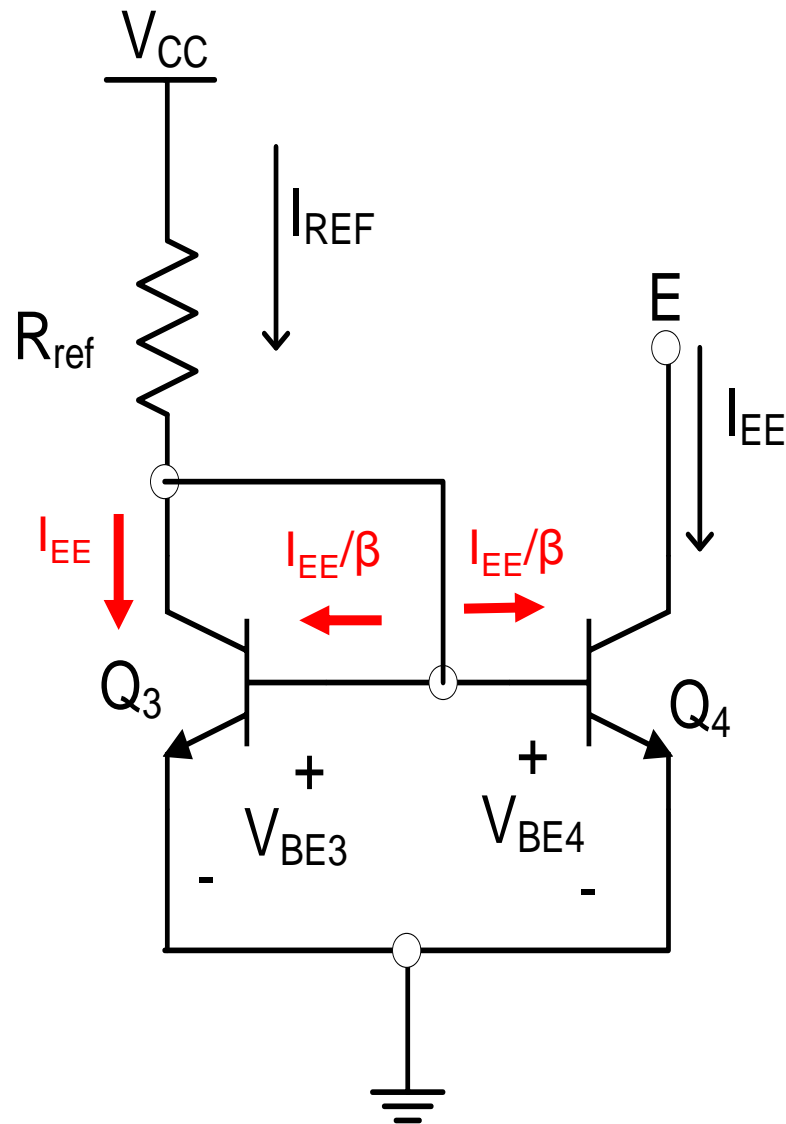
$$I_{REF} = \frac{(V_{CC} - V_{BE3})}{R_{ref}} = \frac{(V_{CC} - 0.7)}{R_{ref}}$$



BJT differential amplifier biased by a current mirror

