

# **Introduction to Transistor Amplifiers: Concept & Biasing**


Lecture notes: Sec. 5

Sedra & Smith (6<sup>th</sup> Ed): Sec. 5.4-5.4.6 & 6.3-6.4

Sedra & Smith (5<sup>th</sup> Ed): Sec. 4.4-4.4.6 & 5.3-5.4

 
# Foundation of Transistor Amplifiers (1)

- A voltage amplifier requires  $v_o/v_i = \text{const.}$  (2 examples are shown below)



- $v_o/v_i$  can be negative (minus sign represents a 180° phase shift)


- MOS transfer function is NOT linear

 



- In saturation, however, transfer function looks linear (but shifted)
 
# Foundation of Transistor Amplifiers (2)


- Let us consider the response if NMOS remain in saturation at all times:
  - $v_{GS}$  should be a combination of a constant value ( $V_{GS}$ ) and a signal ( $v_{gs}$ ).



  The response to a combination of  $v_{GS} = V_{GS} + v_{gs}$  can be found from the transfer function



 
# Response to the signal appears to be linear!




- Response ( $v_o = v_{DS}$ ) is also made of a constant part ( $V_{DS}$ ) and a signal response part ( $v_{ds}$ ).
- Constant part of the response,  $V_{DS}$ , is ONLY related to  $V_{GS}$ , the constant part of the input (Q point on the transfer function of previous slide).
  - i.e., if  $v_{gs} = 0$ , then  $v_{ds} = 0$
- The shape of the time varying portion of the response ( $v_{ds}$ ) is similar to  $v_{gs}$ .
  - i.e.,  $v_{ds}$  is proportional to the input signal,  $v_{gs}$
- **While overall response is non-linear, response to the signal appears to be linear!**
 
# Although the overall response is non-linear, the transfer function for the signal is linear!



 
# An Analogy: How much water is under the keel of a boat?




- Total Height,  $H_b = \text{Bias } (H_B) + \text{response to the added weight } (h_b)$
- Complicated correlation between the total height,  $H_b$ , and the weight of the boat.
- Simple correlation between  $h_b$  and the added weight

# An Analogy (2)

 

 - Bias: zero added weight &  $H_B$
- Bias + Signal: total weight &  $H_b$
- Signal & response: added weight &  $h_b$



- Bias:  $V_{GS}$ ,  $V_{DS}$ ,  $I_D$
- Bias + Signal:  $v_{GS}$ ,  $v_{DS}$ ,  $i_D$
- Signal & response:  $v_{gs}$ ,  $v_{ds}$ ,  $i_d$

- Non-linear correlations among Bias + Signal:  $v_{GS}$ ,  $v_{DS}$ ,  $i_D$
- Simple (and linear) correlation between signal and response to the signal:  $v_{gs}$ ,  $v_{ds}$ ,  $i_d$




# Important Observations!

- **Signal:** We want the response of the circuit to this input.
- **Bias:** State of the system when there is no signal (current and voltages in all elements).
  - Bias is constant in time (may vary very slowly compared to the signal)
  - Purpose of the bias is to ensure that MOS is in saturation at all times.
- **Response** of the circuit (and elements within) to the signal is different than the response of the circuit and its elements to Bias (or to Bias + signal):
  - Different transfer function for the circuit
  - Different  $i$  $v$  characteristics for elements, i.e. relationships among  $v_{gs}$ ,  $v_{ds}$ ,  $i_d$  are different than relationships among  $v_{GS}$ ,  $v_{DS}$ ,  $i_D$ .

**Above observations & conclusions equally apply to a BJT in the active mode!**

# Transistor Amplifier Development

Bias & Signal

 

$$\text{MOS : } v_{GS}, v_{DS}, i_D,$$


$$(v_{GS} = V_{GS} + v_{gs}, \dots)$$

$$R_D : \quad v_R = V_R + v_r$$

$$i_R = I_R + i_r$$

.....

Bias

 


$$\text{MOS : } V_{GS}, V_{DS}, I_D,$$

$$R_D : \quad V_R, I_R$$

.....

Signal only
 
$$= (\text{Bias} + \text{Signal}) - \text{Bias}$$



$$\text{MOS : } v_{gs}, v_{ds}, i_d,$$

$$R_D : \quad v_r, i_r$$

.....

# Issues in developing a transistor amplifier:

- 1. Establish a Bias point** (bias is the state of the system when there is no signal).
  - Stable and robust bias point should be resilient to variations in  $\beta$ ,  $\mu_n C_{ox} (W/L)$ ,  $V_t$ , ... due to temperature and/or manufacturing variability.
- 2. Find the  $i_v$  characteristics of the elements for the signal** (which can be different than their characteristics equation for bias).
  - This will lead to different circuit configurations for bias versus signal:  
**Signal circuit**
- 3. Compute circuit response to the signal & develop transistor amplifier circuits**

# Transistor Biasing

(Bias is the state of the circuit when there is no signal)

1. **Purpose:** BJT should be in active (or MOS should be in saturation) at all times.
  - Bias point impacts the small-signal parameters.
  - Bias point impacts how large a signal can be amplified
2. Bias point should be resilient to variations in  $\beta, \mu_n C_{ox} (W/L), V_t, \dots$  due to temperature and/or manufacturing variability.

# BJT biasing with Base Voltage (Fixed Bias)


$$\text{BE-KVL: } V_{BB} = I_B R_B + V_{BE}$$

$$I_B = \frac{V_{BB} - V_{D0}}{R_B}$$

$$I_C = \beta I_B = \beta \frac{V_{BB} - V_{D0}}{R_B}$$

$$\text{CE-KVL: } V_{CC} = I_C R_C + V_{CE}$$
 
$$V_{CE} = V_{CC} - \frac{\beta R_C}{R_B} (V_{BB} - V_{D0})$$



\* Typically  $V_{BB} = V_{CC}$  in order to reduce the need for additional reference voltages.

Exercise 1: Find  $R_C$  and  $R_B$  such that BJT would be in active with  $I_C = 25$  mA,  $V_{CE} = 5$  V. ( $V_{CC} = 15$  V, Si BJT with  $\beta = 100$  and  $V_A = \infty$ ).

BJT is in Active since  $I_C > 0$  and  $V_{CE} = 5 \geq V_{D0} = 0.7$  V


$$I_B = I_C / \beta = 0.25 \text{ mA}$$

$$\text{BE-KVL: } 15 = I_B R_B + V_{BE} = 0.25 \times 10^{-3} R_B + 0.7$$

$$\underline{R_B = 57.2 \text{ k}}$$

$$\text{CE-KVL: } 15 = I_C R_C + V_{CE} = 25 \times 10^{-3} R_C + 5$$

$$\underline{R_C = 400 \text{ } \Omega}$$

 

Exercise 2: Consider the circuit designed in Exercise 1 ( $R_C = 400$  ,  $R_B = 57.2$  k,  $V_{CC} = 15$  V ). Find the operating point of BJT if  $\beta = 200$ .

Assume BJT is in Active:

$$V_{BE} = 0.7 \text{ V}, I_C > 0 \text{ and } V_{CE} \geq 0.7 \text{ V}$$

$$\text{BE-KVL: } 15 = I_B R_B + V_{BE} = 57.2 \times 10^3 I_B + 0.7$$


$$I_B = 0.25 \text{ mA}$$

$$I_C = \beta I_B = 50 \text{ mA}$$

$$\text{CE-KVL: } 15 = I_C R_C + V_{CE} = 50 \times 10^{-3} \times 400 + V_{CE}$$

$$V_{CE} = -5 \text{ V}$$

**BJT in saturation!**

 

**Note**, compared to Exercise 1:

- $I_B$  is the same.
- $I_C$  increased.
- $V_{CE}$  decreased.

# Why biasing with base voltage (fixed bias) does not work?

- Changes in BJT  $\beta$  changes the bias point drastically.

- BJT can end up in saturation or in cut-off easily.

- In fixed bias,  $I_B$  is set through 
$$I_B = \frac{V_{BB} - V_{D0}}{R_B}$$


- BJT  $\beta$  then sets  $I_C = \beta I_B$  ( $I_C$  changes with  $\beta$ ).

- CE circuit then sets  $V_{CE}$ .

- But, requirements for BJT in active are on  $I_C$  and  $V_{CE}$  and NOT on  $I_B$

- $I_C > 0$ ,  $V_{CE} > V_{D0}$

 - **To make bias point independent of changes in  $\beta$ , the bias circuit should “set”  $I_C$  and NOT  $I_B$  !**





# Biasing with Emitter Degeneration

**Requires a resistor in the emitter circuit!**


$$\text{BE-KVL: } V_{BB} = I_B R_B + V_{BE} + I_E R_E$$

$$V_{BB} - V_{D0} = I_E \left[ \frac{R_B}{\beta + 1} + R_E \right]$$

$$\text{If: } R_B \ll (\beta + 1)R_E$$


$$V_{BB} - V_{D0} \approx I_E R_E$$

 
$$I_C \approx I_E \approx \frac{V_{BB} - V_{D0}}{R_E} \quad \leftarrow \text{Independent of } \beta!$$



Condition of  $R_B \ll (\beta + 1)R_E$  means that the voltage drop across  $R_B$  is small and the bias voltage  $V_{BB} - V_{D0}$  appears across  $R_E$ , setting  $I_E \approx I_C$ .

# Emitter resistor provides negative feedback!

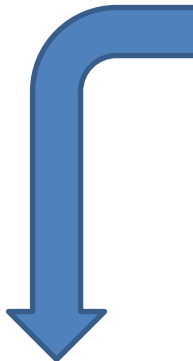 
$$\begin{cases} V_{BB} = I_B R_B + V_{BE} + I_E R_E \\ I_B \propto e^{V_{BE}/V_T} \end{cases}$$



## Negative Feedback:

- If  $I_C \approx I_E \uparrow$  (because  $\beta \uparrow$ ),  $\xrightarrow{\text{BE-KVL}} V_{BE} \downarrow \xrightarrow{\text{BE junction}} I_B \downarrow \xrightarrow{\beta} I_C \approx I_E \downarrow$
- If  $I_C \approx I_E \downarrow$  (because  $\beta \downarrow$ ),  $\xrightarrow{\text{BE-KVL}} V_{BE} \uparrow \xrightarrow{\text{BE junction}} I_B \uparrow \xrightarrow{\beta} I_C \approx I_E \uparrow$


# Requirements for Biasing with Emitter Degeneration

- Requires a resistor in the emitter circuit.
- The bias voltage  $V_{BB} - V_{D0}$  should appear across  $R_E$  to set  $I_E \approx I_C$ :

$$V_{BB} - V_{BE} = I_B R_B + I_E R_E$$


1.  $I_B R_B \ll I_E R_E \Rightarrow R_B \ll (\beta + 1) R_E$ 
  - We need to set  $R_B \ll (\beta_{\min} + 1) R_E$  to ensure that this condition is always satisfied!
2.  $V_{BE} \approx V_{D0}$ . In reality,  $V_{BE} = V_{D0} \pm \Delta V_{BE}$  with  $\Delta V_{BE} \approx 0.1 \text{ V}$ 
  - We need to set  $I_E R_E \gg 0.1 \text{ V}$  or

$$I_E R_E \geq 1 \text{ V}$$

 

# Emitter Degeneration Bias with a voltage divider

Real Circuit

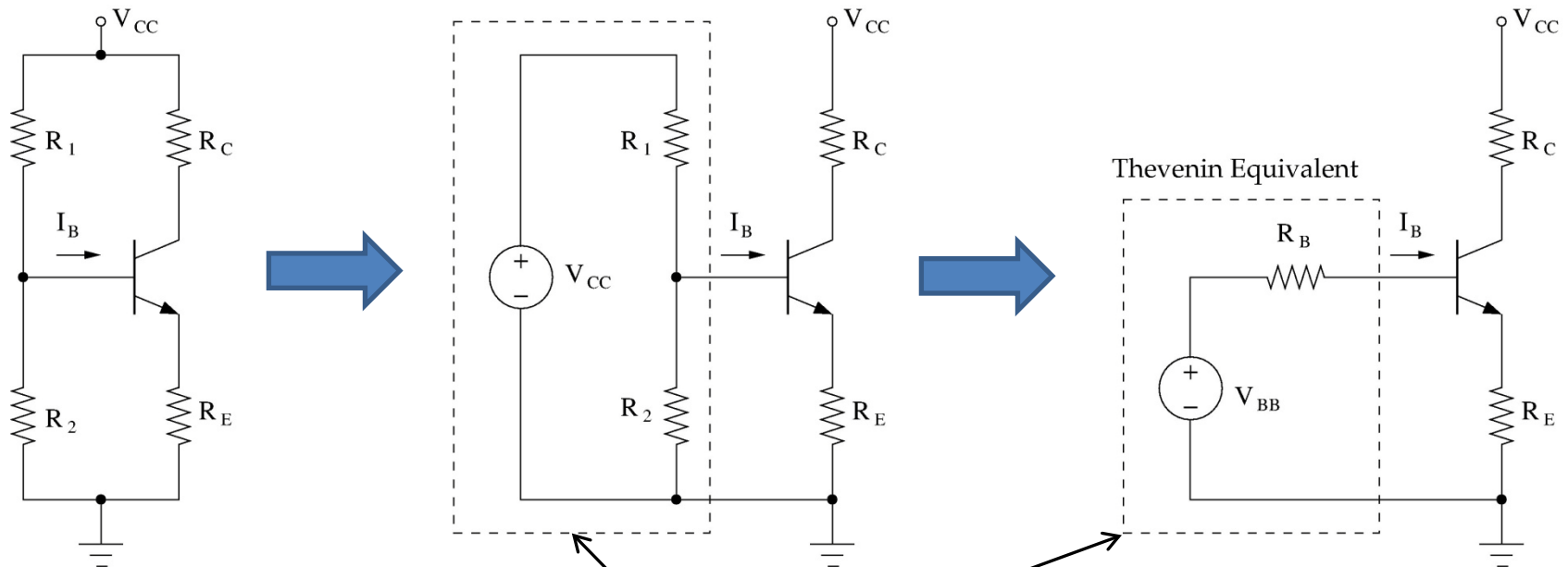

Voltage Divider

$$R_B = R_1 \parallel R_2$$
$$V_{BB} = \frac{R_2}{R_1 + R_2} \times V_{CC}$$

### Exercise 3: Find the bias point of the BJT (Si BJT with $\beta = 200$ and $V_A = \infty$ ).

$$R_B = R_1 \parallel R_2 = 5.9 \text{ k} \parallel 34 \text{ k} = 5.03 \text{ k}$$

$$V_{BB} = \frac{R_2}{R_1 + R_2} \times V_{CC} = \frac{5.9 \text{ k}}{5.9 \text{ k} + 34 \text{ k}} \times 15 = 2.22 \text{ V}$$

Assume BJT is in Active:

$$V_{BE} = 0.7 \text{ V}, I_C > 0 \text{ and } V_{CE} \geq 0.7 \text{ V}$$

$$\text{BE-KVL: } 2.22 = I_B R_B + V_{BE} + I_E R_E$$

$$2.22 = 5.03 \times 10^3 I_E / (\beta + 1) + 0.7 + 510 I_E$$

$$I_E = 2.84 \text{ mA}$$


$$I_C = I_E \times \beta / (\beta + 1) = 2.82 \text{ mA}$$

$$I_B = I_E / (\beta + 1) = 14.1 \text{ } \mu\text{A}$$

$$\text{CE-KVL: } 15 = I_C R_C + V_{CE} + I_E R_E$$

$$15 = 2.82 \times 10^{-3} \times 10^3 + V_{CE} + 2.84 \times 10^{-3} \times 510$$
 
$$V_{CE} = 10.7 \text{ V} > V_{D0} = 0.7 \text{ V}$$



#### Notes:

1. We need to solve the complete BE-KVL as we do not know if  $R_B \ll (\beta + 1)R_E$
2.  $\beta \gg 1$  is a good approximation that reduces the amount of work. Answers using  $\beta \gg 1$  approximation:

$$I_C \approx I_E \approx 2.84 \text{ mA}, I_B = 14.2 \text{ } \mu\text{A}$$

$$V_{CE} = 10.7 \text{ V}$$

**Exercise 4:** Design a BJT bias circuit (emitter degeneration with voltage divider) such that  $I_C = 2.5 \text{ mA}$  and  $V_{CE} = 7.5 \text{ V}$ . ( $V_{CC} = 15 \text{ V}$  Si BJT with  $\beta$  ranging from 50 to 200 and  $V_A = \infty$ ).

**Step 1: Find  $R_C$  and  $R_E$**

CE – KVL:  $15 = I_C R_C + V_{CE} + I_E R_E$


$$15 = 2.5 \times 10^{-3} \times (R_C + R_E) + 7.5$$

$$R_C + R_E = 3.0 \text{ k}$$

Free to choose individual values  $R_E$  &  $R_C$   
(we will see later that amplifier parameters sets the individual values)

Choose:  $R_E = 1.0 \text{ k}$
 
$$R_C = 3.0 \text{ k} - R_E = 2.0 \text{ k}$$



**Circuit  
Prototype**

**Check:**  $I_E R_E \geq 1 \text{ V}$

$$I_E R_E = 2.5 \times 10^{-3} \times 10^3 = 2.5 \geq 1 \text{ V}$$

**Exercise 4 (Cont'd):** Design a BJT bias circuit (emitter degeneration with voltage divider) such that  $I_C = 25 \text{ mA}$  and  $V_{CE} = 5 \text{ V}$ . ( $V_{CC} = 15 \text{ V}$  Si BJT with  $\beta$  ranging from 50 to 200 and  $V_A = \infty$ ).

**Step 2: Find  $R_B$  and  $V_{BB}$**

$$R_B \ll (\beta_{\min} + 1)R_E \rightarrow R_B \leq 0.1 (\beta_{\min} + 1)R_E = 5.1 \text{ k} \rightarrow R_B = 5.1 \text{ k}$$

$\uparrow$   
 Using relative error,  $\varepsilon = 10\%$

$\uparrow$   
 Use largest  $R_B$   
 (Will see later why)

$$V_{BB} = I_B \cancel{R_B} + V_{BE} + I_E R_E$$

$$V_{BB} \approx V_{D0} + I_C R_E = 0.7 + 2.5 \times 10^{-3} \times 10^3 \rightarrow V_{BB} = 3.20 \text{ V}$$

**Step 3: Find  $R_1$  and  $R_2$**

$$R_B = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} = 5.10 \text{ k}$$

$$\frac{V_{BB}}{V_{CC}} = \frac{R_2}{R_1 + R_2} = \frac{3.20}{15} = 0.213$$



$$R_1 = \frac{5.10 \text{ k}}{0.213} = 23.9 \text{ k}$$

$$R_2 = 6.4 \text{ k}$$

**Step 4: Find commercial R values:**

$$R_C = 2 \text{ k}$$

$$R_E = 1 \text{ k}$$

$$R_1 = 24 \text{ k}$$

$$R_2 = 6.4 \text{ k}$$

# Why biasing with base voltage (fixed bias) does not work?

- Changes in BJT  $\beta$  changes the bias point drastically.

- BJT can end up in saturation or in cut-off easily.

- In fixed bias,  $I_B$  is set through 
$$I_B = \frac{V_{BB} - V_{D0}}{R_B}$$


- BJT  $\beta$  then sets  $I_C = \beta I_B$  ( $I_C$  changes with  $\beta$ ).

- CE circuit then sets  $V_{CE}$ .

- But, requirements for BJT in active are on  $I_C$  and  $V_{CE}$  and NOT on  $I_B$


- $I_C > 0$ ,  $V_{CE} > V_{D0}$

 - **To make bias point independent of changes in  $\beta$ , the bias circuit should “set”  $I_C$  and NOT  $I_B$  !**






# Emitter-degeneration bias circuits

 


**Basic Arrangement**

$$V_{BB} = I_B R_B + V_{BE} + I_E R_E$$

 

**Bias with one power supply  
(voltage divider)**

$$V_{BB} = I_B R_B + V_{BE} + I_E R_E$$

 

**Bias with two power supplies**


$$V_{EE} = I_B R_B + V_{BE} + I_E R_E$$

$$0 = I_B R_B + V_{BE} + I_E R_E - V_{EE}$$

# MOS bias with Gate Voltage


$$I_D = 0.5 \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

$$V_{DS} = V_{DD} - I_D R_D$$

 


- This method is NOT desirable as  $\mu_n C_{ox} (W/L)$  and  $V_t$  are not “well-defined.” Bias point (i.e.,  $I_D$  and  $V_{DS}$ ) can change drastically due to temperature and/or manufacturing variability.
  - See S&S Exercise 5.33 (S&S 5<sup>th</sup> Ed: Exercise 4.19): Changing  $V_t$  from 1 to 1.5 V leads to a 75% change in  $I_D$ .
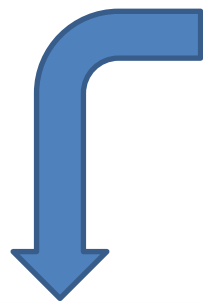
# MOS bias with Source Degeneration (Resistor $R_s$ provides negative feedback!)


 
$$\begin{cases} V_{GS} = V_G - R_s I_D \\ I_D = 0.5 \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2 \end{cases}$$




## Negative Feedback:

- If  $I_D \uparrow$  (because  $\mu_n C_{ox} (W/L) \uparrow$  or  $V_t \downarrow$ )  $\xrightarrow{\text{GS KVL}}$   $V_{GS} \downarrow \xrightarrow{I_D \text{ Eq.}}$   $I_D \downarrow$
- If  $I_D \downarrow$  (because  $\mu_n C_{ox} (W/L) \downarrow$  or  $V_t \uparrow$ )  $\xrightarrow{\text{GS KVL}}$   $V_{GS} \uparrow \xrightarrow{I_D \text{ Eq.}}$   $I_D \uparrow$

➤ Feedback is most effective if  $R_s I_D \gg V_{GS}$


$$V_{GS} - V_G + R_s I_D = 0 \Rightarrow I_D \approx V_G / R_s$$

# Source-degeneration bias circuits

 


**Basic Arrangement**

$$V_G = V_{GS} + I_D R_S$$

 

**Bias with one power supply  
(voltage divider)**

$$V_G = V_{GS} + I_D R_S$$

 

**Bias with two power supplies**

$$V_{SS} = V_{GS} + I_D R_S$$

↑

$$0 = V_{GS} + I_D R_S - V_{SS}$$

**Exercise 5:** Find the bias point for  $V_t = 1 \text{ V}$  and  $\mu_n C_{ox} (W/L) = 1.0 \text{ mA/V}^2$  (Ignore channel-width modulation).

Voltage divider ( $I_G = 0$ )

$$V_G = (7)/(7+8) \times 15 = 7 \text{ V}$$

$$I_D = 0.5 \mu_n C_{ox} \frac{W}{L} V_{OV}^2$$

$$\text{GS-KVL: } V_G = 7 = V_{GS} + R_S I_D$$

$$V_{OV} + V_t + R_S I_D = 7$$

$$V_{OV} + 1 + 10^4 \times (0.5 \times 10^{-3} V_{OV}^2) = 7$$

$$5V_{OV}^2 + V_{OV} - 6 = 0 \rightarrow V_{OV} = 1 \text{ V}$$

$$V_{GS} = V_{OV} + 1 = 2 \text{ V}$$


$$V_S = V_G - V_{GS} = 7 - 2 = 5 \text{ V}$$

$$I_D = V_S / R_S = 0.5 \text{ mA}$$

$$\text{DS-KVL: } 15 = R_D I_D + V_D$$

$$V_D = 15 - R_D I_D = 10 \text{ V}$$

$$V_{DS} = V_D - V_S = 5 \text{ V}$$

 


**Exercise (impact of  $R_S$ ):** Prove that if  $V_t = 1.5 \text{ V}$  (50% change),  $I_D = 0.455 \text{ mA}$  (9% change)


# Biasing in ICs

- Resistors take too much space on the chip. So, biasing with emitter or source degeneration are NOT implemented in ICs.
- Recall that the goal of a good bias is to ensure that  $I_C$  and  $V_{CE}$  (or  $I_D$  and  $V_{DS}$  for MOS) do not change. One can force  $I_C$  (or  $I_D$  for MOS) to be constant using a current source.


Current source  
forces  $I_E = I$

 

Current source  
forces  $I_D = I$

 

# BJT response to a current source

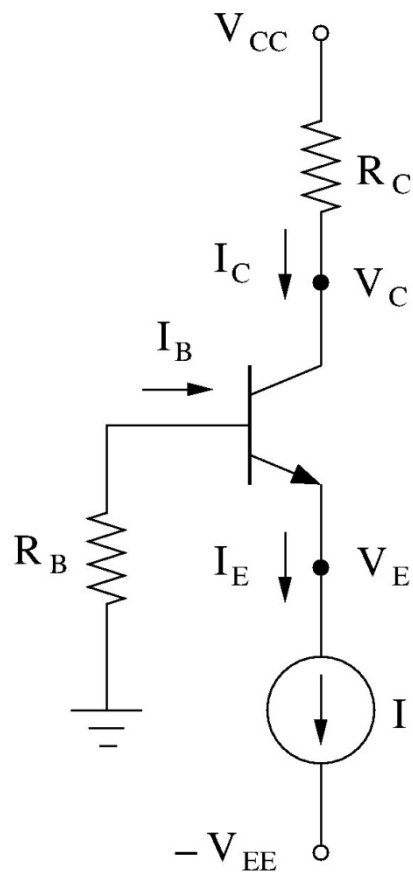

1) Current source forces:

$$I_C \approx I_E = I$$

$$2) I_B = I_C / \beta$$


$$3A) V_C = V_{CC} - R_C I_C$$

3B)  $V_E$  is set by BE-KVL

$$0 = R_B I_B + V_{BE} + V_E$$

$$4) V_{CE} = V_C - V_E$$

# MOS response to a current source

 

1) Current source forces:

$$I_D = I$$

2)  $V_{GS}$  is set by

$$I_D = 0.5 \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

3A)  $V_D = V_{DD} - R_D I_D$

3B)  $V_S = V_G - V_{GS} = -V_{GS}$

4)  $V_{DS} = V_D - V_S$



# Current Mirrors (or Current Steering circuits) are used as current sources for biasing ICs

- $Q_{ref}$  is always in active since

$$i_{C,ref} > 0$$


$$V_{CE,ref} = V_{BE,ref} = V_{D0}$$

- **Identical BJTs and  $v_{BE,ref} = v_{BE1}$** 
  - BJTs will have the same  $i_B$  and the same  $i_C$  (ignoring Early effect)

$$\text{KCL: } I_{ref} = i_{C,ref} + 2i_B = i_C + 2\frac{i_C}{\beta}$$

$$I_1 = i_C = \frac{I_{ref}}{1 + 2/\beta} \approx I_{ref}$$

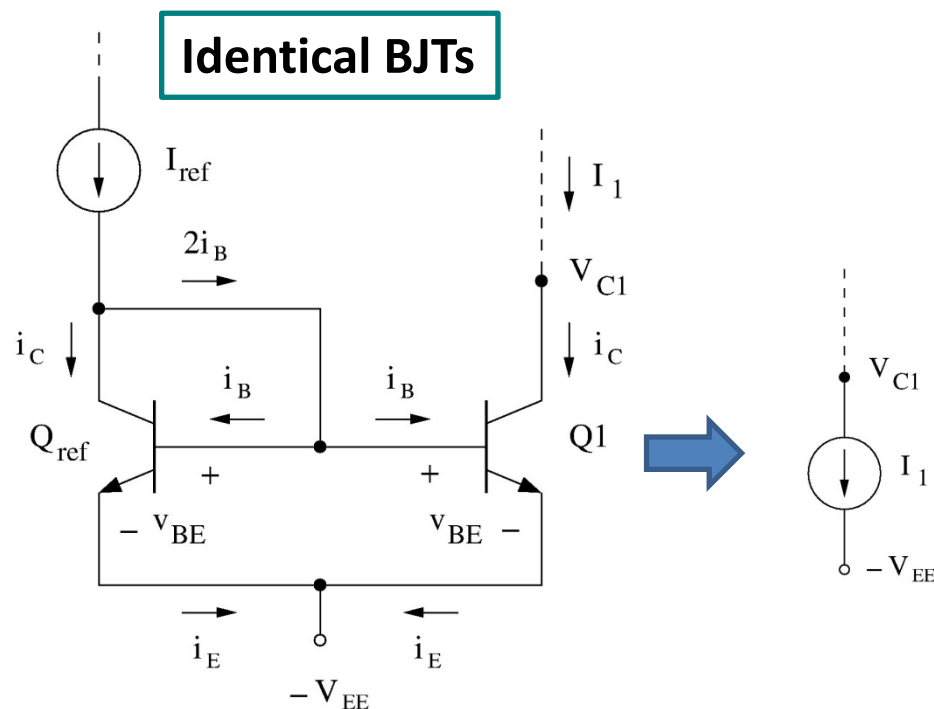- Since  $I_1 = \text{const.}$  regardless of  $V_{C1}$ , this is a current source!




- **For the current mirror to work,  $Q_1$  should be in active:**

$$V_{CE1} = V_{C1} + V_{EE} \geq V_{D0}$$

# An implementation of a BJT Current Mirror


BE-KVL ( $Q_{ref}$ ):  $V_{CC} = R I_{ref} + V_{BE} - V_{EE}$

$$I_1 \approx I_{ref} = \frac{V_{CC} + V_{EE} - V_{BE}}{R}$$

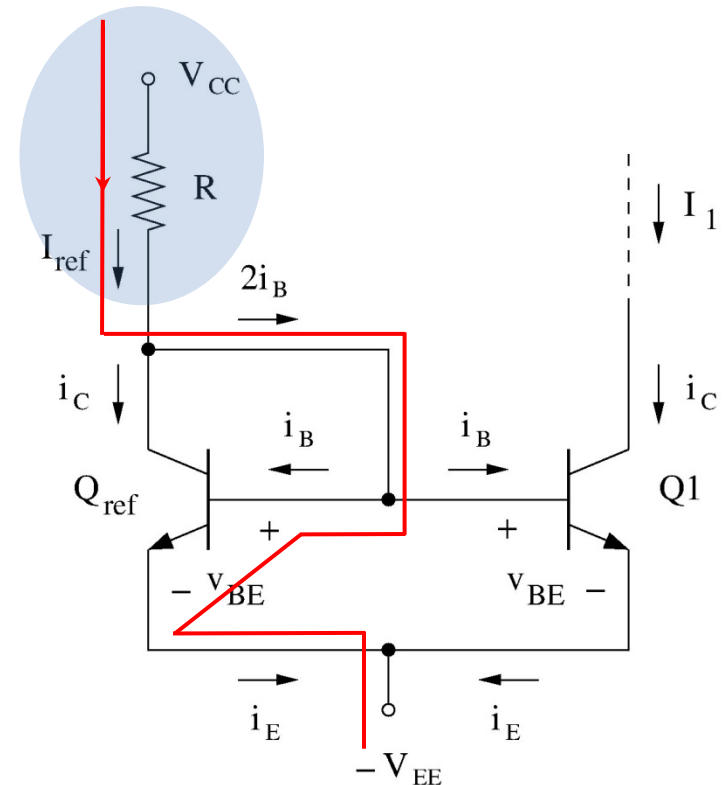

Exercise 6: Find the bias point of Q2 (Si BJT with  $\beta = 100$  and  $V_A = \infty$ ).


Current Mirror

 

$$5 = 2 \times 10^3 I_{ref} + V_{BE} - 5$$

$$I_{ref} = 4.65 \text{ mA}$$
 
$$I_1 \approx I_{ref} = 4.65 \text{ mA}$$



Assume Q2 in active:

$$I_{C2} \approx I_{E2} = I_1 \approx 4.65 \text{ mA}$$

$$I_{B2} = I_{C2} / \beta \approx 46.5 \text{ } \mu\text{A}$$

$$\text{BE2-KVL: } 0 = 10 \times 10^3 I_{B2} + V_{BE2} + V_{E2}$$

$$0 = 10 \times 10^3 \times 46.5 \times 10^{-6} + 0.7 + V_{E2}$$

$$V_{C1} = V_{E2} = -1.165 \text{ V}$$

$$\text{CE2-KVL: } 5 = 10^3 I_{C2} + V_{CE2} + V_{E2}$$

$$V_{CE2} = 5 - 10^3 \times 4.65 \times 10^{-3} - 1.165$$

$$V_{CE2} = 1.56 \text{ V}$$

$$V_{CE2} = 1.56 > V_{D0} = 0.7 \text{ V} \quad \text{Q2 in active!}$$


Check Q1 in active:

$$V_{CE1} = V_{C1} - (-5) = -1.165 + 5 = 3.835 \text{ V}$$


$$V_{CE1} = 3.835 > V_{D0} = 0.7 \text{ V}$$
 
# Examples of BJT current mirrors


- One “reference” BJT feeds many current mirrors
- Integer multiple of  $I_{ref}$  can be made (See Q3 & Q4)



## PNP current Mirror

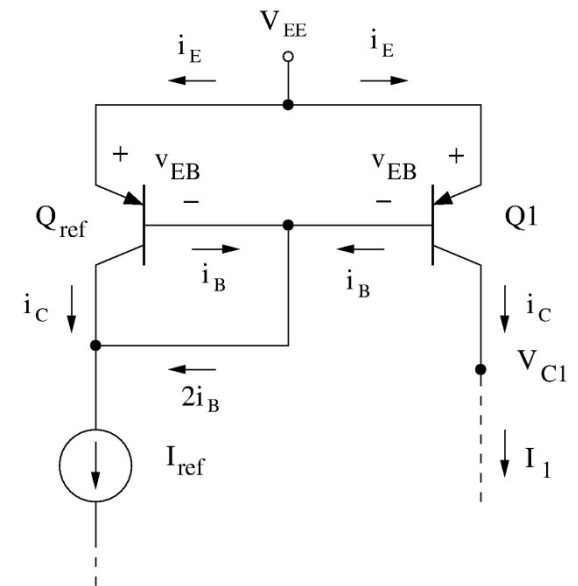

# MOS Current-Steering Circuit

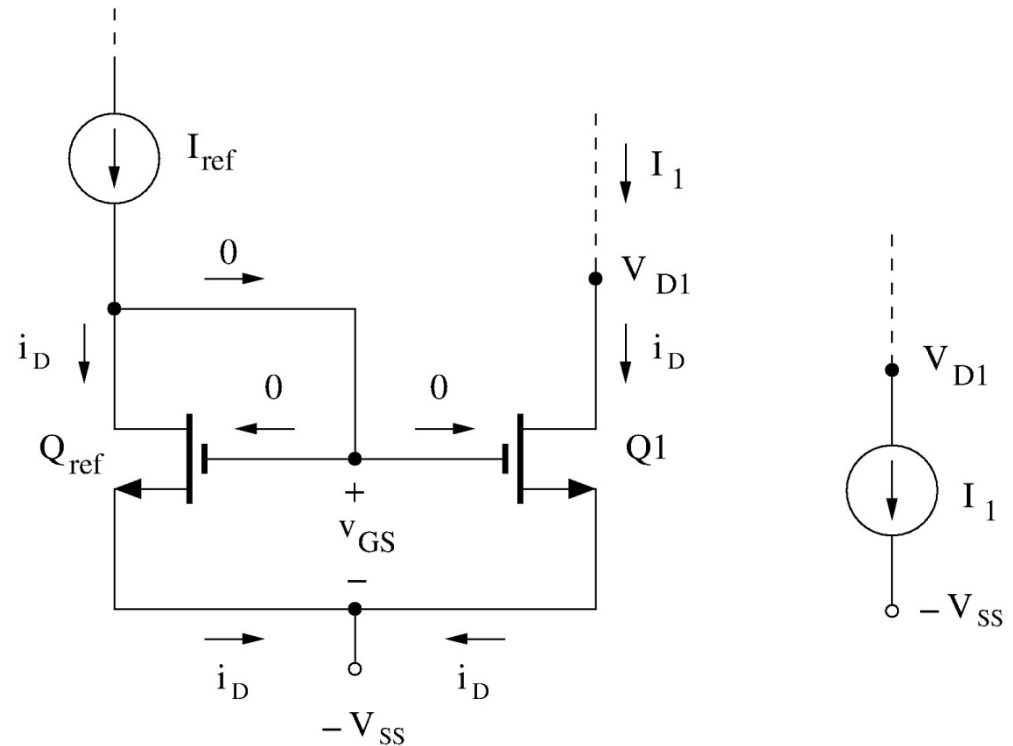

# An implementation of a MOS current steering circuit


$$I_{ref} = i_D = 0.5\mu_n C_{ox} (W/L)_{ref} V_{OV}^2$$

$$\text{GS-KVL } (Q_{ref}): V_{DD} = Ri_D + v_{GS} - V_{SS}$$

$$Ri_D + V_{OV} - V_{SS} - V_{DD} + V_t = 0$$

$$[0.5\mu_n C_{ox} (W/L)_{ref} R] V_{OV}^2 + V_{OV} + [-V_{SS} - V_{DD} + V_t] = 0$$

 
The above quadratic equation gives  $V_{OV}$ .  
 $I_1$  is then found from the MOS  $i_D$  equation.



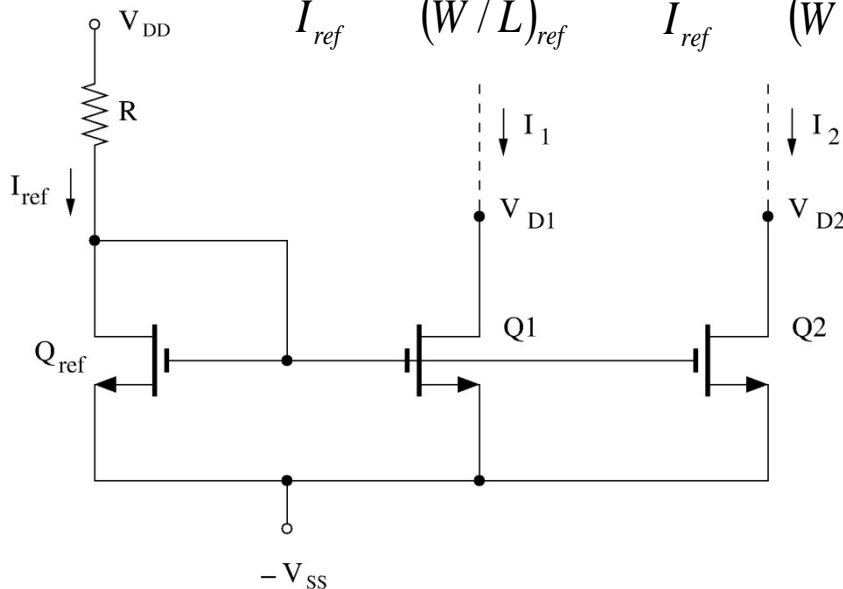
# Examples of MOS current steering circuits

- One “reference” MOS feeds many current steering circuits.
- Any value of  $I_{ref}$  can be made (thus, current-steering circuit instead of current-mirror)


$$\frac{I_1}{I_{ref}} = \frac{(W/L)_1}{(W/L)_{ref}} \quad \frac{I_2}{I_{ref}} = \frac{(W/L)_2}{(W/L)_{ref}}$$



## PMOS current steering circuit

 
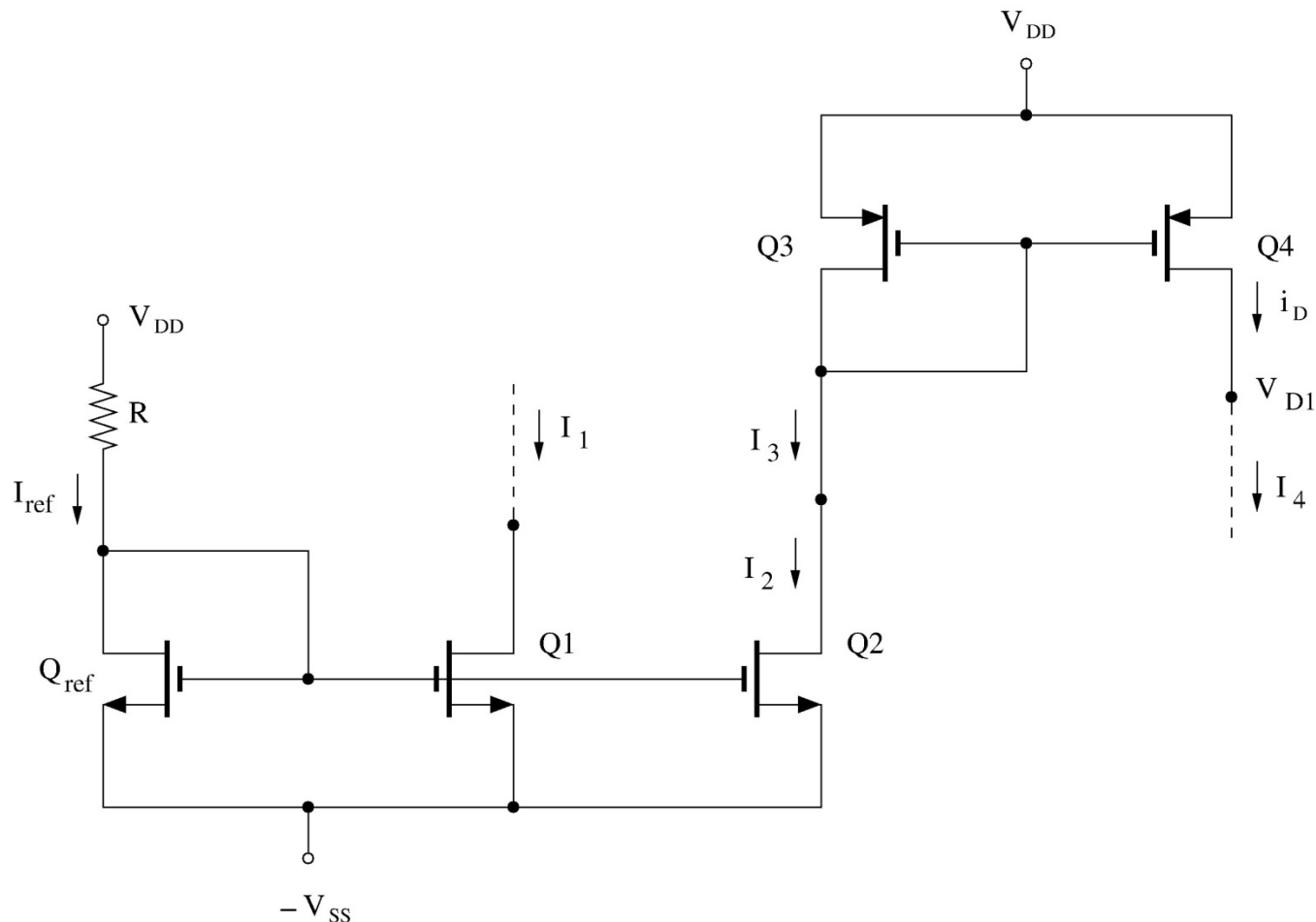
# An implementation of current steering circuit to bias several transistors in an IC



**Exercise:** Compute  $I_4/I_{ref}$