

## **6. Introduction to Transistor Amplifiers: Concepts and Small-Signal Model**


Lecture notes: Sec. 5

Sedra & Smith (6<sup>th</sup> Ed): Sec. 5.4, 5.6 & 6.3-6.4

Sedra & Smith (5<sup>th</sup> Ed): Sec. 4.4, 4.6 & 5.3-5.4

 
# Foundation of Transistor Amplifiers (1)

- A voltage amplifier requires  $v_o/v_i = \text{const.}$  (2 examples below)



- $v_o/v_i$  can be negative (minus sign represents a  $180^\circ$  phase shift)


- MOS transfer function is NOT linear

 

- In saturation, however, transfer function looks linear (but shifted)
 
# Foundation of Transistor Amplifiers (2)

- In saturation, transfer function appear to be linear



Approximate the transfer function with a tangent line at point Q (with a slope of  $-A$ ):

$$v_{DS} - V_{DS} = -A (v_{GS} - V_{GS})$$


$$v_{ds} = -A v_{gs} \quad (\text{linear relationship})$$

for  $v_{ds} = v_{DS} - V_{DS}$  and  $v_{gs} = v_{GS} - V_{GS}$



# Foundation of Transistor Amplifiers (3)

- Let us consider the response if NMOS remains in saturation at all times and  $v_{GS}$  is a combination of a **constant value** ( $V_{GS}$ ) and a **signal** ( $v_{gs}$ ):


$$v_{GS} = V_{GS} + v_{gs}$$

 

  The response to a combination of  $v_{GS} = V_{GS} + v_{gs}$  can be found from the transfer function


 
# Response to the signal appears to be linear



- Response ( $v_o = v_{DS}$ ) is also made of a constant part ( $V_{DS}$ ) and a signal response part ( $v_{ds}$ ).
- Constant part of the response,  $V_{DS}$ , is ONLY related to  $V_{GS}$ , the constant part of the input (Q point on the transfer function of previous slide).
  - i.e., if  $v_{gs} = 0$ , then  $v_{ds} = 0$
- The shape of the time varying portion of the response ( $v_{ds}$ ) is similar to  $v_{gs}$ .
  - i.e.,  $v_{ds}$  is proportional to the input signal,  $v_{gs}$

# Although the overall response is non-linear, the transfer function for the signal is linear!

Constant:  
Bias

Signal and  
response


$$v_{GS} = V_{GS} + v_{gs}$$

$$v_{DS} = V_{DS} + v_{ds}$$

$$i_D = I_D + i_d$$

Non-linear  
relationship among  
these parameters

 Approximately  
Linear  
relationship among  
these parameters



# Important Points and Definitions!

- **Signal:** We want the response of the circuit to this input.
- **Bias:** State of the system when there is no signal.
  - Bias is constant in time (may vary extremely slowly compared to signal)
  - Purpose of the bias is to ensure that MOS is in saturation at all times.
- **Response** of the circuit (and its elements) to the signal is different than its response to the Bias (or to Bias + signal):
  - Signal  $iV$  characteristics of elements are different, i.e. relationships among  $v_{gs}$ ,  $v_{ds}$ ,  $i_d$  is different from relationships among  $v_{GS}$ ,  $v_{DS}$ ,  $i_D$ .
  - Signal transfer function of the circuit is different from the transfer function for total input (Bias + signal).

**Above observations & conclusions equally apply to a BJT in the active mode!**



# Issues in developing a transistor amplifier:


- 1. Find the  $iv$  characteristics of the elements for the signal** (which can be different than their characteristics equation for bias).
  - This will lead to different circuit configurations for bias versus signal
- 2. Compute circuit response to the signal**
  - Focus on fundamental transistor amplifier configurations
- 3. How to establish a Bias point** (bias is the state of the system when there is no signal).
  - Stable and robust bias point should be resilient to variations in  $\mu_n C_{ox} (W/L), V_t$  (or  $\beta$  for BJT) due to temperature and/or manufacturing variability.
  - Bias point details impact small signal response (e.g., gain of the amplifier).

# Signal Circuit

- 1) We will find signal  $iv$  characteristics of various elements.
- 2) In order to use circuit theory tools, we will use the signal  $iv$  characteristics of various elements to assign a circuit symbol. e.g.,
  - We will see that the diode signal  $iv$  characteristics is linear so for signals, diode can be modeled as a “circuit theory” resistor.
  - In this manner, we will arrive at a signal circuit.

# Bias and Signal Circuits

**Bias & Signal**

 

$$\text{MOS : } v_{GS}, v_{DS}, i_D,$$


$$(v_{GS} = V_{GS} + v_{gs}, \dots)$$

$$R_D : \quad v_R = V_R + v_r$$

$$i_R = I_R + i_r$$

.....

**Bias**

 


$$\text{MOS : } V_{GS}, V_{DS}, I_D,$$

$$R_D : \quad V_R, I_R$$

.....

 **Signal only**

$$= (\text{Bias} + \text{Signal}) - \text{Bias}$$



$$\text{MOS : } v_{gs}, v_{ds}, i_d,$$

$$R_D : \quad v_r, i_r$$

.....

# Finding signal circuit elements -- Resistor

Resistor	Voltage	Current	iv Equation
Bias + Signal:	$v_R$	$i_R$	$v_R = R i_R$
Bias:	$V_R$	$I_R$	$V_R = R I_R$
Signal:	$v_r = v_R - V_R$	$i_r = i_R - I_R$	??



$$v_r = v_R - V_R = R i_R - R I_R = R (i_R - I_R) \quad \Rightarrow \quad v_r = R i_r$$

➤ A resistor remains as a resistor in the signal circuit.

# Finding signal circuit elements -- Capacitor

Capacitor	Voltage	Current	iv Equation
Bias + Signal:	$v_C$	$i_C$	$i_C = C dv_C / dt$
Bias:	$V_C$	$I_C$	$I_C = C dV_C / dt$
Signal:	$v_c = v_C - V_C$	$i_c = i_C - I_C$	??

$$i_c = i_C - I_C = C \frac{dv_C}{dt} - C \frac{dV_C}{dt} = C \frac{d(v_C - V_C)}{dt} \quad \Rightarrow \quad i_c = C \frac{dv_c}{dt}$$

- **A capacitor remains as a capacitor in the signal circuit.**
  - Since  $V_C = \text{const.}$ ,  $I_C = 0$  ,  
**i.e., A capacitor acts as an open circuit for bias circuit.**

# Finding signal circuit elements – IVS & ICS

Independent voltage source	Voltage	Current	iv Equation
<b>Bias + Signal:</b>	$v_{IVS}$	$i_{IVS}$	$v_{IVS} = V_{DD} = \text{const}$
<b>Bias:</b>	$V_{IVS}$	$I_{IVS}$	$V_{IVS} = V_{DD} = \text{const}$
<b>Signal:</b>	$v_{ivs} = v_{IVS} - V_{IVS}$	$i_{ivs} = i_{IVS} - I_{IVS}$	??

$$v_{ivs} = v_{IVS} - V_{IVS} = V_{DD} - V_{DD} = 0$$



$$v_{ivs} = 0, \quad i_{ivs} \neq 0$$



➤ **An independent voltage source becomes a short circuit!**

Similarly:

➤ **An independent current source becomes an open circuit!**

**Exercise:** Show that dependent sources remain as dependent sources

# Summary of signal circuit elements

- |   |  |
|---|--|
| ➤ <b>Resistors&amp; capacitors:</b>                               | <u><b>The Same</b></u>                 |
| ○ Capacitor act as open circuit in the bias circuit.              |  |
| ➤ <b>Independent voltage source (e.g., <math>V_{DD}</math>) :</b> | <u><b>Effectively grounded</b></u>     |
| ➤ <b>Independent current source:</b>                              | <u><b>Effectively open circuit</b></u> |
| ➤ <b>Dependent sources:</b>                                       | <u><b>The Same</b></u>                 |
| ➤ <b>Non-linear Elements:</b>                                     | <u><b>Different!</b></u>               |
| ○ Diodes & transistors ?  |  |

# Diode Signal Response




Bias + Signal:  $i_D = I_s \exp\left(\frac{v_D}{nV_T}\right)$

Bias:  $I_D = I_s \exp\left(\frac{V_D}{nV_T}\right)$

Signal:  $i_d = i_D - I_D = I_s \exp\left(\frac{V_D + v_d}{nV_T}\right) - I_s \exp\left(\frac{V_D}{nV_T}\right)$

$$i_d = I_s \exp\left(\frac{V_D}{nV_T}\right) \times \left[ \exp\left(\frac{v_d}{nV_T}\right) - 1 \right]$$
   
$$i_d = I_D \times \left[ \exp\left(\frac{v_d}{nV_T}\right) - 1 \right]$$




- A different iv equation!
- iv equation is non-linear!
- Related to bias value,  $I_D$ !




 
# Diode small-signal model:

$$i_d = I_D \times \left[ \exp\left(\frac{v_d}{nV_T}\right) - 1 \right]$$



Taylor Series Expansion :  $\exp\left(\frac{v_d}{nV_T}\right) = 1 + \left(\frac{v_d}{nV_T}\right) + \frac{1}{2!}\left(\frac{v_d}{nV_T}\right)^2 + \dots$

If  $\frac{v_d}{nV_T} \ll 1$ :  $\exp\left(\frac{v_d}{nV_T}\right) \approx 1 + \left(\frac{v_d}{nV_T}\right)$

$$i_d \approx I_D \times \left[ 1 + \left(\frac{v_d}{nV_T}\right) - 1 \right] = \left(\frac{I_D}{nV_T}\right) v_d$$

$$v_d = \frac{nV_T}{I_D} i_d = r_d i_d$$

# Formal derivation of small signal model

- Signal + Bias for element A ( $i_A, v_A$ ) :  $i_A = f(v_A)$
- Bias for element A ( $I_A, V_A$ ) :  $I_A = f(V_A)$
- Signal for element A ( $i_a, v_a$ ) :  $i_a = g(v_a)$

$$i_A = f(v_A)$$

$$= f(V_A) + f^{(1)}(V_A) \cdot (v_A - V_A) + \frac{f^{(2)}(V_A)}{2!} \cdot (v_A - V_A)^2 + \dots \quad (\text{Taylor Series Expansion})$$

$$= f(V_A) + f^{(1)}(V_A) \cdot v_a + \frac{f^{(2)}(V_A)}{2!} \cdot v_a^2 + \dots$$

$$\approx f(V_A) + f^{(1)}(V_A) \cdot v_a$$

$$i_A = i_a + I_A = I_A + f^{(1)}(V_A) \cdot v_a$$

$$i_a = g(v_a) = f^{(1)}(V_A) \cdot v_a$$

**Small signal means:**

$$\left| f^{(1)}(V_A) \cdot v_a \right| \gg \left| \frac{f^{(2)}(V_A)}{2!} \cdot v_a^2 \right|$$

$$\left| v_a \right| \ll 2 \cdot \left| \frac{f^{(1)}(V_A)}{f^{(2)}(V_A)} \right|$$

# Derivation of diode small signal model


$$i_D = I_S \cdot \left( e^{\frac{v_D}{nV_T}} - 1 \right) = f(v_D) \quad \longleftrightarrow \quad f(v) = I_S \left( e^{\frac{v}{nV_T}} - 1 \right) \quad f^{(1)}(v) = \frac{1}{nV_T} \times I_S e^{\frac{v}{nV_T}}$$

$$I_D = f(V_D) = I_S \cdot \left( e^{\frac{V_D}{nV_T}} - 1 \right) = I_S e^{\frac{V_D}{nV_T}} - I_S$$


$$i_d = f^{(1)}(V_D) \times v_d = \left[ \frac{I_S \cdot e^{\frac{V_D}{nV_T}}}{nV_T} \right]_{v=V_D} \times v_d = \left[ \frac{I_S \cdot e^{\frac{V_D}{nV_T}}}{nV_T} \right] \times v_d = \left[ \frac{I_D + I_S}{nV_T} \right] \times v_d$$

$$i_d = \left[ \frac{I_D + I_S}{nV_T} \right] \times v_d \approx \left[ \frac{I_D}{nV_T} \right] \times v_d$$
 
$$i_d = \frac{v_d}{r_d} \quad r_d \approx \frac{nV_T}{I_D}$$



 Diode can be replaced with a resistor in the signal circuit!




# Small signal model vs $i_v$ characteristics

Small signal model is equivalent to approximating the non-linear  $i_v$  characteristics curve by a line tangent to the  $i_v$  curve at the bias point

$$i_d = f^{(1)}(V_D) \times v_d$$
 
$$r_d = \frac{1}{f^{(1)}(V_D)} \approx \frac{nV_T}{I_D}$$



# Derivation of MOS small signal model (1)

$$\text{MOS iv equations: } \begin{aligned} i_D &= f(v_{GS}, v_{DS}) \\ i_G &= 0 \end{aligned}$$

- Signal + Bias for MOS ( $i_D, v_{GS}, v_{DS}$ ) :  $i_D = f(v_{GS}, v_{DS}), \quad i_G = 0$
- Bias for MOS ( $I_D, V_{GS}, V_{DS}$ ) :  $I_D = f(V_{GS}, V_{DS}), \quad I_G = 0$
- Signal for MOS ( $i_d, v_{gs}, v_{ds}$ ) :  $i_d = g(v_{gs}, v_{ds}), \quad i_g = 0$

$$I_D + i_d = i_D = f(v_{GS}, v_{DS})$$

(Taylor Series Expansion in 2 variables)

$$\begin{aligned} &= f(V_{GS}, V_{DS}) + \left. \frac{\partial f}{\partial v_{GS}} \right|_{V_{GS}, V_{DS}} \cdot (v_{GS} - V_{GS}) + \left. \frac{\partial f}{\partial v_{DS}} \right|_{V_{GS}, V_{DS}} \cdot (v_{DS} - V_{DS}) + \dots \\ &\approx I_D + \left. \frac{\partial f}{\partial v_{GS}} \right|_{V_{GS}, V_{DS}} \times v_{gs} + \left. \frac{\partial f}{\partial v_{DS}} \right|_{V_{GS}, V_{DS}} \times v_{ds} \end{aligned}$$



$$i_d \approx \left. \frac{\partial f}{\partial v_{GS}} \right|_{V_{GS}, V_{DS}} \times v_{gs} + \left. \frac{\partial f}{\partial v_{DS}} \right|_{V_{GS}, V_{DS}} \times v_{ds}$$

# Derivation of MOS small signal model (2)

$$i_D = 0.5\mu_n C_{ox} \frac{W}{L} (v_{GS} - V_t)^2 (1 + \lambda v_{DS}) = f(v_{GS}, v_{DS})$$


$$i_d = \left. \frac{\partial f}{\partial v_{GS}} \right|_{V_{GS}, V_{DS}} \cdot v_{gs} + \left. \frac{\partial f}{\partial v_{DS}} \right|_{V_{GS}, V_{DS}} \cdot v_{ds}$$

$$\begin{aligned} \left. \frac{\partial f}{\partial v_{GS}} \right|_{V_{GS}, V_{DS}} &= 2 \times 0.5\mu_n C_{ox} \frac{W}{L} (v_{GS} - V_t)(1 + \lambda v_{DS}) \Big|_{V_{GS}, V_{DS}} \\ &= 2 \times \frac{0.5\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS})}{(V_{GS} - V_t)} = \frac{2I_D}{V_{OV}} \equiv g_m \end{aligned}$$


$$\begin{aligned} \left. \frac{\partial f}{\partial v_{DS}} \right|_{V_{GS}, V_{DS}} &= \lambda \times 0.5\mu_n C_{ox} \frac{W}{L} (v_{GS} - V_t)^2 \Big|_{V_{GS}, V_{DS}} \\ &= \lambda \times \frac{0.5\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS})}{(1 + \lambda V_{DS})} = \frac{\lambda I_D}{(1 + \lambda V_{DS})} \approx \lambda I_D \equiv \frac{1}{r_o} \end{aligned}$$

$$i_d = g_m \cdot v_{gs} + \frac{v_{ds}}{r_o} \quad i_g = 0$$

# MOS small signal “circuit” model

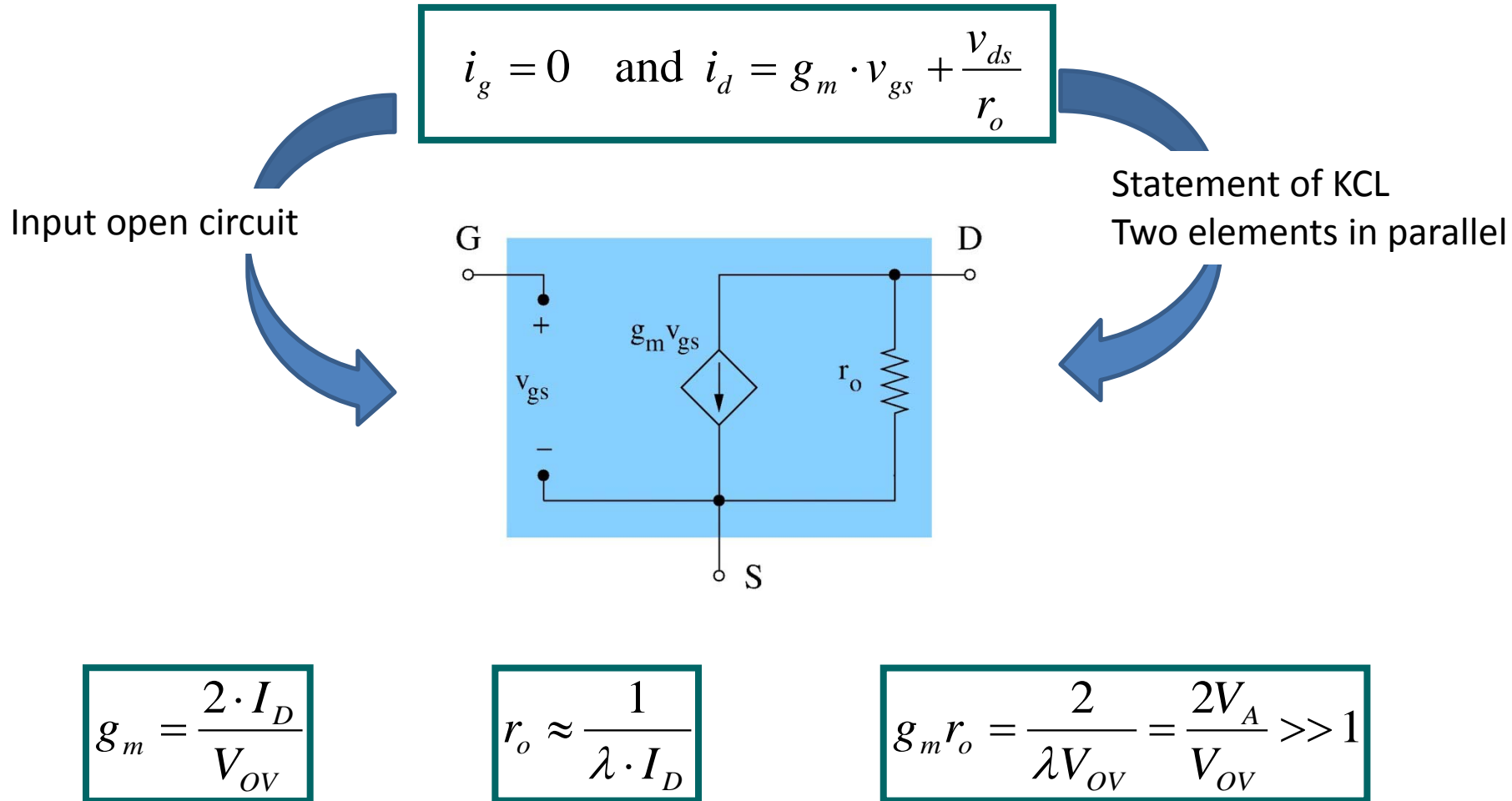
 
# PMOS small signal model is identical to NMOS



## ➤ PMOS small-signal circuit model is identical to NMOS

- We will use NMOS circuit model for both!
- For both NMOS and PMOS, while  $i_D \geq 0$  and  $I_D \geq 0$ , signal quantities:  $i_d$ ,  $v_{gs}$ , and  $v_{ds}$ , can be negative!

**Exercise:** Derive PMOS small signal model (follow derivation of NMOS small-signal model)



# Derivation of BJT small signal model (1)

BJT iv equations:

$$i_B = f_1(v_{BE})$$

$$i_C = f_2(v_{BE}, v_{CE})$$

$$i_B = (I_s / \beta) e^{\frac{v_{BE}}{V_T}}$$

$$i_C = I_s e^{\frac{v_{BE}}{V_T}} \left( 1 + \frac{v_{CE}}{V_A} \right)$$

- Signal + Bias for BJT ( $i_B, i_C, v_{BE}, v_{CE}$ ) :
 
$$i_B = f_1(v_{BE}),$$

$$i_C = f_2(v_{BE}, v_{CE})$$
- Bias for BJT ( $I_B, I_C, V_{BE}, V_{CE}$ ) :
 
$$I_B = f_1(V_{BE}),$$

$$I_C = f_2(V_{BE}, V_{CE})$$
- Signal for BJT ( $i_b, i_c, v_{be}, v_{ce}$ ) :
 
$$i_b = g_1(v_{be}),$$

$$i_c = g_2(v_{be}, v_{ce})$$

We need to perform Taylor Series Expansion in 2 variables for both  $i_B$  and  $i_C$ .

$$i_b \approx \left. \frac{df_1}{dv_{BE}} \right|_{V_{BE}, V_{CE}} \times v_{be}$$

$$i_c \approx \left. \frac{\partial f_2}{\partial v_{BE}} \right|_{V_{BE}, V_{CE}} \times v_{be} + \left. \frac{\partial f_2}{\partial v_{DCE}} \right|_{V_{BE}, V_{CE}} \times v_{ce}$$

# Derivation of BJT small signal model (2)

$$i_B = (I_s / \beta) e^{\frac{v_{BE}}{V_T}} = f_1(v_{BE})$$

$$I_B = (I_s / \beta) e^{\frac{V_{BE}}{V_T}}$$

$$\left. \frac{df_1}{dv_{BE}} \right|_{V_{BE}, V_{CE}} = \frac{1}{V_T} (I_s / \beta) e^{\frac{v_{BE}}{V_T}} \bigg|_{V_{BE}} = \frac{I_B}{V_T} \equiv \frac{1}{r_\pi}$$

$$i_b \approx \left. \frac{df_1}{dv_{BE}} \right|_{V_{BE}, V_{CE}} \times v_{be} = \frac{1}{r_\pi} \times v_{be}$$

$$i_C = I_s e^{\frac{v_{BE}}{V_T}} \left( 1 + \frac{v_{CE}}{V_A} \right)$$

$$I_C = I_s e^{\frac{V_{BE}}{V_T}} \left( 1 + \frac{V_{CE}}{V_A} \right) = I_s e^{\frac{V_{BE}}{V_T}} \times \frac{V_A + V_{CE}}{V_A}$$

$$\left. \frac{df_2}{dv_{BE}} \right|_{V_{BE}, V_{CE}} = \frac{I_s}{V_T} e^{\frac{v_{BE}}{V_T}} \left( 1 + \frac{v_{CE}}{V_A} \right) \bigg|_{V_{BE}, V_{CE}} = \frac{I_C}{V_T} \equiv g_m$$

$$\left. \frac{df_2}{dv_{CE}} \right|_{V_{BE}, V_{CE}} = \frac{I_s}{V_A} e^{\frac{v_{BE}}{V_T}} \bigg|_{V_{BE}, V_{CE}} = \frac{I_C}{V_A + V_{CE}} \equiv \frac{1}{r_o}$$



$$i_b = \frac{v_{be}}{r_\pi} \quad i_c = g_m v_{be} + \frac{v_{ce}}{r_o}$$

# BJT small signal “circuit” model


$$i_b = \frac{v_{be}}{r_\pi} \quad i_c = g_m v_{be} + \frac{v_{ce}}{r_o}$$

A resistor,  $r_\pi$ ,  
between B & E

$$r_\pi = \frac{V_T}{I_B}$$

We follow S&S:

$v_{be}$  is denoted as  $v_\pi$

 

Statement of KCL  
Two elements in parallel


$$g_m = \frac{I_C}{V_T}$$

$$r_o = \frac{V_A + V_{CE}}{I_C} \approx \frac{V_A}{I_C}$$


Similar to NMOS/PMOS, the small circuit model  
for a PNP BJT is the same as that of a NPN.

# Alternative BJT small signal “circuit” model

$g_m$  Model

 

$\beta i_b$  Model

 


$$g_m = \frac{I_C}{V_T} = \frac{I_C}{I_B} \times \frac{I_B}{V_T} = \frac{\beta}{r_\pi}$$
$$g_m v_\pi = \frac{\beta}{r_\pi} \times v_\pi = \beta i_\pi$$


# Summary of transistor small signal models

$$g_m = \frac{2 \cdot I_D}{V_{OV}} \quad r_o \approx \frac{1}{\lambda \cdot I_D}$$

 
Example 1: Construct the signal circuit and replace the transistor with its small-signal model (assume capacitors are short for signal).



 
IVS  $\rightarrow 0$   
R remains  
Caps short




Ground at the bottom

 


Replace MOS with its  
small signal model

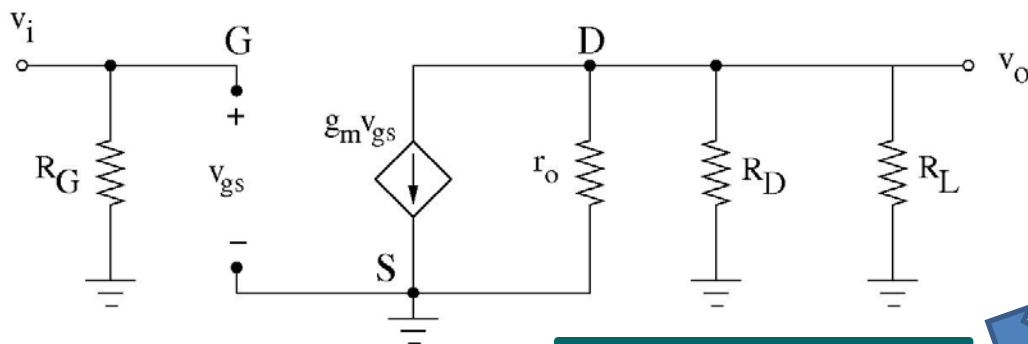

Example 2: Construct the signal circuit and replace the transistor with its small-signal model (assume capacitors are short for signal).

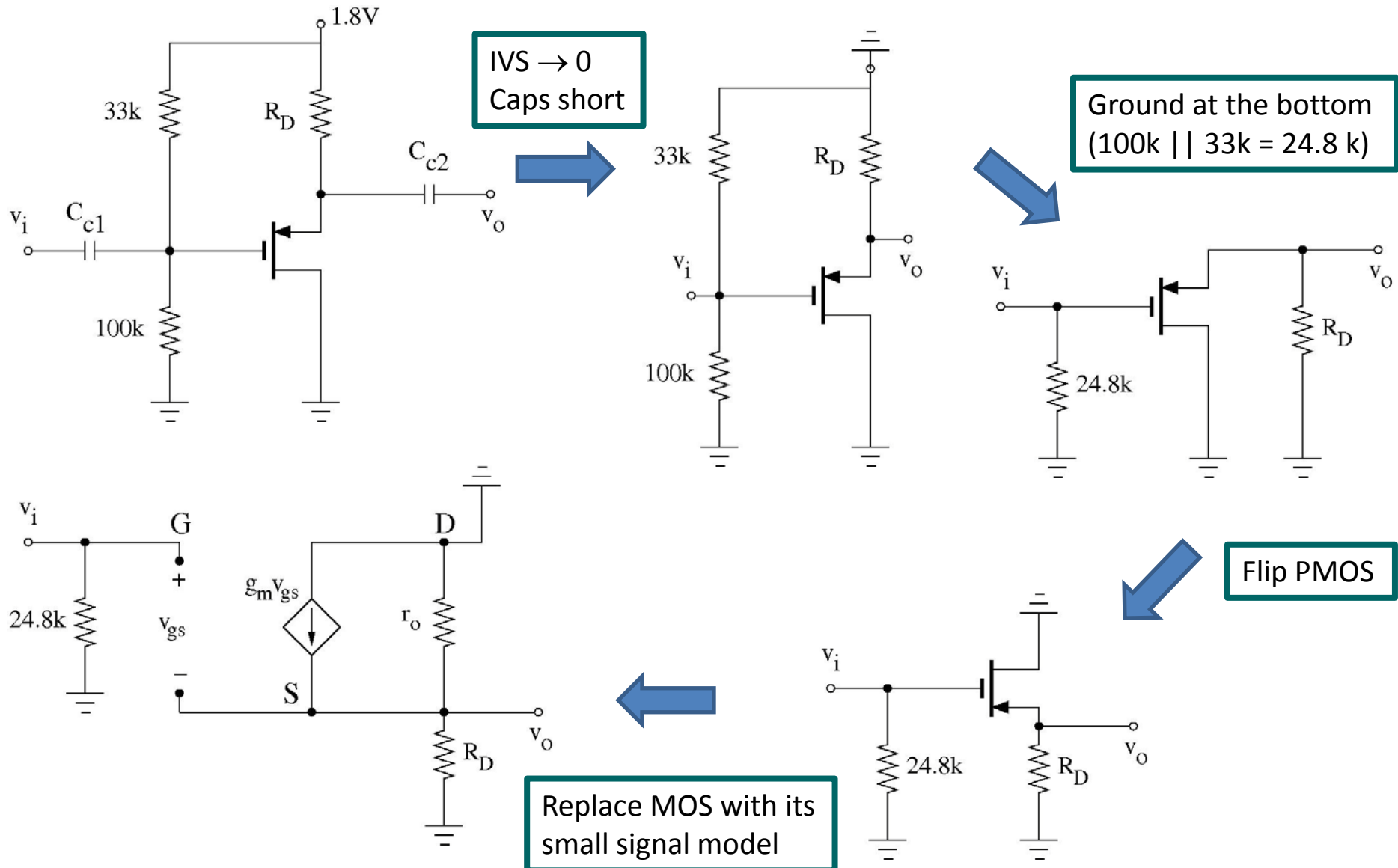


 
Example 3: Construct the signal circuit and replace the transistor with its small-signal model (assume capacitors are short for signal).



$I_{VS} \rightarrow 0$   
Caps short



  $I_{CS} \rightarrow 0$   
(This makes  $I_{CS}$  an open circuit)



Replace MOS with its  
small signal model