

Integrated Combinational Circuits As Building Blocks

In combinational logic design there are several common structures (such as adders, multiplexers, decoders) that are used regularly as building blocks in larger systems.

Instead of designing every complex function with basic logic gates, using these common structures makes the design simpler.

Their level of functionality often matches a designer's level of thinking when partitioning the large problem into smaller chunks. (As functions in programming.)

These structures are manufactured and sold as integrated circuits (ICs).


Generations of ICs according to integration scale factors:

- **Small-Scale Integration (SSI)**: These digital circuits contain transistors numbering in the tens and provide a few logic gates.
- **Medium-Scale Integration (MSI)**: They contain hundreds (up to 1000) of transistors. Adders, decoders.
- **Large-Scale Integration (LSI)**: Tens of thousands of transistors per chip. First memory and microprocessor chips
- **Very Large-Scale Integration (VLSI)**: Hundreds of thousands of transistors in the early 1980s, and continues beyond several billion transistors as of 2009.
- **Ultra-large-scale integration (ULSI)**: More than 1 million transistors.

Half Adder:

It adds two 1-bit numbers (without carry input).

Truth table:

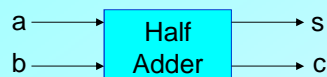


a: First number
b: Second number
s: Result
c: Carry output

a	b	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

From the truth table the logical expression is obtained.

$$s = ab' + a'b$$


$$c = ab$$

 

The circuit can also be implemented with EXOR gates.

$$s = a \oplus b$$

$$c = ab$$

 

Full Adder:

It adds two 1-bit numbers with a carry input.

Truth table:



a: First number
b: Second number
 c_i : Carry Input
s: Result
 c_o : Carry Output

a	b	c_i	c_o	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

s	bc_i	00	01	11	10
a	0	0	1	0	1
a	1	1	0	1	0

$$s = a'b'c_i + a'bc_i' + ab'c_i' + abc_i$$

$$s = a \oplus (b \oplus c_i)$$

$$s = a \oplus b \oplus c_i$$

c_o	bc_i	00	01	11	10
a	0	0	0	1	0
a	1	0	1	1	1


$$c_o = ac_i + bc_i + ab$$

n-Bit Binary Parallel Adder:

It adds two n-bit binary numbers.

Depending on the size of the numbers, 1-bit full adders (FA) can be connected to implement binary parallel adders.

 Internal structure of a 4-bit binary parallel adder is shown below:





7483 IC is a 4-bit binary parallel adder.

1. Number: $A_3A_2A_1A_0$
2. Number: $B_3B_2B_1B_0$
Result : $S_3S_2S_1S_0$
Carry In : c_0
Carry Out: c_4

Example:

 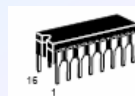1. Num.: 0110
2. Num.: 1100
Result : 0010
Carry : 1



Subtraction Circuit

Subtraction is performed as "add with 2's complement".


A subtraction circuit can be implemented with an n-bit adder and NOT gates.

Example: A 4-bit subtraction circuit

$$S = A - B$$


2's complement of B is added with A.
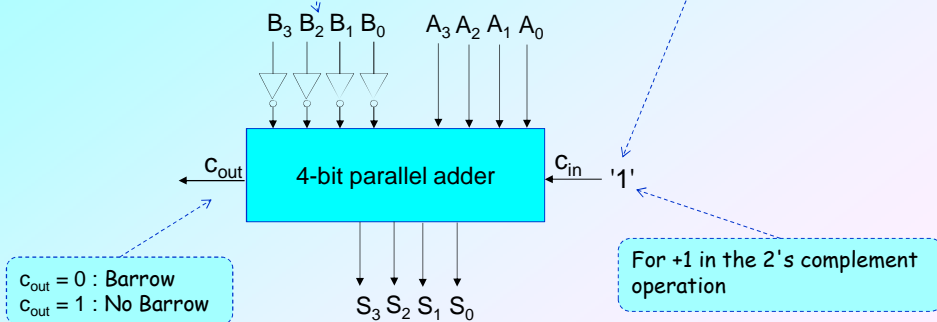
$$S = A - B = A + 2's \text{ complement}(B) = A + (B' + 1)$$





Multiplexer:

 - 2^n data inputs (I), n selector (control) inputs (S), 1 data output (Z).
- It selects one of data input signals and forwards the selected input into a single output.
- Select lines are used to select which input line of 2^n to send to the output.
- Multiplexers are named according to the number of data inputs as m:1. Here m is the number of data inputs.



  Example: 2:1 Multiplexer (Read as "2 to 1 multiplexer".)



Function Table:

s	Z
0	I ₀
1	I ₁

Truth Table:

I ₁	I ₀	s	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


Logical Expression:

$$Z = s' I_0 + s I_1$$


Parallel connection of multiplexers:

To make selection between two n-bit data n units of 2:1 multiplexers have to be connected parallel.

 The circuit that's block diagram is given at the right side, forwards one of the n-bit numbers A or B to the output Z according to the selector line x.



 
Example: A circuit that forwards one of the 4-bit numbers A or B to the output Z.




In this circuit selector lines of all multiplexers are connected (short circuit).

An Example of Usage of Multiplexers:

 
The same adder circuit can be used to add different numbers from different sources.



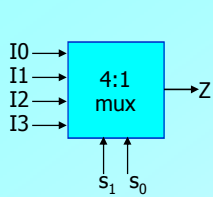Other Multiplexer (MUX) Examples:

Function Table:

$s_1 s_0$	Z
0 0	I_0
0 1	I_1
1 0	I_2
1 1	I_3

 

Function Table:

$s_2 s_1 s_0$	Z
0 0 0	I_0
0 0 1	I_1
0 1 0	I_2
0 1 1	I_3
1 0 0	I_4
1 0 1	I_5
1 1 0	I_6
1 1 1	I_7

Logical Expressions:

2:1 mux: $Z = s' I_0 + s I_1$

4:1 mux: $Z = s_1' s_0' I_0 + s_1' s_0 I_1 + s_1 s_0' I_2 + s_1 s_0 I_3$

8:1 mux: $Z = s_2 s_1' s_0' I_0 + s_2 s_1' s_0 I_1 + s_2 s_1 s_0' I_2 + s_2 s_1 s_0 I_3 + s_2 s_1' s_0' I_4 + s_2 s_1' s_0 I_5 + s_2 s_1 s_0' I_6 + s_2 s_1 s_0 I_7$



General Expression (k:1 Mux): $Z = \sum_{j=0}^{k-1} (m_j I_j)$ $k=2^n$, $m_j = j$. minterm

Example Integrated Circuit:



The IC 74151 contains an 8:1 multiplexer.

Multiplexers can be implemented using logical gates.

2:1 mux

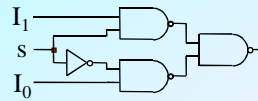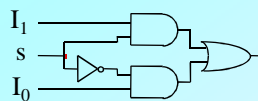


4:1 mux

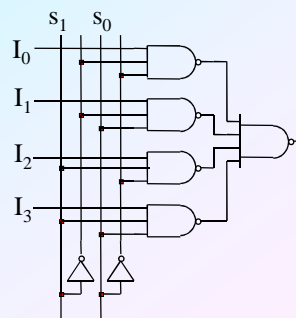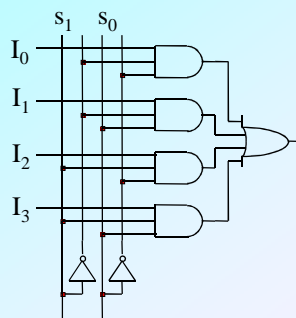

Multiplexers of bigger sizes can be implemented by using smaller multiplexers. Following examples show implementation of an 8:1 multiplexer using other multiplexers in two different ways.

1. Method:

 


Here, s_0 and s_1 selector lines are common for 4:1 multiplexers.

Same inputs of both multiplexers are selected.

Which multiplexers output is to be selected is determined by s_2 .

2. Method:

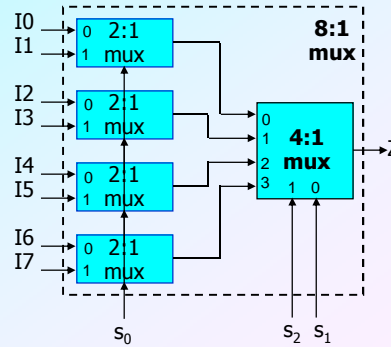

Design of Logic Circuits Using Multiplexers 1:


A logic circuit with n inputs and one output can be implemented by using only one $2^n:1$ multiplexer and without any other logic gate.

Method:

- The n inputs of the function (circuit) to be implemented are connected to the n selector lines of the multiplexer.
- As each binary value of selector lines corresponds to an input combination, by considering the truth table of the function "0" or "1" constant values are connected to the proper data input of the multiplexer.

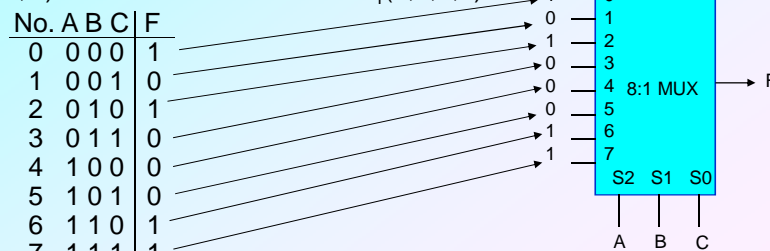Example:

$$F(A,B,C) = m_0 + m_2 + m_6 + m_7 = \cup_1(0,2,6,7)$$



Design of Logic Circuits Using Multiplexers 2:

A logic circuit with n inputs and one output can be implemented by using only one $2^{n-1}:1$ multiplexer and in addition with an NOT gate.


Method:

- $n-1$ inputs (variables) of the function are connected to the $n-1$ select lines of the multiplexer.
- The remaining variable or its complement is connected according to the truth table to the data inputs of the multiplexer.

Example:

$$F(A,B,C) = m_0 + m_2 + m_6 + m_7 = \cup_1(0,2,6,7)$$

Solution with a 4:1 MUX:

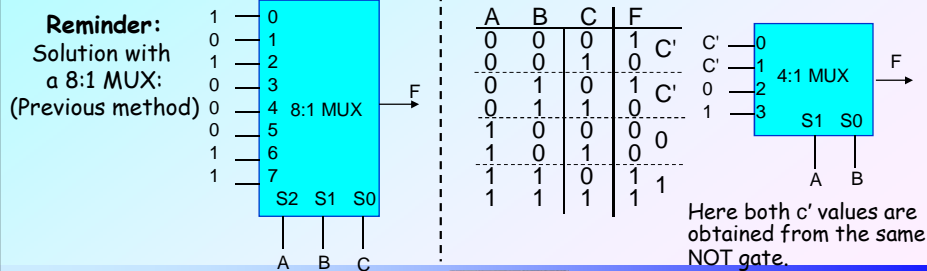

<http://www.faculty.itu.edu.tr/buzluca>
<http://www.buzluca.info>



2011-2012


Dr. Feza BUZLUCA

5.13

Demultiplexer:

- 1 data input, n select (control) lines, 2^n data outputs.
- It selects one of the many data output lines, which is connected to the single input.
- The binary value on the select inputs determines the output line to which the data input is forwarded.
- The value on the not-selected output lines is "0".
- Demultiplexers are named according to the number of data outputs 1:m.

Example: 1:2 Demultiplexer

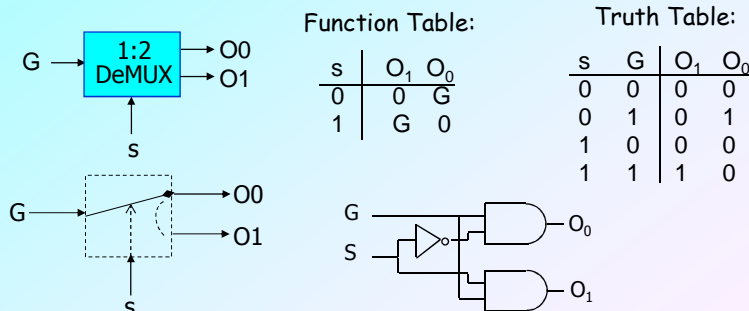

<http://www.faculty.itu.edu.tr/buzluca>
<http://www.buzluca.info>





2011-2012

Dr. Feza BUZLUCA

5.14

Decoder:

- n select (control) inputs, 2^n outputs.
- According to the value on the select lines only one output gets the value "1" and other outputs are "0".
- Decoder can be considered as a demultiplexer that has a constant "1" on its input.
- Decoders are named as $n:2^n$ according to their lines. Here, n is the number of select lines and 2^n is the number of outputs.

 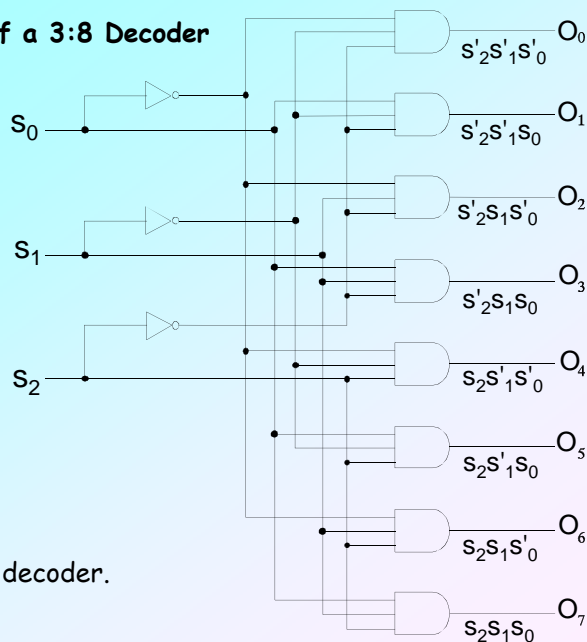Example: 3:8 Decoder**Internal Structure of a 3:8 Decoder****An Example IC:**

74138 includes a 3:8 decoder.

Design of Logic Circuits Using Decoders:


A general logic circuit with n inputs and m outputs can be implemented by using only one $n:2^n$ decoder and in addition with OR gates.

Method:

- n inputs (variables) of the function are connected to the n select lines of the decoder.
- Each output of a decoder corresponds to a minterm.
- The outputs of the decoder, which correspond to the minterms of the function are added by using an OR gate.

Example:


$$F(A,B,C) = m_0 + m_2 + m_6 + m_7 = \cup_1(0,2,6,7)$$

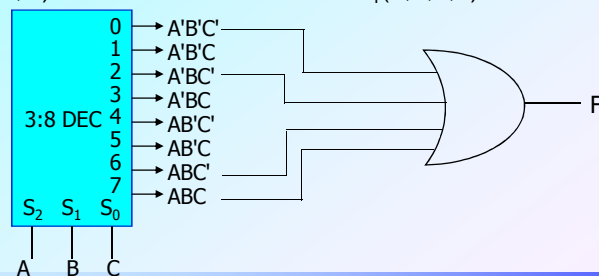**Example: Implementation of a function with 4 inputs and 3 outputs**

$$F_1(A,B,C,D) = A' B C' D + A' B' C D + A B C D$$

$$F_2(A,B,C,D) = A B C' D' + A B C$$

$$F_3(A,B,C,D) = (A' + B' + C' + D')$$

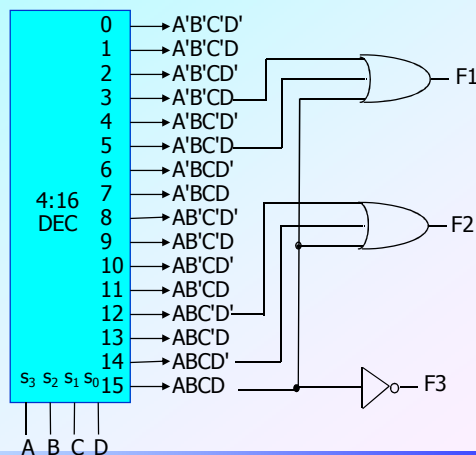


A decoder with an Enable (EN) input:

Decoders may also have an "enable" (EN) input.

If EN input is "1" decoder performs normally.

If EN input is "0" all outputs of the decoder become "0".

A 2:4 decoder with enable input is shown below:

 **An example for the usage of the decoders:**


In some systems it is required that only one unit (device) in a group is active at certain instant in time.

In other words, two devices can not be active at the same time.

These type of devices have chip select (CS) inputs, which are used to activate or deactivate them.

Decoders can be used to select the active unit.

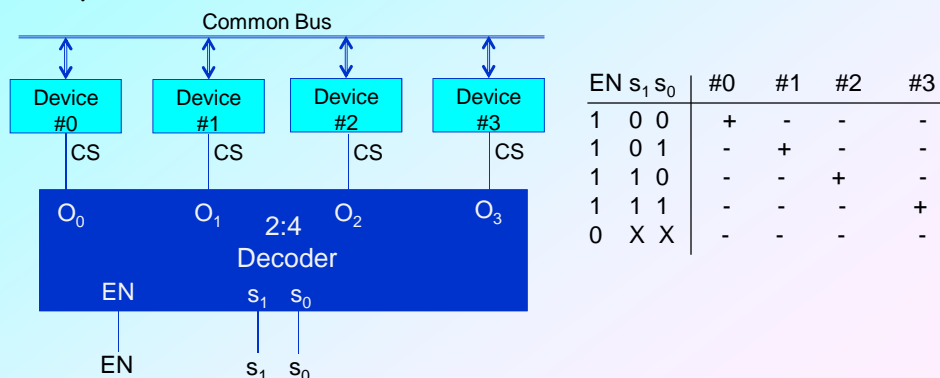Example: A decoder that controls 4 devices.



Programmable Logic Device (PLD)

Today, complicated digital circuits are implemented using programmable logic devices.

These devices are integrated circuits that include many reconfigurable logic gates. (From several hundreds to several millions).

Some PLDs also include memory units (flip-flops).

The designer can reconfigure the connections between logical gates in the PLD by using a programming language and a programming device.

It is possible to implement complicated digital circuits with only one IC (PLD).

There are different kinds of PLDs:

- *Programmable Logic Array - PLA*
- *Programmable Array Logic - PAL®*
- *Generic Array Logic - GAL*
- *Complex PLD - CPLD*
- *Field-Programmable Gate Array - FPGA*

PAL is a registered trademark of Lattice Semiconductor Corp.

Programming of PLDs:

In early versions of PLDs (PLA, PAL) bipolar transistors were used (See Chapter 9). They have fuses on the connection points between gates, which provide reconfiguration (programming) of devices.

In these devices fuses can be blown only once; therefore they are called as one-time programmable (OTP).

Today's devices (GAL, CPLD, FPGA) are made of CMOS transistors and they consist memory units for programming.

They can be erased and reprogrammed many times.

To program PLDs various Hardware Description Languages (HDL) and programming devices are used.

Some examples of HDLs:

PALASM


ABEL

Verilog

VHDL (*Very high speed integrated circuits* HDL)

Programmable Logic Array - PLA

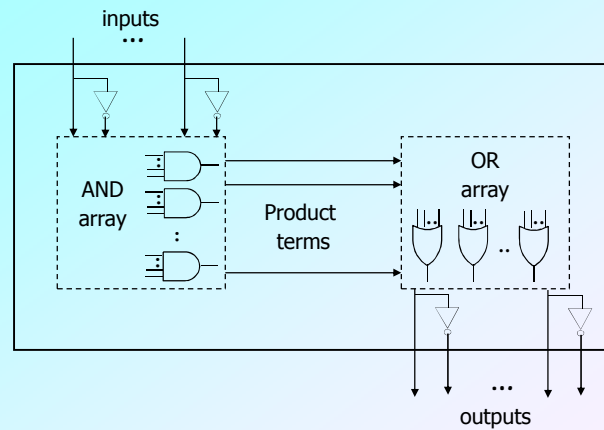It includes AND (product) units in the input layer and OR (sum) units in the output layer.



Both AND, OR arrays are flexible programmable.

Parameters that determine the limits of a PLA:

Inputs: n

Outputs: m

AND gates (products): p


Such a device is called, " $n \times m$ PLA with p products".

On the right internal structure of a 3x4 PLA with 5 products is shown.

In real, PLAs include about 100 gates.


Example: 82S100

16 inputs, 8 outputs, 48 products

 

 Example:

$$\begin{aligned} F0 &= A + B' C' \\ F1 &= A C' + A B \\ F2 &= B' C' + A B \\ F3 &= B' C + A \end{aligned}$$




Internal connections of a 3x4 PLA with 5 products after programming are shown. Unnecessary fuses are blown.

Simple Representation:

For the sake of simplicity all connections in a PLA are not shown. Instead, we put an 'X' on the connection points which are connected to the inputs of gates.

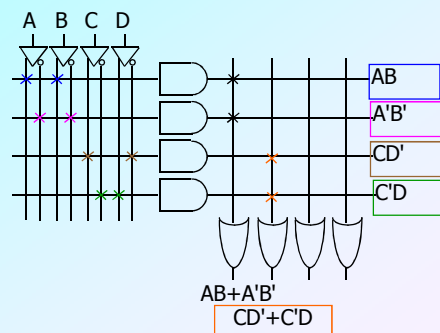Example:

$$\begin{aligned} F0 &= A B + A' B' \\ F1 &= C D' + C' D \end{aligned}$$



Programmable Array Logic - PAL

Inputs of AND gates can be flexible programmed as in PLAs.

But inputs of OR gates are fixed. To each OR gate only outputs of certain AND gates can be connected.

For example to the inputs of the first OR gate only outputs of the first two AND gates can be connected.

PALs can be easily programmed, they are cheaper than PLAs and they can contain more gates.


PALs are introduced by the company Monolithic Memories, Inc. (MMI).

MMI obtained a registered trademark on the term PAL for use in "Programmable Semiconductor Logic Circuits".

The trademark is currently held by Lattice Semiconductor Corporation.

MMI, was acquired by Advanced Micro Devices (AMD).

 Programmable logic division of AMD (Vantis) was then acquired by Lattice Semiconductor.




Example: A part of PAL 16L8 device is shown below:

16 inputs,
8 outputs,
64 products
(AND)

Each AND gate
has 2x16 inputs
(itself and
complement).

PAL16L8		
1	I1	O1
2	I2	IO2
3	I3	IO3
4	I4	IO4
5	I5	IO5
6	I6	IO6
7	I7	IO7
8	I8	IO8
9	I9	IO9
10	I10	IO10

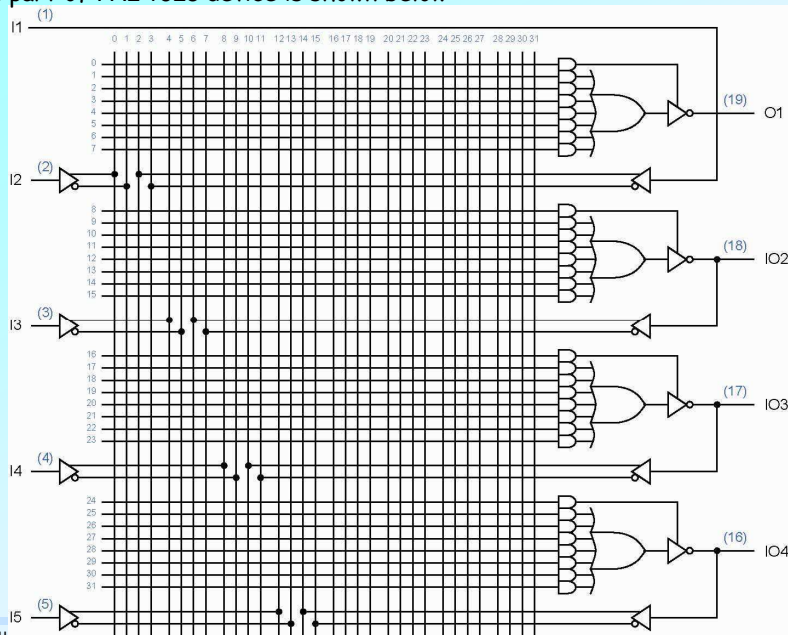

Generic Array Logic - GAL

Its logical properties are similar to PAL.

It is made of CMOS transistors. It can be many times erased and programmed.

It is introduced by Lattice Semiconductor.

Example: GAL16V8

Complex PLD - CPLD

It is an IC that contains several PLDs (*macro cell*).

Each internal PLD (macro cell) has GAL properties.

A typical CPLD may include from thousand to ten thousand gates.

Internal structures of macro cells and connections between them can be programmed.

Example: Atmel ATF1500

32 input/output + 4 inputs

32 PLDs (*macro cell*).

Field-Programmable Gate Array - FPGA

They contain many logical blocks and interconnections between these blocks.

Can be erased and programmed many times.

Number of logical gates is between several thousands and several millions.

Can be used to implement complex digital circuits (for example special purpose microprocessors).

Compared to CPLDs FPGAs are more flexible and they can implement more complicated circuits.

But their delay cost is higher.

Example: Atmel AT6010

204 input/output

30000 gates