



IMPORTANT: Besides your **calculator** and the sheets you use for calculations you are only allowed to have an A4 sized **"copy sheet"** during this exam. Notes, problems and alike are not permitted. **Please submit your "copy sheet" along with your solutions.** You may get your "copy sheet" back after your solutions have been graded. **Do not forget to write down units and convert units carefully! Cell phones are not allowed and should be placed on the front desk before the exam.**

ELE222E INTRODUCTION TO ELECTRONICS (21071)

Midterm Exam #1  25 March 2013  9.30-11.30


İnci ÇİLESİZ, PhD, Hacer ATAR YILDIZ, MSE

- You have a diode with the following doping properties: $N_D = 10^{18} / \text{cm}^3$, and $N_A = 10^{15} / \text{cm}^3$. Other important parameters to consider are $n_i = 1,5 \cdot 10^{10} / \text{cm}^3$, $q = 1,602 \cdot 10^{-19} \text{ C}$, $\epsilon_r = 12$, $\mu_n = 1600 \text{ cm}^2/\text{Vs}$, $\mu_p = 400 \text{ cm}^2/\text{Vs}$, $\epsilon_0 = 8,85 \cdot 10^{-12} \text{ F/m}$, $V_T = 25 \text{ mV}$. (35 points)
 - Find majority and minority carrier concentrations in n- and p-type doped silicon. (6 points)
 - Find the barrier voltage. (5 points)
 - Calculate the specific conductivities of n- and p-type doped silicon. (2x3 points)
 - Determine the depletion zone width. How large is the depletion zone in n- and p-typed doped silicon around the junction? (7 points)
 - What is the maximum value of the electrical field in unbiased state? (6 points)
 - Calculate the junction capacitance for a junction area of 1 mm^2 . (5 points)
- Look at the circuits below and complete look-up tables (like the one shown) for both (a) and (b). Assuming logic 0 \equiv low voltage; such as 0 V and logic 1 \equiv high voltage ; such as 5 V Which logic functions do these circuits realize? You need to analyze states for $A < B$, $A > B$, and $A = B$ with $V_D = 0,6 \text{ V}$, $V_+ = 5\text{V}$. (30 points)

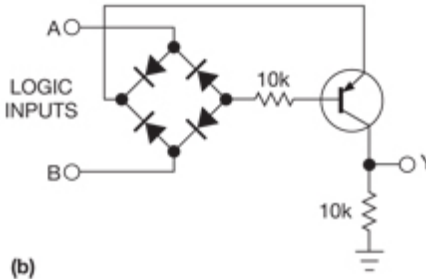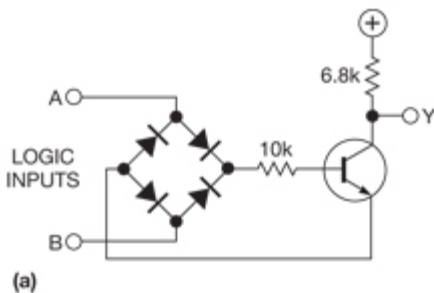

$A \downarrow B \rightarrow$	Logic 0	Logic 1
Logic 0		
Logic 1		

- Study DC characteristics of the 2-stage BJT amplifier circuit shown on the right with $|V_{BE}| = 0,6 \text{ V}$, and $h_{FE} = 200$ for all three transistors. (35 points)

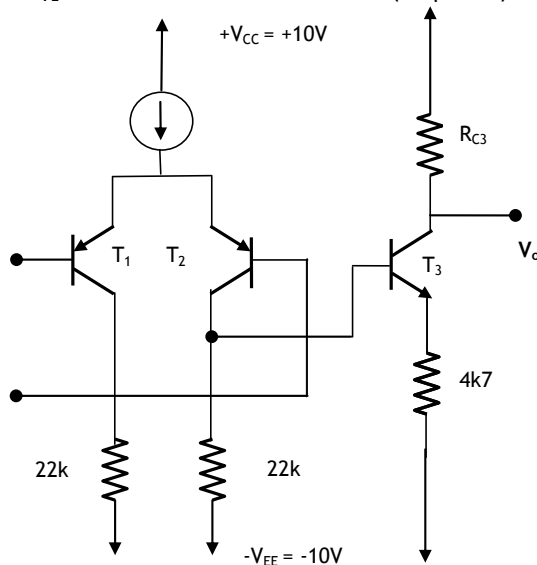

- Design a current source that will provide 0,4 mA biasing current to the differential stage. (10 points)
- Choose R_{C3} such that $V_0 = 0\text{V}$. Do NOT neglect base currents. (25 points)

GOOD LUCK

SOLUTIONS:

1. Using the given parameters

a.

region	Majority carriers	Mainority carriers
n-type	$n_n = N_D = 10^{18} / \text{cm}^3$	$p_n = n_i^2 / N_D = 225 / \text{cm}^3$
p-type	$p_p = N_A = 10^{15} / \text{cm}^3$	$n_p = n_i^2 / N_A = 2,25 \cdot 10^5 / \text{cm}^3$

$$b. \quad V_B = -V_T \cdot \ln\left(\frac{n_i^2}{N_A \cdot N_D}\right) = \underline{\underline{728mV}}$$

$$c. \quad \sigma_n = q\mu_n N_D = 256 / \Omega \cdot \text{cm}; \sigma_p = q\mu_p N_A = 0,06 / \Omega \cdot \text{cm}$$

$$d. \quad \text{Since } x_n N_D = x_p N_A \text{ and } \frac{N_D}{N_A} = 1000 \Rightarrow w \cong x_p, \text{ that is } \frac{x_p}{x_n} = 1000 \Rightarrow w \cong x_p$$

$$w = \sqrt{\frac{2 \cdot \epsilon_o \cdot \epsilon_r \cdot V_B}{q} \left[\frac{1}{N_D} + \frac{1}{N_A} \right]} = \underline{\underline{0,98 \mu m}} \Rightarrow x_p \cong \underline{\underline{0,98 \mu m}} \Rightarrow x_n = \frac{x_p}{1000} = \underline{\underline{0,98 nm}}$$

$$e. \quad \text{We need to find the electrical field at the junction } V_p(x) = \frac{q \cdot N_A}{2 \cdot \epsilon_o \cdot \epsilon_r} x^2 - \frac{q \cdot N_A}{\epsilon_o \cdot \epsilon_r} x_p \cdot x. \text{ Thus,}$$

$$E(x) = -\frac{dV(x)}{dx} = \frac{q \cdot N_A}{\epsilon_o \cdot \epsilon_r} x - \frac{q \cdot N_A}{\epsilon_o \cdot \epsilon_r} x_p \Rightarrow E(x=0) = \underline{\underline{14,8 kV/cm}}$$


$$f. \quad C = \epsilon_o \cdot \epsilon_r \frac{A}{w} = \underline{\underline{130 nF}}$$

2. Lookup tables

A ↓ \ B →	Logic 0	Logic 1
Logic 0	1	0
Logic 1	0	1

A ↓ \ B →	Logic 0	Logic 1
Logic 0	0	1
Logic 1	1	0

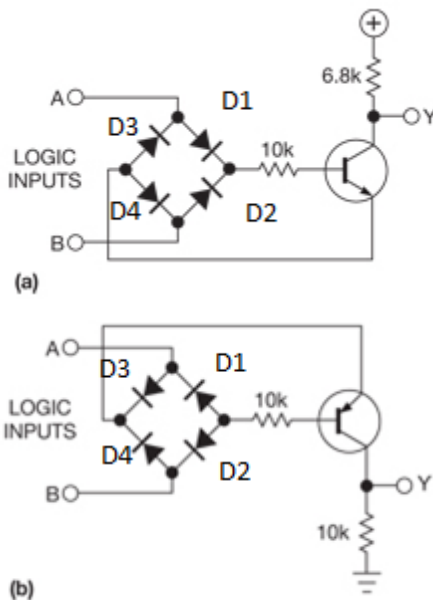It looks like (a) realizes an XNOR and (b) realizes an XOR functions. Let us see how this works:



With AB, 00, none of the diodes are conducting, thus, the transistor is obviously in cut off. With no collector current flowing $Y = 5V$ (logic 1)

Likewise with AB, 11.

With AB, 10, D1 and D4 are conducting, a base current flows. The collector is at a higher voltage than the base of the npn, thus collector current flows. The collector current initiates a voltage drop on 6k8 and $Y \rightarrow 0$ (logic 0)

With AB, 01, D2 and D3 are conducting a base current flows. The collector is at a higher voltage than the base of the npn, thus collector current flows. The collector current initiates a voltage drop on 6k8 and $Y \rightarrow 0$ (logic 0)

With AB, 00, none of the diodes are conducting, thus, the transistor is obviously in cut off. With no collector current flowing $Y = 0V$ (logic 0)

Likewise with AB, 11.

With AB, 10, D3 and D2 are conducting, a base current flows. The collector is at a lower voltage than the base of the pnp, thus collector current flows. The collector current initiates a voltage drop on 10k and Y increases (logic 1)


With AB, 01, D1 and D4 are conducting, a base current flows. The collector is at a lower voltage than the base of the pnp, thus collector current flows. The collector current initiates a voltage drop on 10k and Y increases (logic 1).

For more information look at <http://jjackson.eng.ua.edu/courses/ece380/lectures/lect11-4.pdf>

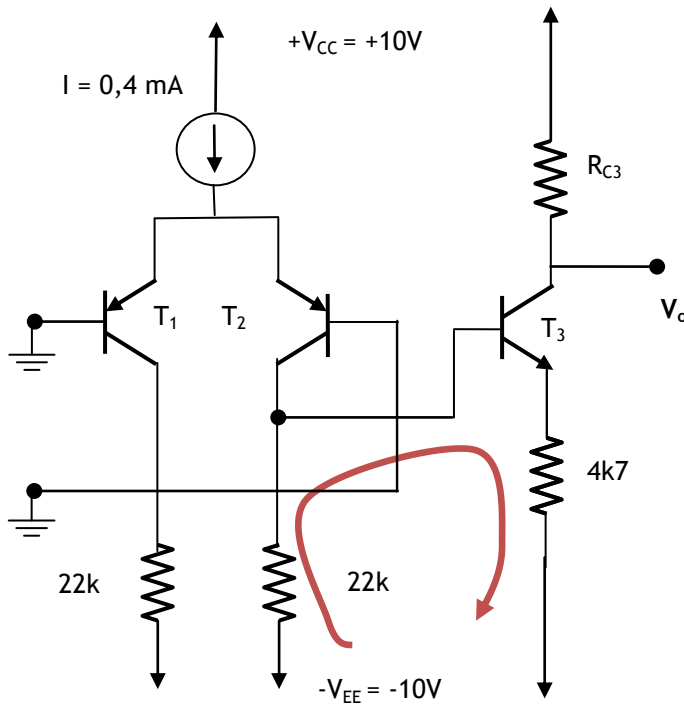3. Exactly the same problem as in ELE222E INTRODUCTION TO ELECTRONICS (11245) Midterm Exam #2.... You can easily design the current mirror. So this part is left to you. Without neglecting the base currents of the differential (the very first) stage, for $V_i = 0$ V

$$I_{C1} = I_{C2} = \frac{h_{FE}}{h_{FE} + 1} \cdot \frac{I_{ref}}{2} = \frac{200}{200 + 1} \cdot \frac{0,4mA}{2} \Rightarrow I_{C1} = I_{C2} = \underline{\underline{0,199mA}}$$

Following the brown loop shown in the sketch $-(I_{C2} - I_{B3})22k + V_{BE3} + (h_{FE} + 1)I_{B3}4k7 = 0$



$$I_{C3} = h_{FE} \frac{22k * I_{C2} - V_{BE3}}{(h_{FE} + 1)4k7 + 22k} = 200 \frac{22k * 0,199mA - 0,6V}{(200 + 1)4k7 + 22k} = \underline{\underline{0,782mA}}$$

$$V_o = 0V \Rightarrow I_{C3}R_{C3} = V_{CC} = 10V \Rightarrow R_{C3} = \frac{V_{CC} - V_o}{I_{C3}} = \frac{10V}{0,782mA} = \underline{\underline{12k8}}$$