

 



## Unstable circuit – Ring oscillator

 



## Bistable circuit

 


## NOR-based SR flipflop

 


S	R	$Q_{n+1}$	$Q'_{n+1}$	Operation
0	0	$Q_n$	$Q'_n$	hold
1	0	1	0	set
0	1	0	1	reset
1	1	0	0	undefined

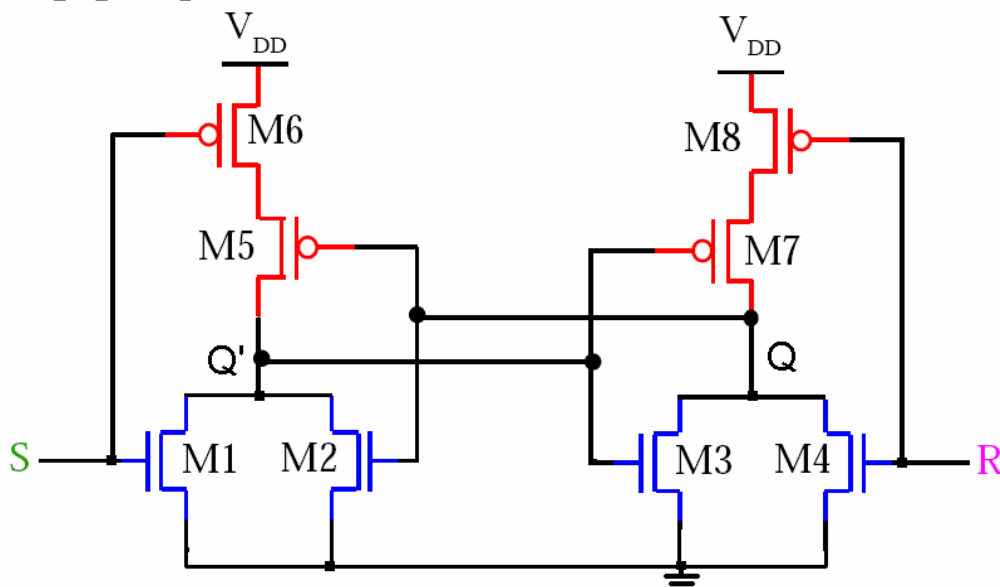 


## Clock-triggered SR flipflop

 

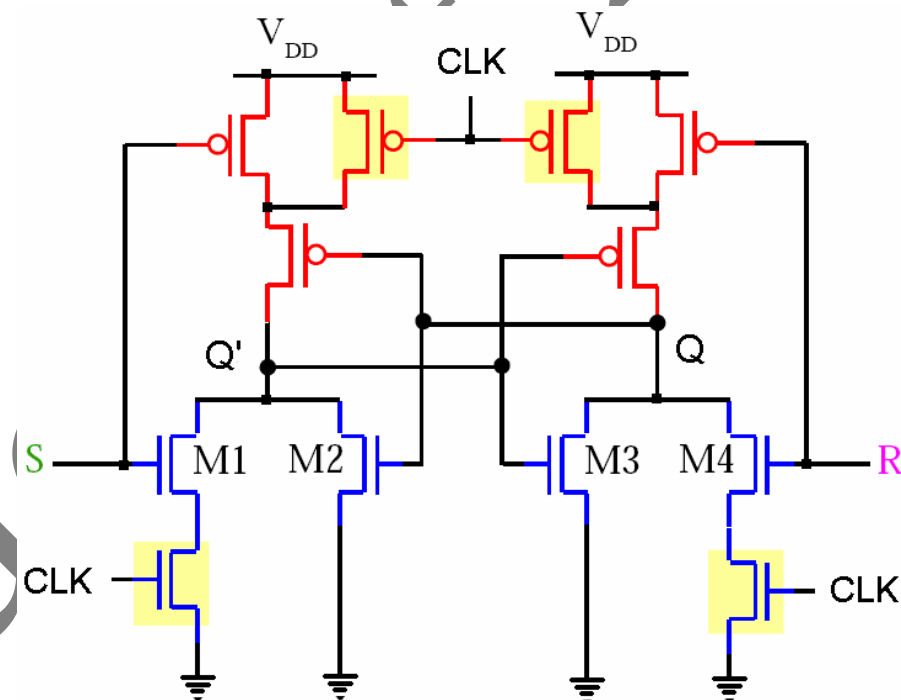
$CK = 0 \Rightarrow S, R$  has no effect on  $Q, Q' \Rightarrow$  hold  
 $CK = 1, S = 1, R = 0 \Rightarrow$  set  
 $CK = 1, S = 0, R = 1 \Rightarrow$  reset  
 $CK = 1, S = 1, R = 1 \Rightarrow$  undefined



## NAND-based SR flipflop

 

S	R	$Q_{n+1}$	$Q'_{n+1}$	Operation
0	0	0	0	undefined
0	1	1	0	set
1	0	0	1	reset
1	1	$Q_n$	$Q'_n$	hold

 

## D flip-flop

