

Istanbul Technical University
Faculty of Computer and Informatics




BLG322E Computer Architecture
Homework 2


Cem Yusuf Aydoğdu
150120251

Date of Submission : 7.4.2015


1) a. Representation of the system

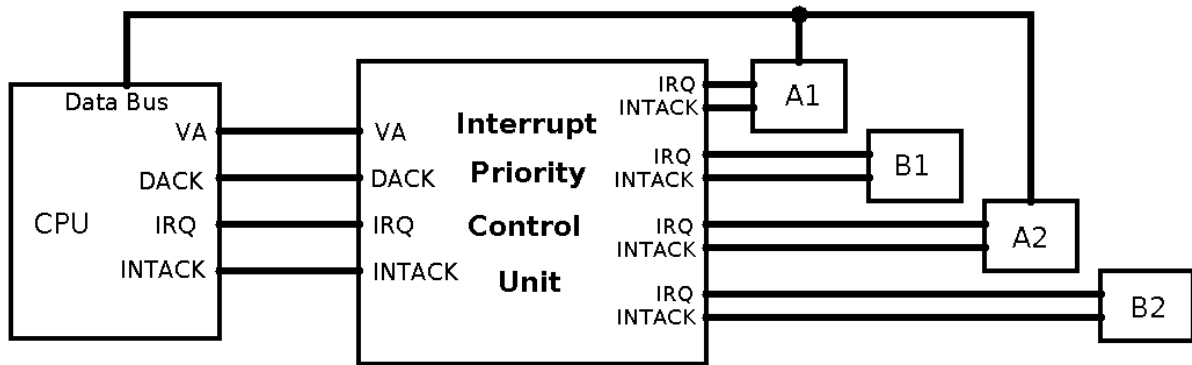

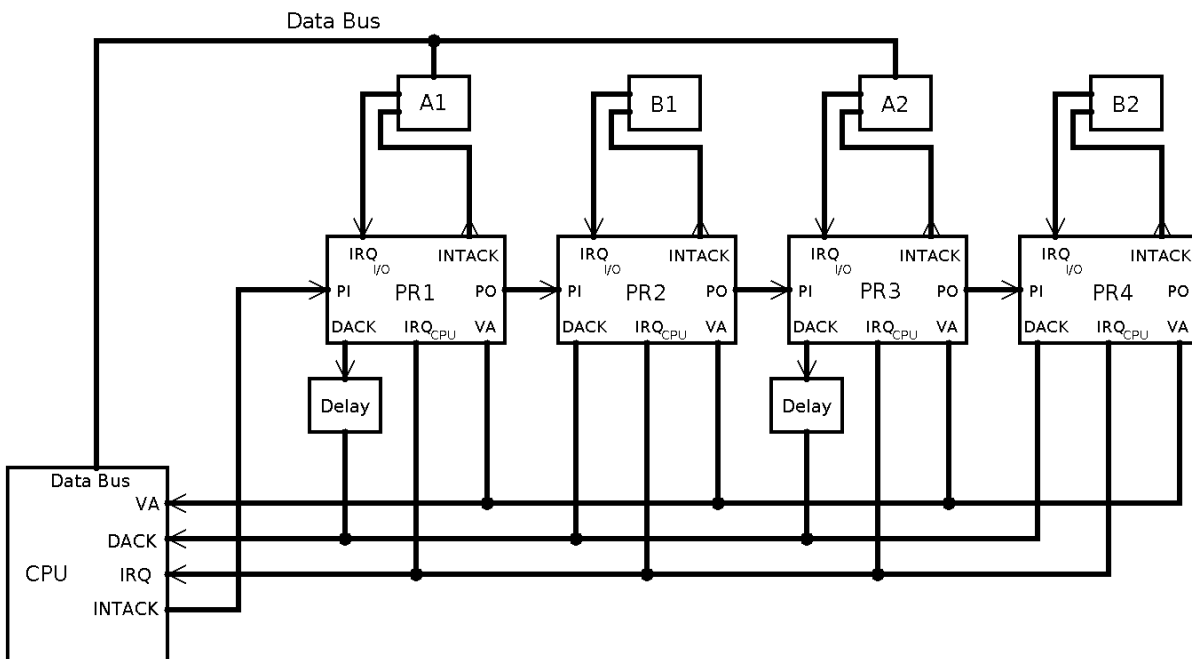
1) b. Serial priority circuit and connections




Inside priority chains for A:

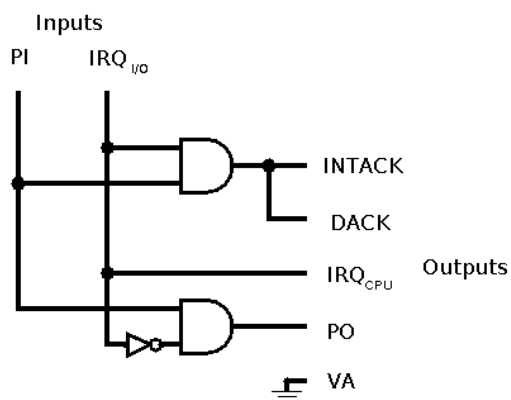


Inside priority chain for B₁:

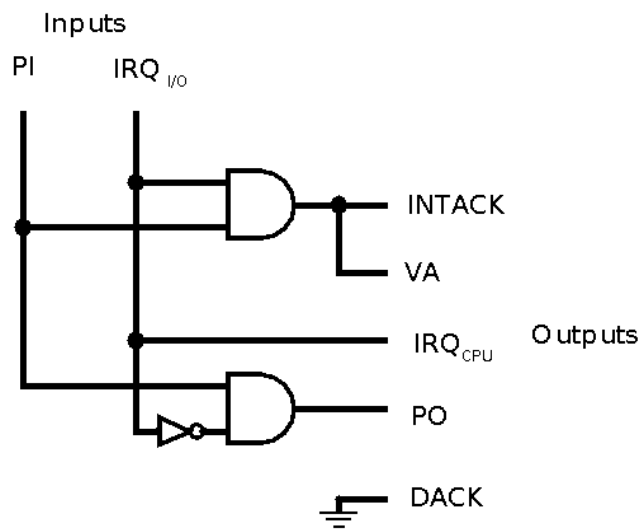

Inside priority chain for B₂:

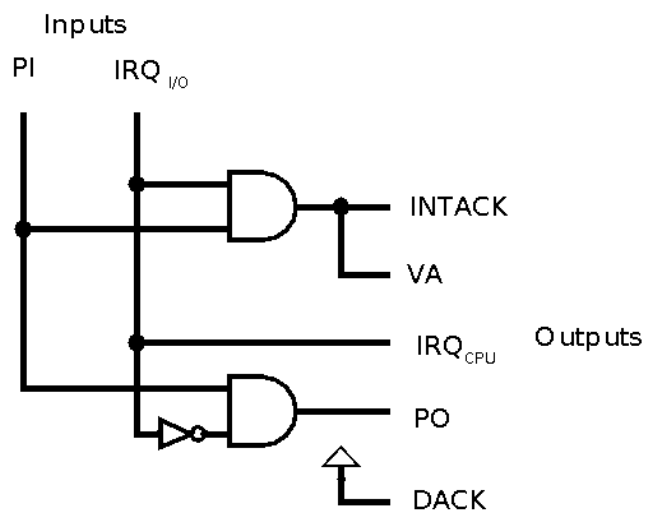

1) c. Parallel circuit

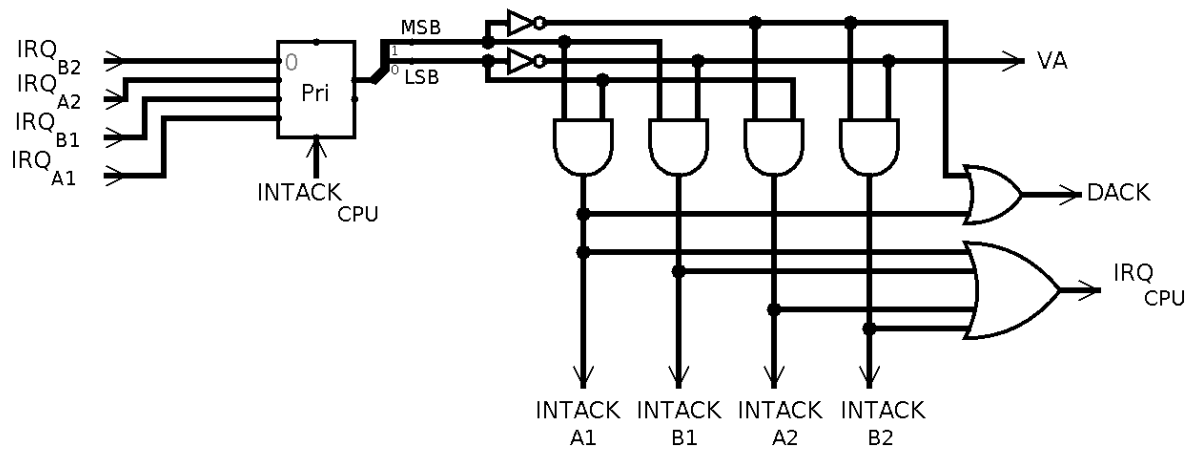

- 2) In both connection types, if the request comes from one of the A devices, chain circuit outputs $VA=0$ and $DACK=1$, and the relevant device puts its interrupt address to the data bus. If the B_1 device requests an interrupt, chain circuit outputs $VA=1$ and $DACK=0$. If the B_2 device requests an interrupt, its chain circuit outputs $VA=1$ and $DACK=1$.