

PowerPoint Slides
to accompany
Digital Principles and Design


Donald D. Givone

Chapter 8
Algorithmic State Machines




Partitioning of a digital system.

Figure 8.1

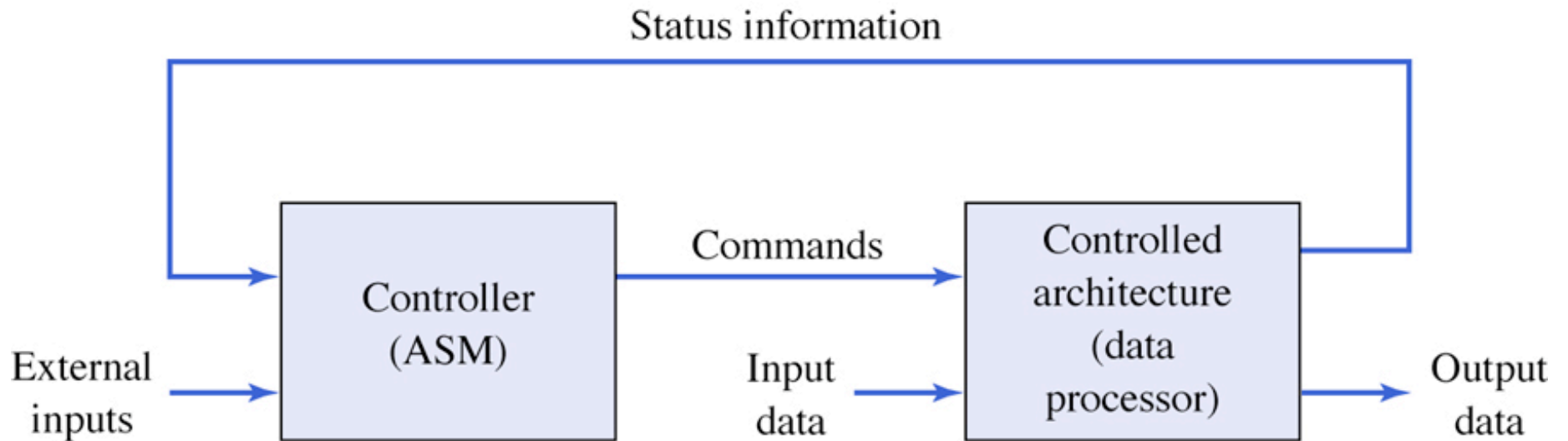


Model of an algorithmic state machine.

Figure 8.2

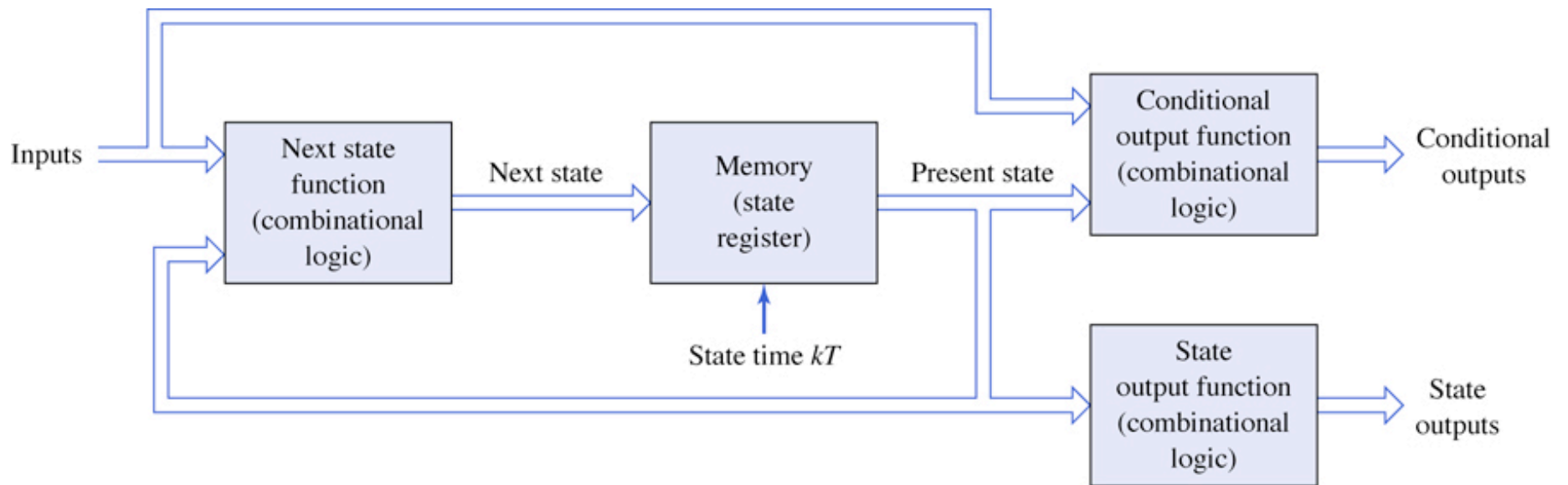

Blocks define states

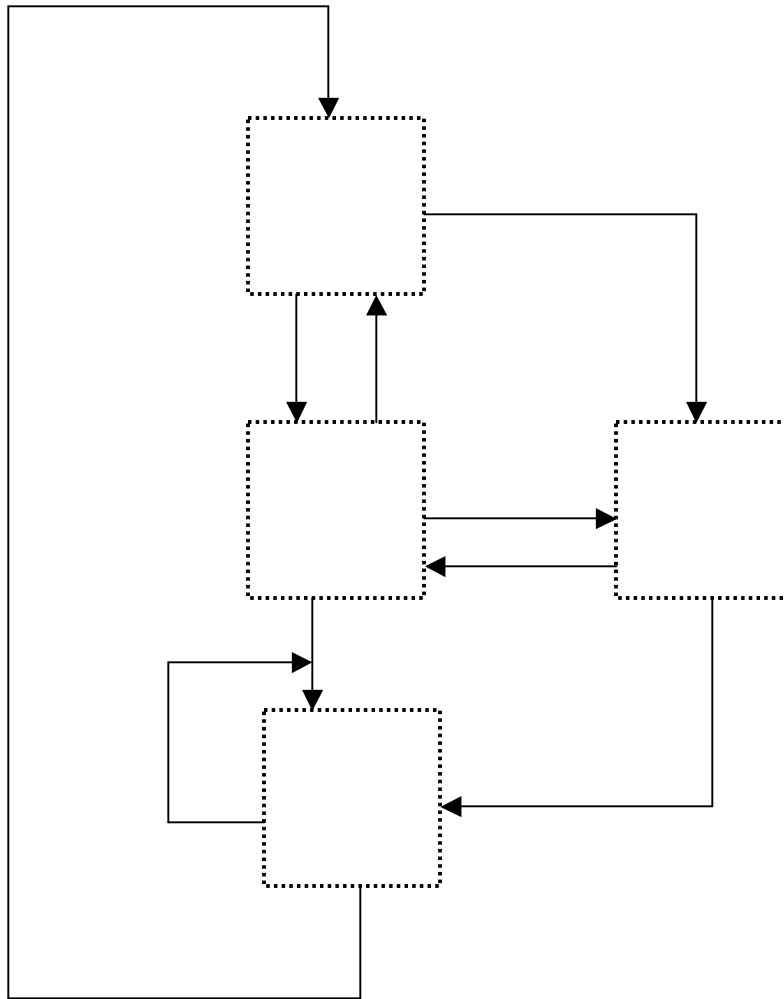
Transition & output logic
contained within




Compare with Mealy/Moore

Timing of an algorithmic state machine.

Figure 8.3

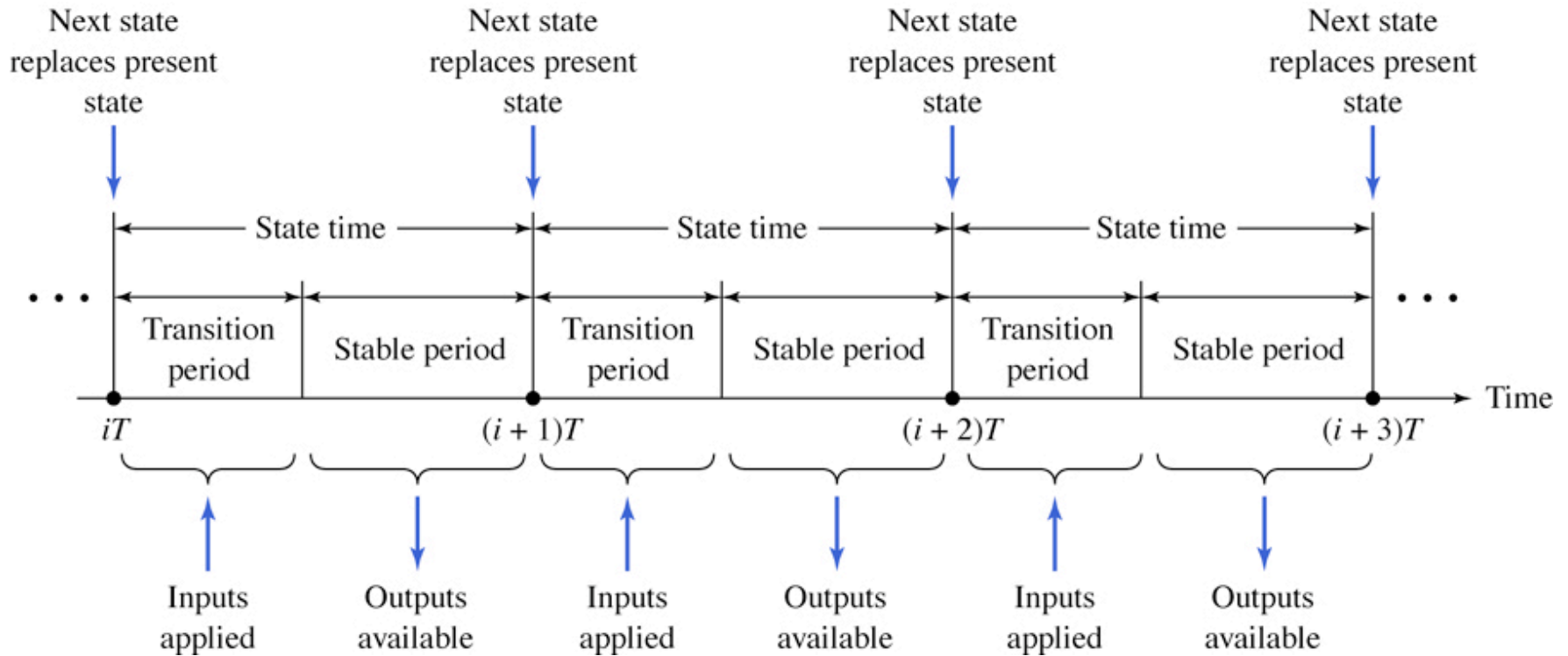


Example ASM Block

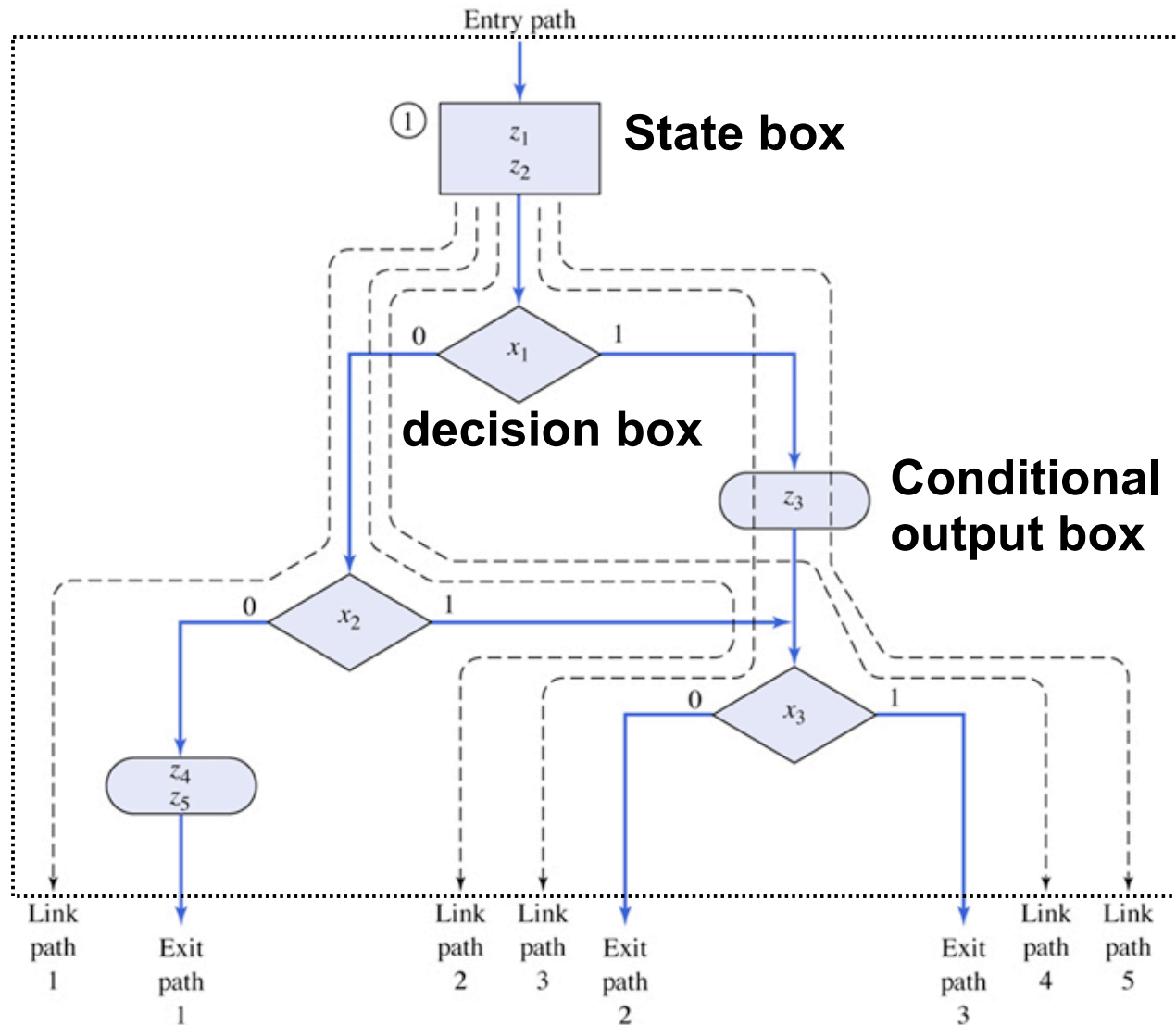


The state box.

Figure 8.4

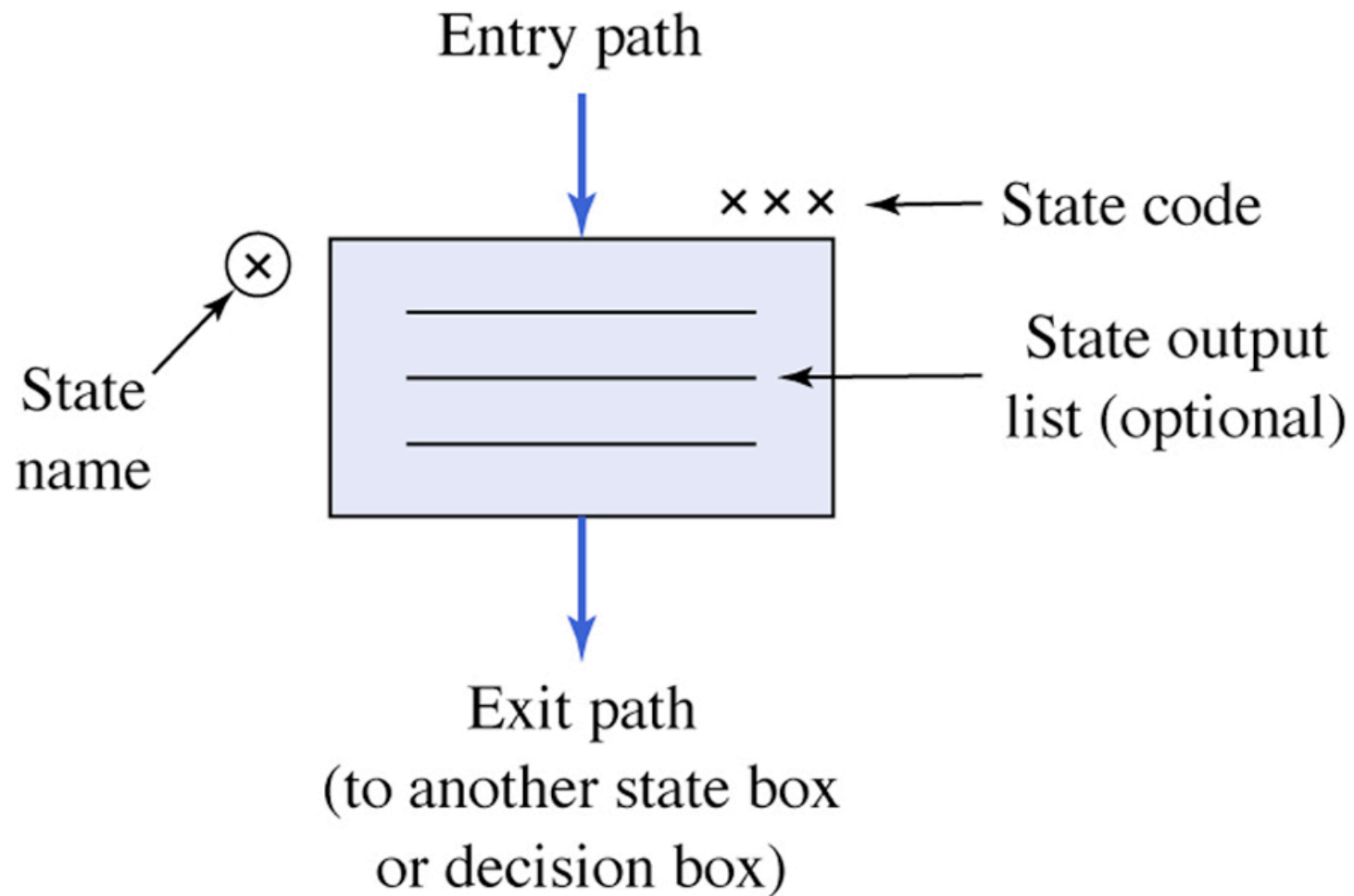


The decision box. (a) Symbol. (b) Alternate symbol.

Figure 8.5

 


(a)

 

(b)


The conditional output box.

Figure 8.6


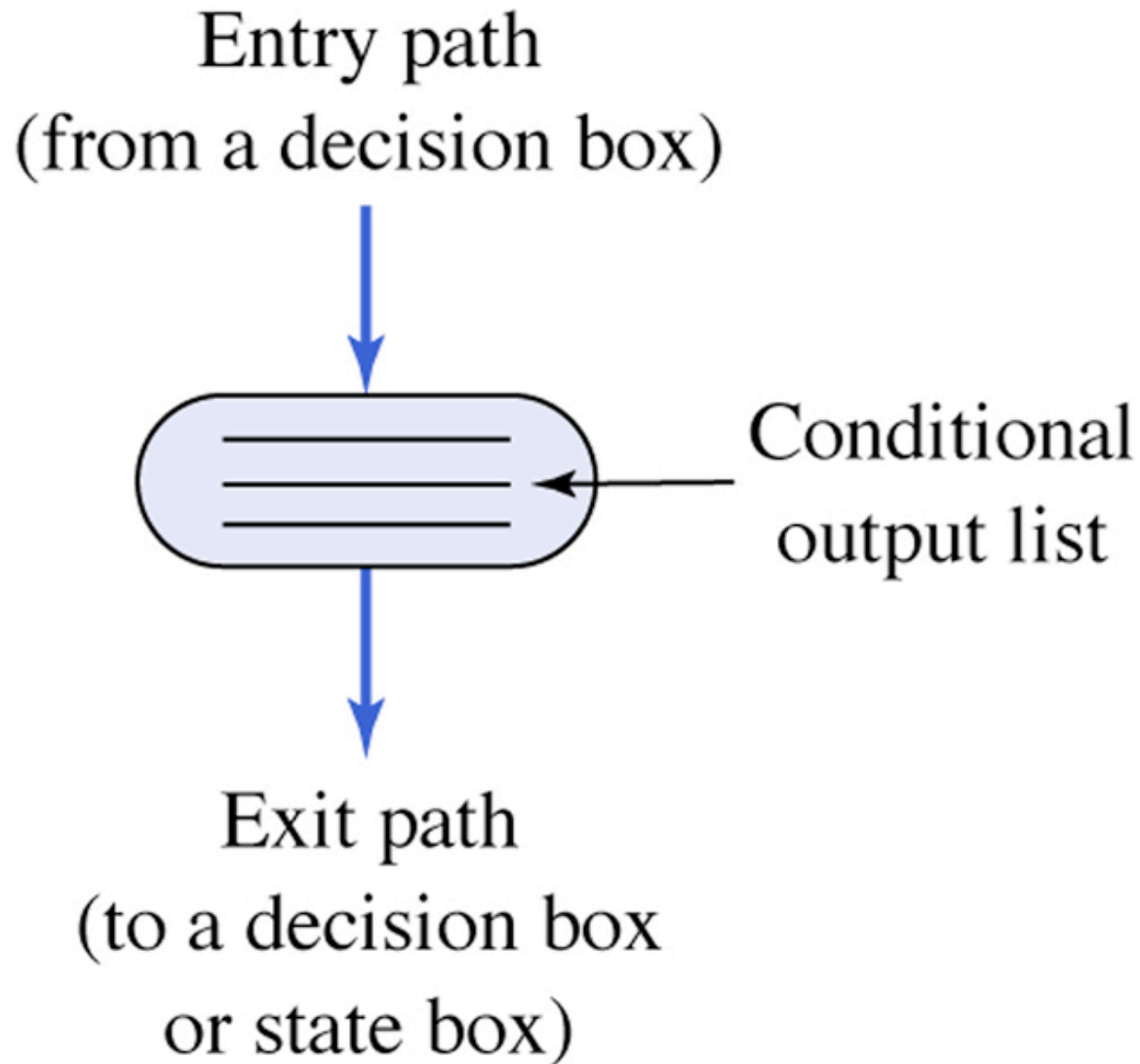


Example of an ASM block and its link paths.

Figure 8.7

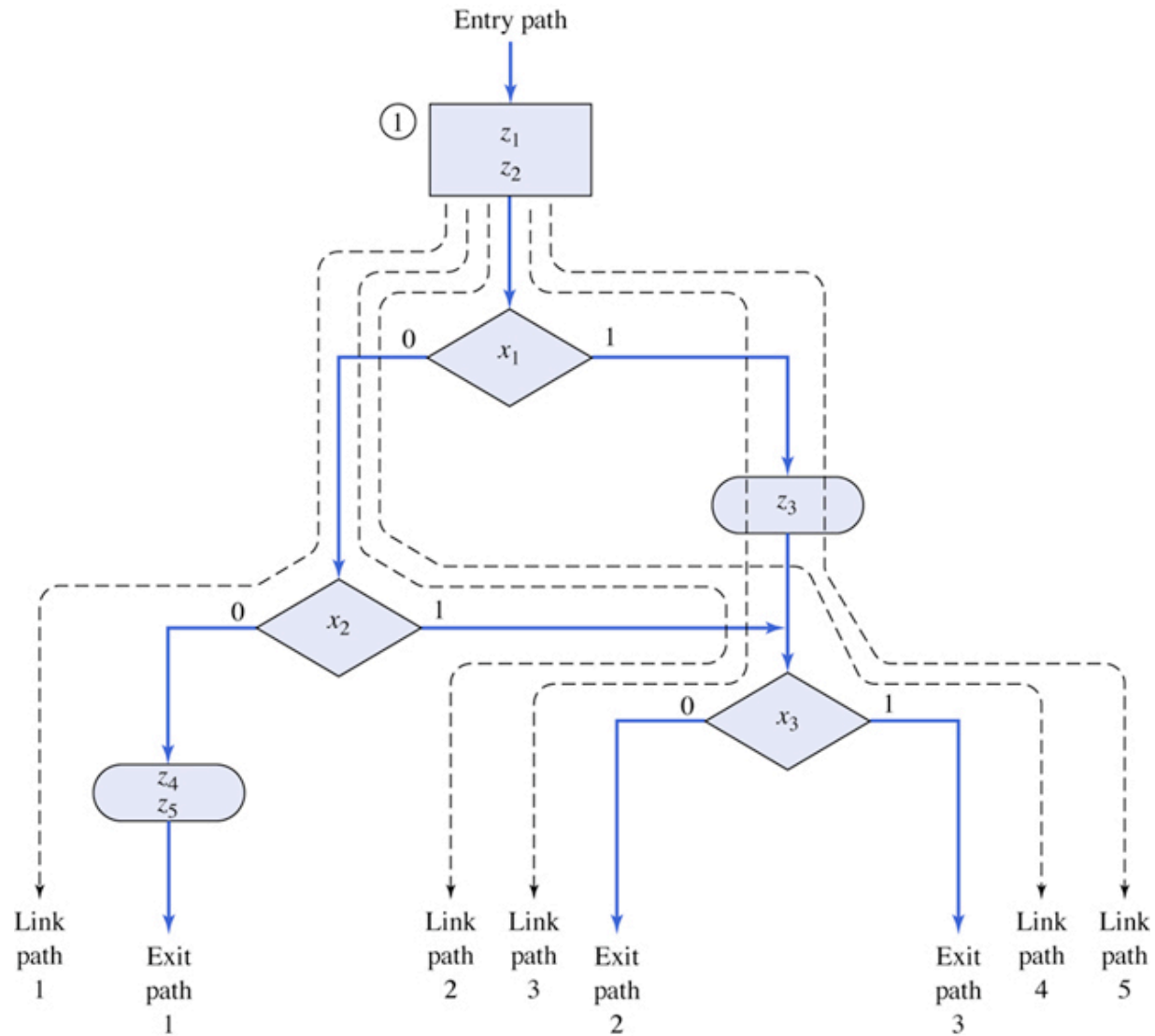

Two equivalent ASM blocks.

  


Two blocks are equivalent if

- same state output variables named in state box
- for every setting of input values
 - the same next state is chosen
 - the same set of output variables are named in the set of conditional output boxes traversed


Two equivalent ASM blocks. (a) Using a single decision box. (b) Using several decision boxes.

Figure 8.9

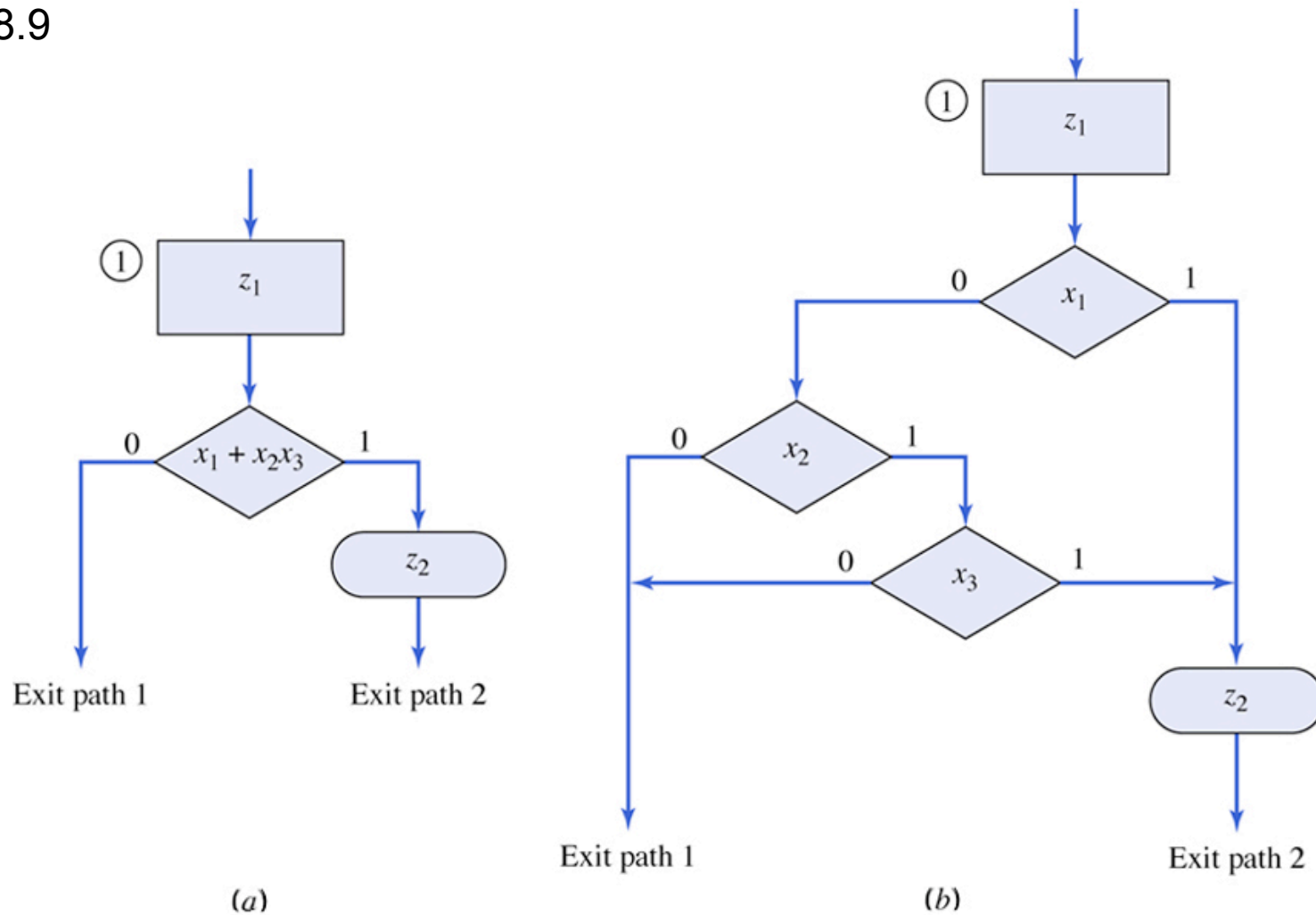


Two equivalent ASM books blocks. (a) Parallel decision boxes. (b) Serial decision boxes.

Figure 8.10

 

Invalid ASM block having nonunique next states.


Figure 8.11

 


**Both exits selected when
both inputs are 1**

Looping. (a) Incorrect. (b) Correct.

 Any closed loop must contain at least one state box




(a)

 

(b)

ASM chart for a mod-8 binary counter.


Figure 8.13

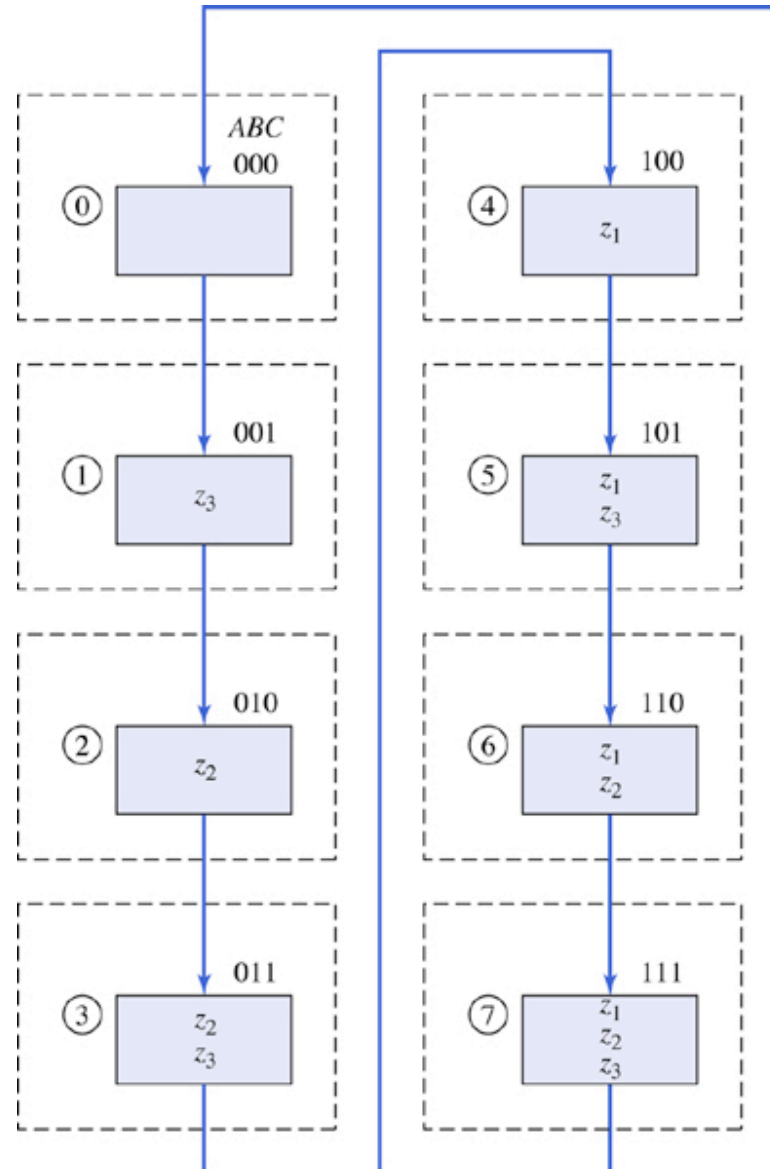

State output is
state code



ASM chart for a mod-8 binary up-down counter.

Input I
controls
direction

 



Moore sequential network. (a) State diagram. (b) ASM chart.

Figure 8.15

  


Mealy sequential network. (a) State diagram. (b) ASM chart.

Figure 8.16

  

ASM chart to recognize the sequence $x_1x_2 = 01, 01, 11, 00$.

Figure 8.17

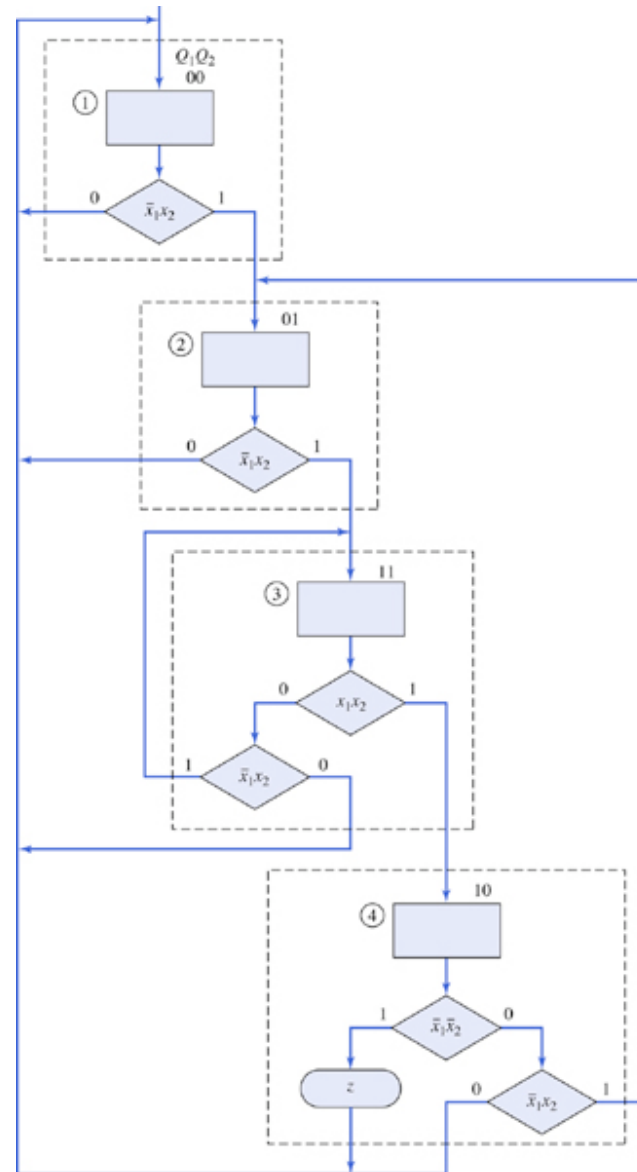


Binary multiplication. (a) Pencil-and-paper approach. (b) Add-shift approach.

Figure 8.18

1010	Multiplicand
× 1101	Multiplier
1010	} Array of partial products
0000	
1010	
1010	
10000010	Product


(a)

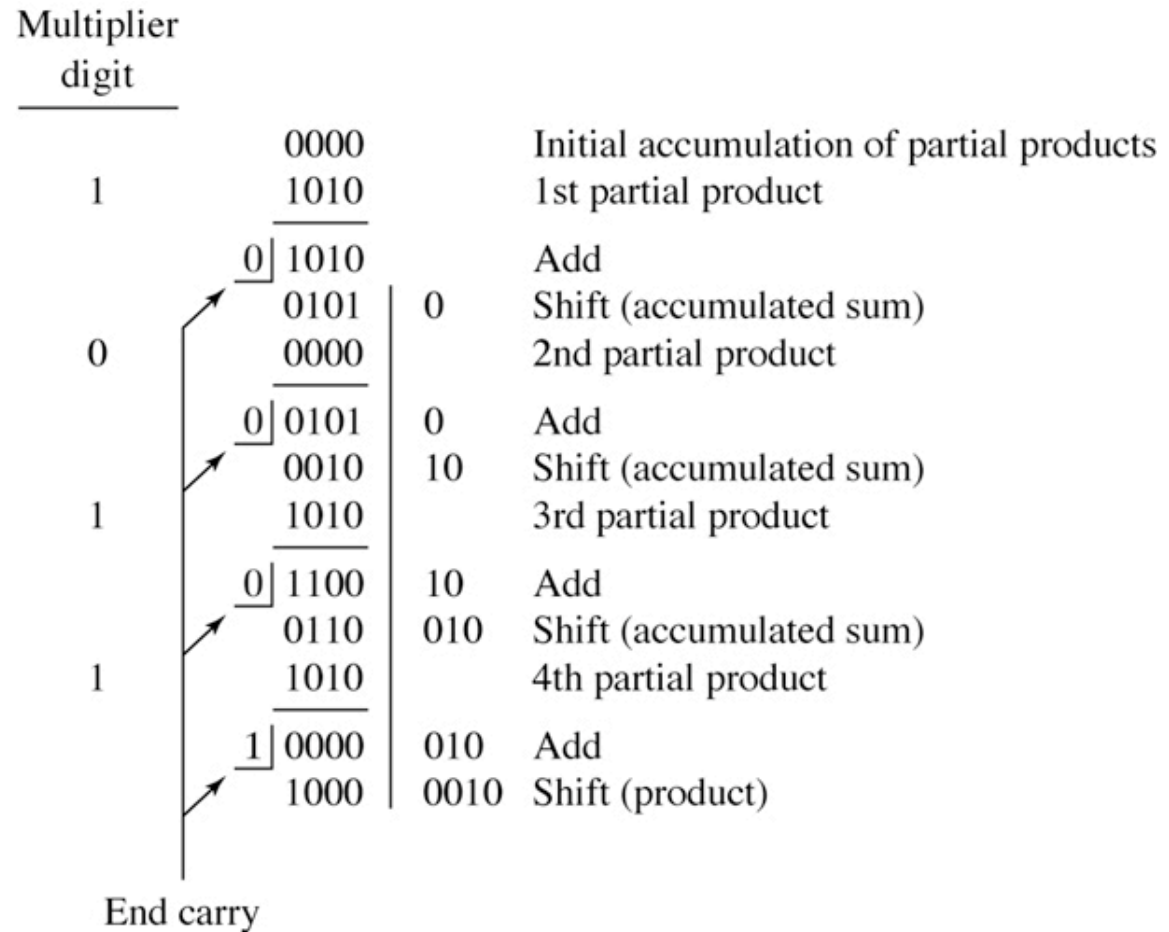

(b)

Architecture for a binary multiplier.


Figure 8.19

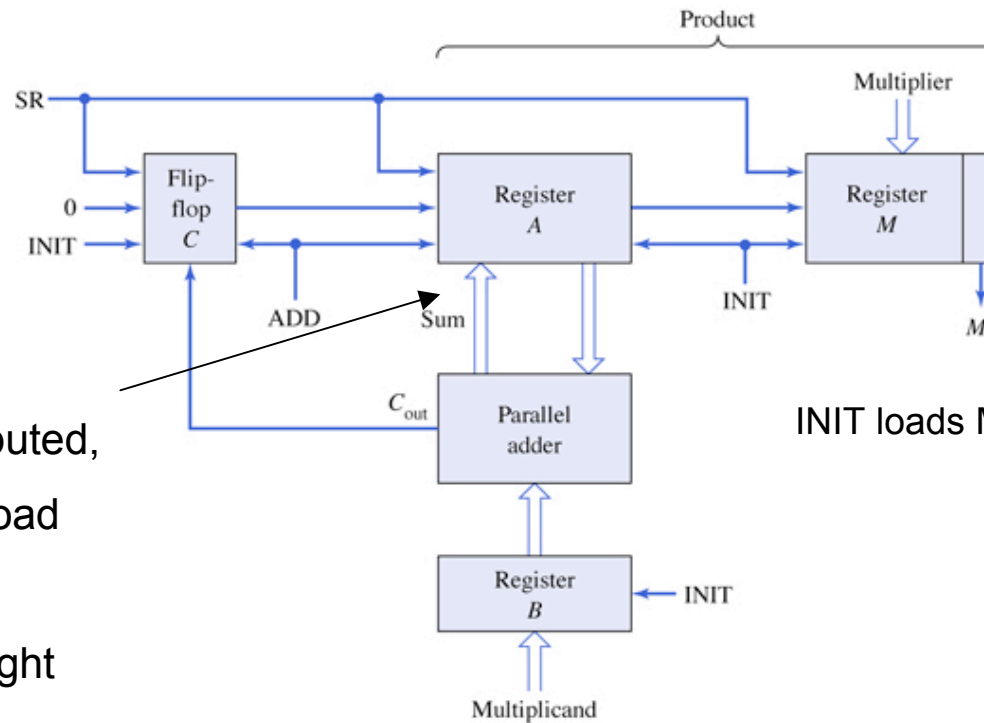

Sum always computed,
ADD tells A,C to load


INIT loads M,B, Counter, clears C

SR shifts C A M right

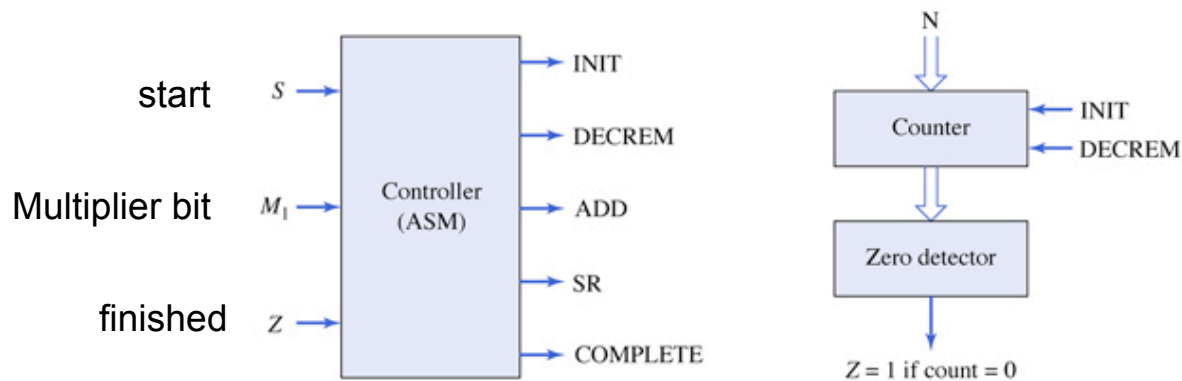


ASM chart for a binary multiplier.

Figure 8.20

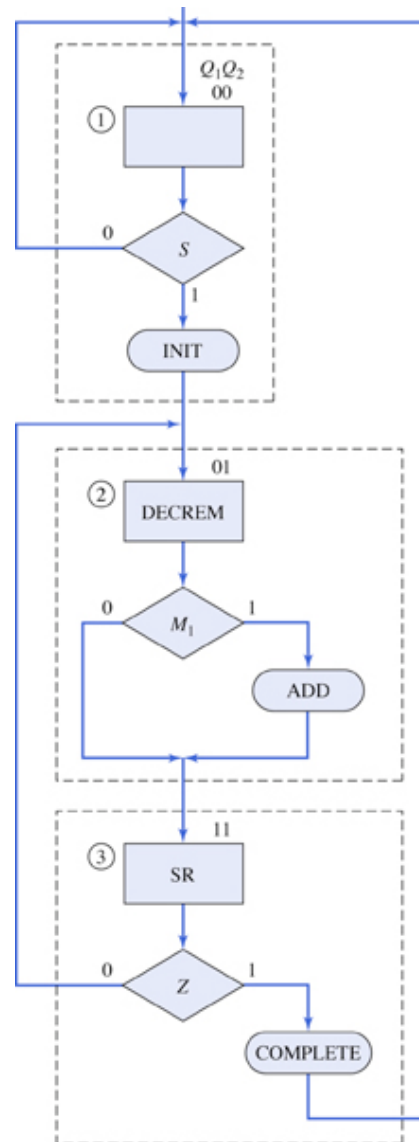

Assigned ASM Table

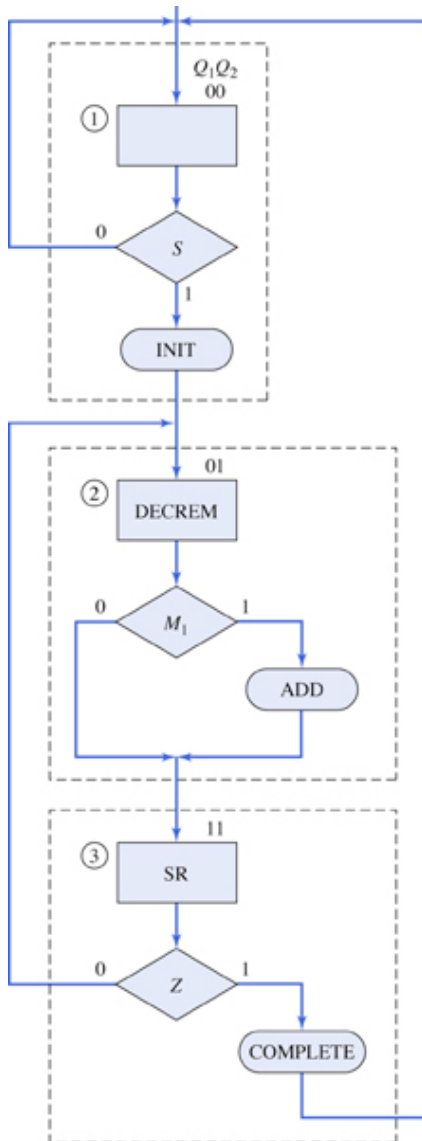

Link path	Present state			Inputs			Next state			Outputs				
	Sym	Q_1	Q_2	S	M_1	Z	Sym	Q_1^+	Q_2^+	INIT	DECREM	ADD	SR	COMPLETE
L_1	1	0	0	0	-	-	1	0	0	0	0	0	0	0
L_2	1	0	0	1	-	-	2	0	1	1	0	0	0	0
L_3	2	0	1	-	0	-	3	1	1	0	1	0	0	0
L_4	2	0	1	-	1	-	3	1	1	0	1	1	0	0
L_5	3	1	1	-	-	0	2	0	1	0	0	0	1	0
L_6	3	1	1	-	-	1	1	0	0	0	0	0	1	1

(b)

Note grouping of link paths

An ASM chart to illustrate state assignment.

Figure 8.21

A -> A,B

B -> A,C,D


C -> C,D

D -> E

E -> A

3 state bits needed

Assign codes to each state

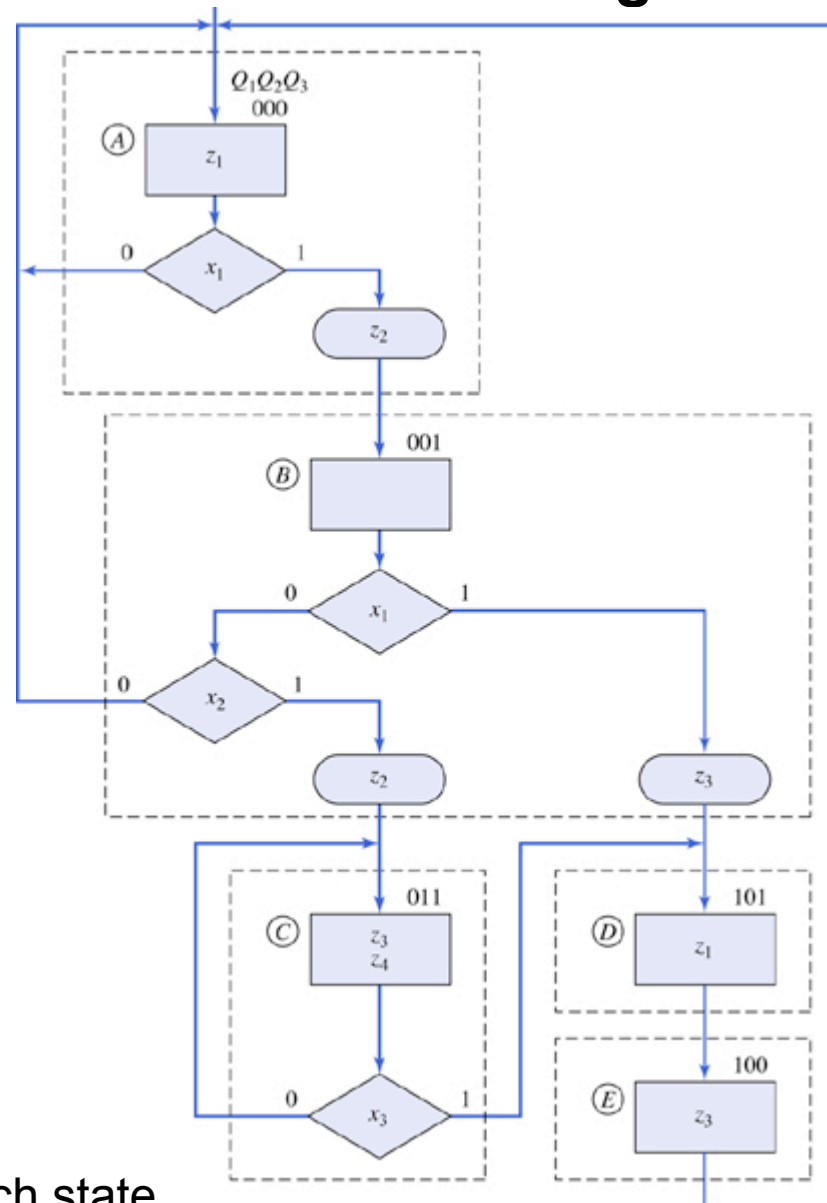

A minimum state locus assignment for the ASM chart of Fig. 8.21. (a) State-assignment map. (b) State locus.

Figure 8.22

		Q_2Q_3			
		00	01	11	10
Q_1	0	A	B	C	—
	1	E	D	—	—

(a)

State transition A	→	B = 000	→	001	1 bit change
State transition B	→	A = 001	→	000	1 bit change
State transition B	→	C = 001	→	011	1 bit change
State transition B	→	D = 001	→	101	1 bit change
State transition C	→	D = 011	→	101	2 bit changes
State transition D	→	E = 101	→	100	1 bit change
State transition E	→	A = 100	→	000	1 bit change
					<hr/>
					Total = 8 = state locus

(b)

Table 8.1 ASM tables for Fig. 8.21. (a) ASM transition table. (b) Assigned ASM transition table

Link path	Present state	Inputs			Next state	Outputs			
		x_1	x_2	x_3		z_1	z_2	z_3	z_4
L_1	A	0	—	—	A	1	0	0	0
L_2	A	1	—	—	B	1	1	0	0
L_3	B	0	0	—	A	0	0	0	0
L_4	B	0	1	—	C	0	1	0	0
L_5	B	1	—	—	D	0	0	1	0
L_6	C	—	—	0	C	0	0	1	1
L_7	C	—	—	1	D	0	0	1	1
L_8	D	—	—	—	E	1	0	0	0
L_9	E	—	—	—	A	0	0	1	0


(a)

Link path	Sym	Present state			Inputs			Sym	Next state			Outputs			
		Q_1	Q_2	Q_3	x_1	x_2	x_3		Q_1^+	Q_2^+	Q_3^+	z_1	z_2	z_3	z_4
L_1	A	0	0	0	0	—	—	A	0	0	0	1	0	0	0
L_2	A	0	0	0	1	—	—	B	0	0	1	1	1	0	0
L_3	B	0	0	1	0	0	—	A	0	0	0	0	0	0	0
L_4	B	0	0	1	0	1	—	C	0	1	1	0	1	0	0
L_5	B	0	0	1	1	—	—	D	1	0	1	0	0	1	0
L_6	C	0	1	1	—	—	0	C	0	1	1	0	0	1	1
L_7	C	0	1	1	—	—	1	D	1	0	1	0	0	1	1
L_8	D	1	0	1	—	—	—	E	1	0	0	1	0	0	0
L_9	E	1	0	0	—	—	—	A	0	0	0	0	0	1	0

(b)

Karnaugh map for simplifying the Q_1^+ function of Table 8.1b.

Figure 8.23

 

ASM Excitation Table defines FF input equations


Table 8.5 ASM excitation table for Table 8.1*b*

Link path	Present state				Inputs			Next state				Excitations						Outputs			
	Sym	Q_1	Q_2	Q_3	x_1	x_2	x_3	Sym	Q_1^+	Q_2^+	Q_3^+	J_1	K_1	J_2	K_2	J_3	K_3	z_1	z_2	z_3	z_4
L_1	A	0	0	0	0	–	–	A	0	0	0	0	–	0	–	0	–	1	0	0	0
L_2	A	0	0	0	1	–	–	B	0	0	1	0	–	0	–	1	–	1	1	0	0
L_3	B	0	0	1	0	0	–	A	0	0	0	0	–	0	–	–	1	0	0	0	0
L_4	B	0	0	1	0	1	–	C	0	1	1	0	–	1	–	–	0	0	1	0	0
L_5	B	0	0	1	1	–	–	D	1	0	1	1	–	0	–	–	0	0	0	1	0
L_6	C	0	1	1	–	–	0	C	0	1	1	0	–	–	0	–	0	0	0	1	1
L_7	C	0	1	1	–	–	1	D	1	0	1	1	–	–	1	–	0	0	0	1	1
L_8	D	1	0	1	–	–	–	E	1	0	0	–	0	0	–	–	1	1	0	0	0
L_9	E	1	0	0	–	–	–	A	0	0	0	–	1	0	–	0	–	0	0	1	0


Using variable-entered Karnaugh maps to obtain a discrete-gate realization with clocked D flip-flops

Link path	Sym	Present state			Inputs			Sym	Next state			Outputs			
		Q_1	Q_2	Q_3	x_1	x_2	x_3		Q_1^+	Q_2^+	Q_3^+	z_1	z_2	z_3	z_4
L_1	A	0	0	0	0	–	–	A	0	0	0	1	0	0	0
L_2	A	0	0	0	1	–	–	B	0	0	1	1	1	0	0
L_3	B	0	0	1	0	0	–	A	0	0	0	0	0	0	0
L_4	B	0	0	1	0	1	–	C	0	1	1	0	1	0	0
L_5	B	0	0	1	1	–	–	D	1	0	1	0	0	1	0
L_6	C	0	1	1	–	–	0	C	0	1	1	0	0	1	1
L_7	C	0	1	1	–	–	1	D	1	0	1	0	0	1	1
L_8	D	1	0	1	–	–	–	E	1	0	0	1	0	0	0
L_9	E	1	0	0	–	–	–	A	0	0	0	0	0	1	0


(b)

 
 
$$Q_1^+ = D_1 = x_1\bar{Q}_2Q_3 + x_3Q_2 + Q_1Q_3$$



 
$$Q_2^+ = D_2 = \bar{x}_1x_2\bar{Q}_1\bar{Q}_2Q_3 + \bar{x}_3Q_2$$



$$Q_3^+ = D_3 = x_1\bar{Q}_1 + x_2\bar{Q}_1Q_3 + Q_2$$

Using variable-entered Karnaugh maps to obtain a discrete-gate realization with clocked D flip-flops for the ASM chart of Fig. 8.21.

Figure 8.25

 

Using variable-entered Karnaugh maps to obtain a discrete-gate realization with clocked *JK* flip-flops for the ASM chart of Fig. 8.21.

	Q_2Q_3			
	00	01	11	10
Q_1 0	A	B	C	–
1	E	D	–	–

State-assignment map

	Q_2Q_3			
	00	01	11	10
Q_1 0	0	x_1	x_3	–
1	–	–	–	–

$$J_1 = x_1\bar{Q}_2Q_3 + x_3Q_2$$

	Q_2Q_3			
	00	01	11	10
Q_1 0	0	\bar{x}_1x_2	–	–
1	0	0	–	–

$$J_2 = \bar{x}_1x_2\bar{Q}_1Q_3$$

	Q_2Q_3			
	00	01	11	10
Q_1 0	x_1	–	–	–
1	0	–	–	–

$$J_3 = x_1\bar{Q}_1$$

	Q_2Q_3			
	00	01	11	10
Q_1 0	–	–	–	–
1	1	0	–	–

$$K_1 = \bar{Q}_3$$

	Q_2Q_3			
	00	01	11	10
Q_1 0	–	–	x_3	–
1	–	–	–	–

$$K_2 = x_3$$

	Q_2Q_3			
	00	01	11	10
Q_1 0	–	$\bar{x}_1\bar{x}_2$	0	–
1	–	1	–	–

$$K_3 = \bar{x}_1\bar{x}_2\bar{Q}_2 + Q_1$$


Assignment of inputs to a multiplexer for each excitation and output function.

Link path	Sym	Present state			Inputs			Sym	Next state			Outputs			
		Q_1	Q_2	Q_3	x_1	x_2	x_3		Q_1^+	Q_2^+	Q_3^+	z_1	z_2	z_3	z_4
L_1	A	0	0	0	0	—	—	A	0	0	0	1	0	0	0
L_2	A	0	0	0	1	—	—	B	0	0	1	1	1	0	0
L_3	B	0	0	1	0	0	—	A	0	0	0	0	0	0	0
L_4	B	0	0	1	0	1	—	C	0	1	1	0	1	0	0
L_5	B	0	0	1	1	—	—	D	1	0	1	0	0	1	0
L_6	C	0	1	1	—	—	0	C	0	1	1	0	0	1	1
L_7	C	0	1	1	—	—	1	D	1	0	1	0	0	1	1
L_8	D	1	0	1	—	—	—	E	1	0	0	1	0	0	0
L_9	E	1	0	0	—	—	—	A	0	0	0	0	0	1	0


(b)

One mux per function

 Each input function corresponds to cell function in variable-entered K-map




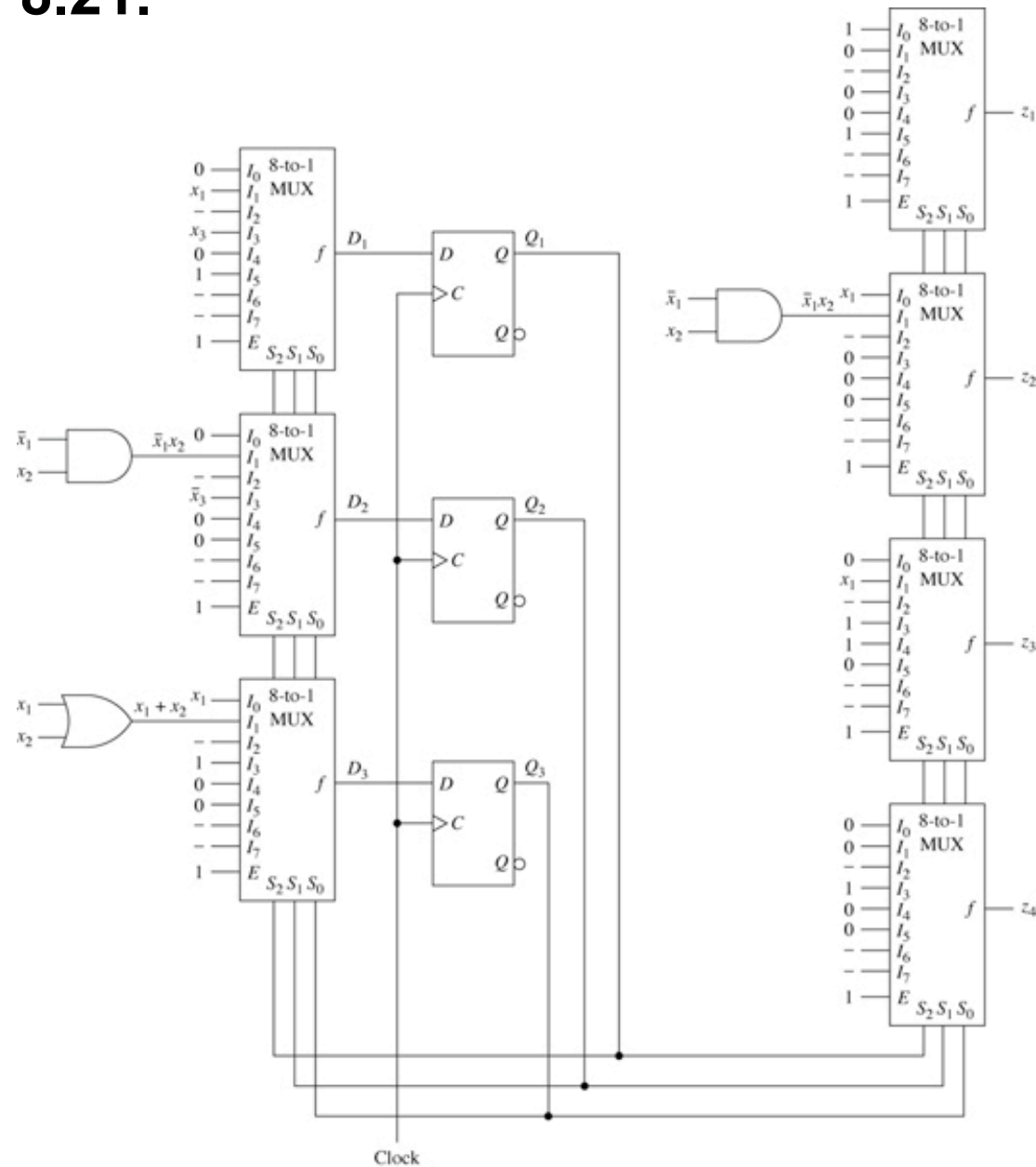
Multiplexer realization with clocked D flip-flops for the ASM chart of Fig. 8.21.



Fragments of ASM charts illustrating problems associated with asynchronous inputs. (a) Transition race. (b) Output race.

Figure 8.31

* Means asynchronous w.r.t. ASM clock

  

Using a clocked D flip-flop to synchronize an asynchronous input.

Figure 8.32

