 


Problems for Introduction to MOS

Lecture notes: Sec. 4

Exercise 1: Compute i_D ($\mu_p C_{ox} (W/L) = 0.4 \text{ mA/V}^2$, $V_{tp} = -3 \text{ V}$ and $\lambda = 0$).

- PMOS with $v_{SG} = 5 \text{ V}$ and $v_{GD} = 6 \text{ V}$.
- $V_{OV} = v_{SG} - |V_{tp}| = 5 - 3 = 2 \text{ V}$
 - $V_{OV} > 0 \rightarrow \text{MOS is ON}$
- $v_{SD} = v_{SG} + v_{GD} = 5 + 6 = 11 \text{ V}$
 - $v_{SD} = 11 > V_{OV} = 2 \rightarrow \text{MOS in saturation}$
- $i_D = 0.5 \mu_p C_{ox} \frac{W}{L} V_{OV}^2 = 0.5 \times 0.4 \times 10^{-3} (2)^2 = 0.8 \text{ mA}$



Exercise 2: Find V_S ($\mu_n C_{ox} (W/L) = 0.5 \text{ mA/V}^2$, $V_{tn} = 0.8 \text{ V}$ and $\lambda = 0$).

- Since $i_D = 10 \text{ } \mu\text{A}$, MOS is ON
- Assume MOS in saturation

$$i_D = 0.5 \mu_n C_{ox} \frac{W}{L} V_{OV}^2$$


$$10 \times 10^{-6} = 0.5 \times 0.5 \times 10^{-3} V_{OV}^2 \rightarrow V_{OV} = 0.2 \text{ V}$$

$$v_{GS} = V_{OV} + V_t = 0.2 + 0.8 = 1 \text{ V}$$

$$v_{GS} = V_G - V_S = 0 - V_S \rightarrow \underline{V_S = -1 \text{ V}}$$

$$v_{DS} = V_D - V_S = 7 - (-1) = 8 \text{ V}$$

$$v_{DS} = 8 > V_{OV} = 0.2 \text{ V} \quad (\text{MOS in saturation})$$

 


Exercise 3: Consider this PMOS with $\mu_p C_{ox} (W/L) = 0.6 \text{ mA/V}^2$, $V_{tp} = -1 \text{ V}$ and $\lambda = 0$.

- A) For what values of V_G , PMOS will be ON?
- B) For what values of V_D , PMOS will be in triode? (in terms of V_G)
- C) For what values of V_D , PMOS will be in saturation? (in terms of V_G)

$$v_{SG} = V_S - V_G = 5 - V_G$$

$$v_{SD} = V_S - V_D = 5 - V_D$$

$$V_{OV} = v_{SG} - |V_{tp}| = 5 - V_G - |V_{tp}| = 4 - V_G$$

 

- A) Range of V_G for MOS ON?

$$V_{OV} \geq 0 \rightarrow 4 - V_G \geq 0 \rightarrow \underline{V_G \leq 4 \text{ V}}$$

- B) Range of V_D for MOS in triode?

$$v_{SD} \leq V_{OV} \rightarrow 5 - V_D \leq 4 - V_G \rightarrow \underline{V_D \geq V_G + 1}$$

- C) Range of V_D for MOS in saturation?

$$v_{SD} \geq V_{OV} \rightarrow 5 - V_D \geq 4 - V_G \rightarrow \underline{V_D \leq V_G + 1}$$

Exercise 4: Find v_{GS} , v_{DS} , and i_D ($\mu_n C_{ox} (W/L) = 0.4 \text{ mA/V}^2$, $V_{tn} = 3 \text{ V}$ and $\lambda = 0$).

$$\text{GS-KVL: } 0 = 10^6 i_G + v_{GS} + 10^3 i_D - 15 = V_{OV} + V_t + 10^3 i_D - 15$$

$$\rightarrow 12 = V_{OV} + 10^3 i_D$$

$$\text{DS-KVL: } 15 = 10^3 i_D + v_{DS} + 10^3 i_D - 15$$

$$\rightarrow 30 = v_{DS} + 2 \times 10^3 i_D$$

➤ Not in cut-off as for $i_D = 0$, GS-KVL gives $V_{OV} = 12 \text{ V} > 0$.

➤ Assume MOS in saturation

$$i_D = 0.5 \mu_n C_{ox} \frac{W}{L} V_{OV}^2$$

$$\text{GS-KVL: } 12 = V_{OV} + 10^3 \times 0.5 \times 0.4 \times 10^{-3} V_{OV}^2$$


$$0.2 V_{OV}^2 + V_{OV} - 12 = 0$$

$$V_{OV} = -10.64 \text{ V} \quad (\text{incorrect, need } V_{OV} > 0)$$

$$V_{OV} = 5.64 \text{ V} \rightarrow v_{GS} = 8.64 \text{ V}$$

$$\text{GS-KVL: } 12 = V_{OV} + 10^3 i_D \rightarrow i_D = 6.36 \text{ mA}$$
 
$$\text{DS-KVL: } 30 = v_{DS} + 2 \times 10^3 i_D \rightarrow \underline{v_{DS} = 17.27 \text{ V}}$$



$$v_{DS} = 17.3 > V_{OV} = 5.64 \text{ V} \quad (\text{MOS in saturation})$$


Exercise 5: Find R such that PMOS is in saturation with $V_{OV} = 0.6$ V ($\mu_p C_{ox} = 0.1$ mA/V², $W/L = 10/0.18$, $V_{tp} = -0.4$ V and $\lambda = 0$).

In an IC, W/L (typically specified as a fraction) is a design parameter for MOS circuits.

$$i_D = 0.5 \mu_p C_{ox} \frac{W}{L} V_{OV}^2 = 0.5 \times 0.1 \times 10^{-3} \times (10/0.18) \times (0.6)^2 = 1 \text{ mA}$$

$$\begin{aligned} \text{SG - KVL: } 1.8 &= R i_D + v_{SG} \\ &= 10^{-3} R + V_{OV} + |V_{tp}| \\ 1.8 &= 10^{-3} R + 0.6 + 0.4 \\ \underline{R} &= 800 \, \Omega \end{aligned}$$

$$\begin{aligned} \text{SD - KVL: } 1.8 &= R i_D + v_{SD} \rightarrow v_{SD} = 1.0 \text{ V} \\ v_{SD} = 1.0 &> V_{OV} = 0.6 \rightarrow \text{MOS in saturation} \end{aligned}$$

 

Exercise 6: Find V_D ($\mu_n C_{ox} (W/L) = 0.5 \text{ mA/V}^2$, $V_{tn} = 0.8 \text{ V}$ and ignore channel-width modulation).

- When the gate and drain of a MOS are connected to each other, MOS becomes a 2-terminal device.
 - Called diode-connected transistor
- If MOS is ON ($v_{DS} = v_{GS} \geq V_{tn}$), MOS will always be in saturation!
 - $v_{DS} = v_{GS} \geq v_{GS} - V_{tn} = V_{OV}$

$$i_D = 0.5 \mu_n C_{ox} \frac{W}{L} V_{OV}^2$$


DS/GS - KVL: $5 = 10^3 i_D + v_{GS} = 10^3 \times 0.5 \times 0.5 \times 10^{-3} V_{OV}^2 + V_{OV} + V_m$

$$0.25 V_{OV}^2 + V_{OV} - 4.2 = 0$$

$$V_{OV} = -6.56 \text{ V} \quad (\text{incorrect, need } V_{OV} > 0)$$

$$V_{OV} = 2.56 \text{ V}$$

$$v_{GS} = V_{OV} + V_m \rightarrow V_D = v_{DS} = v_{GS} = 3.36 \text{ V}$$

 

Exercise 7: Find V_1 and V_2 ($\mu_n C_{ox} (W/L) = 5 \text{ mA/V}^2$, $V_t = 1 \text{ V}$ and ignore channel-width modulation).

$$\text{GS1-KVL: } 0 = v_{GS1} + 10^3 i_D - 2.5 = V_{OV1} + V_t + 10^3 i_D - 2.5$$


$$\rightarrow V_{OV1} + 10^3 i_D = 1.5$$

$$\text{GS2-KVL: } 2.5 = v_{GS2} + v_{DS1} + 10^3 i_D - 2.5$$

$$\text{DS-KVL: } 2.5 = v_{DS2} + v_{DS1} + 10^3 i_D - 2.5$$

$$\text{KCL: } i_{D1} = i_{D2} = i_D$$

 - Q1 is not in cut-off as for $i_{D1} = 0$, GS1-KVL gives $V_{OV} = 1.5 \text{ V} > 0$.
 - Q2 is not in cut-off either as $i_{D1} = i_{D2} > 0$



Exercise 7 (cont'd) : Find V_1 and V_2 ($\mu_n C_{ox} (W/L) = 5 \text{ mA/V}^2$, $V_t = 1 \text{ V}$ and ignore channel-width modulation).

Assume both MOS in saturation

$$i_D = i_{D1} = 0.5 \mu_n C_{ox} \frac{W}{L} V_{OV1}^2$$

$$\text{GS1-KVL: } 1.5 = V_{OV1} + 10^3 i_D = V_{OV1} + 10^3 \times 0.5 \times 5 \times 10^{-3} V_{OV1}^2$$

$$2.5 V_{OV1}^2 + V_{OV1} - 1.5 = 0$$

$$V_{OV1} = -1.0 \text{ V} \quad (\text{incorrect, need } V_{OV} > 0)$$

$$V_{OV1} = 0.60 \text{ V}$$


Both MOS in saturation, $i_{D2} = i_{D1}$ and $\lambda = 0$: $V_{OV2} = V_{OV1} = 0.60 \text{ V}$

$$v_{GS1} = V_{OV1} + V_t = 0.6 + 1 = 1.6 \text{ V}$$

$$v_{GS1} = V_{G1} - V_{S1} = 0 - V_2 \rightarrow V_2 = -1.6 \text{ V}$$

$$v_{GS2} = V_{OV2} + V_t = 0.6 + 1 = 1.6 \text{ V}$$
 
$$v_{GS2} = V_{G2} - V_{S2} = 2.5 - V_1 \rightarrow V_1 = 0.9 \text{ V}$$



Exercise 7 (cont'd) : Find V_1 and V_2 ($\mu_n C_{ox} (W/L) = 5 \text{ mA/V}^2$, $V_t = 1 \text{ V}$ and ignore channel-width modulation).


Need to confirm our assumption of both MOS in saturation

$$v_{DS1} = V_{D1} - V_{S1} = V_1 - V_2 = 0.90 - (-1.6) = 2.5 \text{ V}$$

$$v_{DS1} = 2.5 > V_{OV1} = 0.6 \text{ V}$$

$$v_{DS2} = V_{D2} - V_{S2} = 2.5 - V_1 = 2.5 - 0.9 = 1.6 \text{ V}$$
 
$$v_{DS2} = 1.6 > V_{OV2} = 0.6 \text{ V}$$



For circuits with multiple transistors, it is usually advantageous to keep track of node voltages (at transistor terminals!)