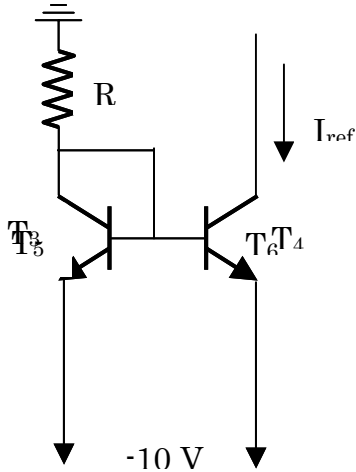


# ELE222E INTRODUCTION TO ELECTRONICS (21271)

Midterm Exam #2 ✍ 14 April 2004 🕒 10.00-12.00

İnci ÇİLESİZ, PhD, Özgür ATEŞ, BSE

## SOLUTIONS




1. Design a current mirror based constant current source for 1 mA DC current using pnp transistors. **HINT:** On the left is a current mirror designed with npn transistors. (30 points)

The current mirror shown on the left is not suitable for use with the 3-stage amplifier of (2) because of the direction  $I_{ref}$  flows. However, with a simple modification like shown on the right we can use that current mirror to bias the differential first stage in (2).

Neglecting base currents we can find the resistor value as follows
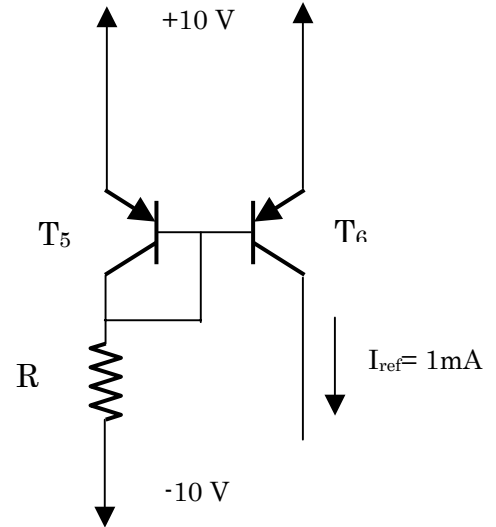
$$R = \frac{+10V - (-10V) - 0,6V}{1mA} = 19k.$$



2. Using the current mirror designed in (1) find  $R_1$ ,  $R_3$ ,  $I_{C3}$  and  $I_{C4}$  in the 3-stage amplifier circuit given below for  $V_o = 0V$  and  $r_o = 50\Omega$ . **Note,**  $h_{FE} = h_{fe} = 250$ ,  $V_T = 25$  mV,  $|V_{BE}| = 0,6$  V,  $h_{oe} = h_{re} = 0$ . (30 points)


Since the last stage on the right is an emitter follower, the  $50\Omega$  output resistance will be determined by the AC output resistance

$$r_o = R_{e4} \parallel R_3 \cong R_{e4}$$

where

$$R_{e4} = r_{e4} + \frac{r_{o3}}{h_{fe}} = \frac{V_T}{I_{C4}} + \frac{10k}{250}$$

Thus

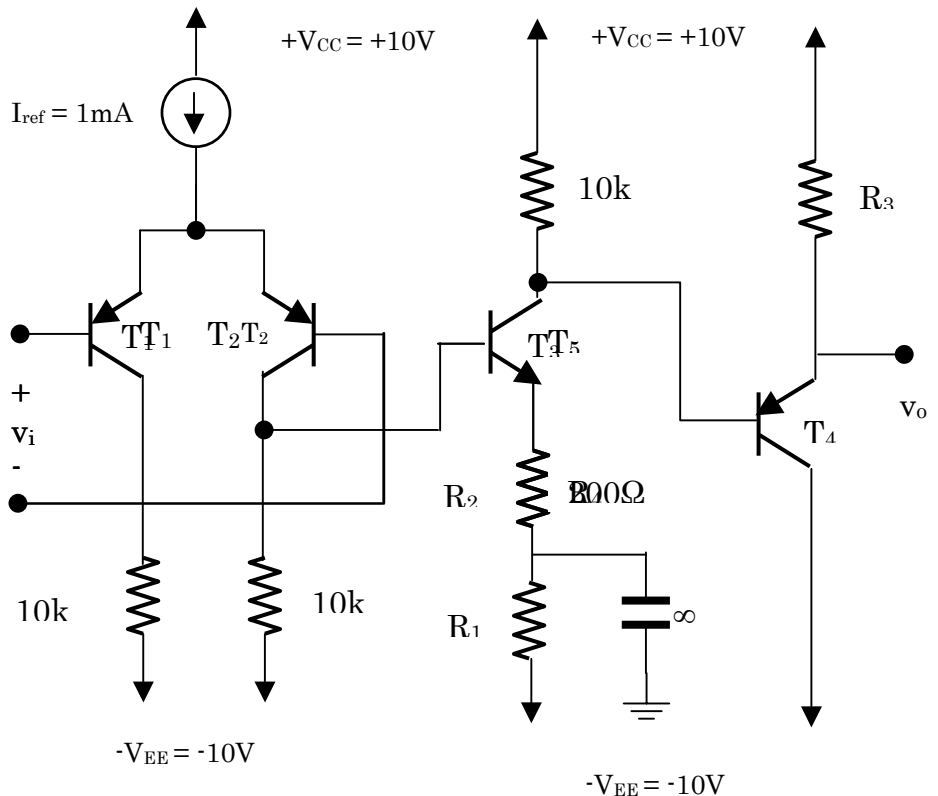

$$I_{C4} = \frac{25mV}{50\Omega - \frac{10k}{250}} = \underline{\underline{2,5mA}}$$

$$\Rightarrow I_{E4} = 2,51mA$$

$$R_3 = \frac{+V_{CC} - V_o}{I_{E4}} = \frac{10V - 0V}{2,51mA} = \underline{\underline{3,98k\Omega}}$$

Let's check the output resistance:

$$r_o = R_{e4} \parallel R_3 = 50\Omega \parallel 3k98 = 49,4\Omega$$

Using  $R_4$ ,  $T_4$ ,  $R_3$  loop

$$(I_{C3} - I_{B4})R_4 + V_{BE4} - I_{E4}R_3 = 0$$

$$\Rightarrow I_{C3} = \frac{I_{E4}R_3 + I_{B4}R_4 - V_{BE4}}{R_4} = \frac{2,51mA * 3k98 + 10\mu A * 10k + 0,6V}{10k} = \underline{\underline{1,07mA}}$$

Using  $R_{C2}$ ,  $T_3$ ,  $R_2$  loop

$$-(0,5mA - I_{B3})R_{C2} + V_{BE3} + I_{E3}(R_1 + R_2) = 0$$

$$\Rightarrow R_1 = \frac{(0,5mA - I_{B3})R_{C2} - V_{BE3}}{I_{E3}} - R_2 = \frac{(0,5mA - 4,28\mu A)10k - 0,6V}{1,073mA} - 200\Omega = \underline{\underline{3k86}}$$

3. Using the biasing current values you found in (2) do the AC analysis of the circuit below and find the total voltage gain, CMRR, and the differential input resistance. (40 points)

**If you could not find the collector currents correctly in (2), use the following values and do the AC analysis:**

$$R_1 = R_3 = 4k;$$

$$I_{C3} = I_{C4} = 1 \text{ mA}$$

Let's first find the transistor AC resistances:

$$r_{e1} = r_{e2} = \frac{V_T}{0,5mA} = 50\Omega; r_{e3} = \frac{V_T}{1,07mA} = 23,3\Omega; r_{e4} = \frac{V_T}{2,5mA} = 10\Omega$$

$$A_v = \frac{v_o}{v_i} = \frac{v_o}{v_{b4}} \cdot \frac{v_{b4}}{v_{b3}} \cdot \frac{v_{b3}}{v_i} = + \frac{R_{e4}}{r_{e4} + R_{e4}} \cdot \left[ - \frac{R_{C3} \parallel r_{i4}}{r_{e3} + R_{e3}} \right] \cdot \left[ - \frac{R_{C2} \parallel r_{i3}}{2r_{e1}} \right]$$

$$r_{i3} = h_{fe}(r_{e3} + R_{e3}) = 250(23,3 + 200) = \underline{\underline{55k8}}; r_{i4} = h_{fe}(r_{e4} + R_{e4}) = 250(10 + 3k98) = \underline{\underline{997k5}}$$

$$\Rightarrow A_v = \frac{3k98}{10 + 3k98} \cdot \left[ - \frac{10k \parallel 997k5}{23,3 + 200} \right] \cdot \left[ - \frac{10k \parallel 55k8}{100} \right] \cong \underline{\underline{3748}}$$

$$CMRR = 20 \log \left| \frac{2R_e + r_{e1}}{r_{e1}} \right|, \text{ since the current source is ideal } R_e \text{ is infinite, thus } CMRR \rightarrow \infty$$

$$\text{and finally } r_{id} = 2h_{fe}r_{e1} = 2 * 250 * 50 = \underline{\underline{25k}}$$