

Lecture 20

Bipolar Junction Transistors (BJT): Part 4

Small Signal BJT Model

Reading:


Jaeger 13.5-13.6, Notes

Further Model Simplifications

(useful for circuit analysis)

$$\begin{array}{ccc} \text{Ebers-Moll} & \text{Forward Active Mode} & \text{Neglect Small Terms} \\ \underbrace{I_C = \alpha_F I_{F0} \left(e^{V_{EB}/V_T} - 1 \right) - I_{R0} \left(e^{V_{CB}/V_T} - 1 \right)} & \Rightarrow \underbrace{I_C = \alpha_F I_{F0} \left(e^{V_{EB}/V_T} - 1 \right) + I_{R0}} & \Rightarrow \underbrace{I_C = I_S e^{V_{EB}/V_T}} \end{array}$$

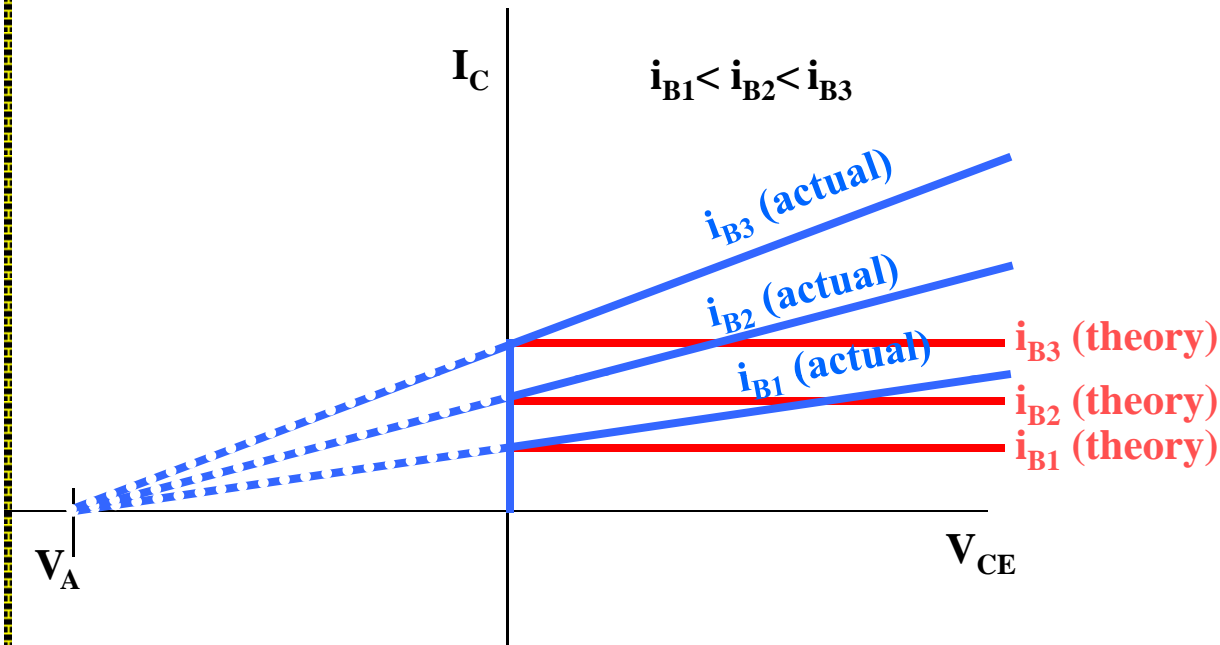Modeling the “Early Effect” (non-zero slopes in IV curves)



- Base width changes due to changes in the base-collector depletion width with changes in V_{CB} .

- This changes α_T , which changes I_C , α_{DC} and B_F


Major BJT Circuit Relationships

$$i_C = I_S e^{V_{EB}/V_T} \Rightarrow i_C = I_S e^{V_{EB}/V_T} \left[1 + \frac{V_{CE}}{V_A} \right] \quad \beta_F = \beta_{FO} \left[1 + \frac{V_{CE}}{V_A} \right] \quad i_B = \frac{i_C}{\beta_F} = \frac{I_S}{\beta_{FO}} e^{V_{EB}/V_T}$$

Small Signal Model of a BJT

- Just as we did with a p-n diode, we can break the BJT up into a large signal analysis and a small signal analysis and “linearize” the non-linear behavior of the Ebers-Moll model.
- Small signal Models are only useful for Forward active mode and thus, are derived under this condition. (Saturation and cutoff are used for switches which involve very large voltage/current swings from the on to off states.)
- Small signal models are used to determine amplifier characteristics (Example: “Gain” = Increase in the magnitude of a signal at the output of a circuit relative to it’s magnitude at the input of the circuit).
- Warning: Just like when a diode voltage exceeds a certain value, the non-linear behavior of the diode leads to distortion of the current/voltage curves (see previous lecture), if the inputs/outputs exceed certain limits, the full Ebers-Moll model must be used.


Consider the BJT as a two-port Network

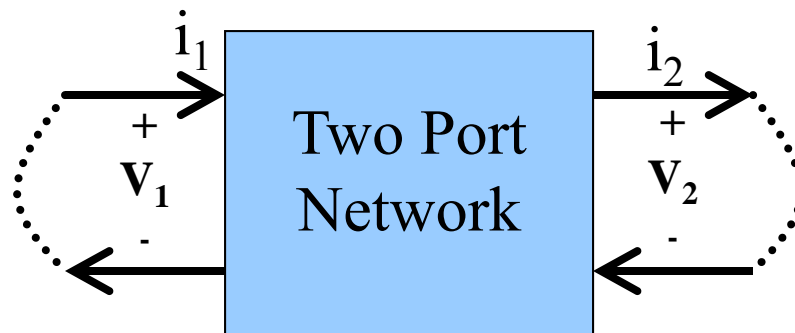

General “y-parameter” Network

$$i_1 = y_{11}v_1 + y_{12}v_2$$


$$i_2 = y_{21}v_1 + y_{22}v_2$$

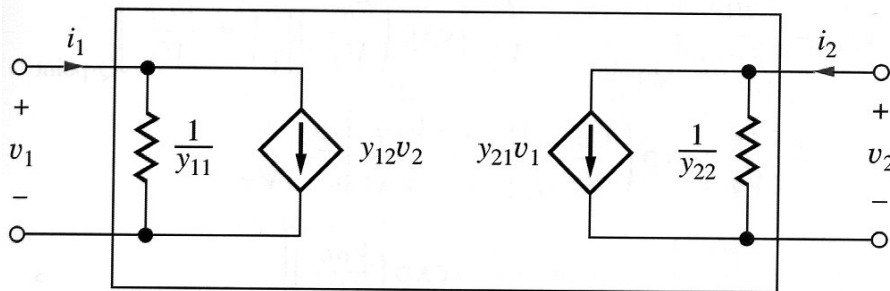

BJT “y-parameter” Network

$$i_b = y_{11}v_{be} + y_{12}v_{ce}$$


$$i_c = y_{21}v_{be} + y_{22}v_{ce}$$

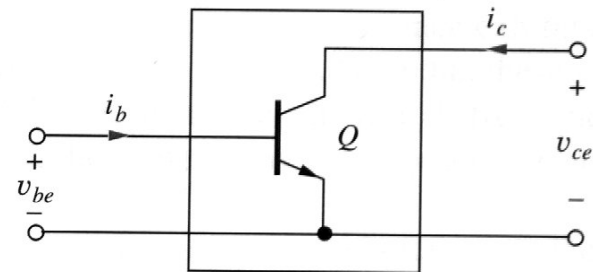

Consider the BJT as a two-port Network

$$i_b = y_{11}v_{be} + y_{12}v_{ce}$$

$$i_c = y_{21}v_{be} + y_{22}v_{ce}$$

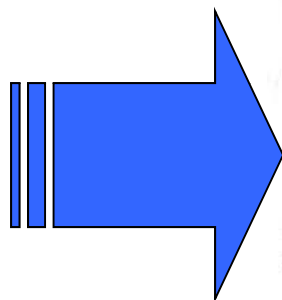

$$y_{11} = \left. \frac{i_b}{v_{be}} \right|_{v_{ce}=0} = \left. \frac{\partial i_B}{\partial v_{BE}} \right|_{Q\text{-point}}$$

$$y_{12} = \left. \frac{i_b}{v_{ce}} \right|_{v_{be}=0} = \left. \frac{\partial i_B}{\partial v_{CE}} \right|_{Q\text{-point}}$$

$$y_{21} = \left. \frac{i_c}{v_{be}} \right|_{v_{ce}=0} = \left. \frac{\partial i_C}{\partial v_{BE}} \right|_{Q\text{-point}}$$

$$y_{22} = \left. \frac{i_c}{v_{ce}} \right|_{v_{be}=0} = \left. \frac{\partial i_C}{\partial v_{CE}} \right|_{Q\text{-point}}$$

Consider the BJT as a two-port Network

$$y_{11} = \left. \frac{i_b}{v_{be}} \right|_{v_{ce}=0} = \left. \frac{\partial i_B}{\partial v_{BE}} \right|_{Q\text{-point}}$$

$$y_{12} = \left. \frac{i_b}{v_{ce}} \right|_{v_{be}=0} = \left. \frac{\partial i_B}{\partial v_{CE}} \right|_{Q\text{-point}}$$

$$y_{21} = \left. \frac{i_c}{v_{be}} \right|_{v_{ce}=0} = \left. \frac{\partial i_C}{\partial v_{BE}} \right|_{Q\text{-point}}$$

$$y_{22} = \left. \frac{i_c}{v_{ce}} \right|_{v_{be}=0} = \left. \frac{\partial i_C}{\partial v_{CE}} \right|_{Q\text{-point}}$$

$$y_{12} = \left. \frac{\partial i_B}{\partial v_{CE}} \right|_{Q\text{-point}} = 0$$

$$y_{21} = \left. \frac{\partial i_C}{\partial v_{BE}} \right|_{Q\text{-point}} = \frac{I_S}{V_T} \left[\exp\left(\frac{v_{BE}}{V_T}\right) \right] \left[1 + \frac{v_{CE}}{V_A} \right]_{Q\text{-point}}$$

$$y_{21} = \frac{I_S}{V_T} \left[\exp\left(\frac{V_{BE}}{V_T}\right) \right] \left[1 + \frac{V_{CE}}{V_A} \right] = \frac{I_C}{V_T}$$

$$y_{22} = \left. \frac{\partial i_C}{\partial v_{CE}} \right|_{Q\text{-point}} = \frac{I_S}{V_A} \left[\exp\left(\frac{v_{BE}}{V_T}\right) \right]_{Q\text{-point}}$$

$$y_{22} = \frac{I_S}{V_A} \left[\exp\left(\frac{V_{BE}}{V_T}\right) \right] = \frac{I_C}{V_A + V_{CE}}$$

$$y_{11} = \left. \frac{\partial i_B}{\partial v_{BE}} \right|_{Q\text{-point}} = \left[\frac{1}{\beta_F} \frac{\partial i_C}{\partial v_{BE}} - \frac{i_C}{\beta_F^2} \frac{\partial \beta_F}{\partial v_{BE}} \right]_{Q\text{-point}}$$

$$y_{11} = \frac{1}{\beta_F} \frac{\partial i_C}{\partial v_{BE}} \left[1 - \frac{i_C}{\beta_F} \frac{\partial \beta_F}{\partial i_C} \right]_{Q\text{-point}} = \frac{I_C}{\beta_F V_T} \left[1 - \left(\frac{i_C}{\beta_F} \frac{\partial \beta_F}{\partial i_C} \right)_{Q\text{-point}} \right]$$

$$y_{11} = \left[\frac{1}{\beta_F} \frac{\partial i_C}{\partial v_{BE}} - \frac{i_C}{\beta_F^2} \frac{\partial \beta_F}{\partial i_C} \frac{\partial i_C}{\partial v_{BE}} \right]_{Q\text{-point}}$$

$$y_{11} = \frac{I_C}{\beta_o V_T}$$

$$\text{where } \beta_o = \frac{\beta_F}{\left[1 - I_C \left(\frac{1}{\beta_F} \frac{\partial \beta_F}{\partial i_C} \right)_{Q\text{-point}} \right]}$$

β_o is most often taken as a constant, β_F


Alternative Representations

Transconductance $g_m = y_{21} = \frac{I_C}{V_T} \approx 40I_C$


Input Resistance $r_\pi = \frac{1}{y_{11}} = \frac{\beta_o V_T}{I_C} = \frac{\beta_o}{g_m}$

Output Resistance $r_o = \frac{1}{y_{22}} = \frac{V_A + V_{CE}}{I_C}$

Y-parameter Model

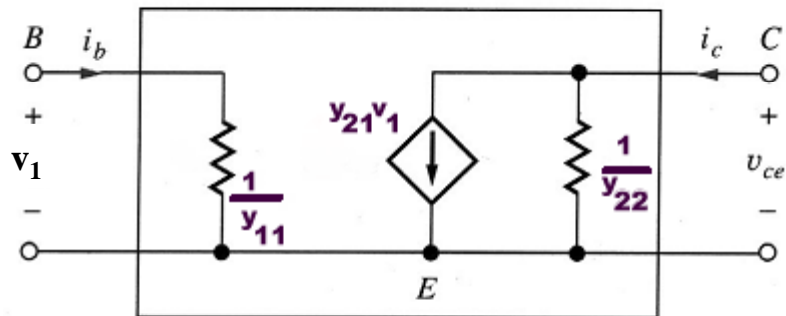


Hybrid-pi Model

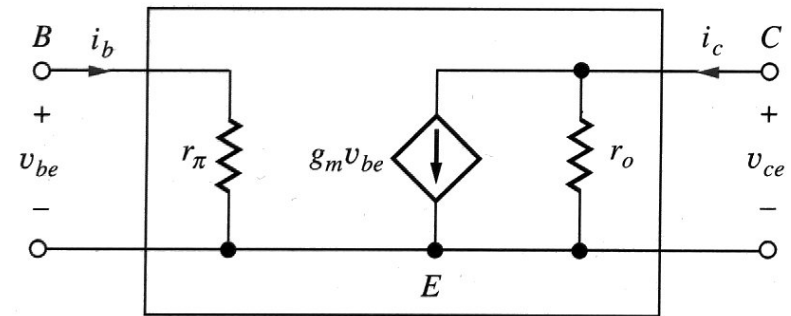


Alternative Representations

$$g_m v_{be} = g_m r_\pi i_b = \beta_o i_b$$

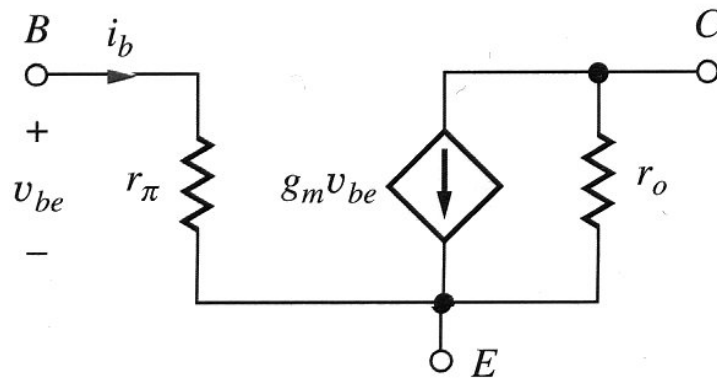Voltage Controlled Current
source version of Hybrid-pi
Model



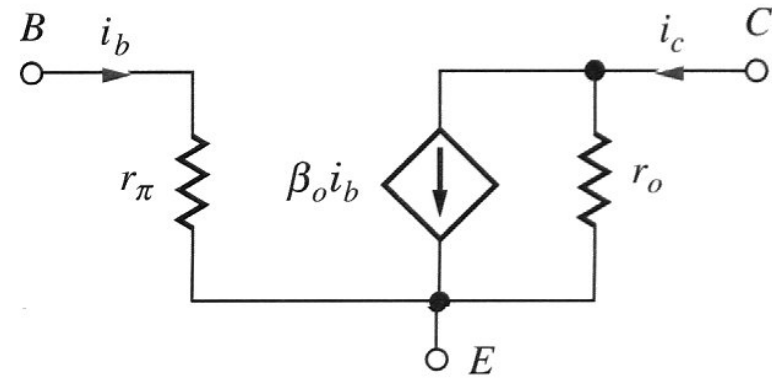Current Controlled Current
source version of Hybrid-pi
Model




Single Transistor Amplifier Analysis: Summary of Procedure

Important!


Steps to Analyze a Transistor Amplifier

- 1.) Determine DC operating point and calculate small signal parameters (see next page)
- 2.) Convert to the AC only model.
 - DC Voltage sources are shorts to ground
 - DC Current sources are open circuits
 - Large capacitors are short circuits
 - Large inductors are open circuits
- 3.) Use a Thevenin circuit (sometimes a Norton) where necessary. Ideally the base should be a single resistor + a single source. **Do not confuse this with the DC Thevenin you did in step 1.**
- 4.) Replace transistor with small signal model
- 5.) Simplify the circuit as much as necessary.
- 6.) Calculate the small signal parameters (r_π , g_m , r_o etc...) and then gains etc...


Step 1

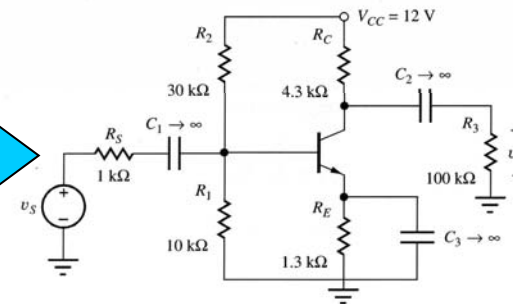


Step 2

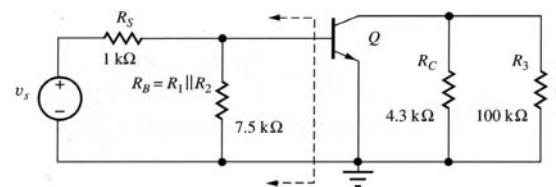


Step 3

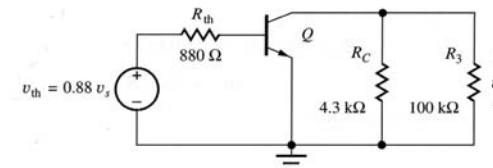

Step 4

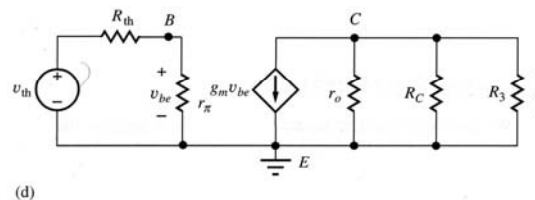

Step 5

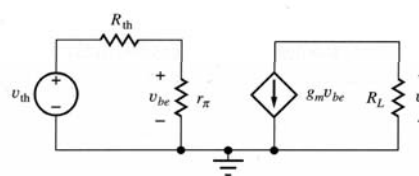


Single Transistor Amplifier Analysis

Step 1 detail

DC Bias Point

Important!

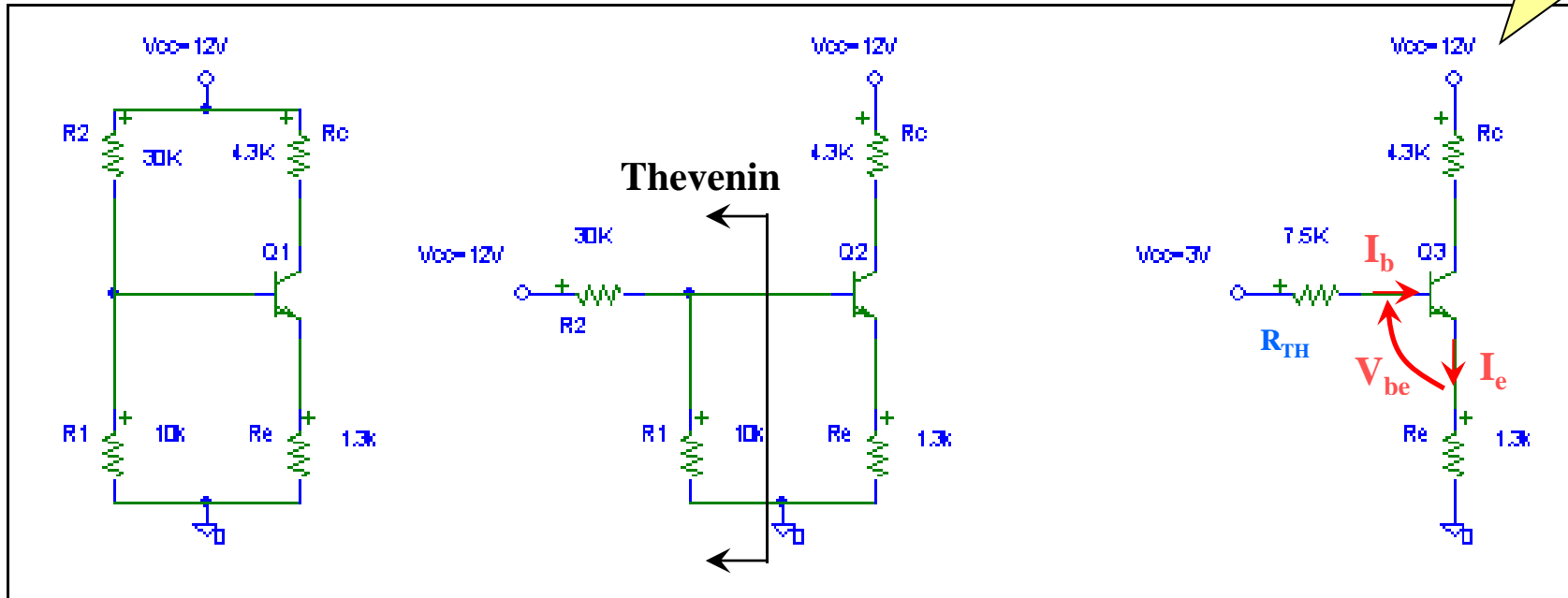

$$3V = I_E R_E + V_{be} + I_B R_{TH}$$

$$3V = I_C ((\beta_o + 1) / \beta_o) R_E + 0.7V + I_B R_{TH}$$

$$3V = I_B \beta_o ((\beta_o + 1) / \beta_o) R_E + 0.7V + I_B R_{TH}$$

$$3V = I_B (100 + 1) 1300 + 0.7 + I_B 7500$$

$$I_B = 16.6 \mu A, I_C = I_B \beta_o = 1.66 \text{ mA}, I_E = (\beta_o + 1) I_C / \beta_o = 1.67 \text{ mA}$$

Single Transistor Amplifier Analysis

Step 6 detail


Calculate small signal parameters

Important!

Transconductance $g_m = y_{21} = \frac{I_C}{V_T} \approx 40 I_C = 0.0664 \text{ S}$

Input Resistance $r_\pi = \frac{1}{y_{11}} = \frac{\beta_o V_T}{I_C} = \frac{\beta_o}{g_m} = 1506 \text{ } \Omega$

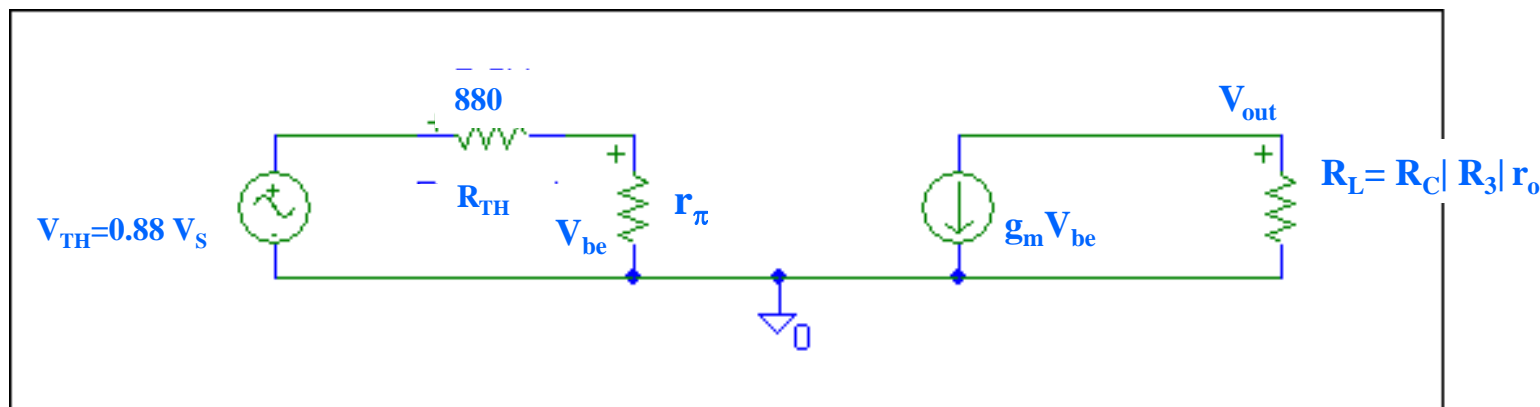Output Resistance $r_o = \frac{1}{y_{22}} = \frac{V_A + V_{CE}}{I_C} \approx \frac{V_A}{I_C} = 45.2 \text{ K } \Omega$



$$v_{out} = -g_m v_{be} R_L \text{ and } v_{be} = v_{Th} \frac{r_\pi}{R_{Th} + r_\pi} \text{ and } v_{Th} = 0.88 v_S$$

↓

$$A_v \equiv \text{Voltage Gain} = \frac{v_{out}}{v_S} = \left(\frac{v_{out}}{v_{be}} \right) \left(\frac{v_{be}}{v_{th}} \right) \left(\frac{v_{th}}{v_S} \right) = (-g_m R_L) \left(\frac{r_\pi}{R_{Th} + r_\pi} \right) (0.88)$$

$$A_v = (- (0.0664) (45,200 \parallel 4300 \parallel 100,000)) \left(\frac{1506}{880 + 1506} \right) (0.88)$$

$$A_v = -139 \text{ V/V}$$

For Extra Examples see:
Jaeger section 13.6, and
pages 627-630 (top of 630)

Georgia Tech

ECE 3040 - Dr. Alan Doolittle




Important!

**Supplement Added to describe more details of the
Solution of this Problem**

Bipolar Junction Transistors (BJT): Part 5
Details of Amplifier Analysis

Reading:
Jaeger 13.5-13.6, Notes

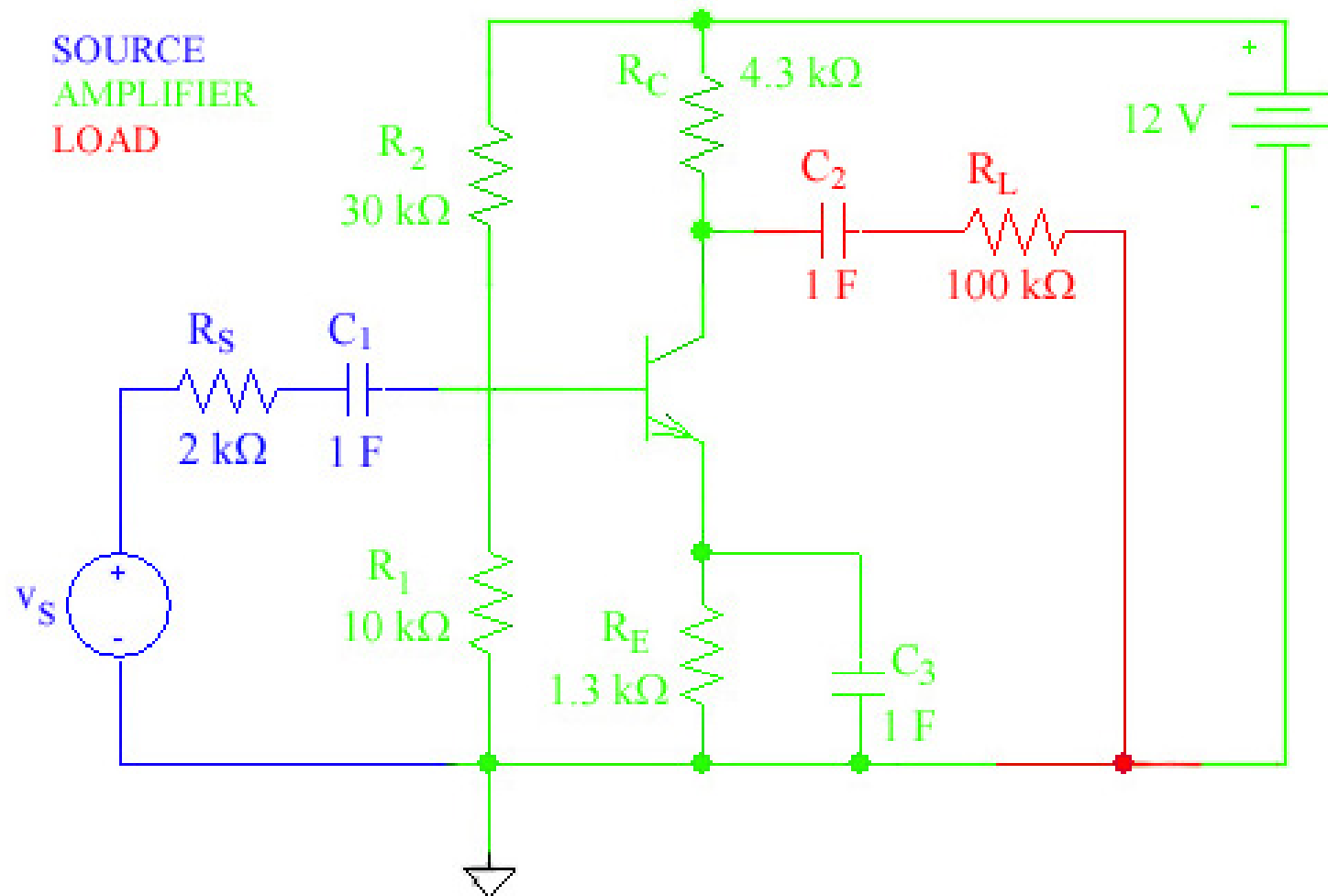Detailed Example: Single Transistor Amplifier Analysis



Notes on slides 14-25 were prepared by a previous student.


Step 1: Determine DC Operating Point

Remove the Capacitors



Because the impedance of a capacitor is $Z = 1/(j\omega C)$, capacitors have infinite impedance or are open circuits in DC ($\omega = 0$).

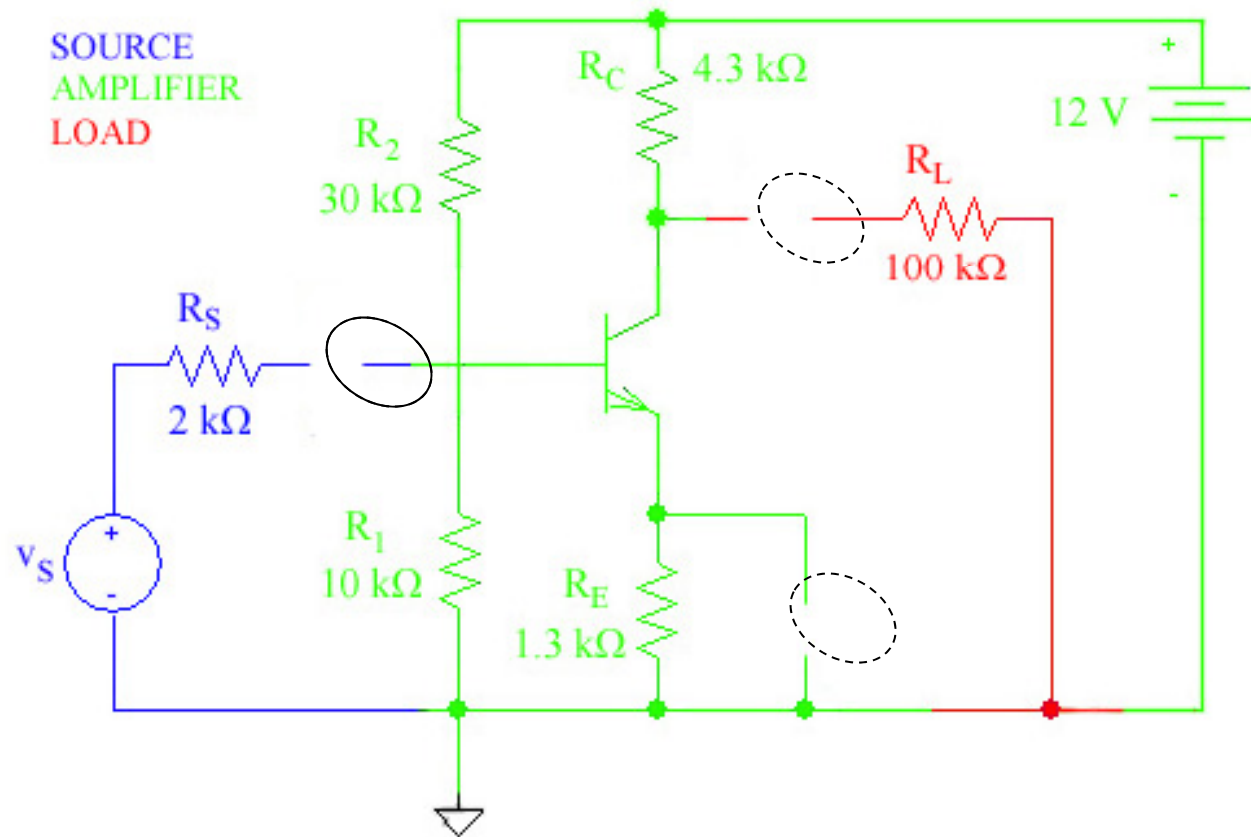Inductors (not present in this circuit) have an impedance $Z = j\omega L$, and are shorts in DC.




Step 1: Determine DC Operating Point

Determine the DC Thevenin Equivalent



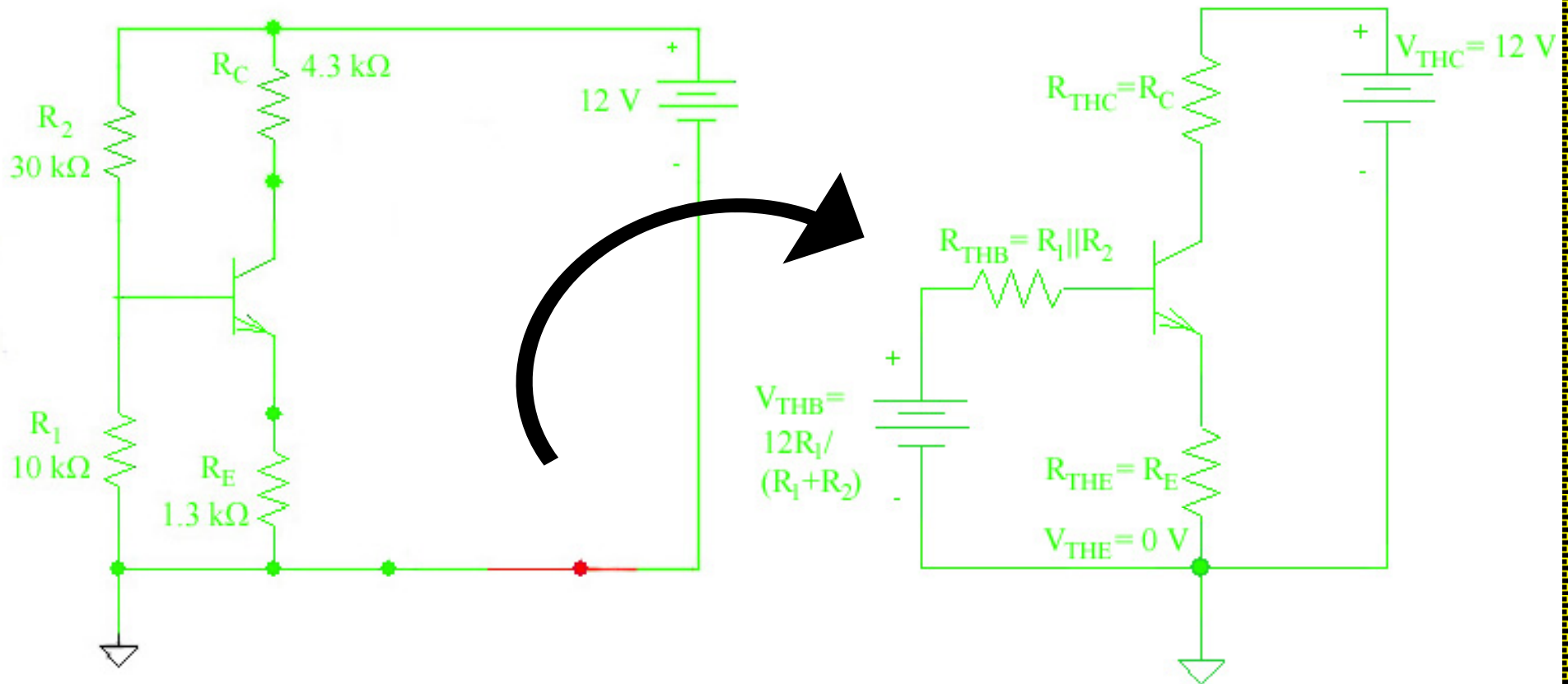Replace all connections to the transistor with their Thevenin equivalents.



Step 1: Determine DC Operating Point

Calculate Small Signal Parameters

Important!

Identify the type of transistor (nnp in this example) and draw the **base**, **collector**, and **emitter** currents in their proper direction and their corresponding voltage polarities.

Applying KVL to the controlling loop (loop 1):

$$V_{THB} - I_B R_{THB} - V_{BE} - I_E R_E = 0$$

Applying KCL to the transistor:


$$I_E = I_B + I_C$$

Because $I_C = \beta I_B$,

$$I_E = I_B + I_C = I_B + \beta I_B = I_B(1 + \beta)$$

Substituting for I_E in the loop equation:
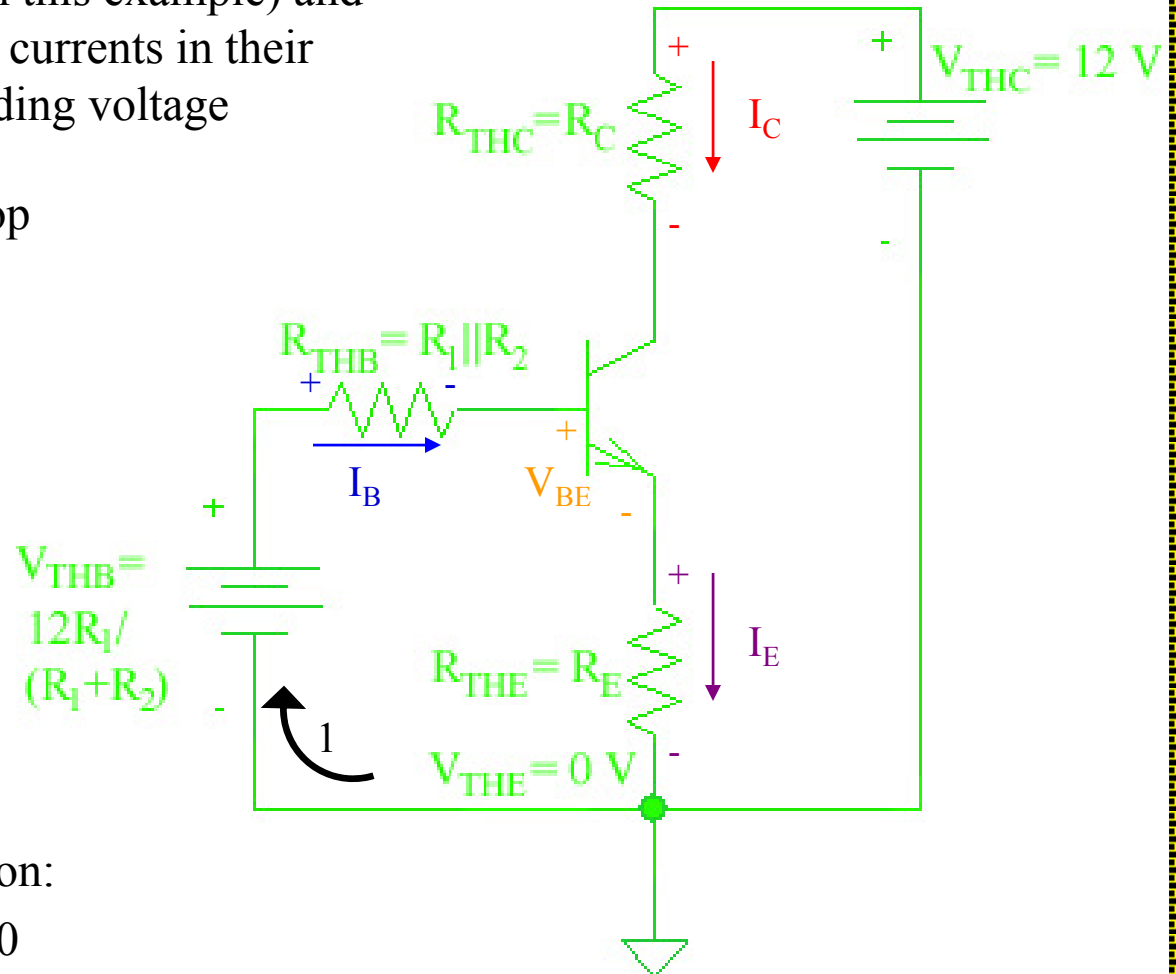
$$V_{THB} - I_B R_{THB} - V_{BE} - I_B(1 + \beta) R_E = 0$$



Step 1: Determine DC Operating Point

Plug in the Numbers

Important!

$$V_{THB} - I_B R_{THB} - V_{BE} - I_B(1+\beta)R_E = 0$$

$$V_{THB} - V_{BE} - I_B(R_{THB} + (1+\beta)R_E) = 0$$

$$V_{THB} = 12R_1/(R_1+R_2) = 3 \text{ V}$$

$$R_{THB} = R_1 \parallel R_2 = 7.5 \text{ k}\Omega$$

$$\text{Assume } V_{BE} = 0.7 \text{ V}$$


Assume β for this particular transistor is given to be 100.

$$3 - 0.7 - I_B(7500 + (1+100)*1300) = 0$$

$$I_B = 16.6 \text{ }\mu\text{A}$$

$$I_C = \beta I_B = 1.66 \text{ mA}$$

$$I_E = I_B + I_C = 1.676 \text{ mA}$$

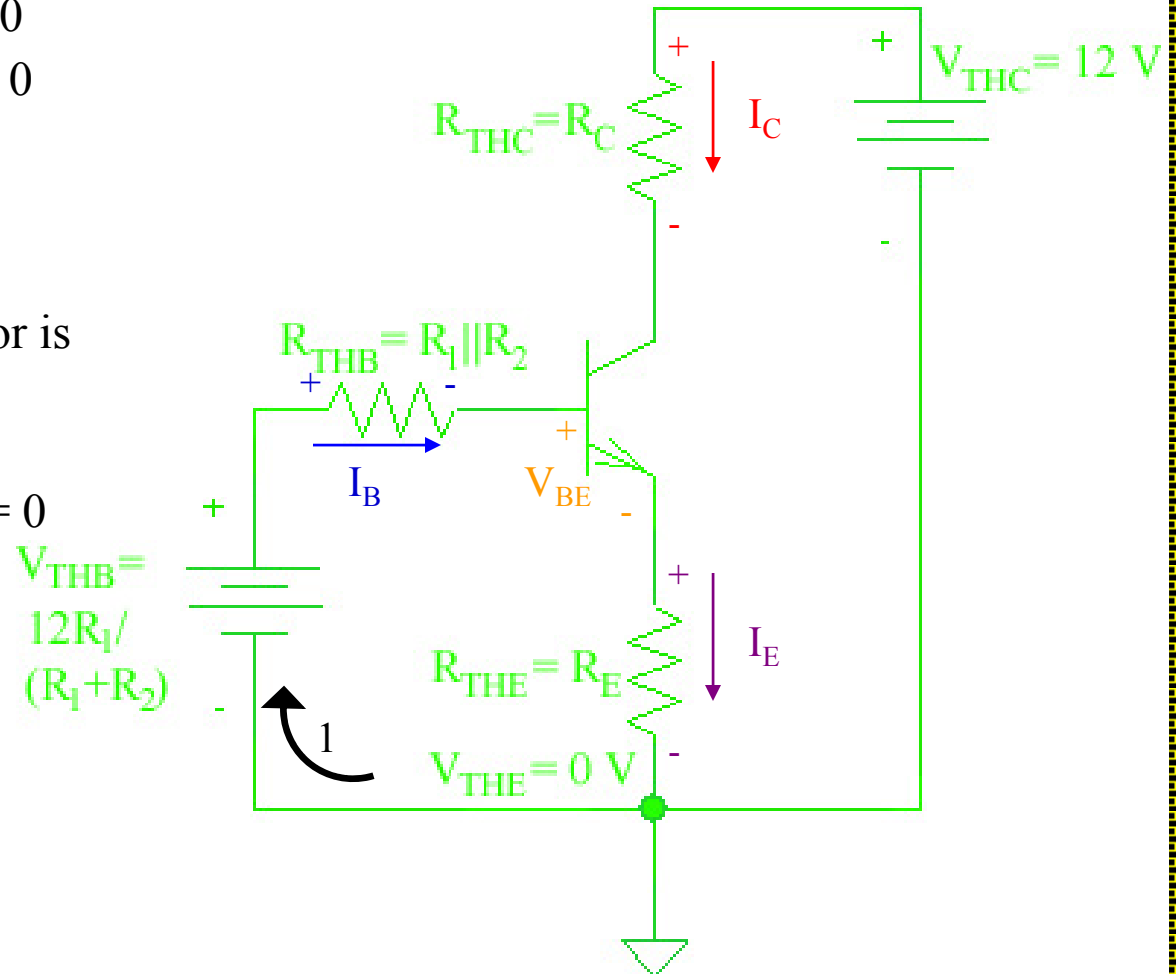

Step 1: Determine DC Operating Point

Check Assumptions: Forward Active?

Important!

$$V_C = 12 - I_C R_C = 12 - (1.66 \text{ mA})(4300) = 4.86 \text{ V}$$

$$V_E = I_E R_E = (1.67 \text{ mA})(1300) = 2.18 \text{ V}$$

$$V_B = V_{THB} - I_B R_{THB} = 3 - (16.6 \mu\text{A})(7500) = 2.88 \text{ V}$$

Check:


For an npn transistor in forward active:

$$V_C > V_B$$

$$4.86 \text{ V} > 2.88 \text{ V}$$

$$V_B - V_E = V_{BE} = 0.7 \text{ V}$$
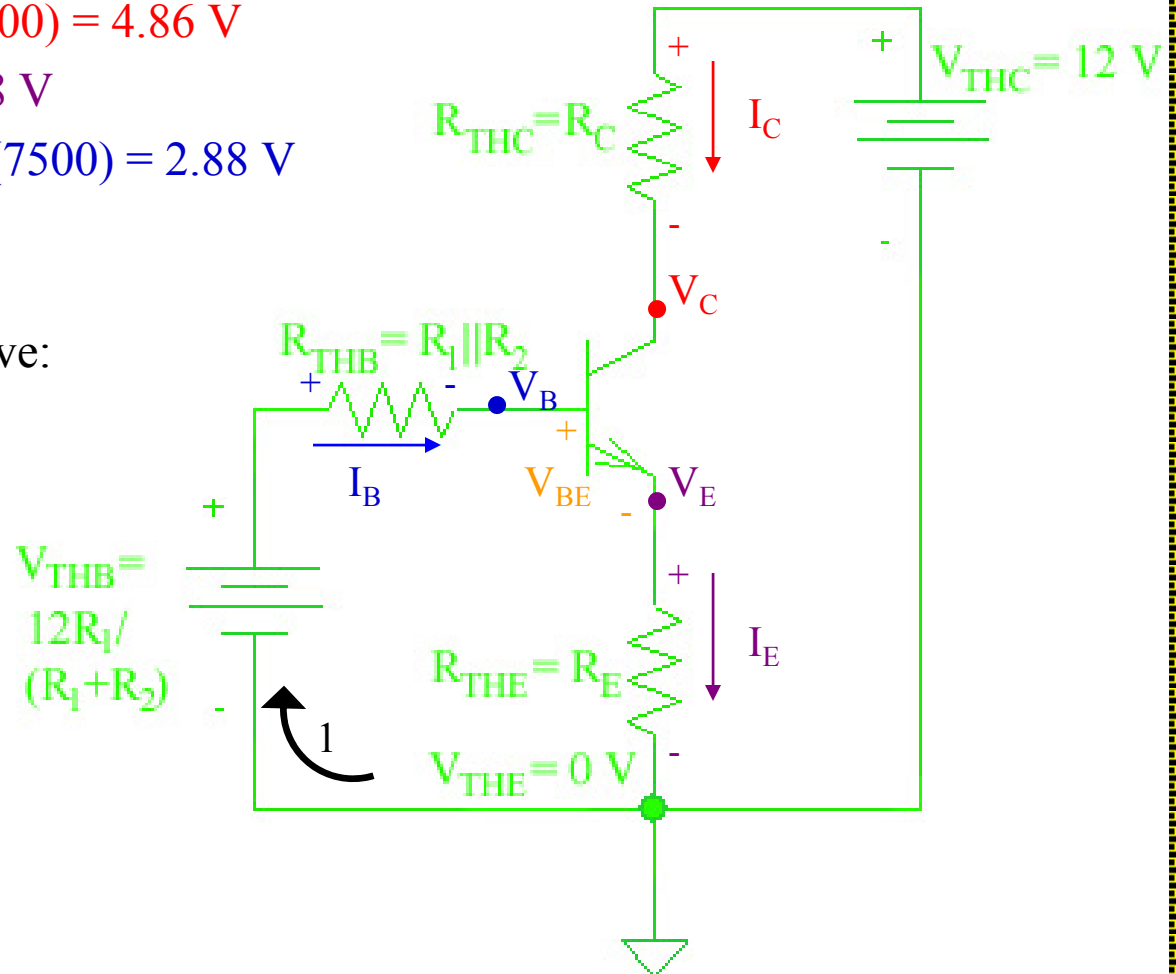
$$2.88 \text{ V} - 2.18 \text{ V} = 0.7 \text{ V}$$




Step 2: Convert to AC-Only Model

Short the Capacitors and DC Current Sources


Important!

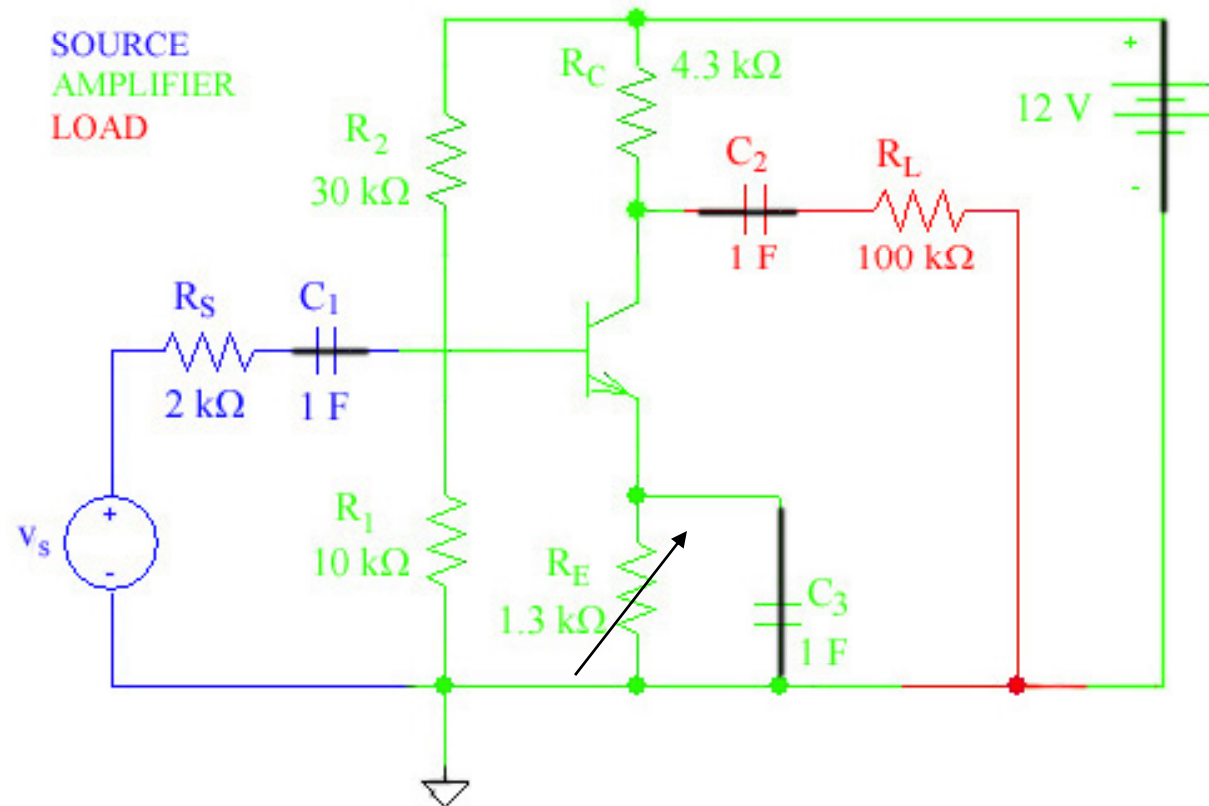- DC voltage sources are shorts (no voltage drop/gain through a short circuit).
- DC current sources are open (no current flow through an open circuit).
- Large capacitors are shorts (if C is large, $1/j\omega C$ is small).
- Large inductors are open (if L is large, $j\omega L$ is large).




Step 2: Convert to AC-Only Model (Optional) Simplify Before Thevenizing

Important!

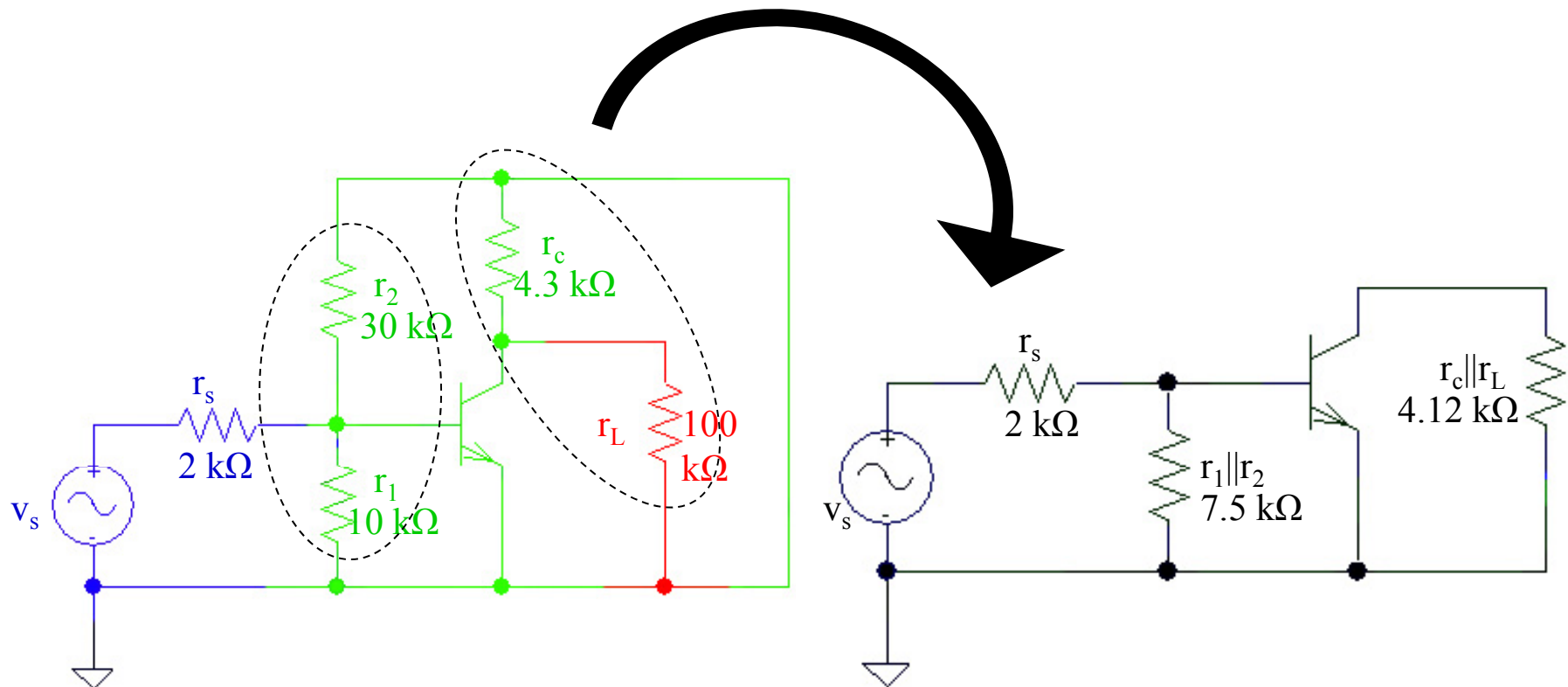


Step 3: Thevenize the AC-Only Model

Important!

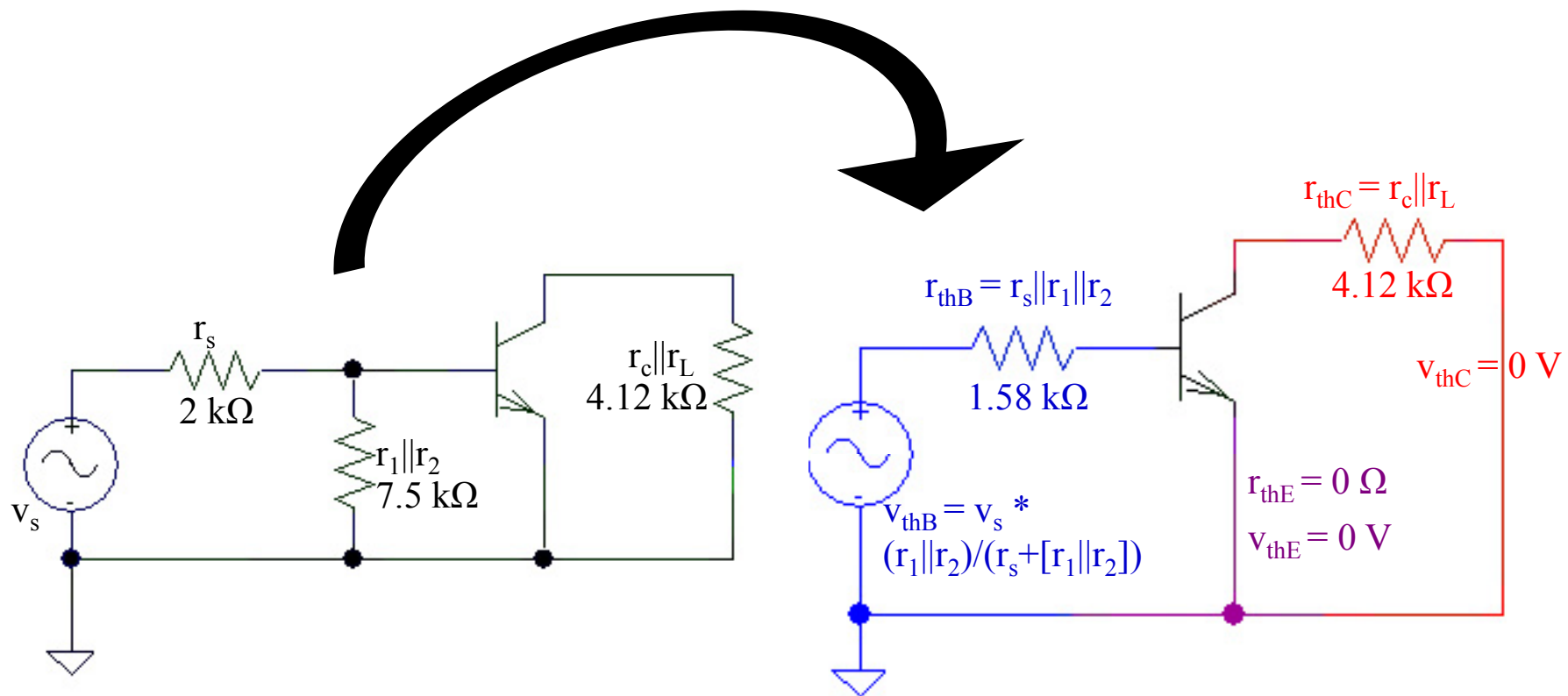

Step 4: Replace Transistor With Small Signal Model


Important!

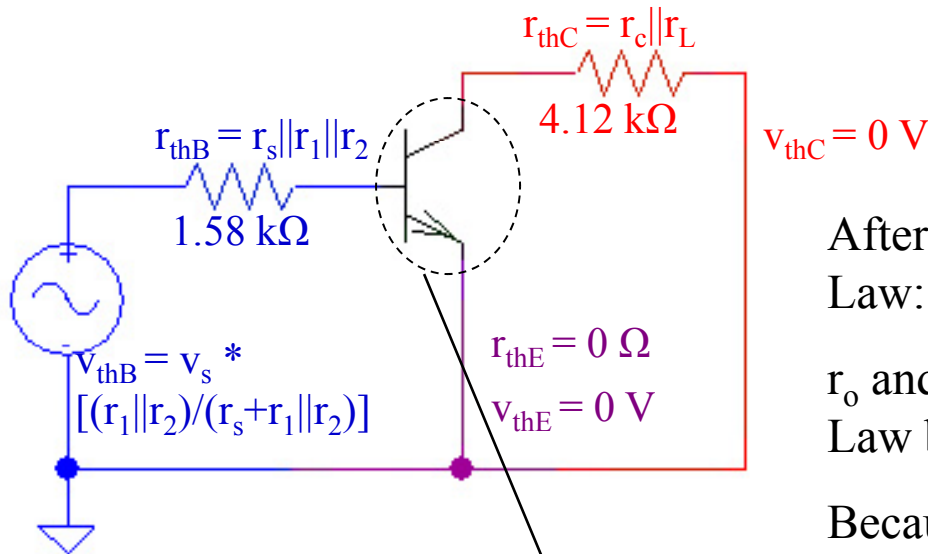

After replacing the transistor, apply Ohm's Law: $V = IR$ to find v_{out} .

r_o and r_{thC} are in parallel, so that Ohm's Law becomes: $v_{out} = -IR = -(g_m v_{BE})(r_o || r_{thC})$

Because $r_{thC} = r_c || r_L$
 $v_{out} = -(g_m v_{BE})(r_o || r_c || r_L)$

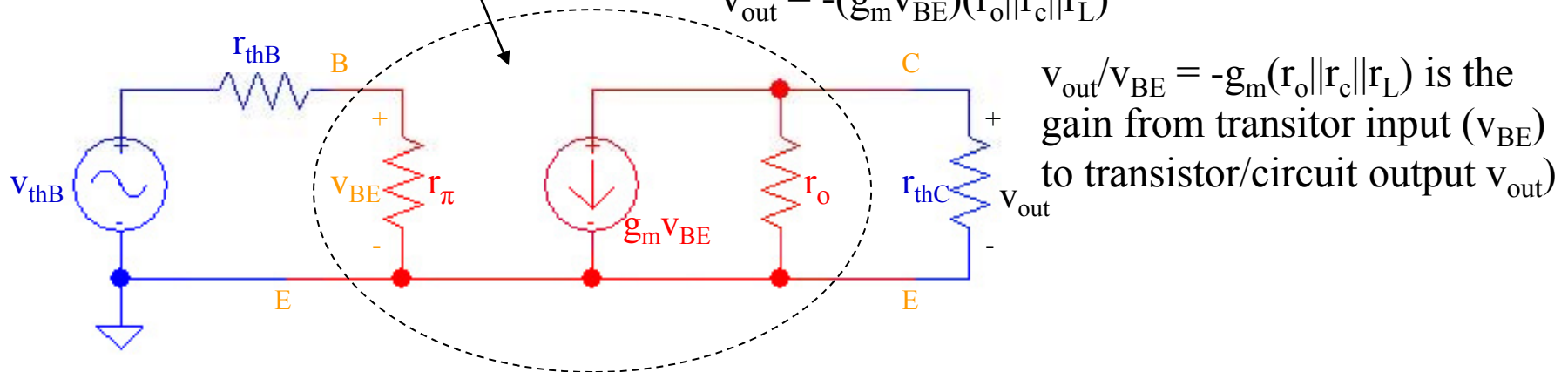


$v_{out}/v_{BE} = -g_m(r_o || r_c || r_L)$ is the gain from transistor input (v_{BE}) to transistor/circuit output v_{out}

TRANSISTOR
EXTERNAL

Step 5: Calculate Gain and Small Signal Parameters

Important!

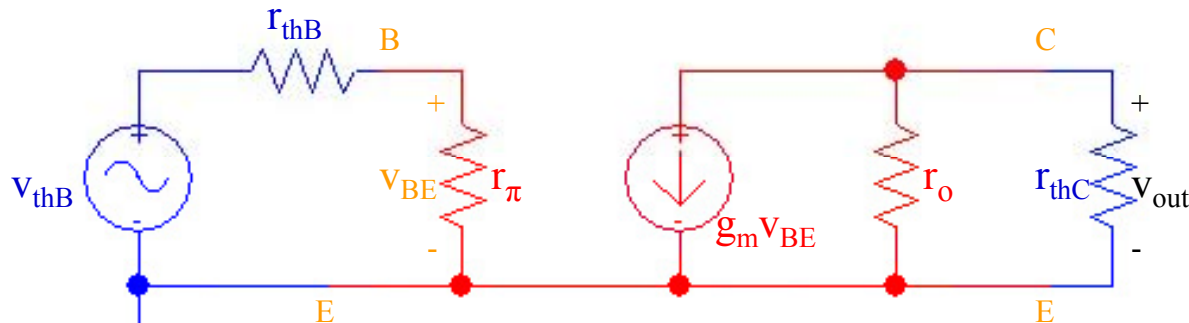

TRANSISTOR
EXTERNAL

$$\text{Gain} = v_{\text{out}}/v_s = (v_{\text{thB}}/v_s)(v_{\text{BE}}/v_{\text{thB}})(v_{\text{out}}/v_{\text{BE}})$$

As previously determined:
 $v_{\text{thB}}/v_s = (r_1 || r_2) / ([r_1 || r_2] + r_s)$

Applying a voltage divider:
 $v_{\text{BE}}/v_{\text{thB}} = r_\pi / (r_\pi + r_{\text{thB}})$

Gain factor:
 $v_{\text{out}}/v_{\text{BE}} = -g_m(r_o || r_c || r_L)$

Because calculating the DC operating point was done *first*, we have equations for g_m , r_π , and r_o in terms of previously calculated DC currents and voltages.

Transconductance $g_m = y_{21} = \frac{I_C}{V_T} \approx 40I_C$

Input Resistance $r_\pi = \frac{1}{y_{11}} = \frac{\beta_o V_T}{I_C} = \frac{\beta_o}{g_m}$

Output Resistance $r_o = \frac{1}{y_{22}} = \frac{V_A + V_{CE}}{I_C}$

Plugging in the numbers:

Gain = $v_{\text{out}}/v_s = -139 \text{ V/V}$

Interpretation/Analysis of Results

Important!

$$\text{Gain} = v_{\text{out}}/v_s = (v_{\text{thB}}/v_s)(v_{\text{BE}}/v_{\text{thB}})(v_{\text{out}}/v_{\text{BE}}) = -139 \text{ V/V}$$

Both terms are *loss factors*, i.e. they can never be greater than 1 in magnitude and thus cause the gain to decrease.

This term is the *gain factor* and is responsible for amplifying the signal.

$$v_{\text{thB}}/v_s = (r_1 || r_2) / ([r_1 || r_2] + r_s)$$

$$v_{\text{BE}}/v_{\text{thB}} = r_\pi / (r_\pi + r_{\text{thB}})$$

$$v_{\text{out}}/v_{\text{BE}} = -g_m(r_o || r_c || r_L)$$

The AC input signal has been amplified 139 times in magnitude. The negative sign indicates there has been a phase shift of 180° .

Completing the Small Signal Model of the BJT

Base Charging Capacitance (Diffusion Capacitance)

In active mode when the emitter-base is forward biased, the capacitance of the emitter-base junction is dominated by the diffusion capacitance (not depletion capacitance).

Recall for a diode we started out by saying:

Sum up all the minority carrier charges on either side of the junction

$$C_{Diffusion} = \frac{dQ_D}{dv_D'} = \frac{dQ_D}{dt} \frac{dt}{dv_D'}$$

Neglect charge injected from the base into the emitter due to p+ emitter in pnp

$$Q_D = qA \int_0^\infty p_{no} \left(e^{v_D'/V_T} - 1 \right) e^{-x/L_p} dx + qA \int_0^\infty n_{po} \left(e^{v_D'/V_T} - 1 \right) e^{-x/L_n} dx$$

Excess charge stored is due almost entirely to the charge injected from the emitter.

Completing the Small Signal Model of the BJT

Base Charging Capacitance (Diffusion Capacitance)

- The BJT acts like a very efficient “siphon”: As majority carriers from the emitter are injected into the base and become “excess minority carriers”, the Collector “siphons them” out of the base.
- We can view the collector current as the amount of excess charge in the base collected by the collector per unit time.
- Thus, we can express the charge due to the excess hole concentration in the base as:

$$Q_B = i_C \tau_F$$

or the excess charge in the base depends on the magnitude of current flowing and the “forward” base transport time, τ_F , the average time the carriers spend in the base.

- It can be shown (see Pierret section 12.2.2) that:

$$\tau_F = \frac{W^2}{2D_B} \quad \text{where,}$$

$W \equiv$ Base Quasi – neutral region width

$D_B \equiv$ Minority carrier diffusion coefficient

Completing the Small Signal Model of the BJT

Base Charging Capacitance (Diffusion Capacitance)

Thus, the diffusion capacitance is,

$$C_B = \left. \frac{\partial Q_B}{\partial v_{BE}} \right|_{Q-\text{point}} = \left(\frac{W^2}{2D_B} \right) \left. \frac{\partial i_C}{\partial v_{BE}} \right|_{Q-\text{point}}$$

$$C_B = \tau_F \frac{I_C}{V_T} = \tau_F g_m$$

The upper operational frequency of the transistor is limited by the forward base transport time: $f \leq \frac{1}{2\pi\tau_F}$

Note the similarity to the Diode Diffusion capacitance we found previously:

$$C_{\text{Diffusion}} = g_d \tau_t \quad \text{where } \tau_t = \frac{[p_{no}L_p + n_{po}L_n]qA}{I_S} \text{ is the transit time}$$

Completing the Small Signal Model of the BJT

Base Charging Capacitance (Total Capacitance)

In active mode for small forward biases the depletion capacitance of the base-emitter junction can contribute to the total capacitance

$$C_{jE} = \frac{C_{jEo}}{\sqrt{1 + \frac{V_{EB}}{V_{bi \text{ for emitter-base}}}}}$$

where,

$C_{jEo} \equiv$ zero bias depletion capacitance

$V_{bi \text{ for emitter-base}} \equiv$ built in voltage for the $E - B$ junction

Thus, the total emitter-base capacitance is:

$$C_{\pi} = C_B + C_{jE}$$

Completing the Small Signal Model of the BJT

Base Charging Capacitance (Depletion Capacitance)

In active mode when the collector-base is reverse biased, the capacitance of the collector-base junction is dominated by the depletion capacitance (not diffusion capacitance).

$$C_{\mu} = \frac{C_{\mu o}}{\sqrt{1 + \frac{V_{CB}}{V_{bi \text{ for collector-base}}}}}$$

where,

$C_{\mu o} \equiv \text{zero bias depletion capacitance}$

$V_{bi \text{ for collector-base}} \equiv \text{built in voltage for the } B - C \text{ junction}$

Completing the Small Signal Model of the BJT

Collector to Substrate Capacitance (Depletion Capacitance)


In some integrated circuit BJTs (lateral BJTs in particular) the device has a capacitance to the substrate wafer it is fabricated in. This results from a “buried” reverse biased junction. Thus, the collector-substrate junction is reverse biased and the capacitance of the collector-substrate junction is dominated by the depletion capacitance (not diffusion capacitance).

$$C_{CS} = \frac{C_{CS}}{\sqrt{1 + \frac{V_{CS}}{V_{bi \text{ for collector-substrate}}}}}$$

where,

$C_{CS} \equiv \text{zero bias depletion capacitance}$

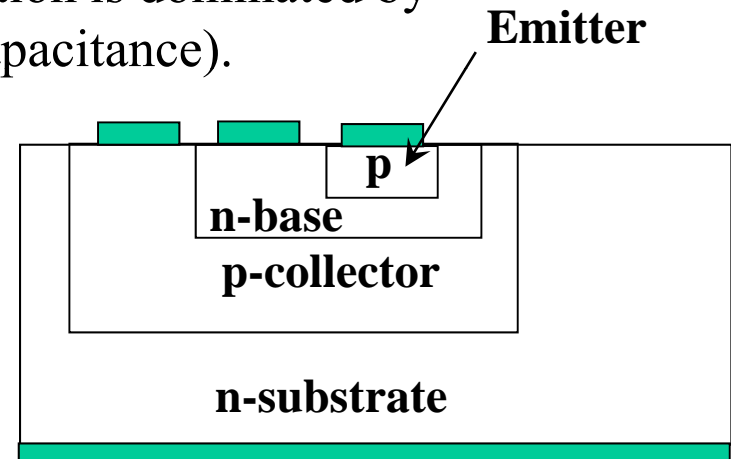$V_{bi \text{ for collector-substrate}} \equiv \text{built in voltage for the C - substrate junction}$



Completing the Small Signal Model of the BJT

Parasitic Resistances

- r_b = base resistance between metal interconnect and B- E junction
- r_c = parasitic collector resistance
- r_{ex} = emitter resistance due to polysilicon contact
- These resistance's can be included in SPICE simulations, but are usually ignored in hand calculations.

Completing the Small Signal Model of the BJT

Complete Small Signal Model

