
 
 
 


# Dynamic Combinational Circuits

- Dynamic circuits
  - Charge sharing, charge redistribution
- Domino logic
- np-CMOS (zipper CMOS)



 
# Dynamic Logic

- *Dynamic* gates use a clocked pMOS pullup
- Two modes: *precharge* and *evaluate*



   
# The Foot


- What if pulldown network is ON during precharge?
- Use series evaluation transistor to prevent fight.



# Dynamic Logic

 

 
- 2 phase operation:
- Precharge
  - Evaluation




# Logical Effort

unfooted


Inverter

 




NAND2

 

NOR2

 


footed

   

# Dynamic Logic

- $N+2$  transistors for  $N$ -input function
  - Better than  $2N$  transistors for complementary static CMOS
  - Comparable to  $N+1$  for ratio-ed logic
- No static power dissipation
  - Better than ratio-ed logic
- Careful design, clock signal  $\Phi$  needed

# Dynamic Logic: Principles

 

- **Precharge**

$\Phi = 0$ , *Out* is precharged to  $V_{DD}$  by  $M_p$ .  
 $M_e$  is turned off, no dc current flows  
(regardless of input values)


- **Evaluation**

$\Phi = 1$ ,  $M_e$  is turned on,  $M_p$  is turned off.  
Output is pulled down to zero depending  
on the values on the inputs. If not,  
precharged value remains on  $C_L$ .

**Important:** Once *Out* is discharged, it cannot be charged again!  
Gate input can make only one transition during evaluation

- Minimum clock frequency must be maintained
- Can  $M_e$  be eliminated?


# Example

 



- **Ratioless**
- **No Static Power Consumption**
- **Noise Margins small ( $NM_L$ )**
- **Requires Clock**



# Dynamic 4 Input NAND Gate

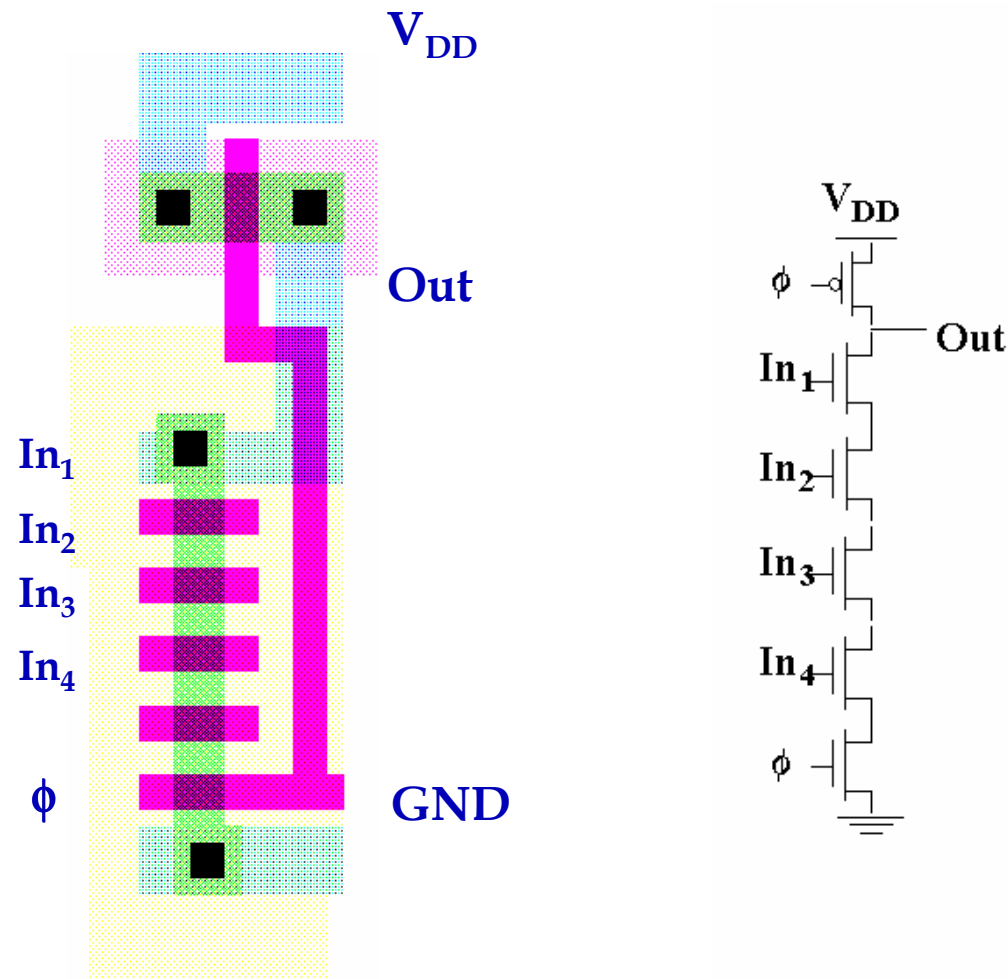

# Cascading Dynamic Gates

  


Internal nodes can only make 0-1 transitions during evaluation period
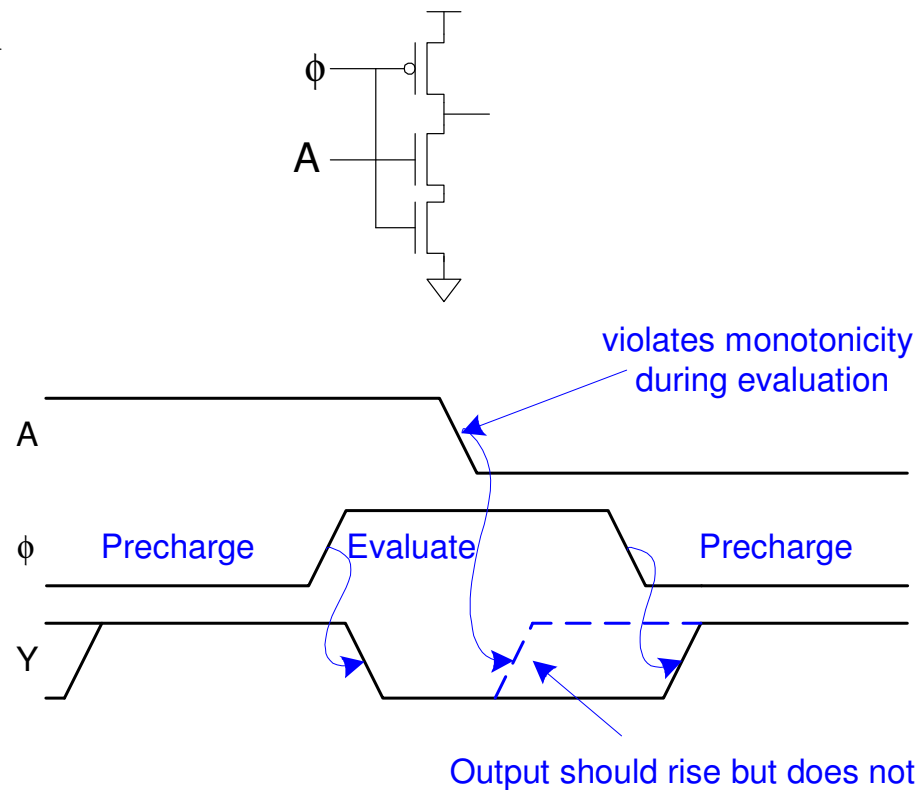
# Monotonicity


- Dynamic gates require *monotonically rising* inputs during evaluation

- 0  $\rightarrow$  0
- 0  $\rightarrow$  1
- 1  $\rightarrow$  1
- But not 1  $\rightarrow$  0



 
# Monotonicity Woes


- But dynamic gates produce monotonically falling outputs during evaluation
- Illegal for one dynamic gate to drive another!




A = 1

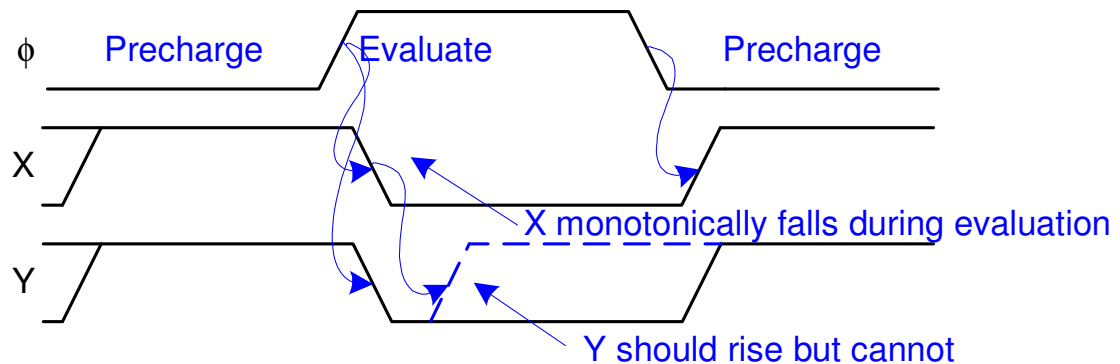

# Reliability Problems — Charge Leakage

 

(a) Leakage sources

 

(b) Effect on waveforms


(1) Leakage through reverse-biased diode of the diffusion area

(2) Subthreshold current from drain to source

**Minimum Clock Frequency: > 1 MHz**

 
# Leakage

- Dynamic node floats high during evaluation
  - Transistors are leaky ( $I_{\text{OFF}} \neq 0$ )
  - Dynamic value will leak away over time
  - Formerly milliseconds, now nanoseconds!
- Use keeper to hold dynamic node
  - Must be weak enough not to fight evaluation


 
# Charge Sharing (redistribution)

- Assume: during precharge, A and B are 0,  $C_a$  is discharged
- During evaluation, B remains 0 and A rises to 1
- Charge stored on  $C_L$  is now redistributed over  $C_L$  and  $C_a$



$$C_L V_{DD} = C_L V_{out}(t) + C_a V_X$$



$$V_X = V_{DD} - V_t, \text{ therefore}$$

$$\delta V_{out}(t) = V_{out}(t) - V_{DD} = -\frac{C_a}{C_L} (V_{DD} - V_t)$$

Desirable to keep the voltage drop below threshold of pMOS transistor (why?)  $\Rightarrow C_a/C_L < 0.2$
 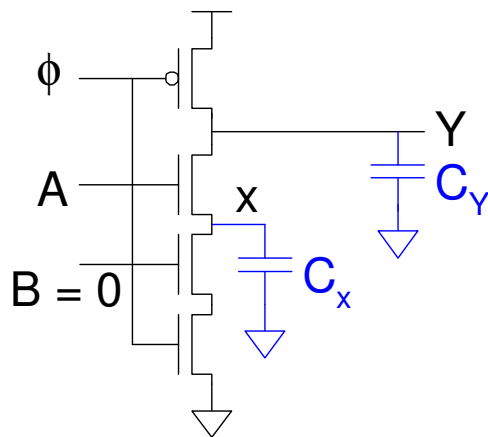
# Charge Sharing


- Dynamic gates suffer from charge sharing




$$V_x = V_Y = \frac{C_Y}{C_x + C_Y} V_{DD}$$



# Charge Redistribution - Solutions

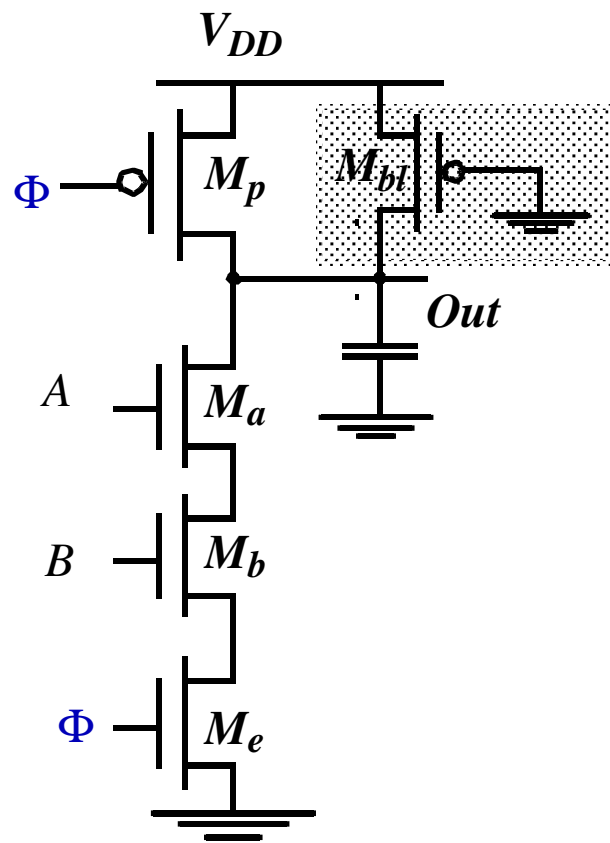


(a) Static bleeder

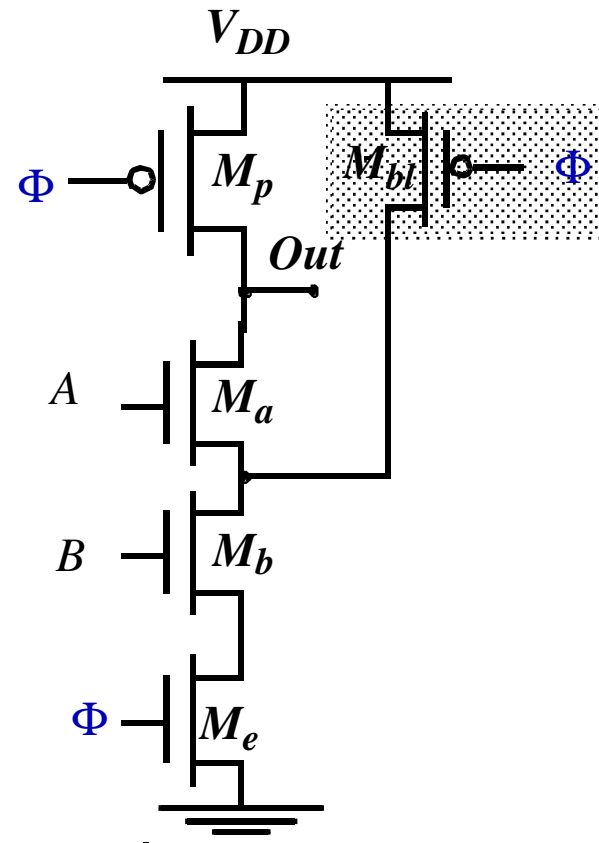


(b) Precharge of internal nodes
 
# Secondary Precharge

- Solution: add secondary precharge transistors
  - Typically need to precharge every other node
- Big load capacitance  $C_Y$  helps as well






# Domino Logic

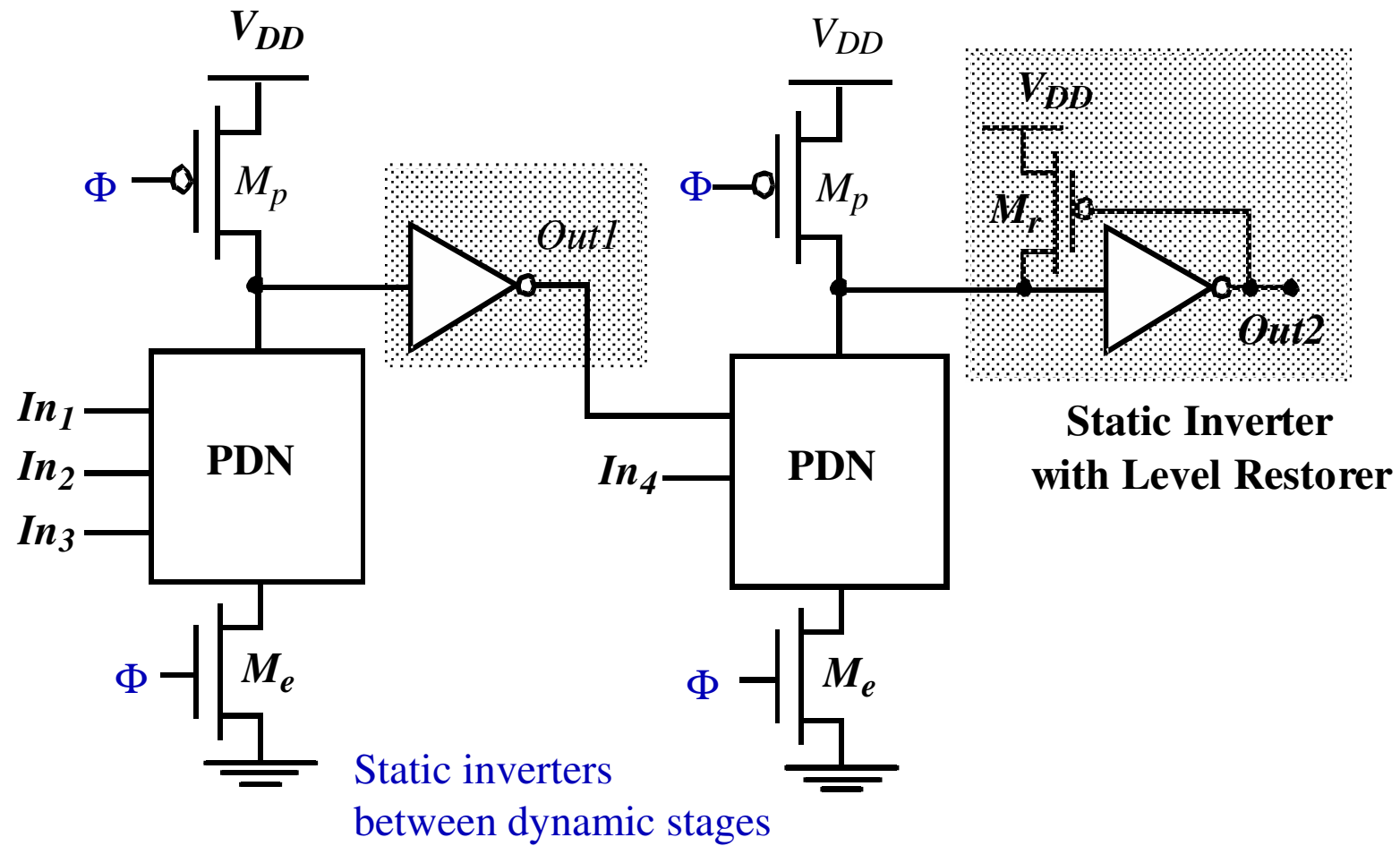
 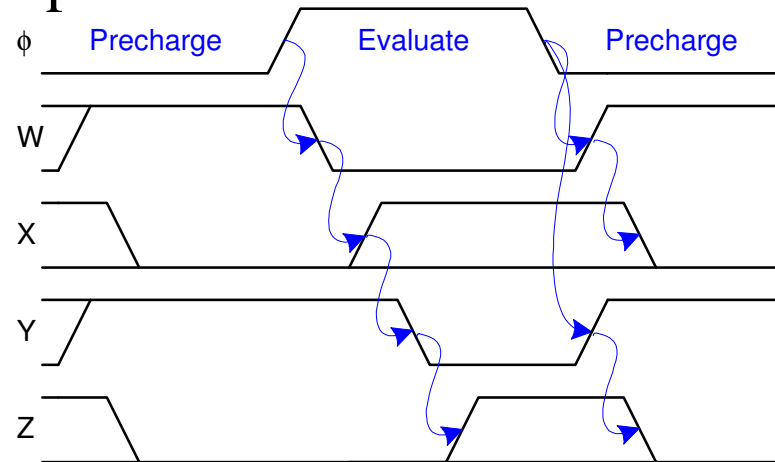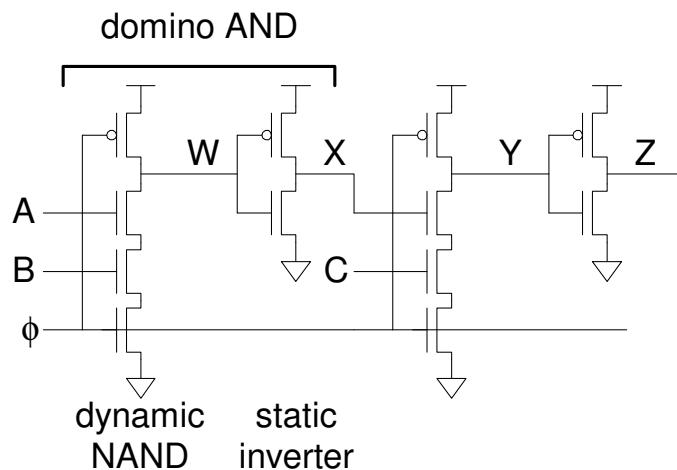
# Domino Gates

- Follow dynamic stage with inverting static gate
  - Dynamic / static pair is called domino gate
  - Produces monotonic outputs




# Domino Logic - Characteristics

- Only non-inverting logic
- Very fast - Only 1->0 transitions at input of inverter
- Precharging makes pull-up very fast
- Adding level restorer reduces leakage and charge redistribution problems
- Optimize inverter for fan-out
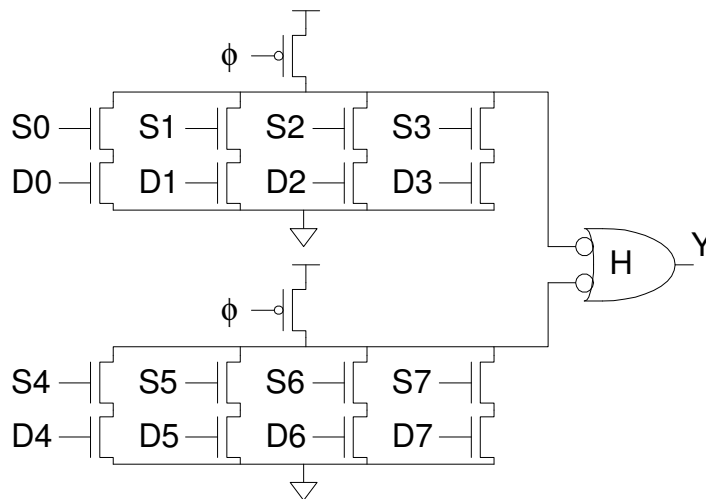
# Domino Optimizations


- Each domino gate triggers next one, like a string of dominos toppling over
- Gates evaluate sequentially but precharge in parallel
- Thus evaluation is more critical than precharge
- HI-skewed static stages can perform logic



# Dual-Rail Domino


- Domino only performs noninverting functions:
  - AND, OR but not NAND, NOR, or XOR
- Dual-rail domino solves this problem
  - Takes true and complementary inputs
  - Produces true and complementary outputs

sig_h	sig_l	Meaning
0	0	Precharged
0	1	'0'
1	0	'1'
1	1	invalid

 
 
# Example: AND/NAND


- Given  $A_h$ ,  $A_l$ ,  $B_h$ ,  $B_l$
- Compute  $Y_h = A * B$ ,  $Y_l = \sim(A * B)$
- Pulldown networks are conduction complements




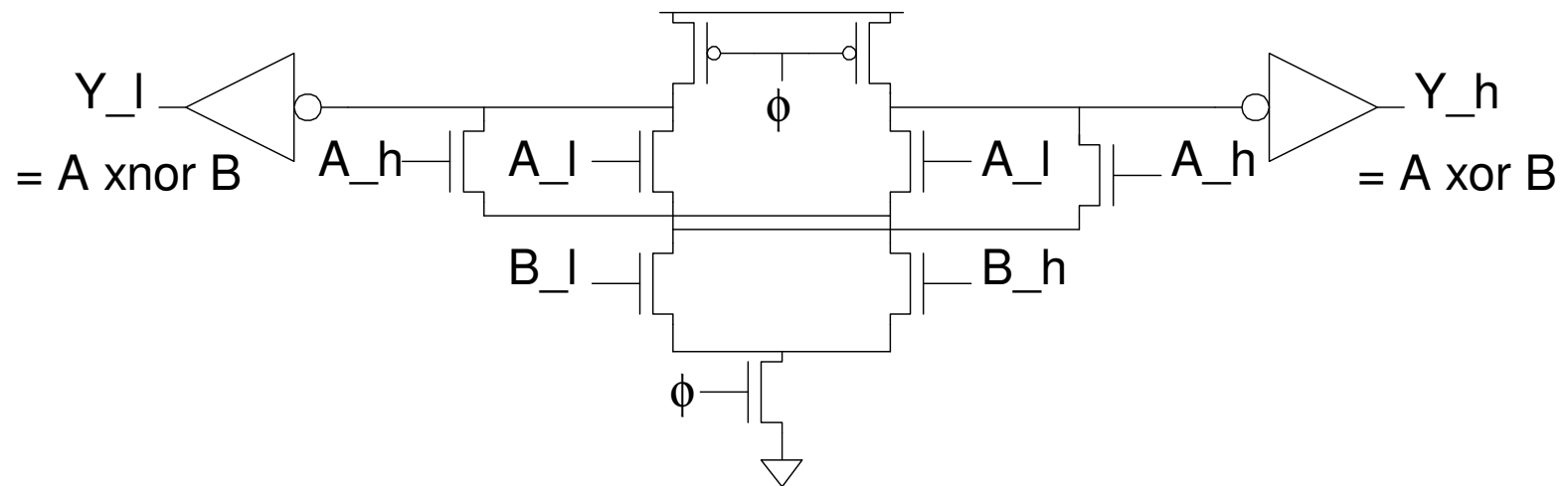
# Example: XOR/XNOR


- Sometimes possible to share transistors



# Domino Summary


- Domino logic is attractive for high-speed circuits
  - 1.5 – 2x faster than static CMOS
  - But many challenges:
    - Monotonicity
    - Leakage
    - Charge sharing
    - Noise
- Widely used in high-performance microprocessors

# np-CMOS (Zipper CMOS)

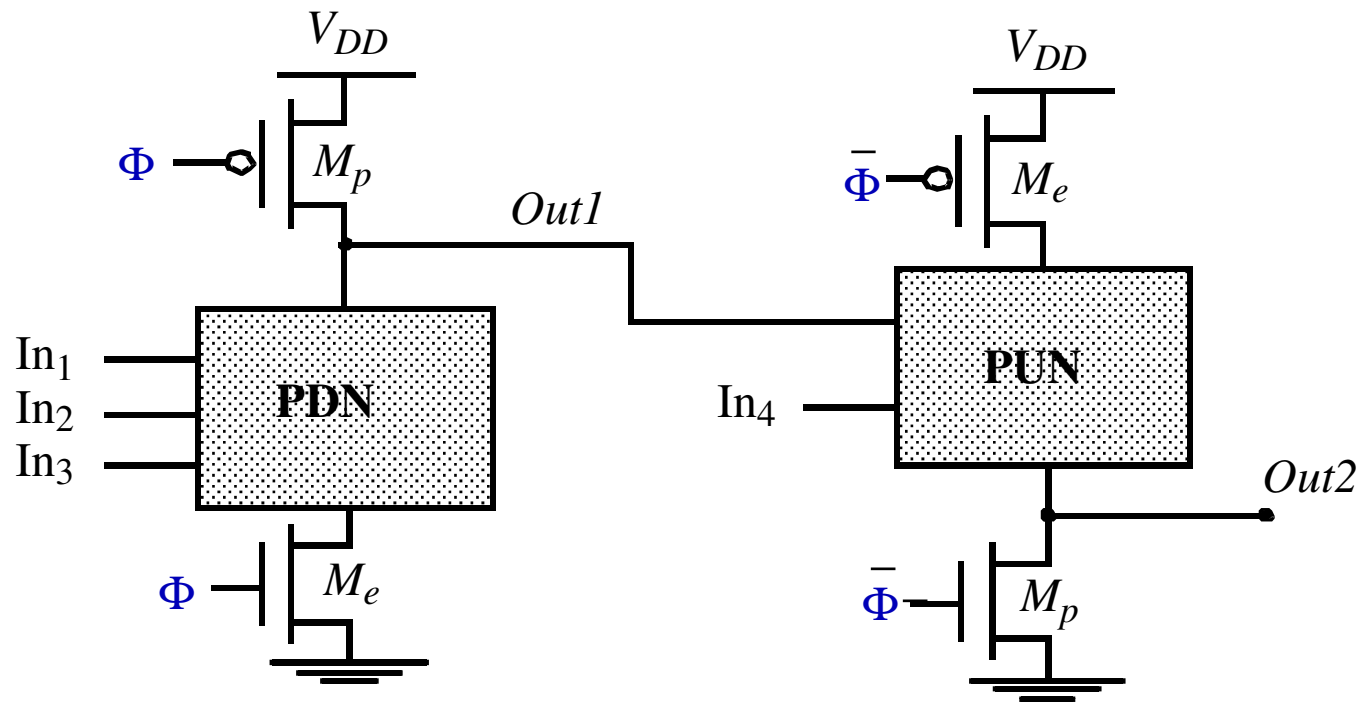

- Only 1-0 transitions allowed at inputs of PUN
- Used a lot in the Alpha design

# np CMOS Adder

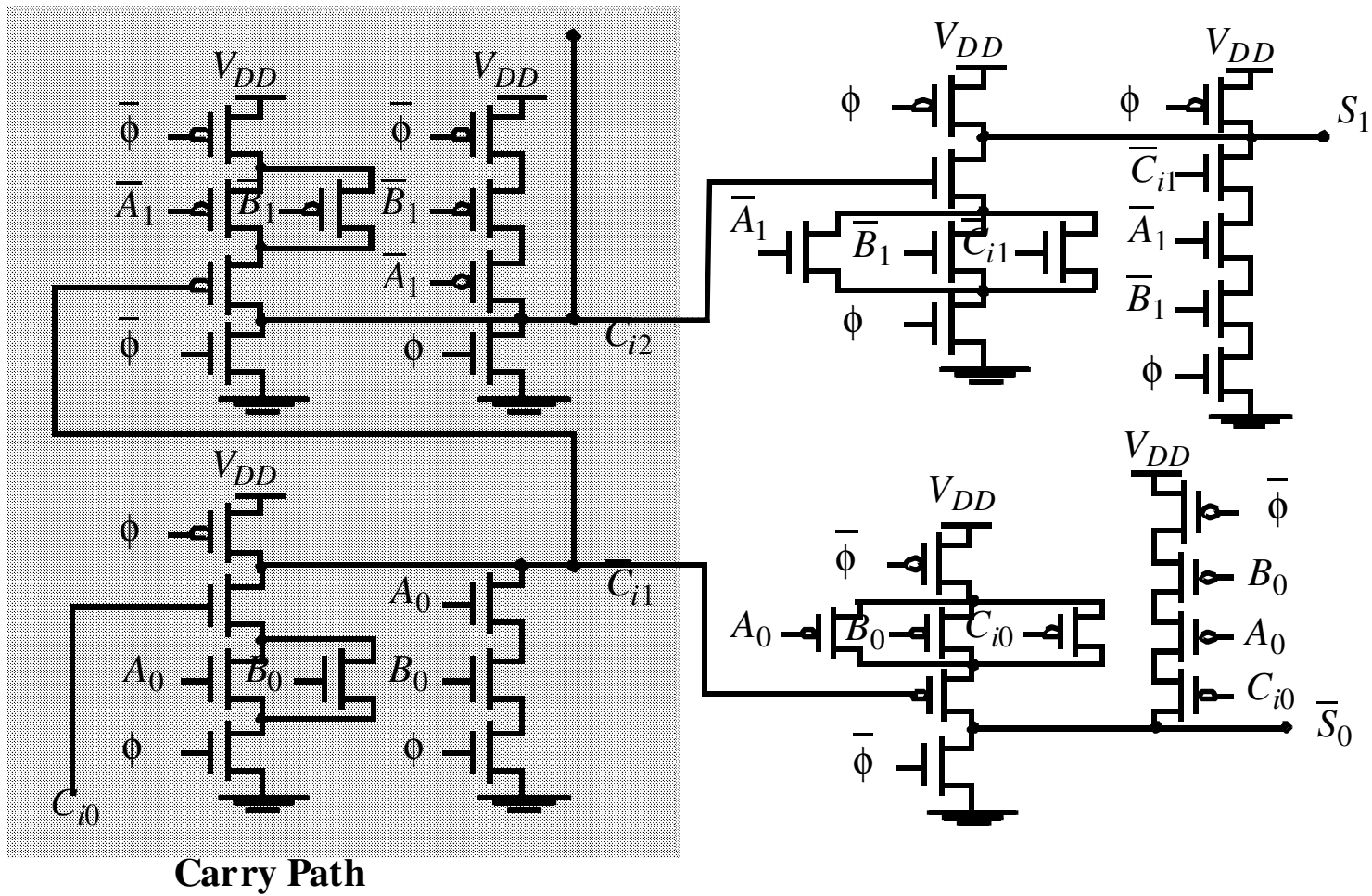

# CMOS Circuit Styles - Summary

Style	Ratioed	Static Power	# transistors	Area ( $\mu\text{m}^2$ )	Propagation Delay (nsec)
Complementary	No	No	8	533	0.61
Pseudo-NMOS	Yes	Yes	5	288	1.49
CPL	No	No	14	800	0.75
Dynamic (NP)	No	No	6	212	0.37

**4-input NAND Gate**