

Lecture 9 -- Dynamic Logic


Outline

- Not going to talk about logical effort today -- realized that the planned schedule wouldn't cover the stuff you need for MP2 in time
- Instead, talk about dynamic logic
 - Concepts
 - Basic Implementations
 - Staging dynamic gates
 - Larger-scale systems

Dynamic Vs. Static Logic


- Static Logic always has a path from power or ground to the output
 - Stable over long periods
 - Simple clocking schemes
- Dynamic Logic relies on capacitance of gates or other structures to hold state
 - Can be faster than static logic
 - Has minimum operating frequency
 - More restrictions about how/when inputs can change
 - Consequence of how we implement dynamic logic

Dynamic Latch

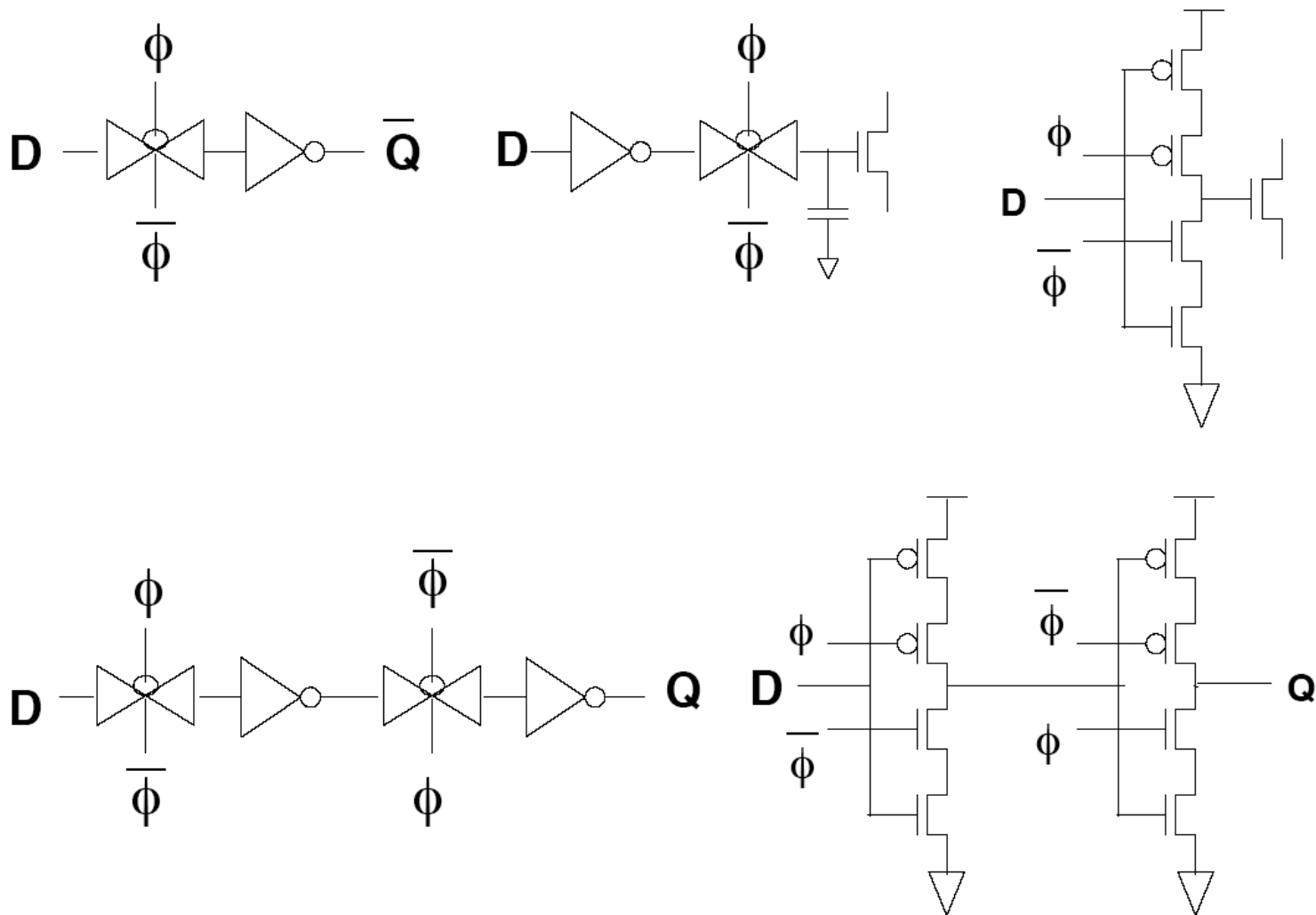

Bad Points of Static CMOS

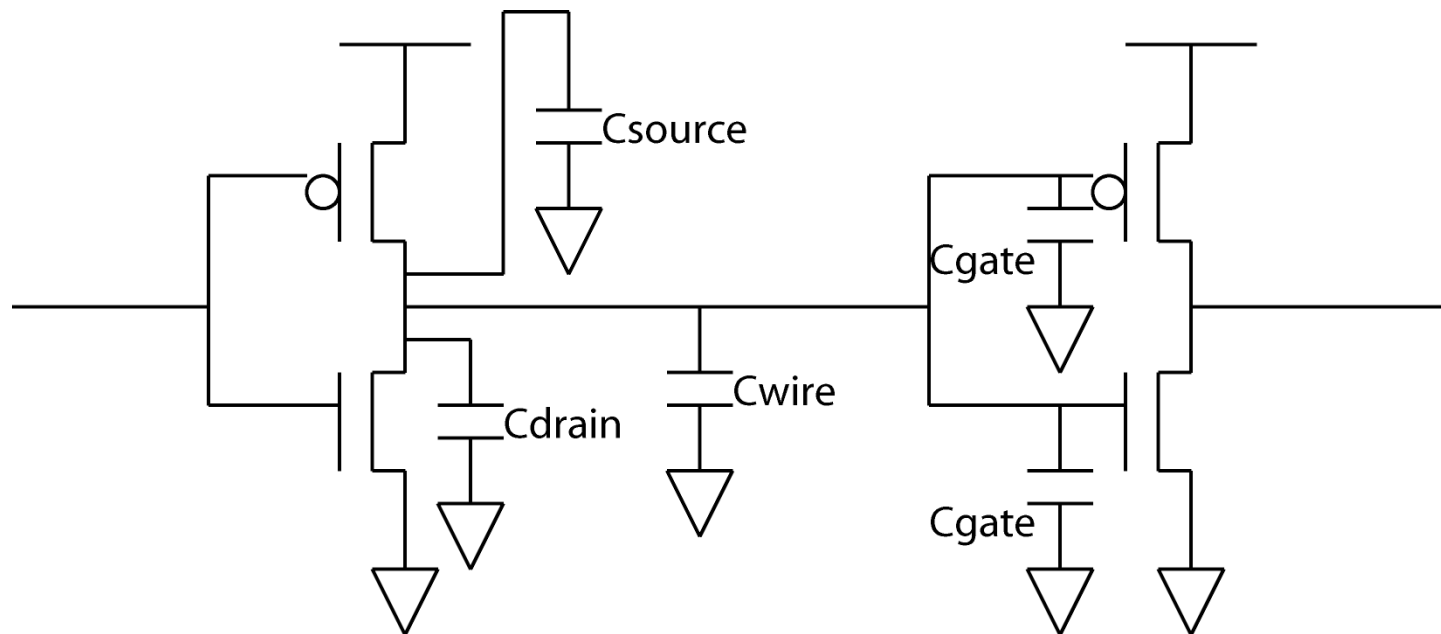- Capacitance on input
 - Two transistors, and P-FET generally 2x N-FET width
- Conflicting drive while input switching
 - During input swing, will have paths from both power and ground to output, increasing delay





Dynamic Logic Concepts

- All dynamic logic we'll look at is clocked
- In one phase of the clock, we'll *precharge* the gate to either 0 or 1.
- In another phase, we'll *evaluate* whether the gate's output should stay at the precharged value or change.
- Doing this will allow us to eliminate either the p- or n-network from each gate
 - Reduces load capacitance
 - Timing of precharge/evaluate phases eliminates delay due to connecting output to both power and ground during input swing time

  Example Dynamic Logic Gates

- These are what your book calls *footed* logic gates
- Some designs don't include the clocked N-FET
 - Reduces load on clock signal
 - Potential for static power dissipation when clock low




$$Z = \overline{A.(B+C) + (D.E)}$$

$$Z = \text{HIGH}$$

$$\text{clk} = 1$$

$$\text{clk} = 0$$


 


$$\text{evaluate}$$

$$\text{precharge}$$


Using Dynamic Logic

  - Inputs may change freely during precharge phase
- Input transitions during evaluate phase may cause problems



Cascading Dynamic Gates

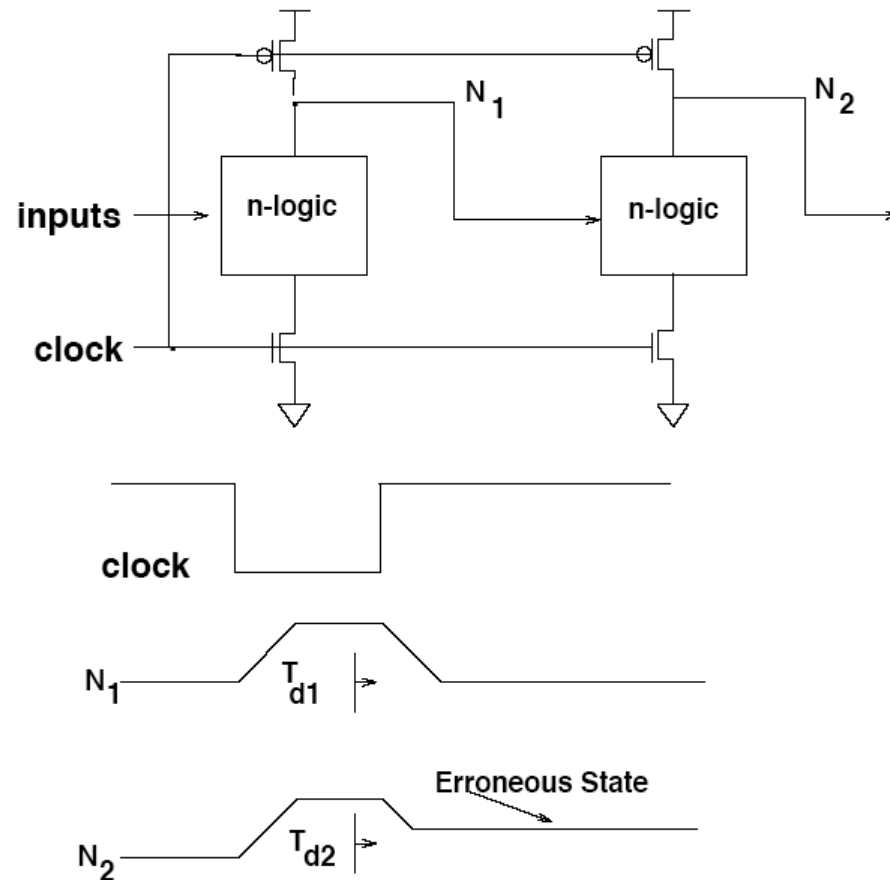
- Just plain doesn't work with the designs we've shown



Domino CMOS

- Add inverter to output of each gate
 - Can now connect gates in sequence
 - As one gate evaluates, it triggers the gates it drives, similar to a set of falling dominoes
- Domino gates can make a single 0-->1 output transition during the evaluate phase
 - No glitches on output
- Still have potential charge-sharing problems
- Can only make non-inverting structures
 - Means that there are logic functions we can't implement with this form of Domino CMOS

Example Domino Gate


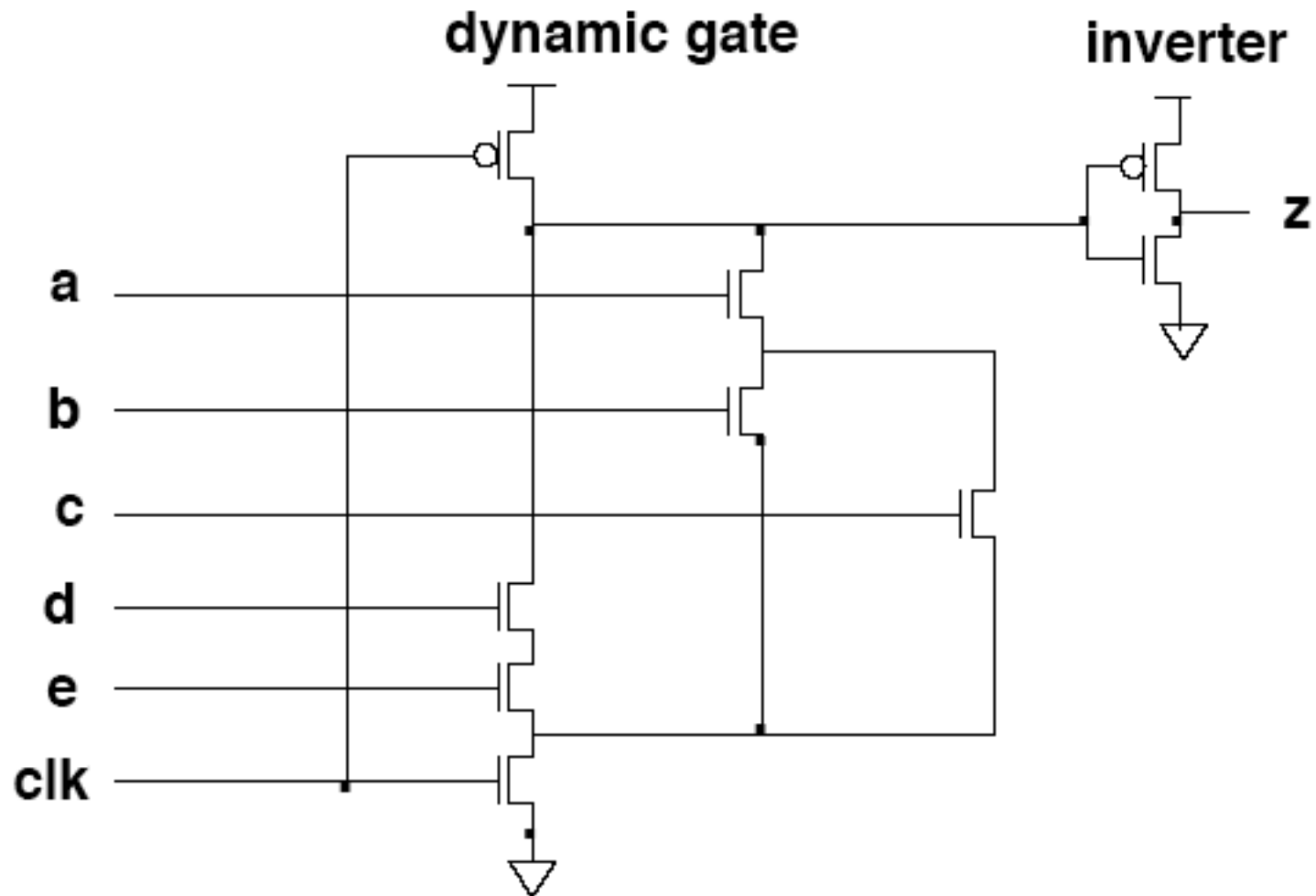


Staticizing Gates

- Often, it's hard to guarantee that a circuit will be clocked fast enough to avoid charge leakage problems on dynamic logic
 - Example: may want to support low-speed testing
- Domino gates are static when outputting a “1”, but rely on charge storage to maintain outputs of “0”
- Can add staticizing logic to domino gate to allow it to drive “0” outputs for long periods of time
 - Some cost in performance, but still faster than static CMOS

Staticized Gates

  
- Make pull-up devices very weak to minimize performance impact
 - Just need to flow enough current to counter leakage



N-P Domino Logic


- Need inverters at output of domino gates because output transition of n-network has the wrong polarity for n-network inputs
 - Decreases performance somewhat
 - Can't build inverting structures
- Alternative: Alternate dynamic gates with n- and p-networks
 - Provides inversion
 - P-networks can take n-network output directly
 - P-FETs are slower than N-FETs for same size
 - Widening P-FETs adds load capacitance

N-P Domino Logic

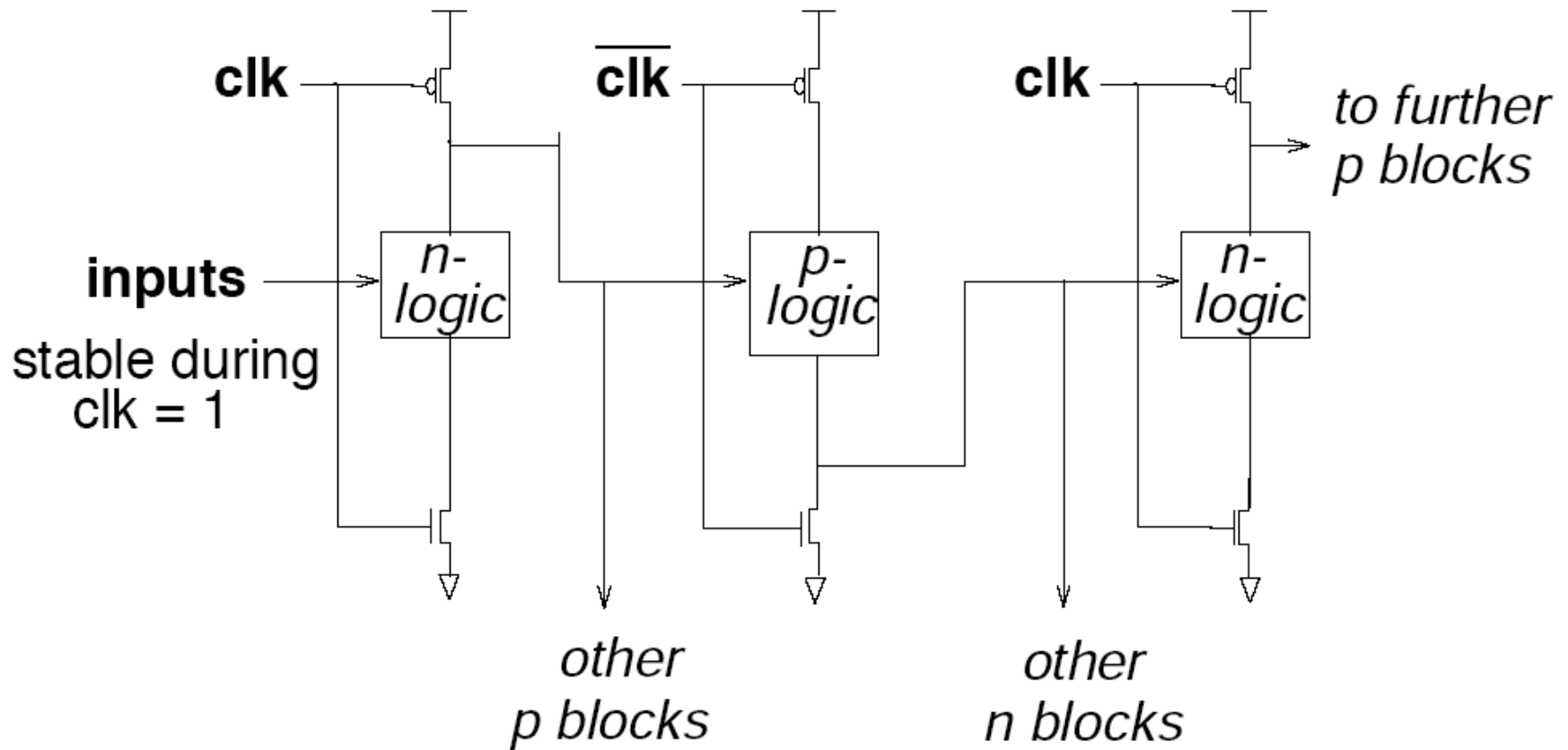


N-P Domino Logic

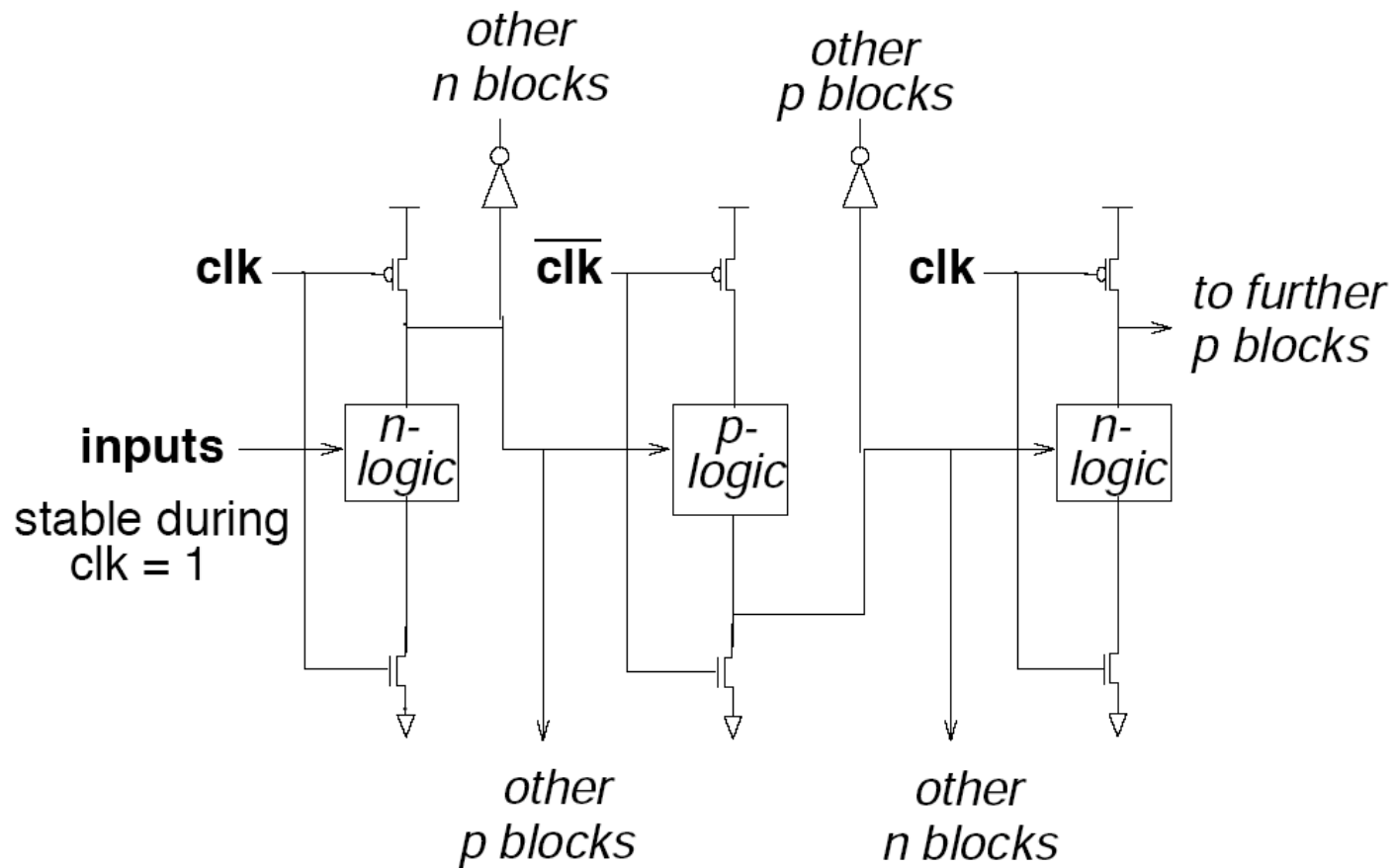- Can add inverters to allow gates to drive both n- and p-gates



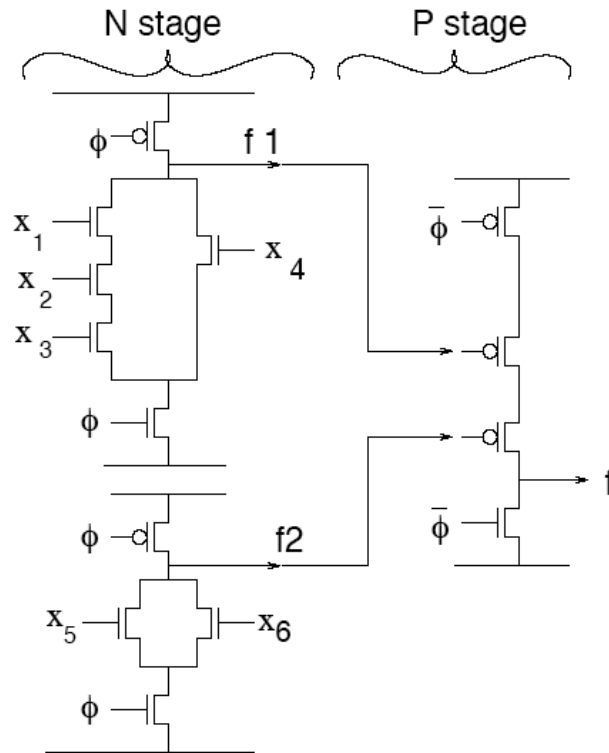Example

- Implement $f = (x_1x_2x_3 + x_4)(x_5 + x_6)$ in N-P CMOS
- Define subfunctions $f_1 = \overline{x_1x_2x_3 + x_4}$, $f_2 = \overline{x_5 + x_6}$
- Then $f = \bar{f}_1\bar{f}_2$ can be implemented as follows:




Clocking Dynamic Logic

- Dynamic logic needs to be clocked to generate precharge, evaluate phases
 - Length of precharge period determined by precharge time of single gate
 - Length of evaluate period determined by sum of gate evaluate times
- Generally don't implement entire chips in dynamic logic
 - Greatly increased design time/gate
 - Most gates not performance-critical
- Typically want latches at dynamic/static boundaries
 - Pipelining
 - Control glitches


Single-Phase Clocking

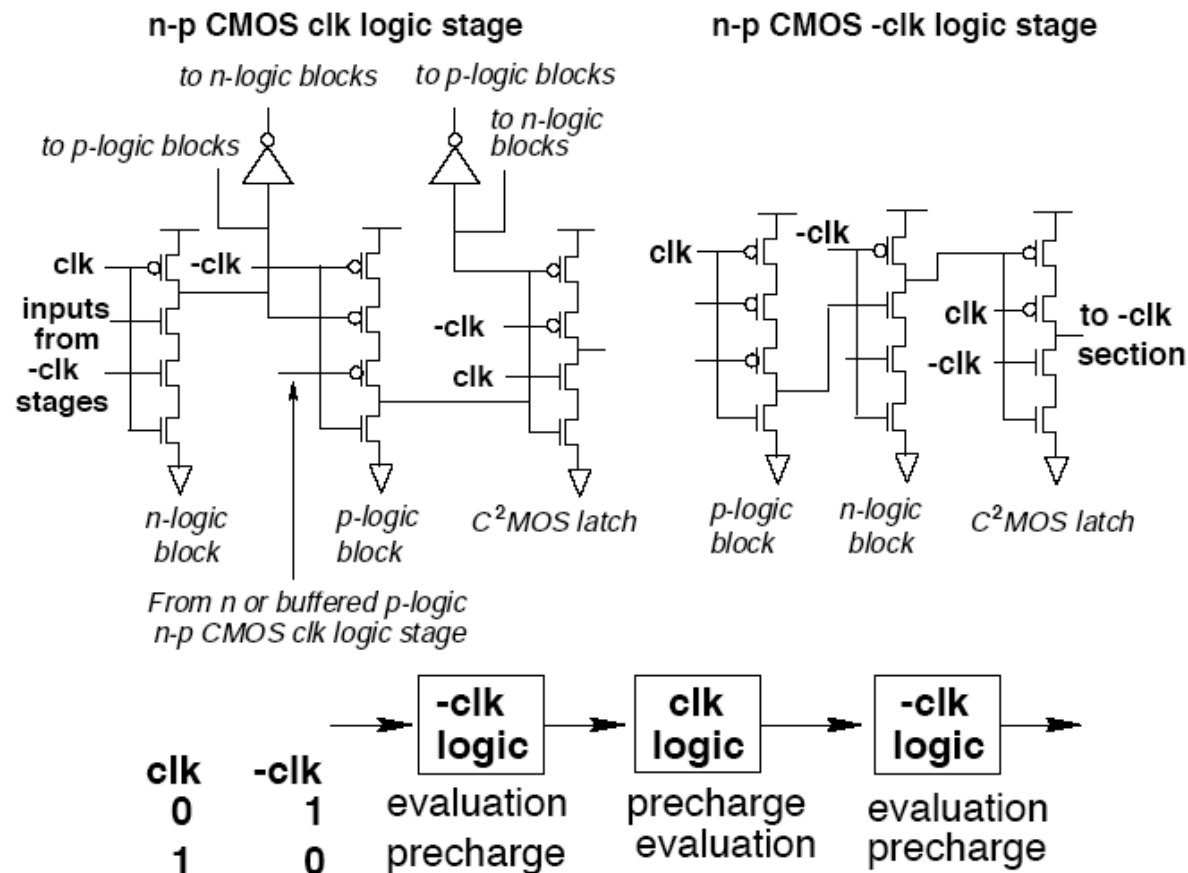- Add clocked latch at the output of each set of dynamic gates




Two-Phase Clocking

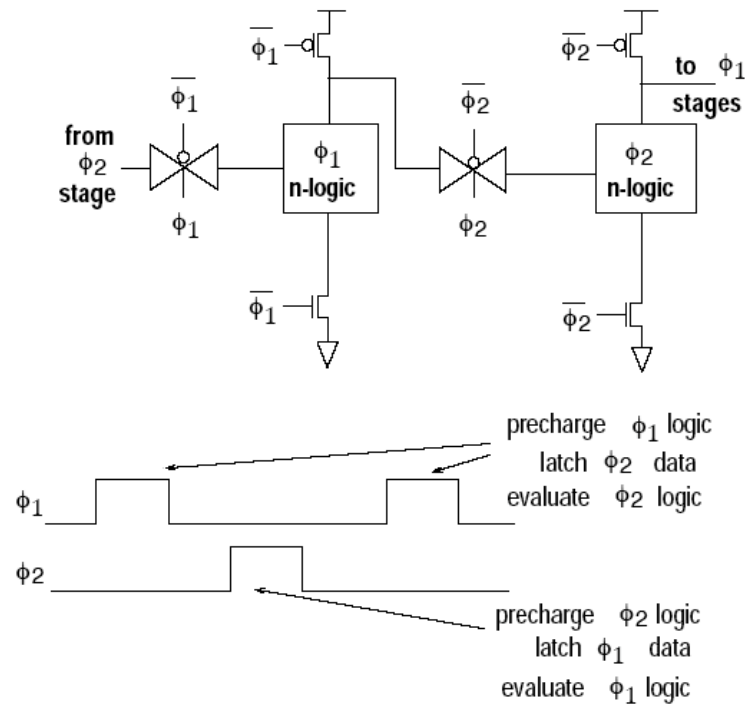- First stage is precharged during ϕ_1 and evaluated during ϕ_2
- While first is evaluated, second is precharged, and first stage outputs stored on second-stage inputs.



Two-Phase Domino Logic

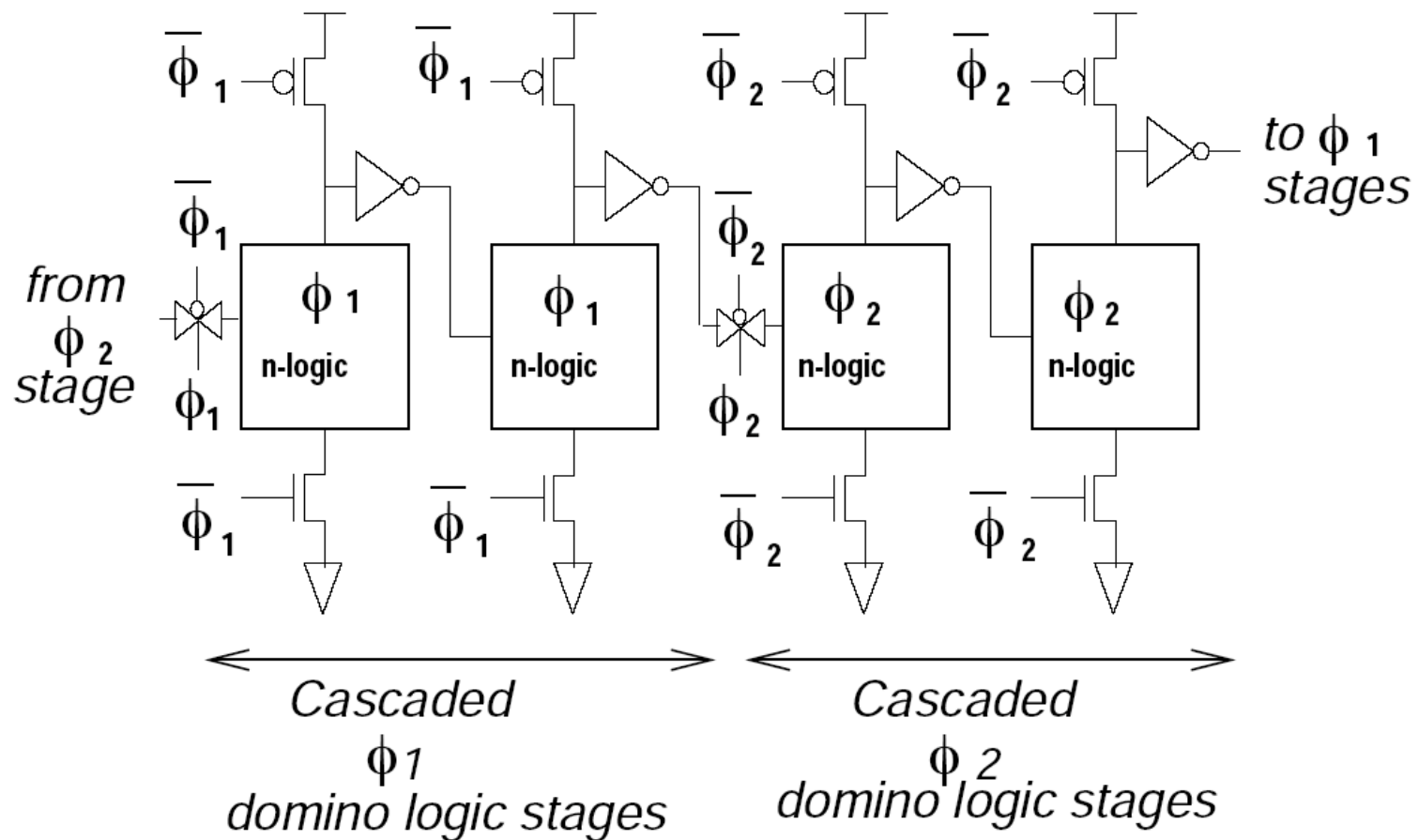- Cascade number of domino logic stages before latching the result



Reading

- Sections 6.2.4 and 6.3 in your book
 - 6.3 in particular covers things that can go wrong with your circuits