



Istanbul Technical University  
Department of Computer Engineering

04.10.2013

## BLG 231E - Digital Circuits Assignment 2

**Due Date:** 10.10.2013, Thursday, 17.00.

- Please **write neatly**.
- If you are not preparing your homework in a computer, please show complement of a symbol by putting a **dash** over the symbol (e.g. do not use  $x'$  use  $\bar{x}$ ).
- Plagiarized assignments will be given a negative mark.
- **No late submissions** will be accepted.

**Submissions:** Please submit your solutions to the Digital Circuits Course Assignment Box at the department secretary's office.

1. The truth table of expression  $f$  is given as follows.

$a$	$b$	$c$	$d$	$f$
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

- Write the first and second canonical form of  $f$ .
- Minimize the second canonical form of the expression by using the axioms and theorems of the Boolean algebra.
- Draw the minimized expression in b by only using 2-input NOR.

## Answers:

a. The first canonical form of the expression

$$\begin{aligned} f(a, b, c, d) &= \sum m(1, 4, 5, 6, 7, 9, 12, 13, 14, 15) \\ &= \bar{a}\bar{b}\bar{c}d + \bar{a}b\bar{c}\bar{d} + \bar{a}b\bar{c}d + \bar{a}bcd + \bar{a}bcd + a\bar{b}\bar{c}d + ab\bar{c}\bar{d} + ab\bar{c}d \\ &\quad + abc\bar{d} + abcd \end{aligned}$$

The second canonical form of the expression

$$\begin{aligned} f(a, b, c, d) &= \prod M(0, 2, 3, 8, 10, 11) \\ &= (a + b + c + d)(a + b + \bar{c} + d)(a + b + \bar{c} + \bar{d})(\bar{a} + b + c + d)(\bar{a} + b \\ &\quad + \bar{c} + d)(\bar{a} + b + \bar{c} + \bar{d}) \end{aligned}$$

b. Minimization of the second canonical form

$$\begin{aligned} f &= (a + b + c + d)(a + b + \bar{c} + d)(a + b + \bar{c} + \bar{d})(\bar{a} + b + c + d)(\bar{a} + b + \bar{c} + d)(\bar{a} + b + \bar{c} + \bar{d}) \\ &= [(a + b + \bar{c})(d + \bar{d})][(a + \bar{a})(b + c + d)][(a + \bar{a})(b + \bar{c} + d)][(\bar{a} + b + \bar{c})(d + \bar{d})] \\ &= (a + b + \bar{c})(b + c + d)(b + \bar{c} + d)(\bar{a} + b + \bar{c}) \\ &= [(a + b + \bar{c})(\bar{a} + b + \bar{c})][(b + c + d)(b + \bar{c} + d)] \\ &= [(a + \bar{a})(b + \bar{c})][(b + d)(\bar{c} + c)] \\ &= (b + \bar{c})(b + d) \end{aligned}$$

c. The given expression has operations with only two parameters. Thus, in PoS form, it can be easily implemented with 2-input NOR gates by just replacing the AND, OR, NOT gates with NOR gates.

