

Bipolar Junction Transistor (BJT)

Lecture notes: Sec. 3

Sedra & Smith (6th Ed): Sec. 6.1-6.4*


Sedra & Smith (5th Ed): Sec. 5.1-5.4*

* Includes details of BJT device operation which is not covered in this course



A BJT consists of three regions

NPN transistor

Simplified physical structure

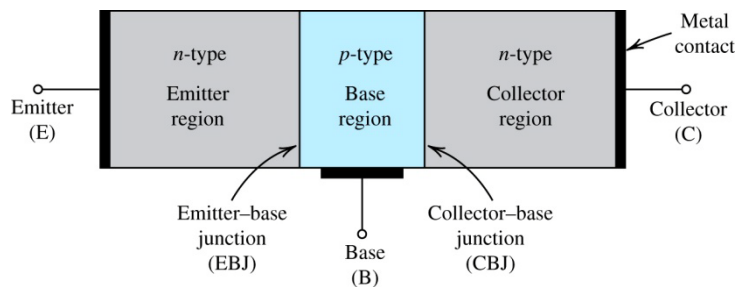

An implementation on an IC

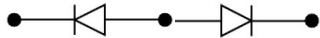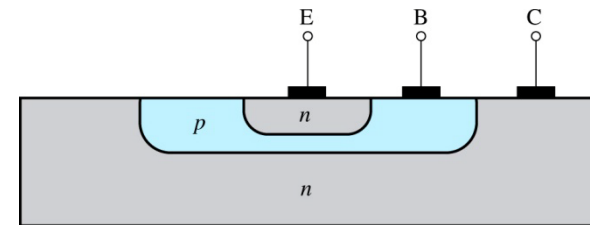


- Device is constructed such that BJT does NOT act as two diodes back to back (when voltages are applied to all three terminals).

- Device construction is NOT symmetric
 - “Thin” base region (between E & C)
 - Heavily doped emitter
 - Large area collector

BJT i v characteristics includes four parameters

NPN transistor

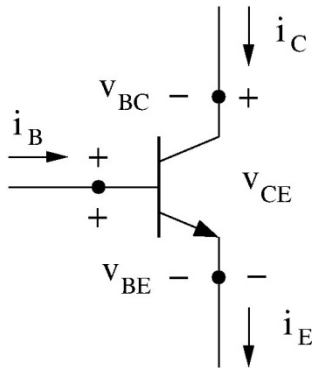

Circuit symbol and
Convention for current directions
(Note: $v_{CE} = v_C - v_E$)

- Six circuit variables: (3 i and 3 v)
- Two can be written in terms of the other four:

$$\text{KCL: } i_E = i_C + i_B$$

$$\text{KVL: } v_{BC} = v_{BE} - v_{CE}$$

- BJT i v characteristics is the relationship among (i_B , i_C , v_{BE} , and v_{CE})
- It is typically derived as

$$i_B = f(v_{BE})$$

$$i_C = g(i_B, v_{CE})$$


BJT operation in the “active” mode

BE junction is forward biased

$$(v_{BE} = V_{D0})$$

As Emitter is heavily doped, a large number of electrons diffuse into the base (only a small fraction combine with holes)

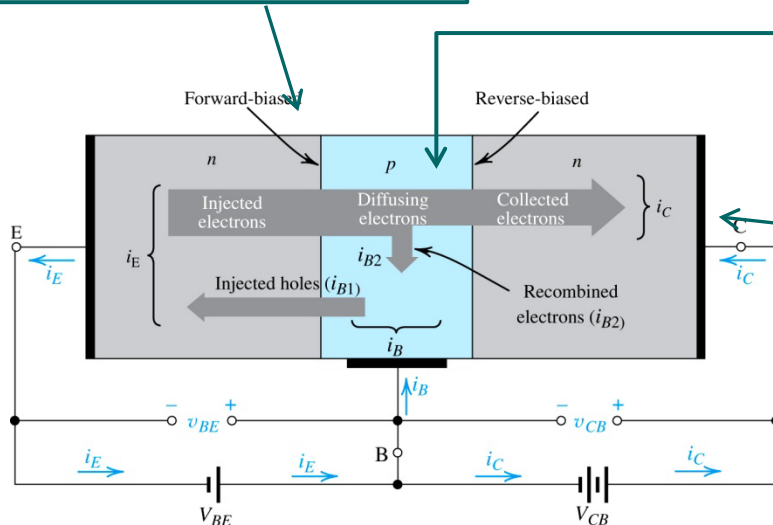The number of these electrons scales as e^{v_{BE}/V_T}



- If the base is “thin” these electrons get near the depletion region of BC junction and are swept into the collector if $v_{CB} \geq 0$ ($v_{BC} \leq 0$: **BC junction is reverse biased!**)

$$i_C = I_S e^{v_{BE}/V_T}$$

- In this picture, i_C is independent of v_{BC} (and v_{CE}) as long as

$$v_{BC} = v_{BE} - v_{CE} = V_{D0} - v_{CE} \leq 0$$

$$v_{CE} \geq V_{D0}$$

Active mode:

$$i_B = \frac{i_C}{\beta} = \frac{I_S}{\beta} e^{v_{BE}/V_T}$$

$$i_C = I_S e^{v_{BE}/V_T}$$

$$v_{CE} \geq V_{D0}$$

- Base current is also proportional to


$$e^{v_{BE}/V_T} \text{ and therefore, } i_C : i_B = i_C / \beta$$

BJT operation in saturation mode

BE junction is forward biased

$$(v_{BE} = V_{D0})$$

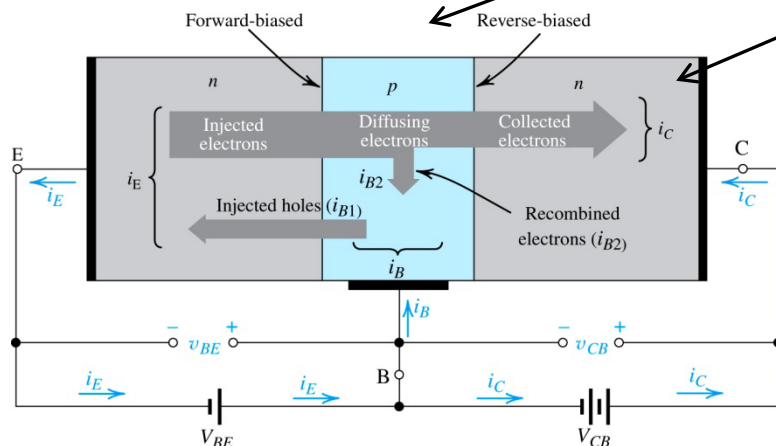Similar to the active mode, a large number of electrons diffuse into the base.



“Deep” Saturation mode:

$$i_B = \frac{I_S}{\beta} e^{v_{BE}/V_T}$$

$$i_C < \beta i_B$$

$$v_{CE} \approx V_{sat}$$


➤ For $v_{BC} \geq 0$ **BC junction is forward biased** and a diffusion current will set up, reducing i_C .

1. Soft saturation: $v_{CE} \geq 0.3 \text{ V (Si)}^*$
 $v_{BC} \leq 0.4 \text{ V (Si)}$, diffusion current is small and i_C is very close to its active-mode level.
2. Deep saturation region: $0.1 < v_{CE} < 0.3 \text{ V (Si)}$
or $v_{CE} \approx 0.2 \text{ V} = V_{sat} \text{ (Si)}$, i_C is smaller than its active-mode level ($i_C < \beta i_B$).
○ Called saturation as i_C is set by outside circuit & does not respond to changes in i_B .
3. Near cut-off: $v_{CE} \leq 0.1 \text{ V (Si)}$
Both i_C & i_B are close to zero.

* Sedra & Smith includes this in the active region, i.e., BJT is in active mode as long as $v_{CE} \geq 0.3 \text{ V}$.


BJT i v characteristics includes four parameters

NPN transistor

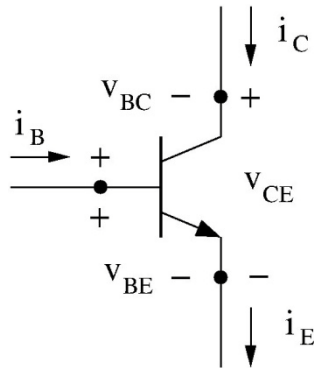

Circuit symbol and
Convention for current directions
(Note: $v_{CE} = v_C - v_E$)

Simplified physical structure

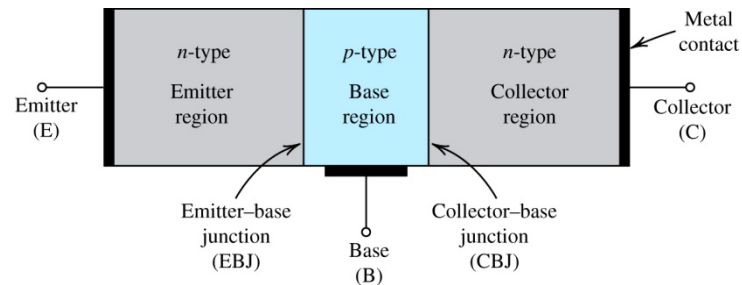

- BJT i v characteristics is the relationship among (i_B , i_C , v_{BE} , and v_{CE})
- It is typically derived as

$$i_B = f(v_{BE})$$

$$i_C = g(i_B, v_{CE})$$

BJT i_v characteristics:

$$i_B = f(v_{BE}) \text{ \& } i_C = g(i_B, v_{CE})$$

Saturation:



BE is forward biased, BC is forward biased

1. Soft saturation: $0.3 \leq v_{CE} \leq 0.7 \text{ V}$, $i_C \approx \beta i_B$
2. Deep saturation: $0.1 \leq v_{CE} \leq 0.3 \text{ V}$, $i_C < \beta i_B$
3. Near cut-off: $v_{CE} \leq 0.1 \text{ V}$, $i_C \approx 0$

Active:

BE is forward biased
BC is reverse biased

$$i_C = \beta i_B$$

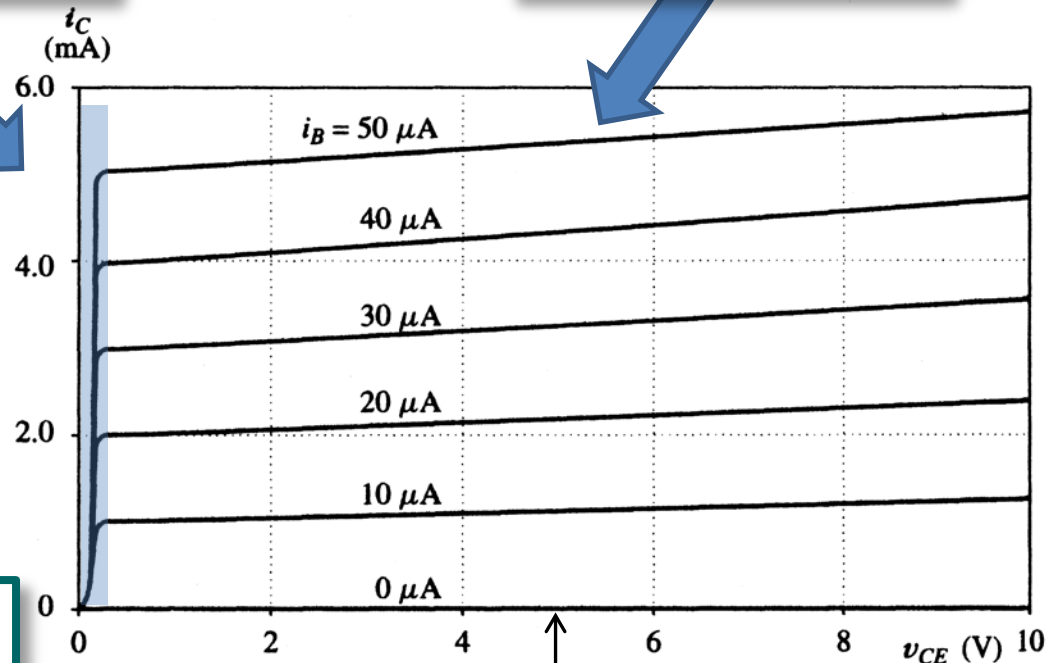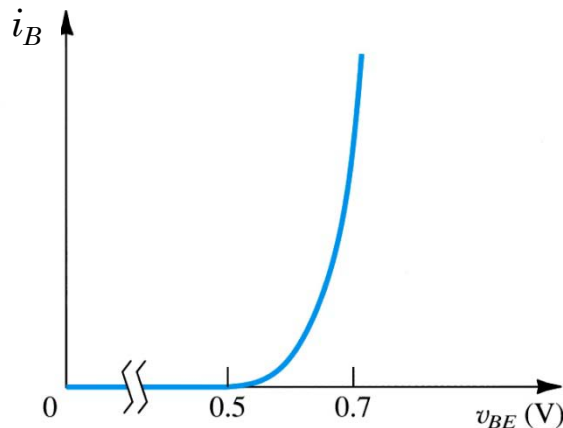

Cut-off :

BE is reverse biased


$$i_B = 0, \quad i_C = 0$$

Early Effect modifies i_C characteristics in the active mode

➤ i_C is NOT constant in the active region.

➤ **Early Effect:** Lines of i_C vs v_{CE} for different i_B (or v_{BE}) coincide at $v_{CE} = -V_A$
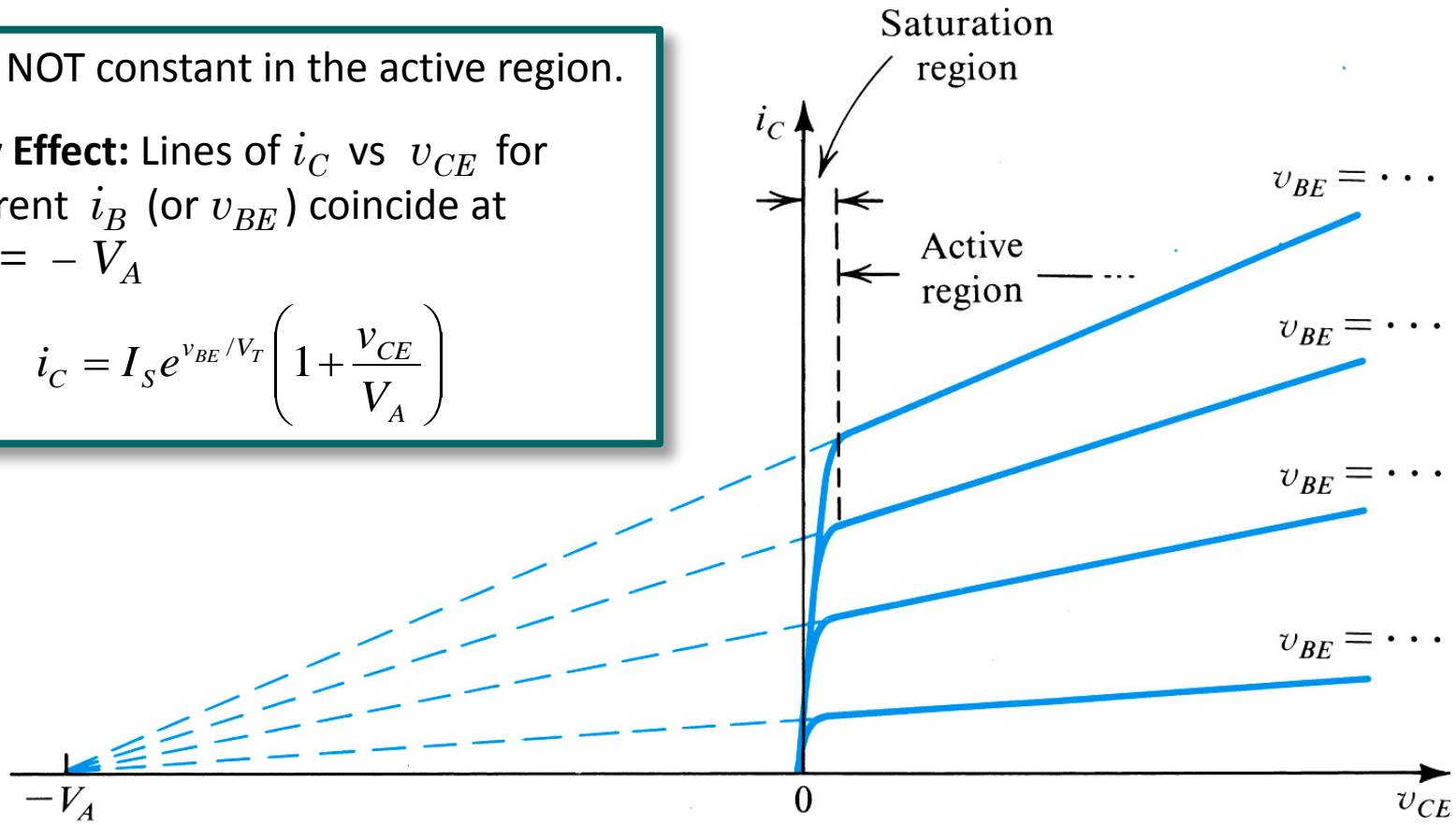
$$i_C = I_S e^{v_{BE}/V_T} \left(1 + \frac{v_{CE}}{V_A} \right)$$



NPN BJT i v equations

Cut-off :

BE is reverse biased

$$i_B = 0, \quad i_C = 0$$

“Linear” model

$$i_B = 0, \quad i_C = 0$$

$$v_{BE} < V_{D0}$$

Active:

BE is forward biased

BC is reverse biased

$$i_B = \frac{i_C}{\beta} = \frac{I_S}{\beta} e^{v_{BE}/V_T}$$

$$i_C = I_S e^{v_{BE}/V_T} \left(1 + \frac{v_{CE}}{V_A} \right)$$

$$v_{BE} = V_{D0}, \quad i_B \geq 0$$

$$i_C = \beta i_B, \quad v_{CE} \geq V_{D0}$$

(Deep) Saturation:

BE is forward biased

BC is reverse biased

$$i_B = \frac{I_S}{\beta} e^{v_{BE}/V_T}$$

$$v_{CE} \approx V_{sat}, \quad i_C < \beta i_B$$


$$v_{BE} = V_{D0}, \quad i_B \geq 0$$

$$v_{CE} = V_{sat}, \quad i_C < \beta i_B$$

For Si, $V_{D0} = 0.7 \text{ V}$, $V_{sat} = 0.2 \text{ V}$

PNP transistor is the analog to NPN BJT

PNP transistor

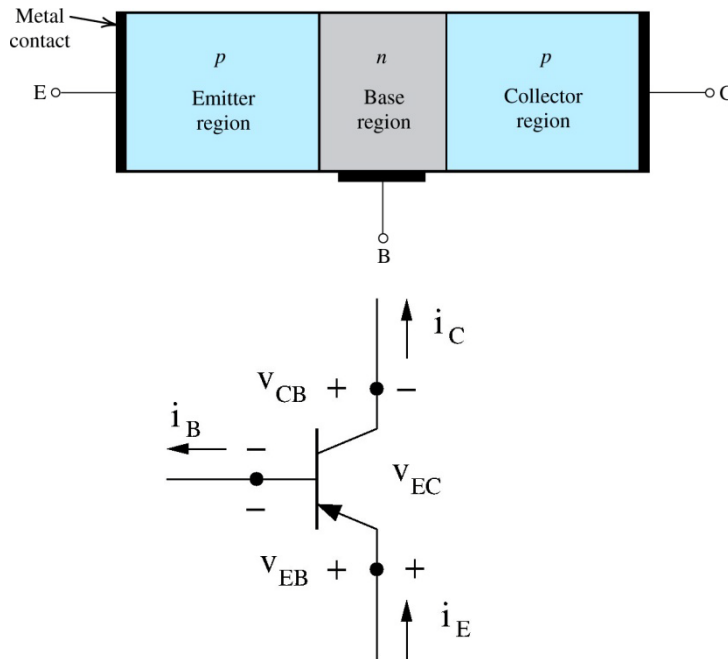

Compared to a NPN:

- 1) Current directions are reversed
- 2) Voltage subscripts "switched"

"Linear" model

Cut-off :

EB is reverse biased

$$i_B = 0, \quad i_C = 0$$

$$v_{EB} < V_{D0}$$

Active:

EB is forward biased

CB is reverse biased

$$v_{EB} = V_{D0}, \quad i_B \geq 0$$

$$i_C = \beta i_B, \quad v_{EC} \geq V_{D0}$$

(Deep) Saturation:

EB is forward biased

CB is reverse biased

$$v_{EB} = V_{D0}, \quad i_B \geq 0$$




$$v_{EC} = V_{sat}, \quad i_C < \beta i_B$$

Notations

Resistors:
Use “subscript” of BJT
terminal: R_C , R_B , R_E .


DC voltages:
Use “Double subscript” of BJT
terminal: V_{CC} , V_{BB} , V_{EE} .

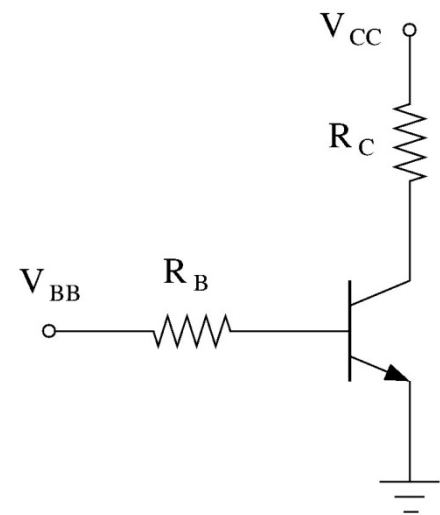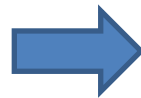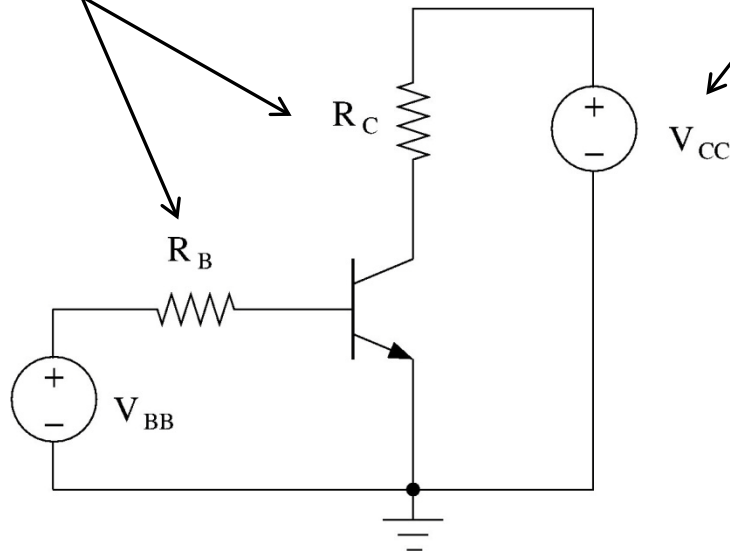Voltage sources are
identified by node
voltage!



Transistor operates like a “valve:”

i_C & v_{CE} are controlled by i_B

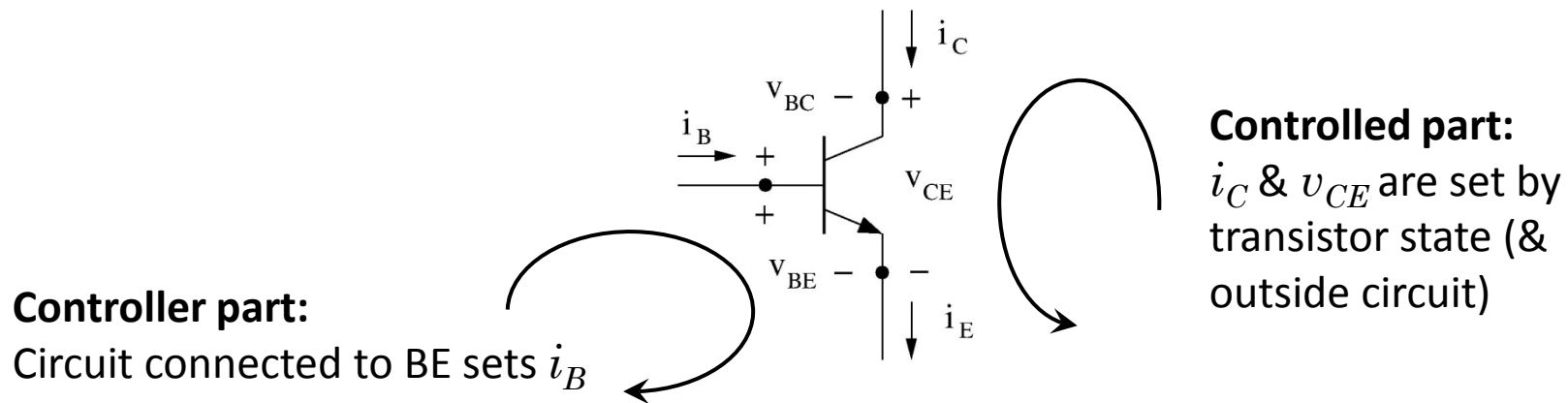

- | | | |
|------------------------------------|-----------------------------|---|
| ➤ Cut-off ($i_B = 0$): | Valve Closed | $i_C = 0$ |
| ➤ Active ($i_B > 0$): | Valve partially open | $i_C = \beta i_B$ |
| ➤ Saturation ($i_B > 0$): | Valve open | $i_C < \beta i_B$
i_C limited by circuit connected to CE terminals, increasing i_B does not increase i_C |

Recipe for solving BJT circuits

(State of BJT is unknown before solving the circuit)

1. Write down BE-KVL and CE-KVL:
2. Assume BJT is OFF, Use BE-KVL to check:
 - a. BJT OFF: Set $i_C = 0$, use CE-KVL to find v_{CE} (Done!)
 - b. BJT ON: Compute i_B
3. Assume BJT in active. Set $i_C = \beta i_B$. Use CE-KVL to find v_{CE} .
If $v_{CE} \geq V_{D0}$, Assumption Correct, otherwise in saturation:
4. BJT in Saturation. Set $v_{CE} = V_{sat}$. Use CE-KVL to find i_C .
(Double-check $i_C < \beta i_B$)

NOTE:

- For circuits with R_E , both BE-KVL & CE-KVL have to be solved simultaneously.

Example 1: Compute transistor parameters (Si BJT with $\beta = 100$).

$$\text{BE - KVL: } 4 = 40 \times 10^3 i_B + v_{BE}$$

$$\text{CE - KVL: } 12 = 10^3 i_C + v_{CE}$$

Assume Cut - off : $i_B = 0$ and $v_{BE} < V_{D0} = 0.7 \text{ V}$

$$\text{BE - KVL: } 4 = 40 \times 10^3 \times 0 + v_{BE} \rightarrow v_{BE} = 4 \text{ V}$$

$v_{BE} = 4 \text{ V} > V_{D0} = 0.7 \text{ V} \rightarrow \text{Assumption incorrect}$

BE ON : $v_{BE} = V_{D0} = 0.7 \text{ V}$ and $i_B \geq 0$


$$\text{BE - KVL: } 4 = 40 \times 10^3 \times i_B + 0.7 \rightarrow \underline{i_B = 8.25 \mu\text{A} > 0}$$

Assume Active: $i_C = \beta i_B$ and $v_{CE} \geq V_{D0} = 0.7 \text{ V}$

$$\underline{i_C = \beta i_B = 100 \times 8.25 \times 10^{-6} = 8.25 \text{ mA}}$$

$$\text{CE - KVL: } 12 = 10^3 \times 8.25 \times 10^{-3} + v_{CE} \rightarrow \underline{v_{CE} = 3.75 \text{ V}}$$

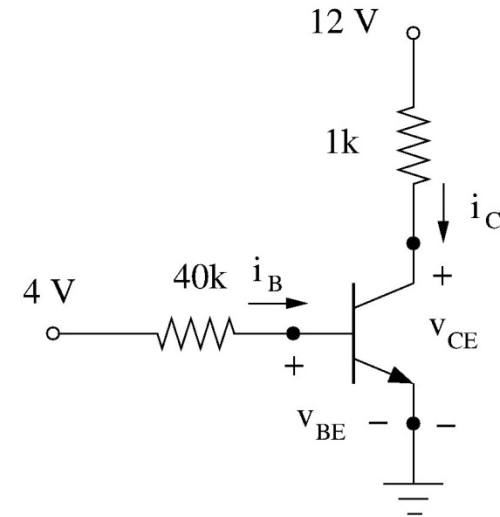$v_{CE} = 3.75 \text{ V} > V_{D0} = 0.7 \text{ V} \rightarrow \text{Assumption correct}$



BJT Transfer Function (1)

$$\text{BE - KVL: } v_i = R_B i_B + v_{BE}$$


$$\text{CE - KVL: } V_{CC} = R_C i_C + v_{CE}$$

$$\text{Cut - off : } i_B = 0 \text{ and } v_{BE} < V_{D0}$$

$$\text{BE - KVL: } v_i = R_B \times 0 + v_{BE} \rightarrow v_{BE} = v_i$$

$$i_C = 0$$
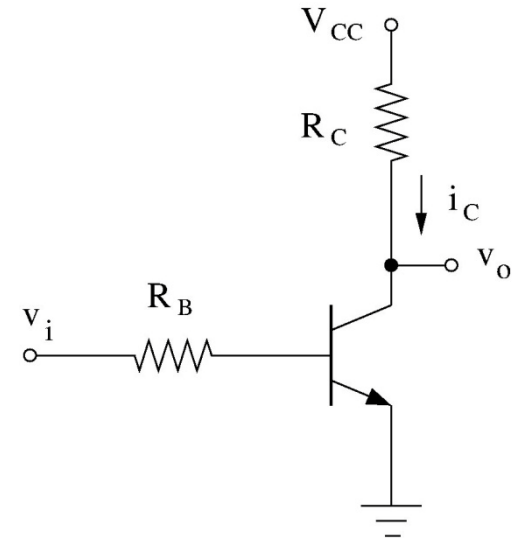
$$\text{CE - KVL: } V_{CC} = R_C \times 0 + v_{CE} \rightarrow v_{CE} = V_{CC}$$



For $v_i < V_{D0} \rightarrow$ BJT in Cutoff

$$i_B = 0, \quad i_C = 0, \quad v_{CE} = V_{CC}$$

$$\text{BE ON: } v_{BE} = V_{D0} \text{ and } i_B \geq 0$$

$$\text{BE - KVL: } v_i = R_B \times i_B + V_{D0} \rightarrow i_B = \frac{v_i - V_{D0}}{R_B}$$

$$i_B \geq 0 \rightarrow v_i \geq V_{D0}$$

BJT Transfer Function (2)

BE ON: $v_{BE} = V_{D0}$ and $i_B = \frac{v_i - V_{D0}}{R_B}$


CE - KVL: $V_{CC} = R_C i_C + v_{CE}$

Active: $i_C = \beta i_B$ and $v_{CE} \geq V_{D0}$

$$i_C = \beta \times \frac{v_i - V_{D0}}{R_B}$$

CE - KVL: $V_{CC} = R_C i_C + v_{CE} \rightarrow v_{CE} = V_{CC} - R_C i_C$
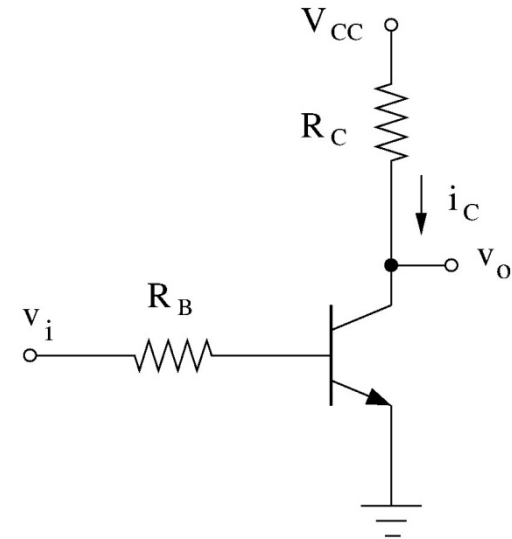
$$v_{CE} \geq V_{D0} \rightarrow v_i \leq V_{D0} + \frac{V_{CC} - V_{D0}}{\beta R_C / R_B}$$



For $V_{D0} \leq v_i \leq V_{D0} + \frac{V_{CC} - V_{D0}}{\beta R_C / R_B} \rightarrow$ BJT in active

BJT Transfer Function (3)


$$\text{BE ON: } v_{BE} = V_{D0} \text{ and } i_B = \frac{v_i - V_{D0}}{R_B}$$

$$\text{CE - KVL: } V_{CC} = R_C i_C + v_{CE}$$

$$\text{Saturation: } v_{CE} = V_{sat} \text{ and } i_c < \beta i_B$$

$$\text{CE - KVL: } V_{CC} = R_C i_C + V_{sat} \rightarrow i_C = \frac{V_{CC} - V_{sat}}{R_C}$$
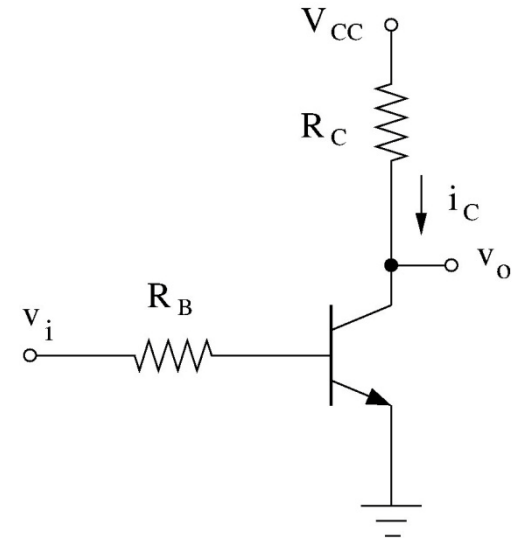
$$i_c < \beta i_B \rightarrow v_i > V_{IH} = V_{D0} + \frac{V_{CC} - V_{sat}}{\beta R_C / R_B}$$






$$\text{For } V_{D0} + \frac{V_{CC} - V_{D0}}{\beta R_C / R_B} < v_i \rightarrow \text{BJT in saturation}$$

BJT Transfer Function (4)

$$v_i < V_{D0} \rightarrow \text{BJT in Cutoff}$$

$$V_{D0} \leq v_i \leq V_{D0} + \frac{V_{CC} - V_{D0}}{\beta R_C / R_B} \rightarrow \text{BJT in active}$$
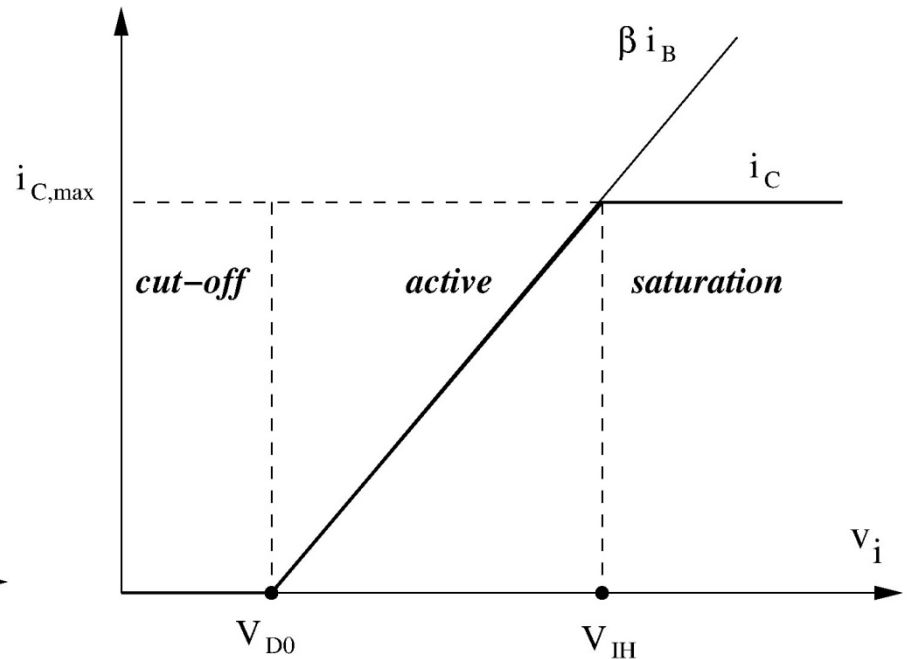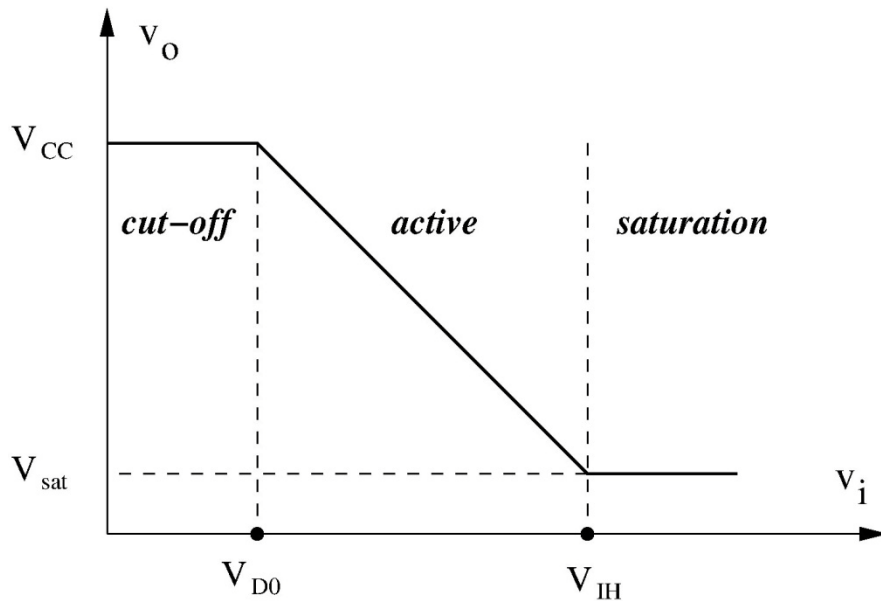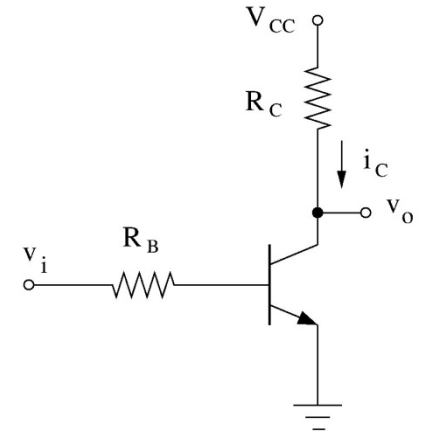
$$V_{D0} + \frac{V_{CC} - V_{sat}}{\beta R_C / R_B} < v_i \rightarrow \text{BJT in deep saturation}$$




BJT transfer function on the load line

Saturation : $V_{IH} < v_i$

i_B increases but i_C unchanged

Load Line (CE - KVL)

$$v_{CE} = V_{CC} - R_C i_C$$



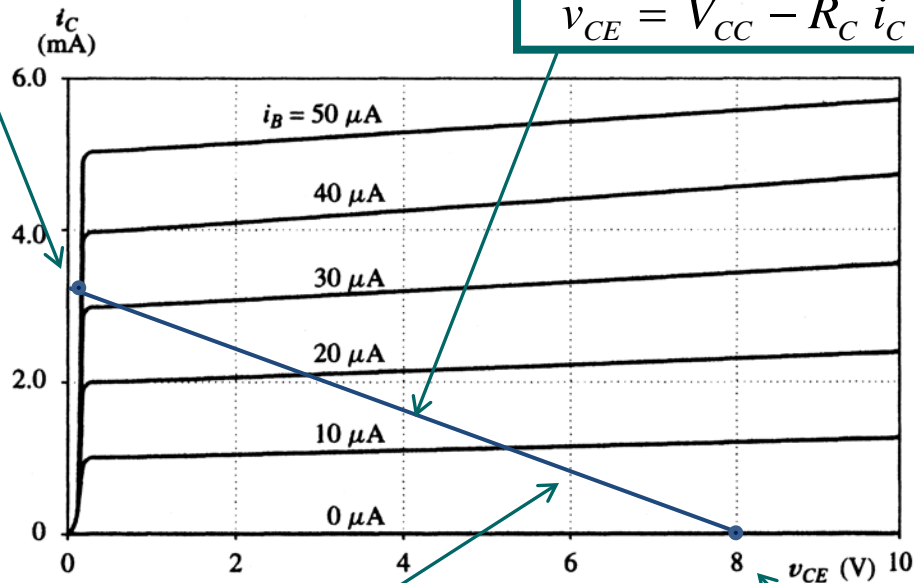


Active : $V_{D0} \leq v_i \leq V_{IH}$


i_B & i_C increase together

Cut - off :

$v_i < V_{D0}$

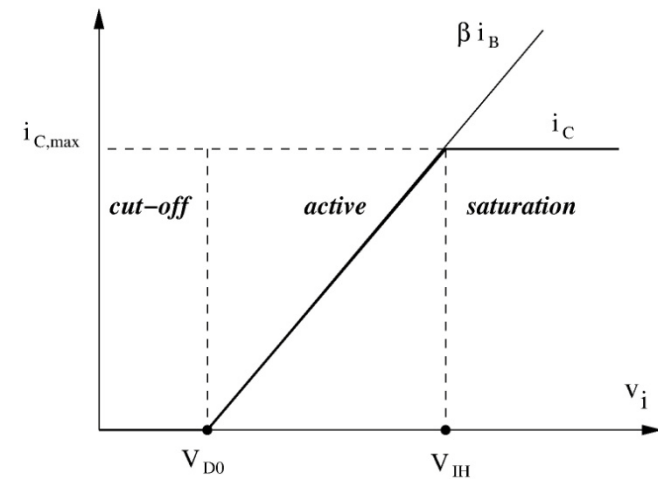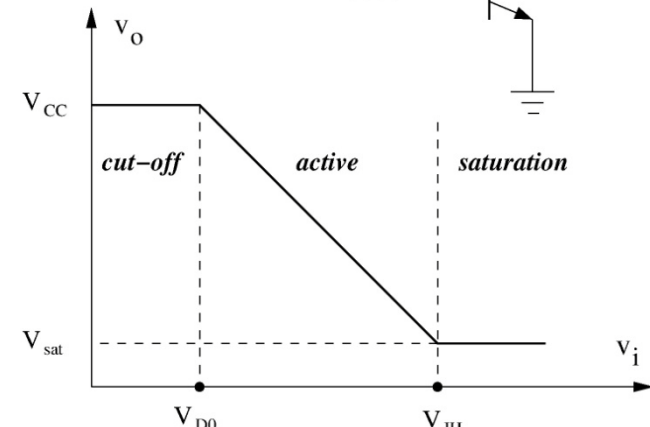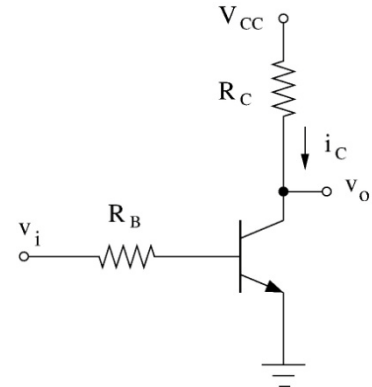

BJT as a switch

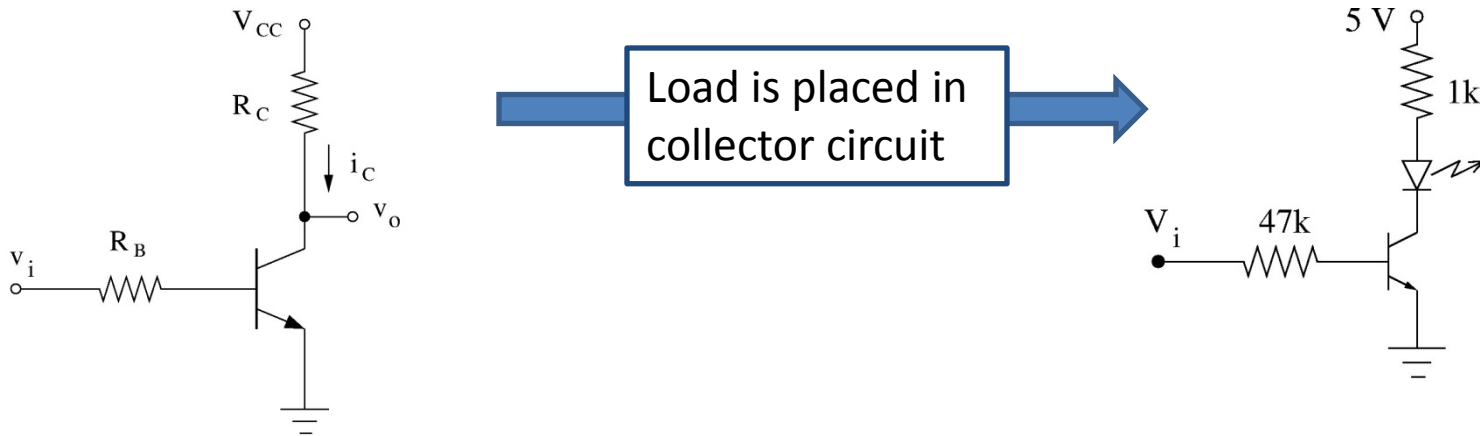

- Use: Logic gate can turn loads ON (BJT in saturation) or OFF (BJT in cut-off)
- i_C is uniquely set by CE circuit (as $v_{ce} = V_{sat}$)
- R_B is chosen such that BJT is in deep saturation with a wide margin (e.g., $i_B = 0.2 i_C / \beta$)


*Lab 4 circuit

Solved in Lecture notes (problems 12 & 13)


BJT as a Digital Gate

Resistor-Transistor logic (RTL)

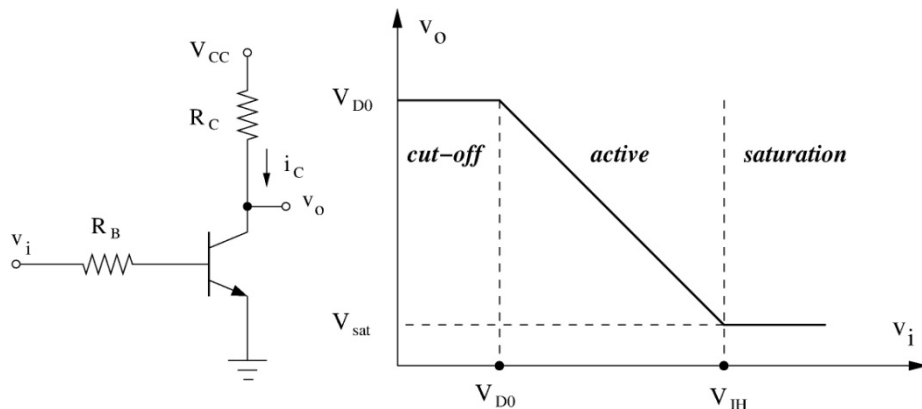
RTL NOT gate ($V_L = V_{sat}$, $V_H = V_{CC}$)



RTL NOR gate*

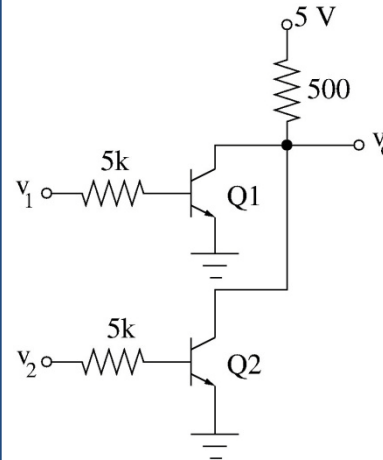

RTL NAND gate*

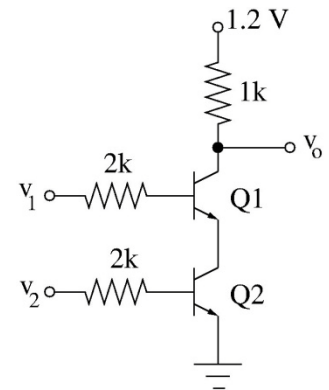

- Other variants: Diode-transistor logic (DTL) and transistor-transistor logic (TTL)
- BJT logic gates are not used anymore except for high-speed emitter-coupled logic circuits
 - Low speed (switching to saturation is quite slow).
 - Large space and power requirements on ICs

BJT β varies substantially

- Our BJT model includes three parameters: V_{D0} , V_{sat} and β
 - V_{D0} and V_{sat} depend on base semiconductor:
 - For Si, $V_{D0} = 0.7$ V, $V_{sat} = 0.2$ V
- Transistor β depends on many factors:
 - Strongly depends on temperature (9% increase per °C)
 - Depends on i_C (not constant as assumed in the model)
 - β of similarly manufactured BJT can vary (manufacturer spec sheet typically gives a range as well as an average value for β)
 - We will use the average β in calculations (PSpice also uses average β but includes temperature and i_C dependence).
 - β_{min} is an important parameter. For example, to ensure operation in deep saturation for all similar model BJTs, we need to set $i_C / i_B < \beta_{min}$