



Microprocessor Systems


Dr. Gökhan İnce



Topics


- I/O Interface
- I/O Transfer Synchronization
- Parallel Communication

Computer Organization

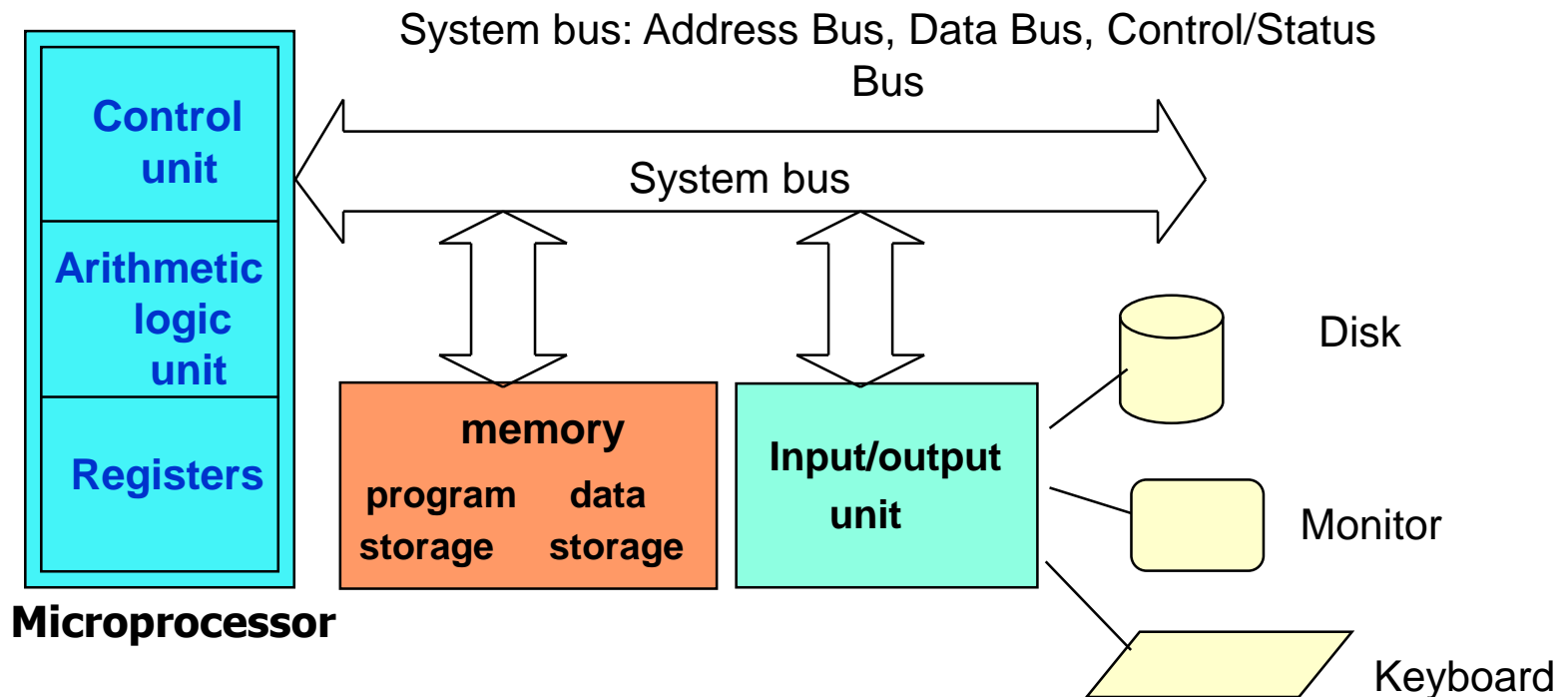

I/O Interface

- Peripheral devices (also called I/O devices) are pieces of equipment that exchange data with a CPU
 - Examples of I/O devices include switches, push-buttons, light-emitting diodes (LED), monitors, printers, modems, keyboards, and disk drives.
- Interface chips are needed to resolve the differences between CPU and I/O devices
 - Provides a method for transferring information between internal storage (such as memory and CPU registers) and external I/O devices

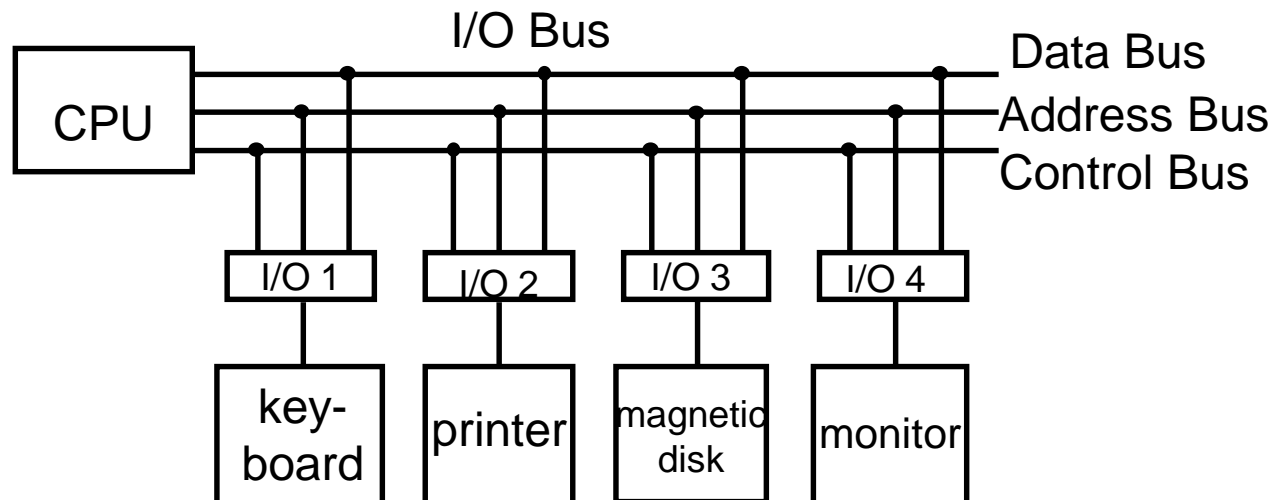




I/O Interfacing

- Resolves the differences between the computer and peripheral devices
 - Peripherals are electromechanical and electromagnetic devices, CPU and memory are electronic devices
 - Data codes and formats in peripherals are different
- A synchronization mechanism is needed.
 - Data transfer rate of peripherals are usually slower
- Data transfer between an I/O device and the CPU can be proceeded bit-by-bit (serial) or in multiple bits (parallel).


I/O Interfacing

- The I/O communication can be Parallel or Serial

Parallel interface example

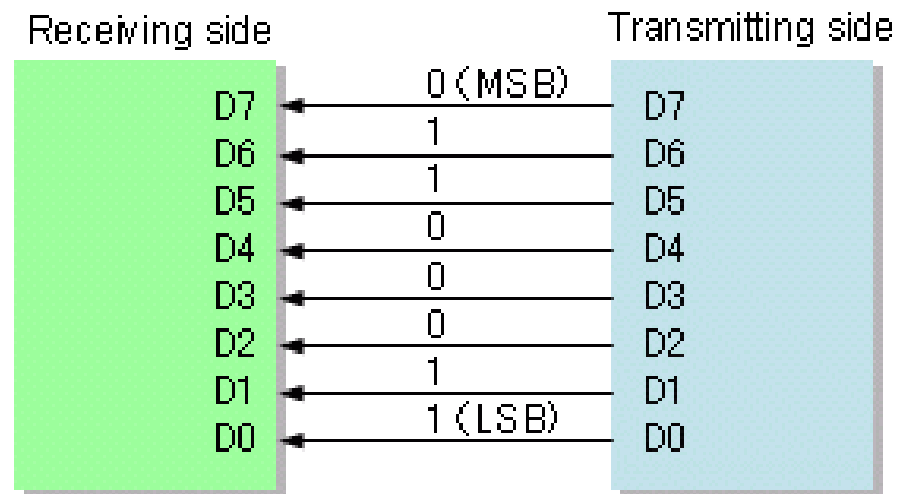

Serial interface example (MSB first)

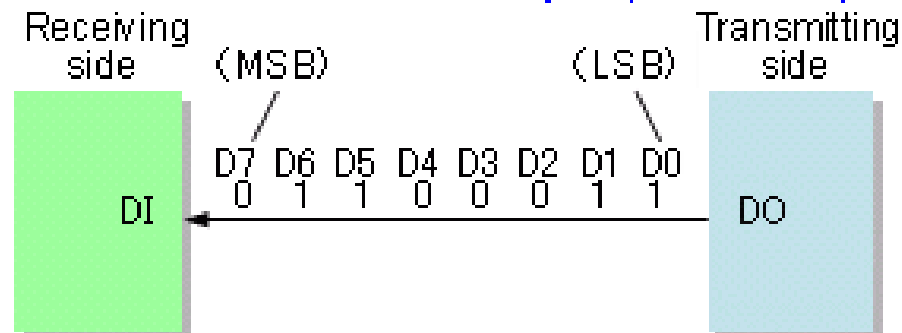




I/O Addresses


- Isolated I/O Map
 - Separate I/O read/write control lines in addition to memory read/write control lines
 - Separate (isolated) memory and I/O address spaces
 - Distinct input and output instructions
- Memory Mapped I/O
 - A single set of read/write control lines (no distinction between memory and I/O transfer)
 - Memory and I/O addresses share the common address space
 - reduces memory address range available
 - No specific input or output instruction
 - The same memory reference instructions can be used for I/O transfers
 - Considerable flexibility in handling I/O operations

Isolated I/O Map-based Interfacing

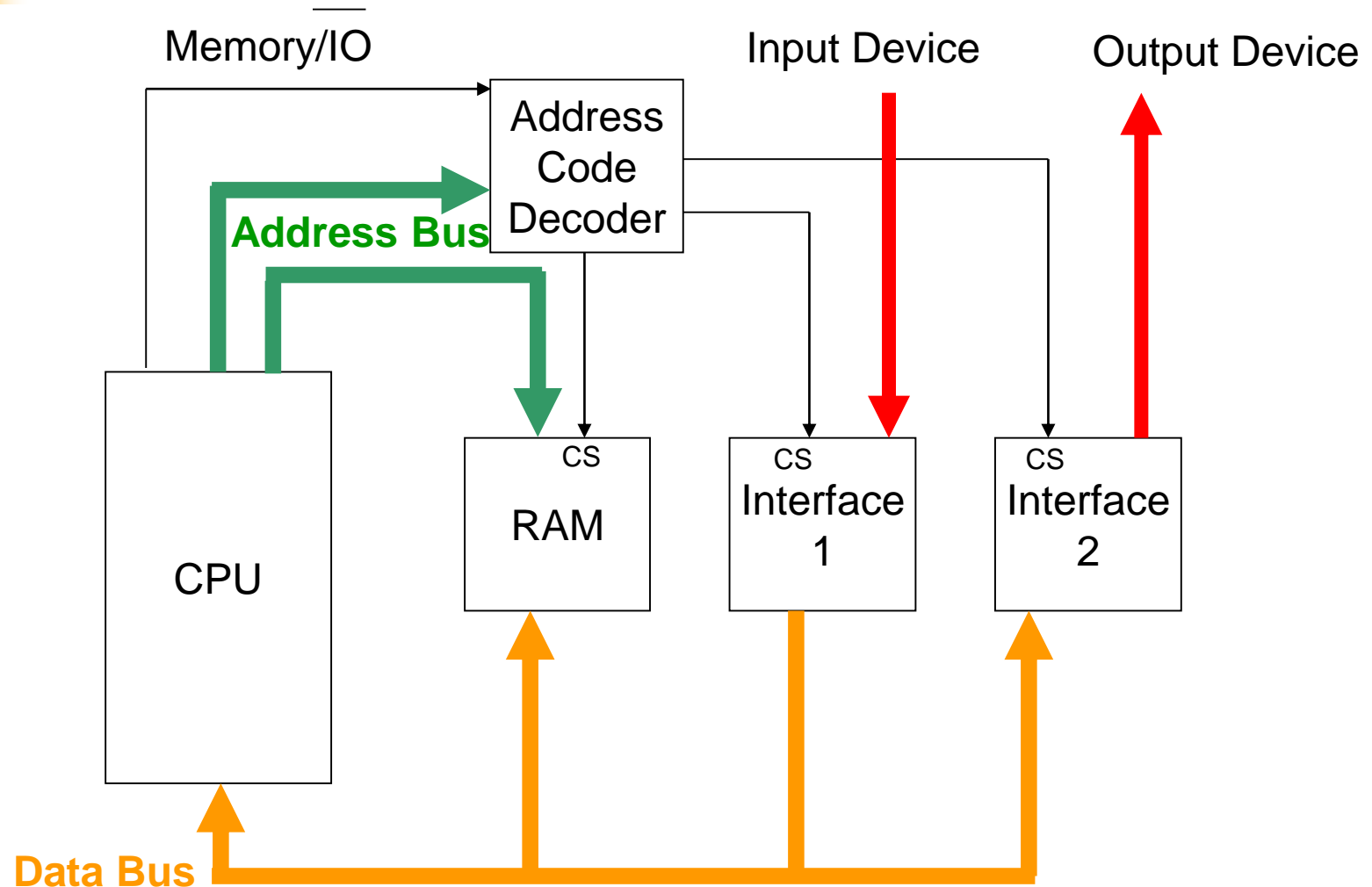


Connection of I/O Interfaces

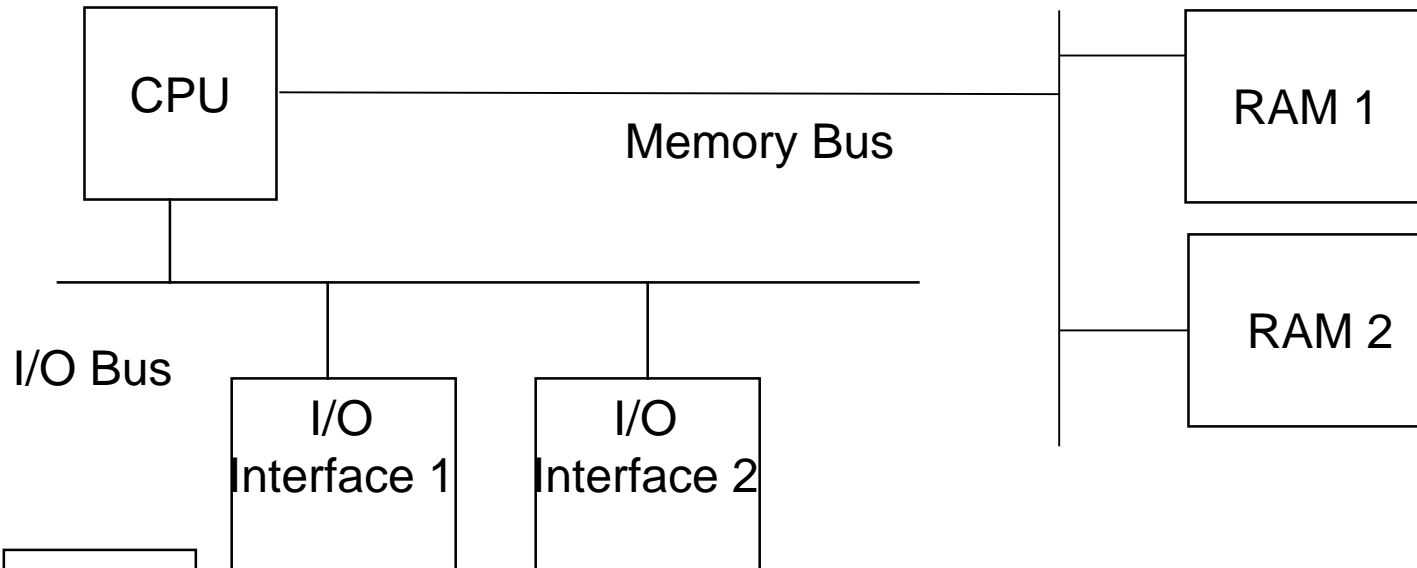
Seperate Data Busses for I/O Interfaces and Memory



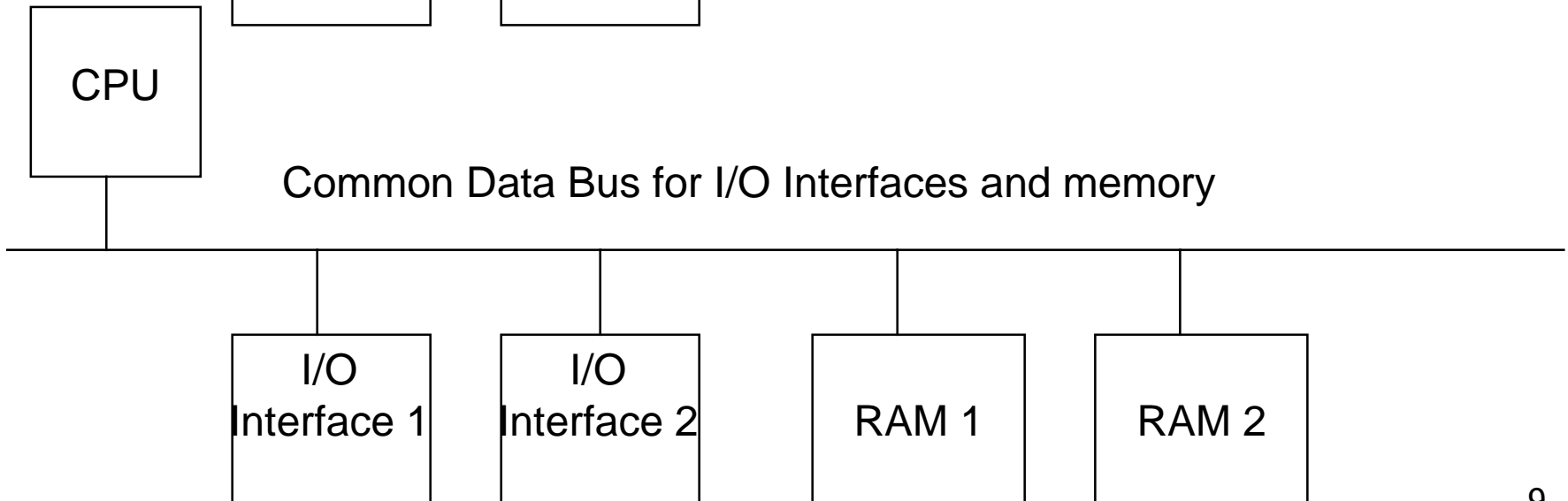Common Data Bus for I/O Interfaces and memory



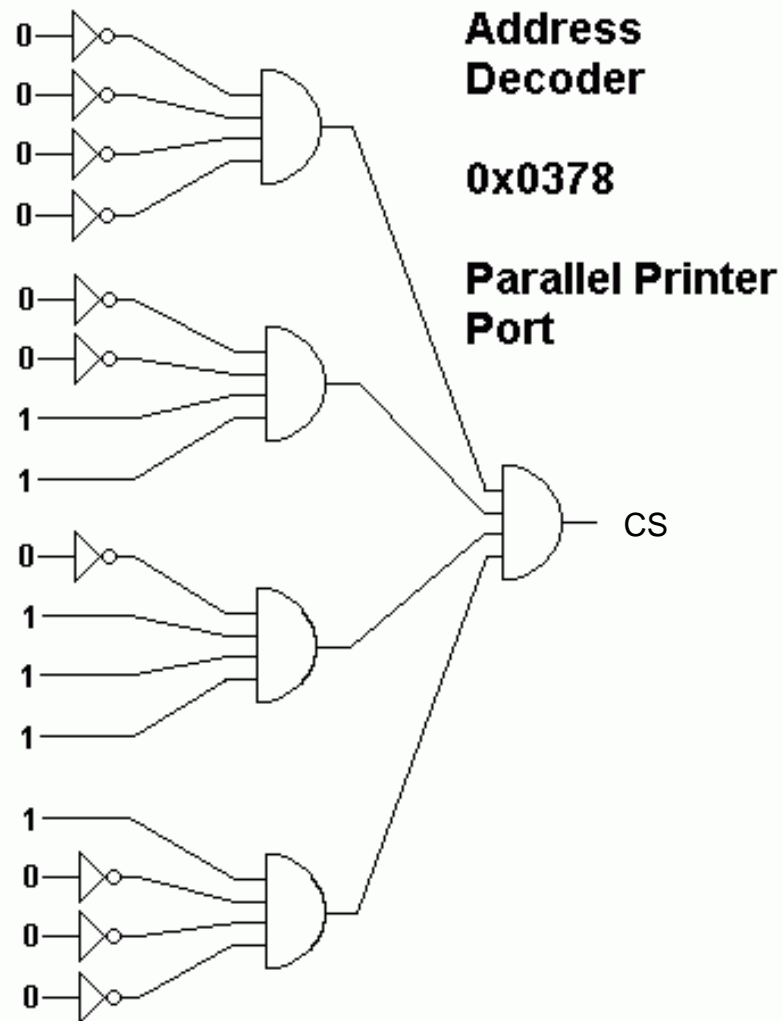Address Decoder for Memory-mapped I/O interface






Topics

- I/O Interface
- I/O Transfer Synchronization
- Parallel Communication

I/O Transfer Synchronization

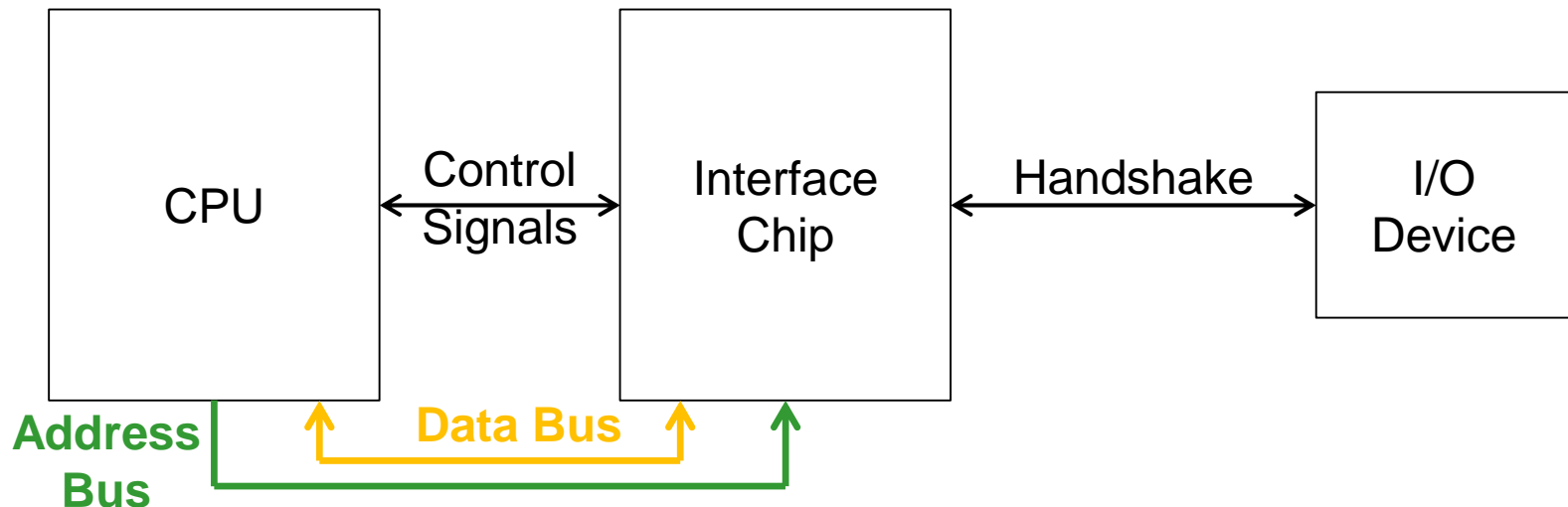- The role of the interface chip
 - Synchronizing data transfer between CPU and interface chip.
 - Programmed I/O
 - Interrupt driven I/O
 - Direct Memory Access (DMA)
 - Synchronizing data transfer between interface chip and I/O device.
 - Handshaking method





CPU and I/O Interfaces


- Programmed I/O
 - Sensing status
 - Read/write commands
 - Transferring data
 - CPU waits for I/O module to complete operation
 - Wastes CPU time
- Interrupt Driven I/O
 - Overcomes CPU waiting
 - No repeated CPU checking of device
 - I/O module interrupts when ready
- Direct Memory Access (DMA)
 - Additional Module (hardware) on bus
 - DMA controller takes over from CPU for I/O operations




Synchronizing the CPU and the Interface Chip

- The polling method:
 - for input -- **the microprocessor** checks a status bit of the interface chip to find out if the interface has received new data from the input device.
 - for output -- **the microprocessor** checks a status bit of the interface chip to find out if it can send new data to the interface chip.
- The interrupt-driven method
 - for input -- **the interface chip** interrupts the microprocessor whenever it has received new data from the input device.
 - for output -- **the interface chip** interrupts the microprocessor whenever it can accept new data from the microprocessor.


CPU and I/O Interfaces

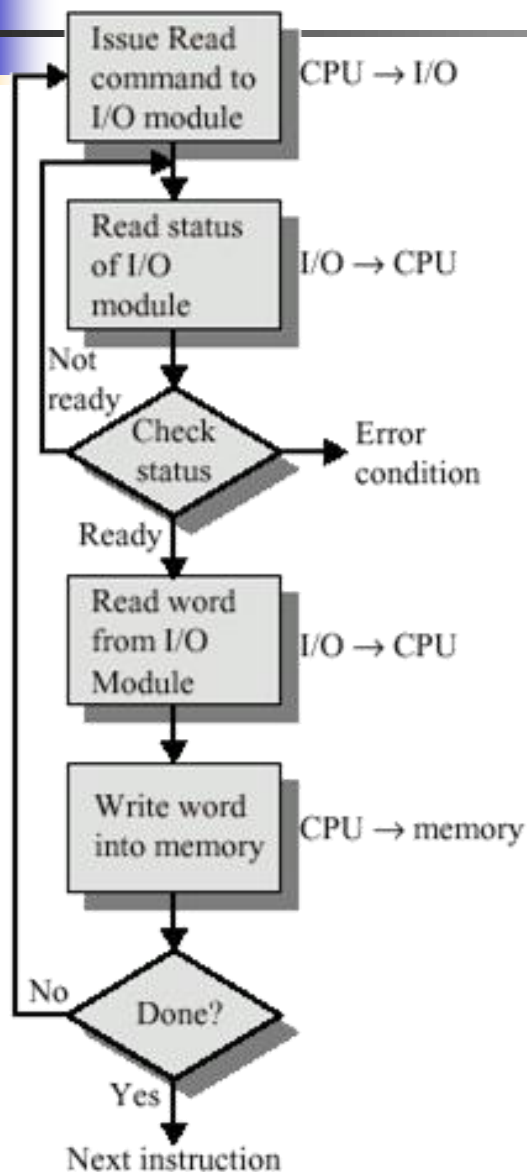

(a) Programmed I/O

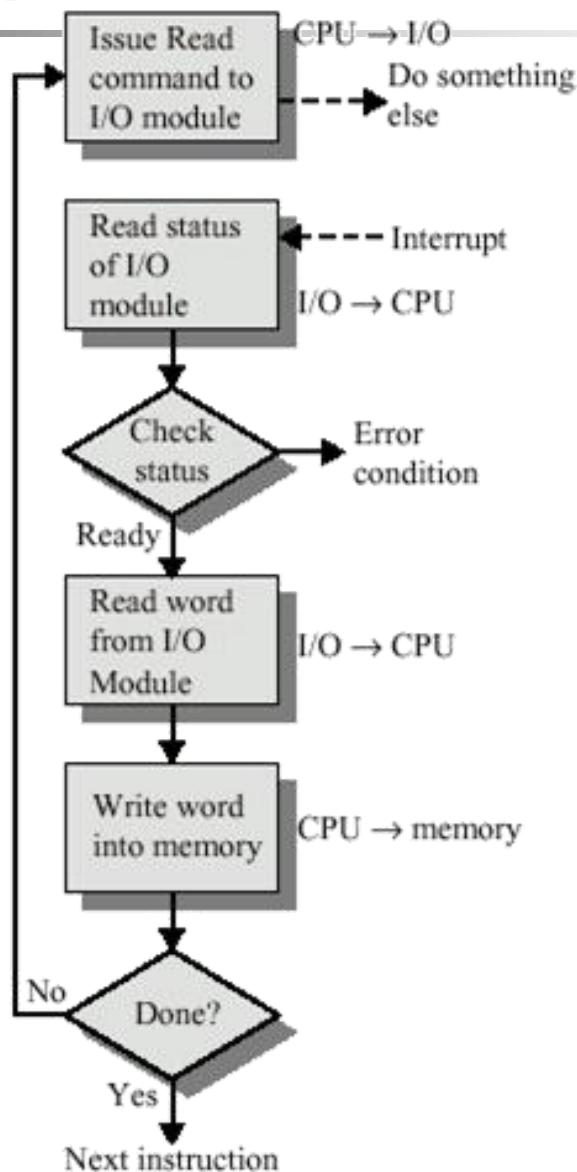


(b) Interrupt-driven I/O

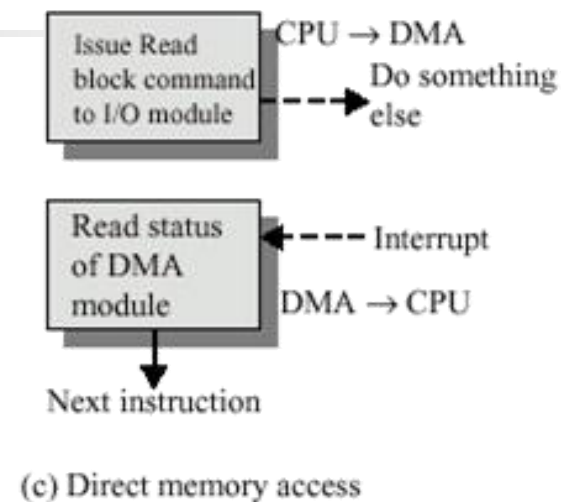


Synchronization of interface chip and peripheral

- Transmitter initiated 2-wire Handshaking
 - In Parallel communication transmitter and receiver uses handshaking protocol
 - In short distance serial communication, handshaking can also be used

Parallel interface example

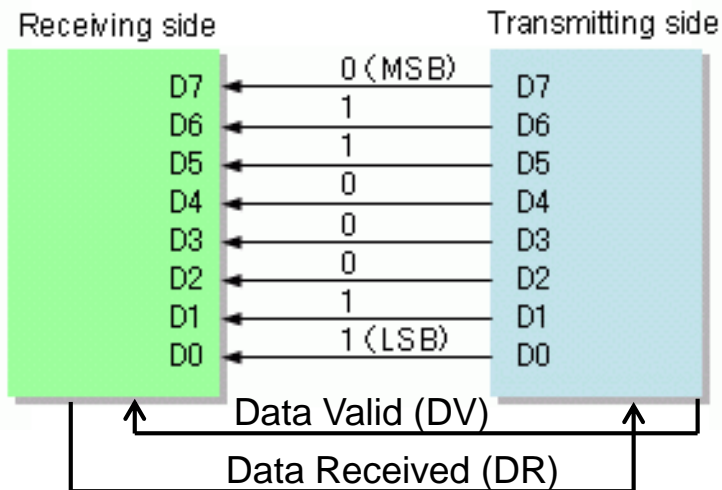


- Transmitter puts the data on the data lines and brings DV low to indicate new data is available
- When the receiver sees the new data is available, it reads the data, then brings DR low to say that it has read the data
- When the sending computer sees DR go low, it brings DV high
- When the receiving computer sees DV go high, it brings DR high
- Both sides are now ready for the next data transfer

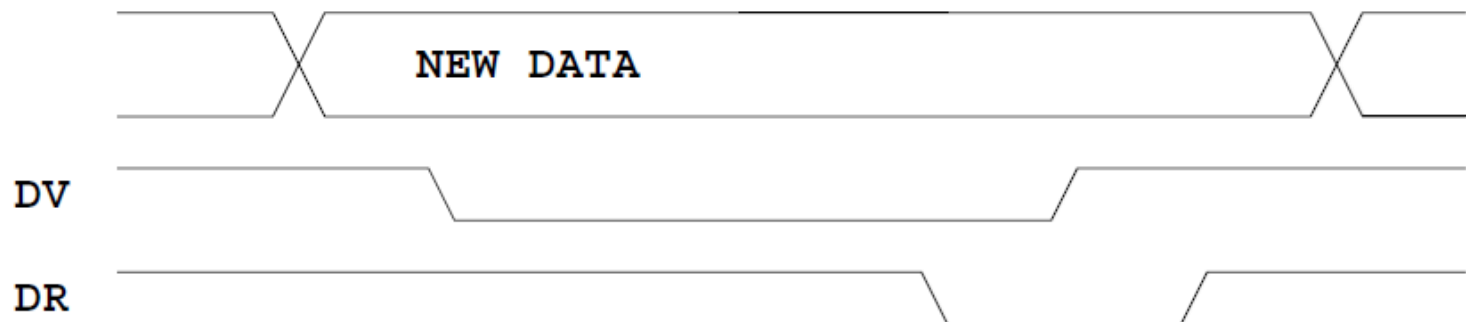

Synchronization of interface chip and peripheral

- Receiver initiated 2-wire Handshaking

Parallel interface example

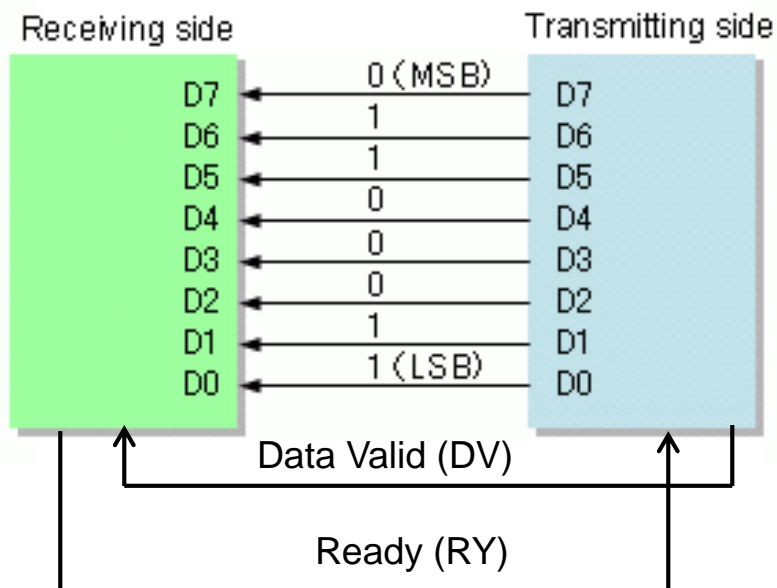

- Receiver brings Ready (RY) to low to indicate it is ready to receive new data
- Transmitter places data on data lines and lowers Data Valid (DV)
- Receiver sees DV and accepts data, then brings RY high
- Transmitter sees RY high and raises DV to high
- Both computers are now ready for the next data transfer




Topics

- I/O Interface
- I/O Transfer Synchronization
- Parallel Communication


Parallel Communication

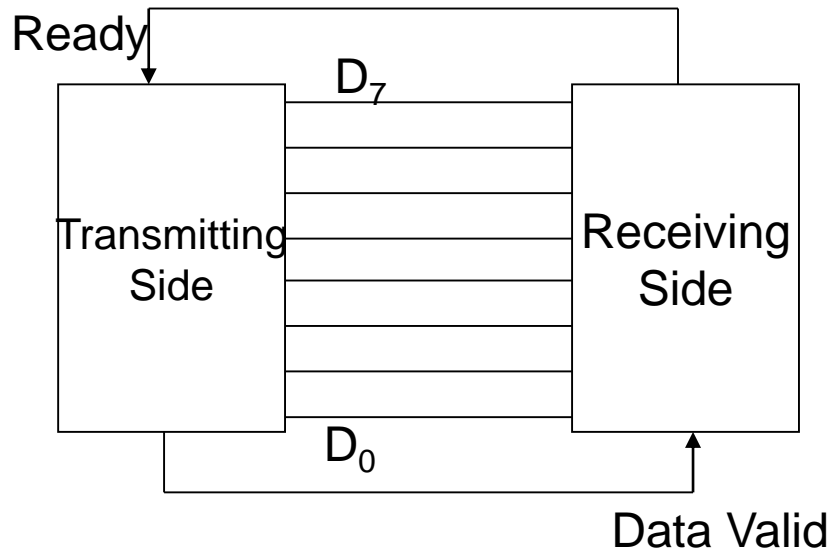- Each bit is transferred along its own line and bits are transferred at the same time
- In addition to eight parallel data lines, other lines are used to read status information and send control signals.




Basic Parallel Input Interface

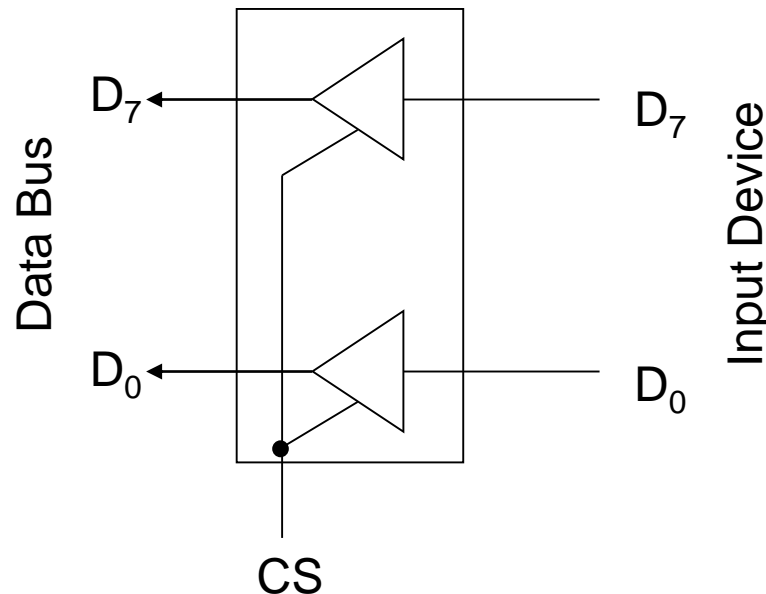- Tri-state buffers are used. (74LS244)
- Output pins connected to CPU Data Bus, Input pins connected to the Input device.



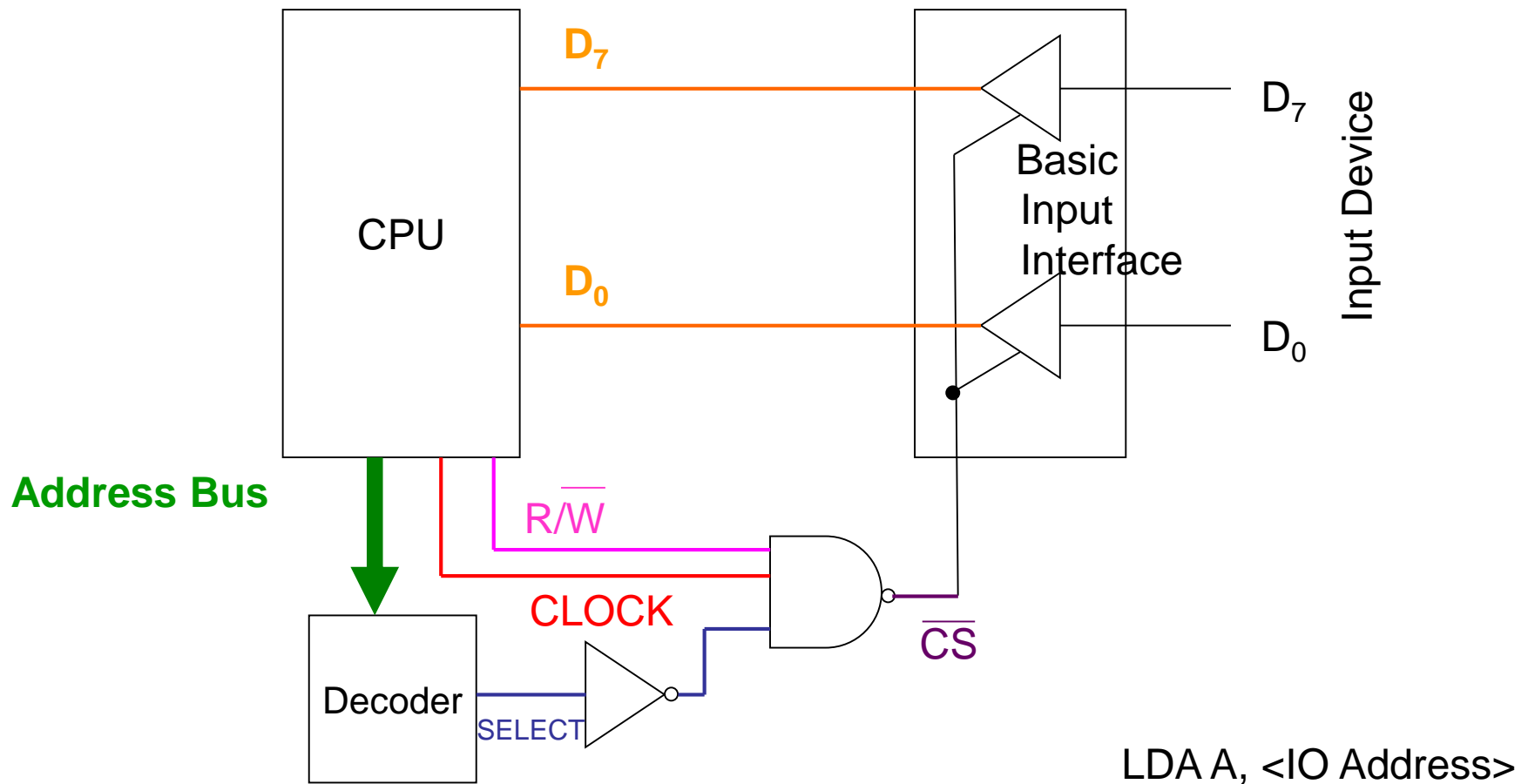
Basic Parallel Input Interface – CPU Connections



Basic Parallel Input Interface

– CPU Control -

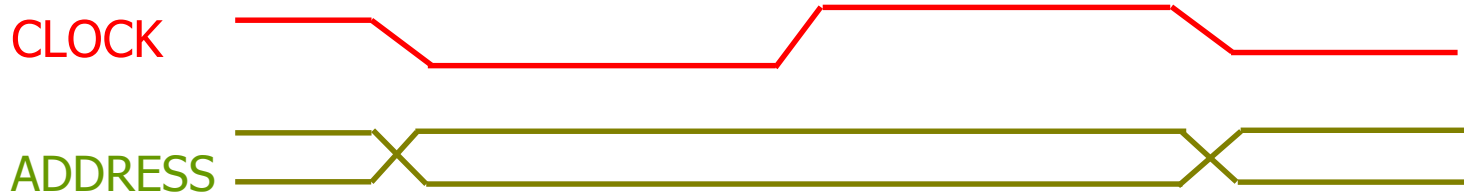
- Address placed on address bus at the falling edge of clock



- Address decoded to form Select




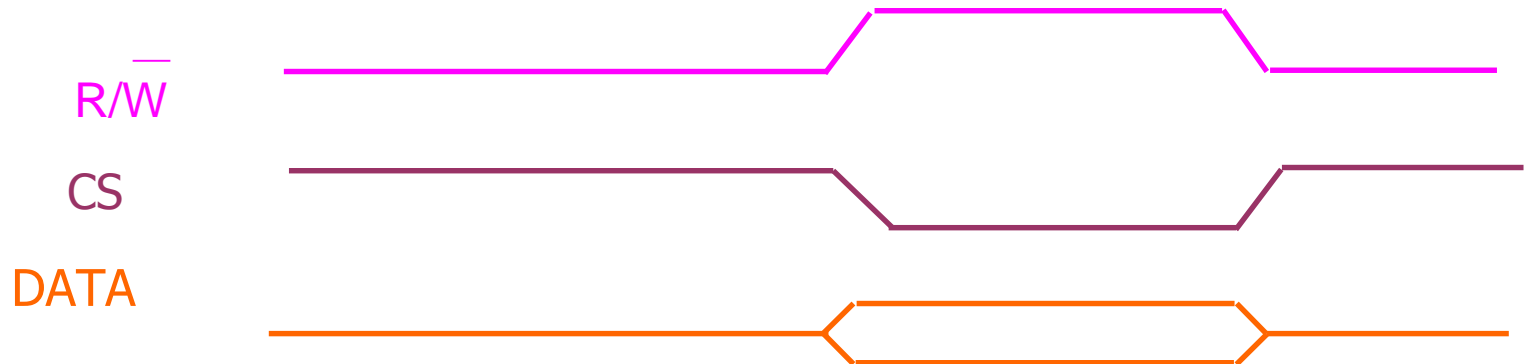- $\text{NAND} \{ \text{CLK}, \overline{\text{SELECT}}, \overline{\text{R/W}} \}$ to form CS




Basic Parallel Output Interface

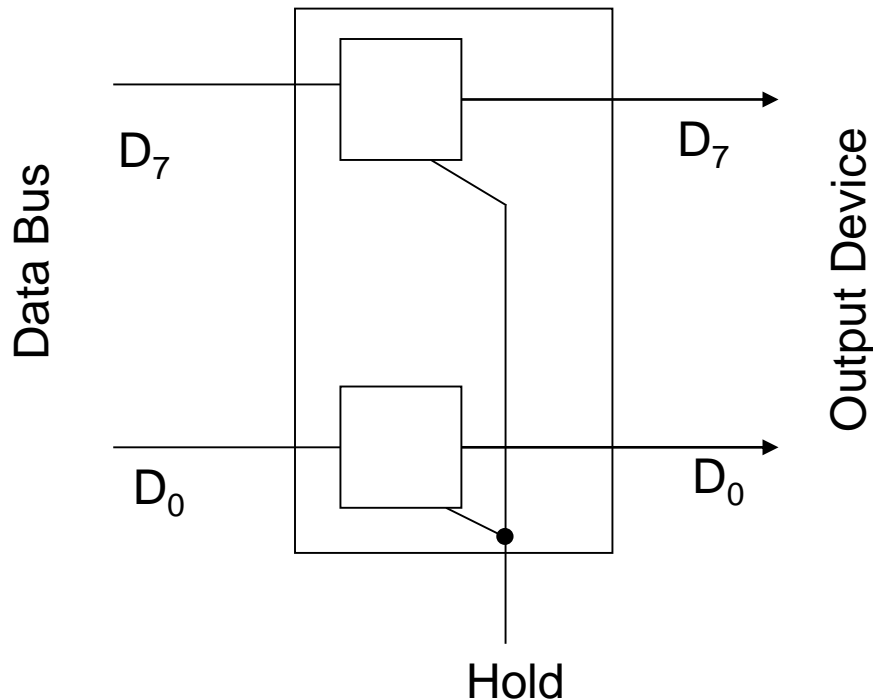- D Latches can be used (74LS374 Octal D Latch)
- Inputs of D latches are connected to the Data Bus. The outputs connected to the output device



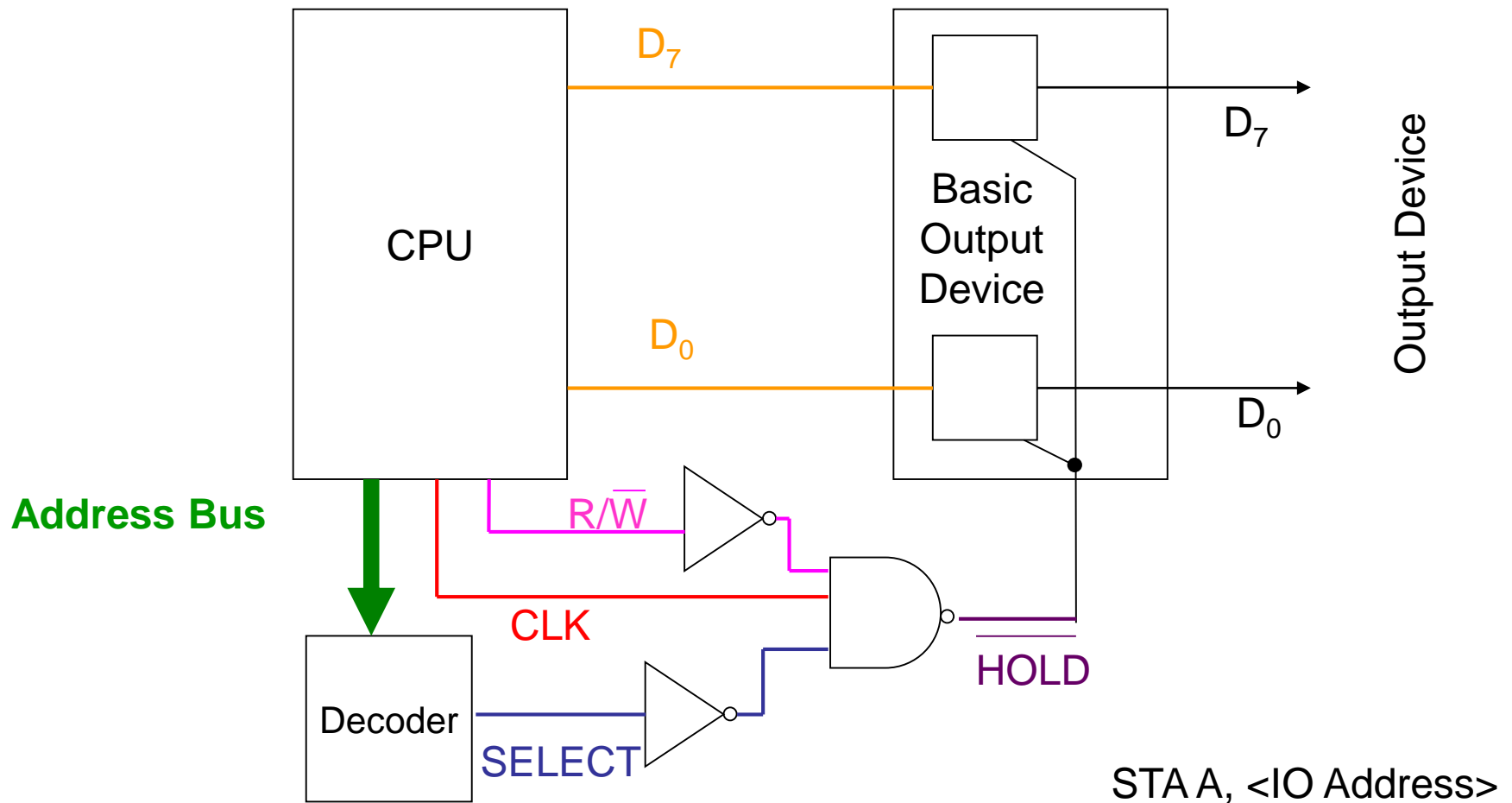Basic Parallel Output Interface – CPU Connections



Basic Parallel Output Interface – CPU Control


- Address placed on address bus at the falling edge of clock



- Data is placed on the data bus



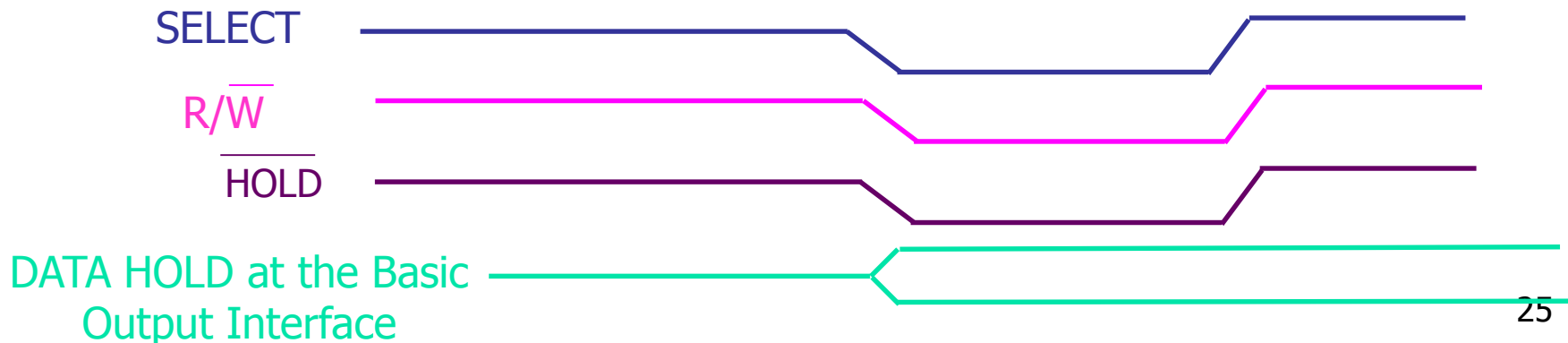- Address decoded to form Select
- $\text{NAND} \{ \text{CLK}, \overline{\text{SELECT}}, \overline{\text{R/W}} \}$ to form HOLD






Peripheral Interface Adapter (EDU-PIA)

- Can be programmed to handle input or output data
- PIA contains
 - Port(s): Connects the PIA to peripheral devices. Each pin of the port can be conditioned as transmit (TX) or receive (RX)
 - Data Direction Register: Conditions the port pins as TX or RX
 - 1 : Pin is Transmitter
 - 0 : Pin is Receiver
 - Control / Status Register:
 - Status bits: Indicates the status of the handshaking bits
 - Control bits: Used to control handshaking signals and interrupt conditions

Peripheral Interface Adapter (EDU-PIA)

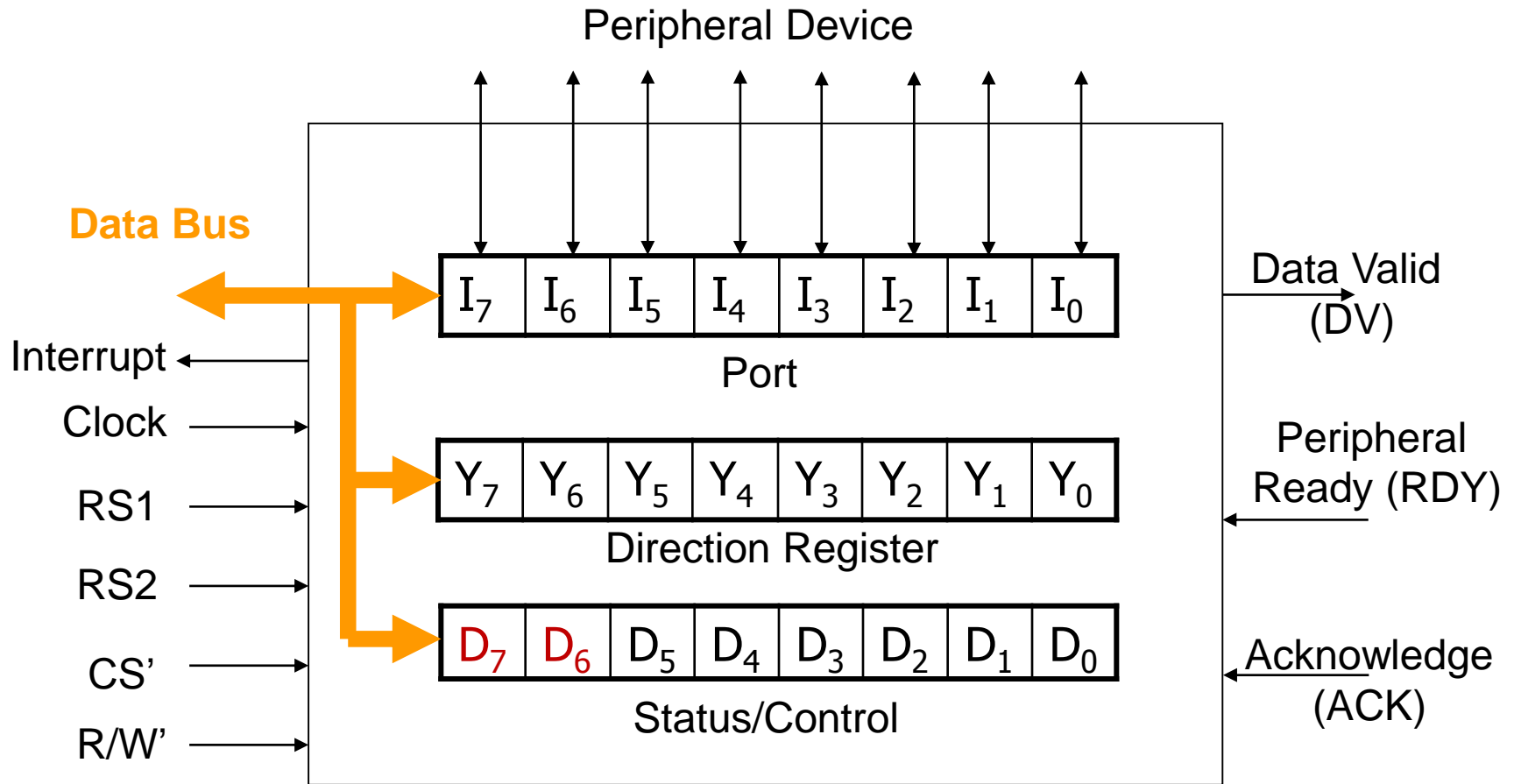

RS: Register Select
CS: Control Signal



Peripheral Interface Adapter (EDU-PIA)

- No consensus on the condition of raising the flag ($1 \rightarrow 0$ or $0 \rightarrow 1$?)
- READY (RDY) Input
 - Indicates whether the peripheral device is ready
 - D7 Status Bit indicates RDY is received
 - Active High
 - D1 and D0 control bits determine whether an interrupt will be generated when RDY is received
 - D7 is cleared when Status/Control register is read

D_1D_0	Ready (RDY) Input	Interrupt Output
0 0	$1 \rightarrow 0 \Rightarrow D_7=1$	High, No interrupt
0 1	$0 \rightarrow 1 \Rightarrow D_7=1$	High, No interrupt
1 0	$1 \rightarrow 0 \Rightarrow D_7=1$	Hi- \rightarrow Low- \rightarrow Hi, Interrupt
1 1	$0 \rightarrow 1 \Rightarrow D_7=1$	Hi- \rightarrow Low- \rightarrow Hi, Interrupt



Peripheral Interface Adapter (EDU-PIA)

- No consensus on the condition of raising the flag ($1 \rightarrow 0$ or $0 \rightarrow 1$?)
- ACKNOWLEDGE (ACK) Input
 - Indicates whether the peripheral device received the data
 - D6 Status Bit indicates ACK is received
 - Active High
 - D3 and D2 control bits determine whether an interrupt will be generated when ACK is received
 - D6 is cleared when Status/Control register is read

D_3D_2	Acknowledge (ACK) Input	Interrupt Output
0 0	$1 \rightarrow 0 \Rightarrow D_6=1$	High, No interrupt
0 1	$0 \rightarrow 1 \Rightarrow D_6=1$	High, No interrupt
1 0	$1 \rightarrow 0 \Rightarrow D_6=1$	Hi->Low->Hi, Interrupt
1 1	$0 \rightarrow 1 \Rightarrow D_6=1$	Hi->Low->Hi, Interrupt




Peripheral Interface Adapter (EDU-PIA)

- No consensus on the handshake conditions
- DATA VALID (DV) Output
 - Indicates valid data is at the Port
 - D5 and D4 control bits determine the DV conditions

D ₅ D ₄	DATA VALID (DV)
0 0	DV is reset (low)
0 1	DV is set (high)
1 0	1 after the data is loaded on the port
1 1	0 after the data is loaded on the port

EDU-PIA / CPU Connections

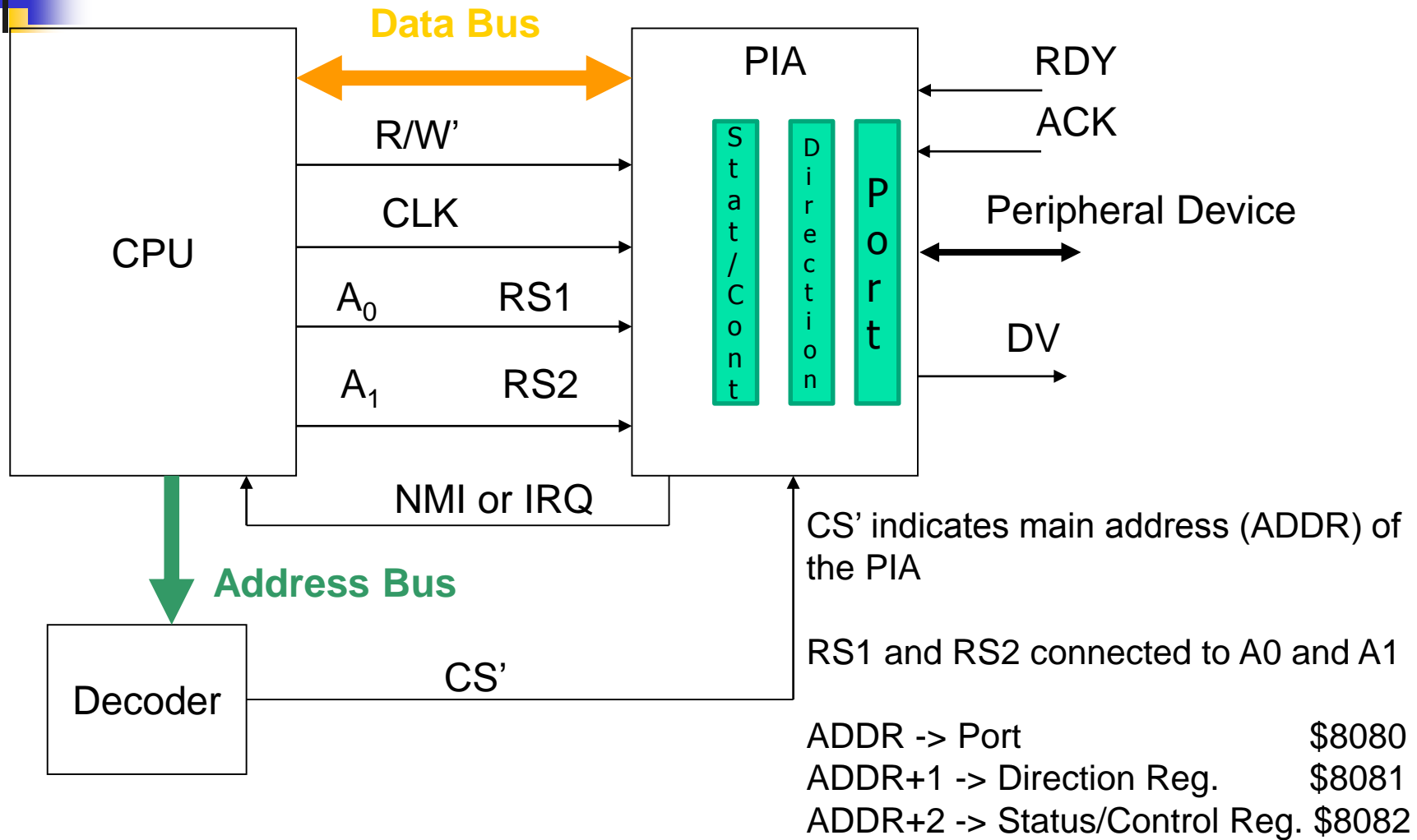

NMI:Non-Maskable Interrupt



EDU-PIA / CPU Connections

- Example I: The EDU-PIA is connected to an 8-bit microprocessor with 16-line address bus. The main address of the PIA is \$A0A0. The first four pins of the PIA are connected to four switches. The remaining four bits of the PIA are connected to LEDs.
 - Design a system that will illuminate the LEDs depending on the switch positions. The LEDs will illuminate after the user arranges the switches and presses a button.

Simple Output Device - LED

■ Case-1




- LED is ON for an output of zero
- Most LEDs drop 1.7 to 2.5 volts and need about 10mA
- Current is $(5-2)/R$

■ Case-2


- Too much current
- Failure of Port or LED

■ Case-3

- Not enough drive (1mA)
- LED too dim

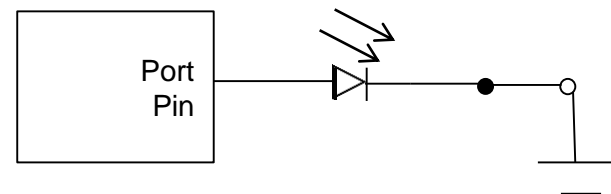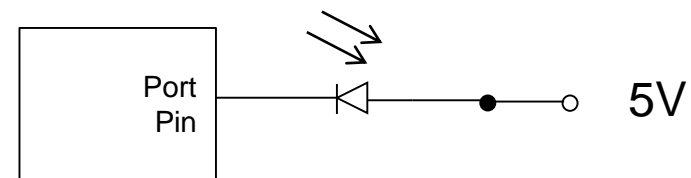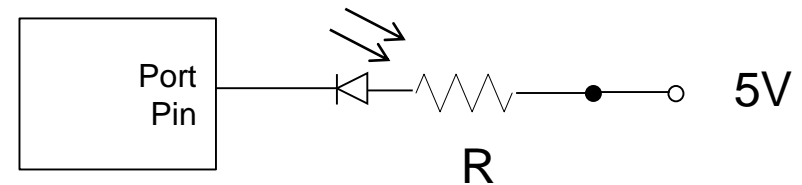


Example-I

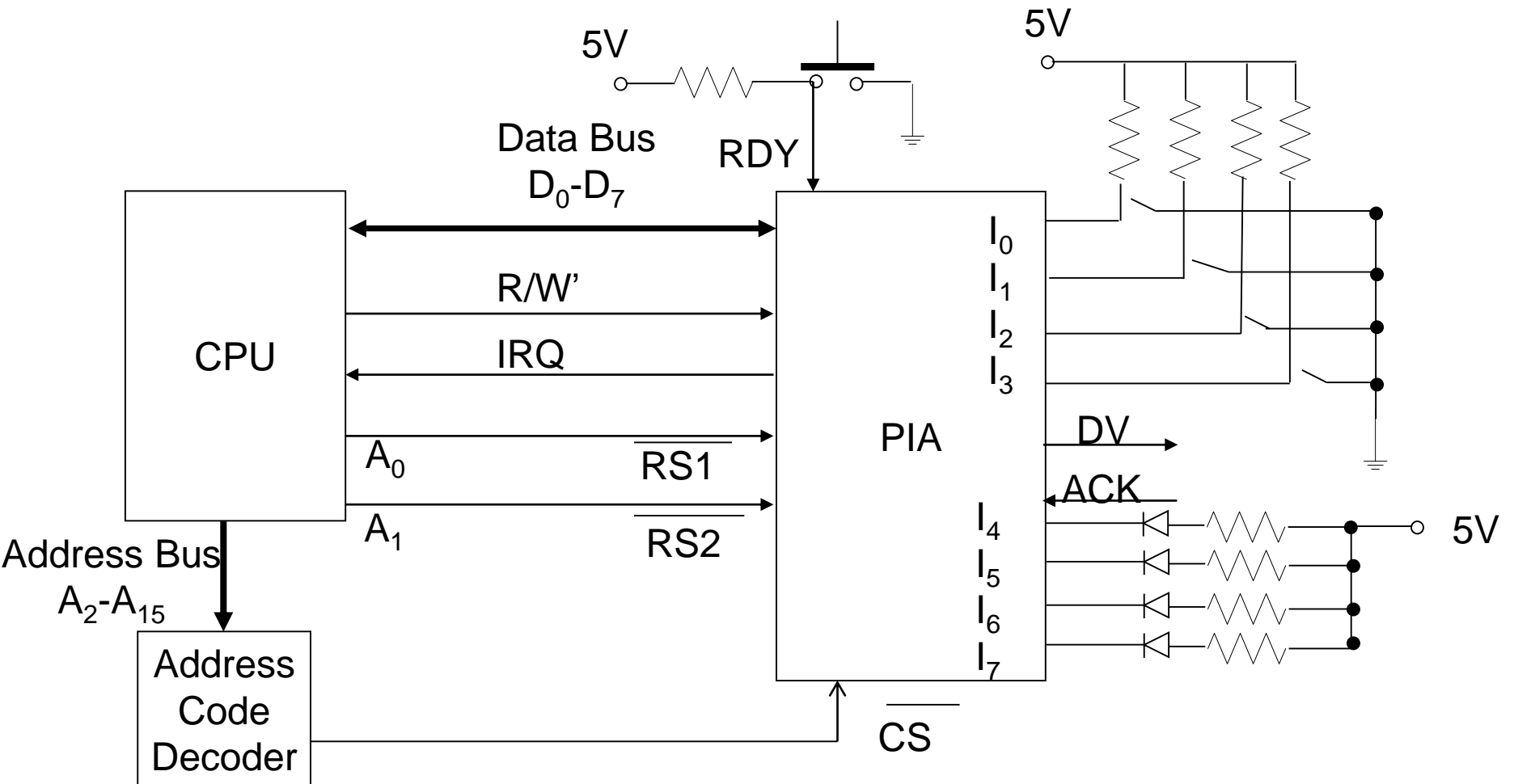

Example-I

PORT	EQ	\$A0A0
DIRECT	EQ	\$A0A1
STATCON	EQ	\$A0A2


START	LDA	A, \$F0
	STA	A, DIRECT
	LDA	A, \$00
REW	STA	A, STATCON
	LDA	A, <STATCON>
	TST	A, \$80
	BEQ	REW
	LDA	A, <PORT>

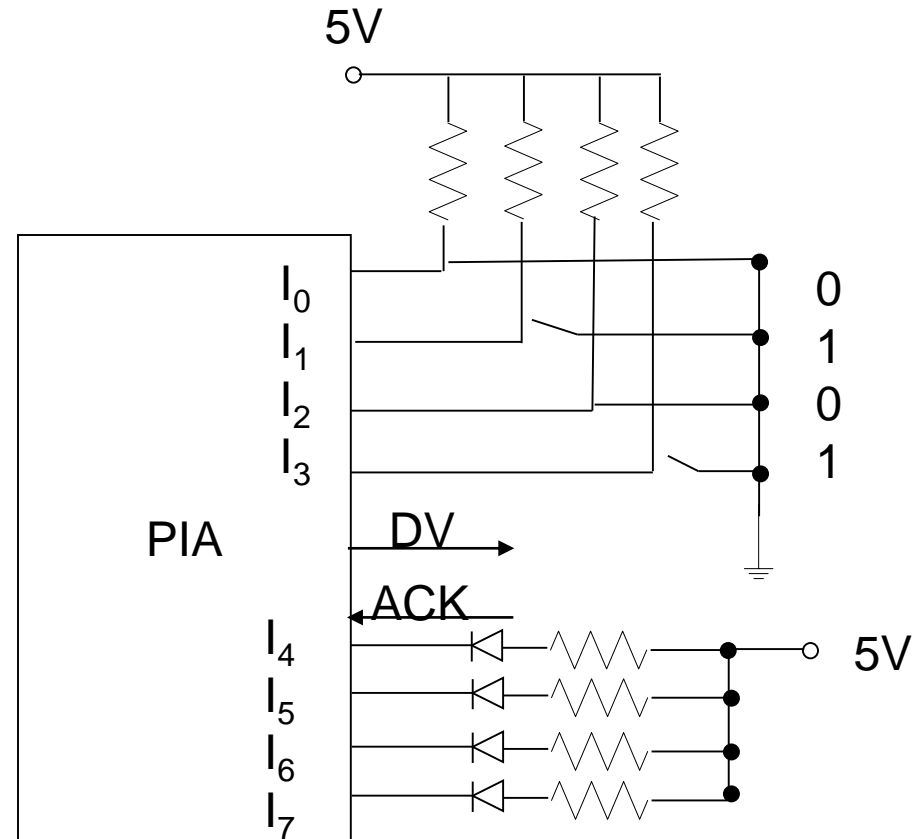

Example-I

PORT	EQ	\$A0A0
DIRECT	EQ	\$A0A1
STATCON	EQ	\$A0A2


START	LDA	A, \$F0
	STA	A, DIRECT
	LDA	A, \$00
REW	STA	A, STATCON
	LDA	A, <STATCON>
	TST	A, \$80
	BEQ	REW
	LDA	A, <PORT>
	SHL	A

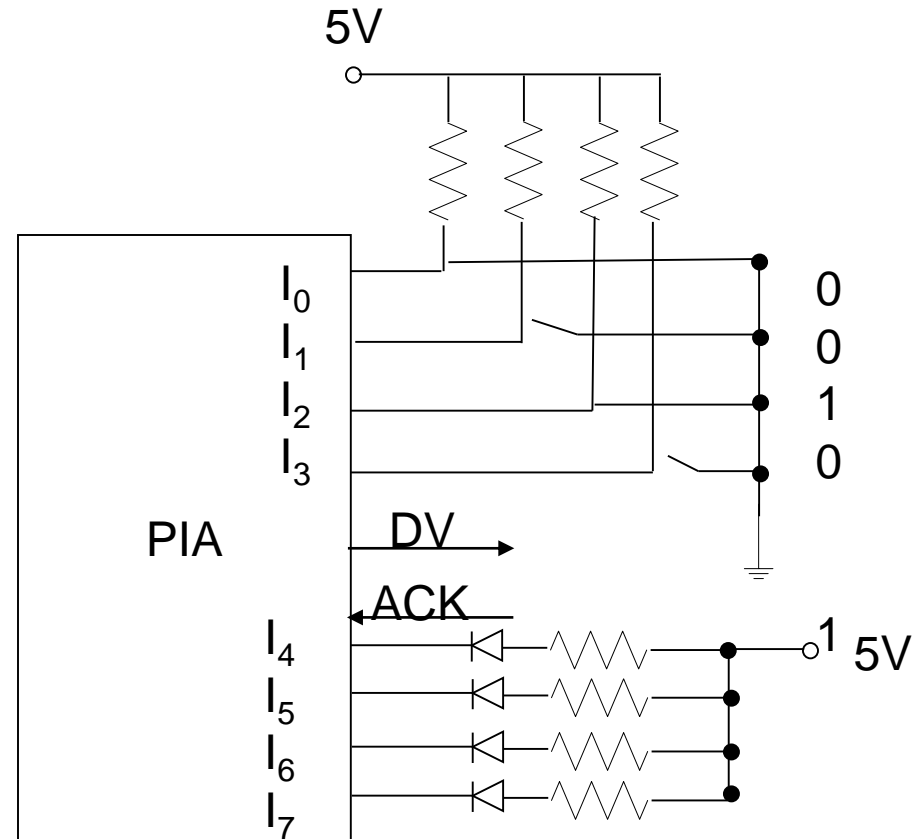

Example-I

PORT	EQ	\$A0A0
DIRECT	EQ	\$A0A1
STATCON	EQ	\$A0A2


START	LDA	A, \$F0
	STA	A, DIRECT
	LDA	A, \$00
REW	STA	A, STATCON
	LDA	A, <STATCON>
	TST	A, \$80
	BEQ	REW
	LDA	A, <PORT>
	SHL	A
	SHL	A

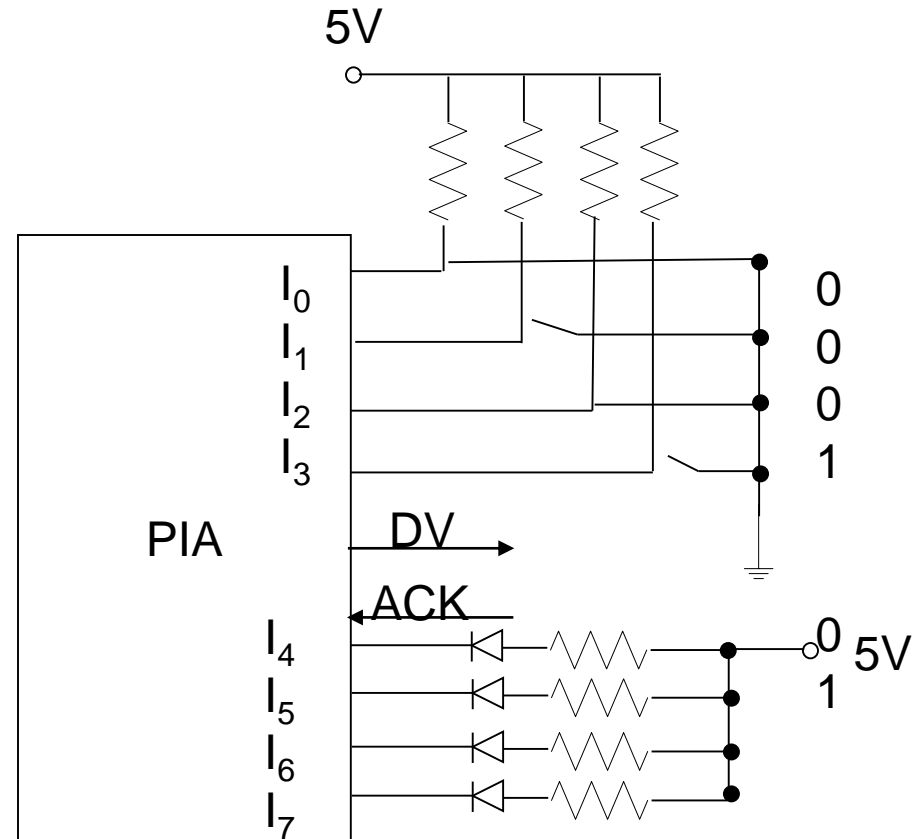

Example-I

PORT	EQ	\$A0A0
DIRECT	EQ	\$A0A1
STATCON	EQ	\$A0A2


START	LDA	A, \$F0
	STA	A, DIRECT
	LDA	A, \$00
	STA	A, STATCON
REW	LDA	A, <STATCON>
	TST	A, \$80
	BEQ	REW
	LDA	A, <PORT>
	SHL	A
	SHL	A
	SHL	A

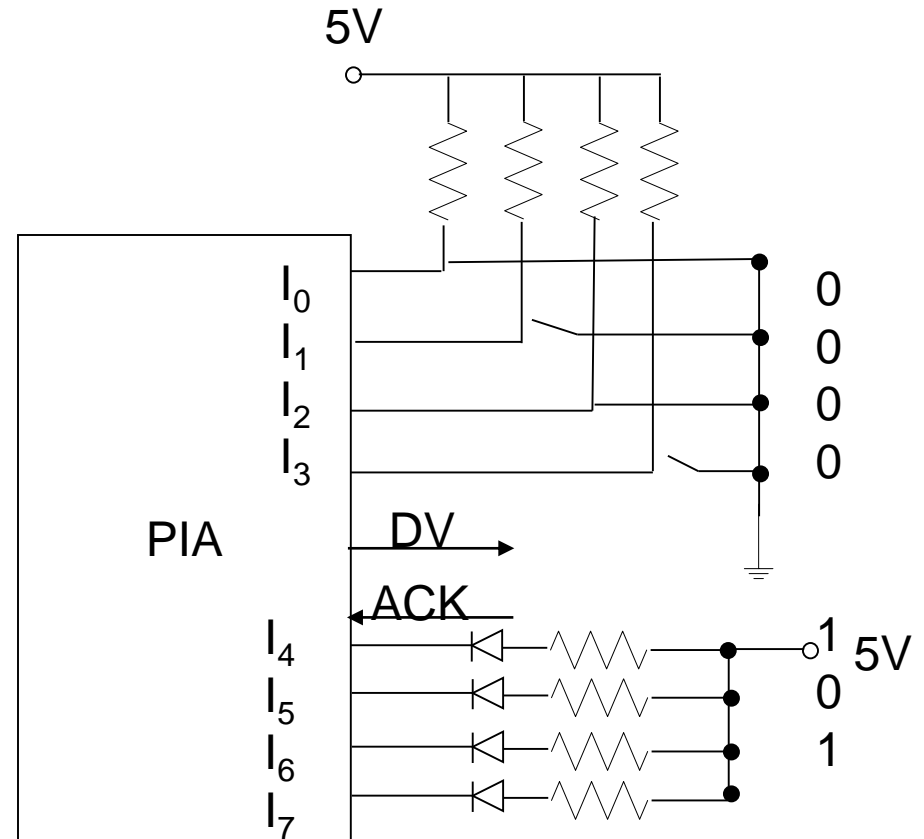

Example-I

PORT	EQ	\$A0A0
DIRECT	EQ	\$A0A1
STATCON	EQ	\$A0A2


START	LDA	A, \$F0
	STA	A, DIRECT
	LDA	A, \$00
	STA	A, STATCON
REW	LDA	A, <STATCON>
	TST	A, \$80
	BEQ	REW
	LDA	A, <PORT>
	SHL	A
	SHL	A
	SHL	A
	SHL	A

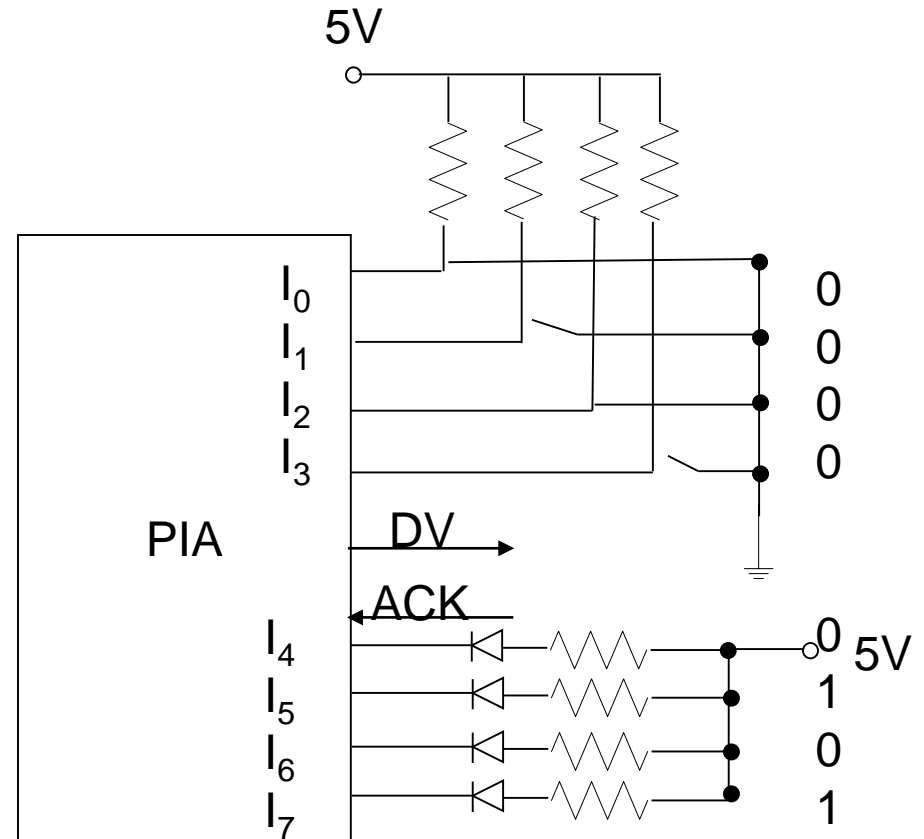

Example-I


PORT	EQ	\$A0A0
DIRECT	EQ	\$A0A1
STATCON	EQ	\$A0A2

START	LDA	A, \$F0
	STA	A, DIRECT
REW	LDA	A, \$00
	STA	A, STATCON
	LDA	A, <STATCON>
	TST	A, \$80
	BEQ	REW
	LDA	A, <PORT>
	SHL	A
	SHL	A
	SHL	A
	STA	A, <PORT>
BR	REW	

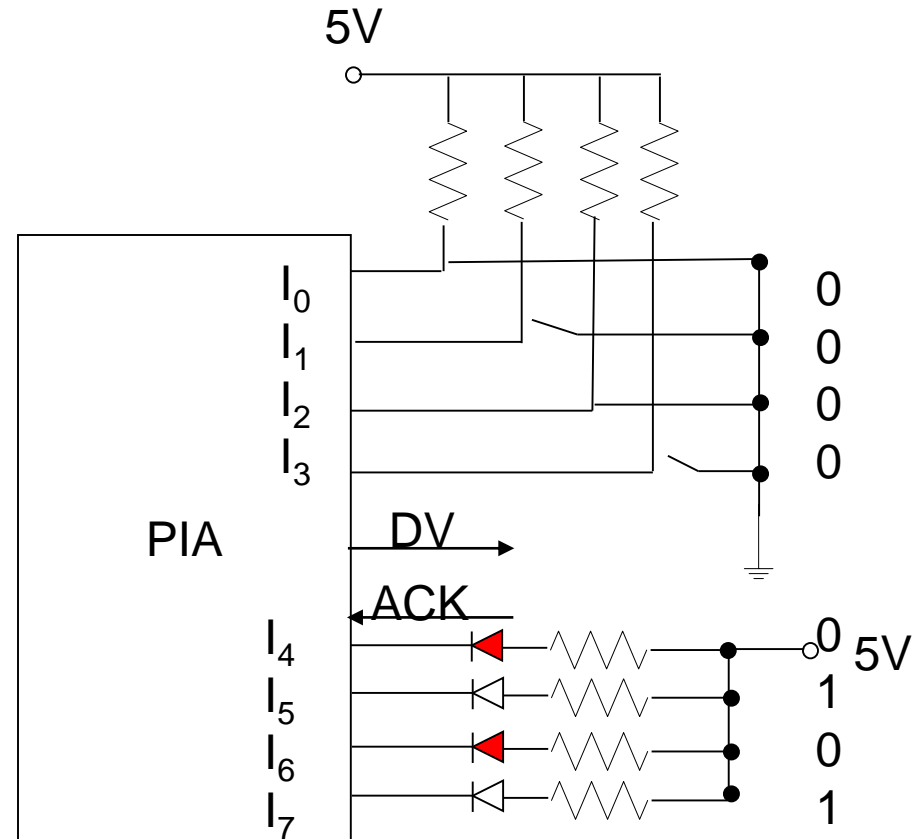

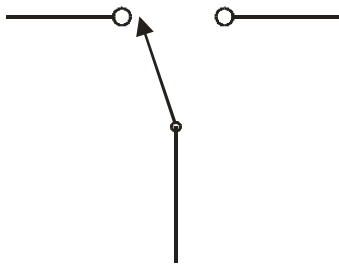
Example-II

- The first three pins (I0, I1 ve I2) of the PIA are connected to three LEDs, and the last two pins (I6, I7) are connected to a switch as shown in the figure. This switch connects either I6 or I7 to ground.



- Design and draw the hardware clearly showing PIA, switch, LEDs and resistors.
- If the switch connects I6 to ground, first the LED connected to I0 will light for 0.5 s. Afterwards the LED connected to I1 will light 0.5 s., then the LED connected to I2 will light for 0.5 s. After 0.5 s. all the LEDs will fade out. If the switch connects I7 to ground, then the same procedure will occur beginning to light the LED connected to I2. Write the program to perform this operation.

Example-II

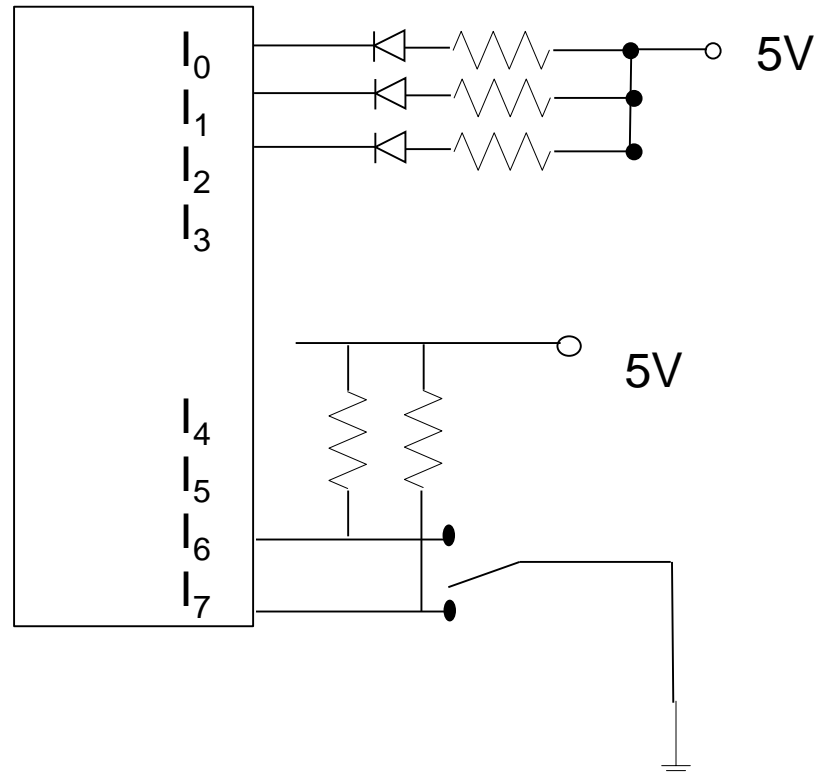



Example-II

START	LDA	SP, \$FFFF	K6	LDA	B, \$03
	BSR	COND		LDA	A, \$FE
	CLR	E	AGN2	STA	A, <PORT>
REW	LDA	A, <PORT>		BSR	DELAY
	TST	A, \$80		SHL	A
	BEQ	K7		DEC	B
	TST	A, \$40		BNEQ	AGN2
	BEQ	K6		BSR	FDO
	BR	REW		BR	REW
K7	LDA	B, \$03			
	LDA	A, \$03	COND	LDA	A, \$07
AGN1	STA	A, <PORT>		STA	A, <DIRECT>
	BSR	DELAY		LDA	A, \$00
	SHR	A		STA	A, <STAT/CON>
	DEC	B		RTS	
	BNEQ	AGN1			
	BSR	FDO	FDO	LDA	A, \$FF
	BR	REW		STA	A, <PORT>
				RTS	



Example-II

```
DELAY    LDA    IX,$F422
DELAY1   DEC     IX                (2 µs)
        BNEQ    DELAY1            (2 µs)
        LDA    IX,$F422
DELAY2   DEC     IX
        BNEQ    DELAY2
        RTS
```

$0,5s = 500.000 \mu s$

$500000 - 12 = 499.988 \mu s$

Time in one iteration: $4 \mu s$

$499.988 / 4 = 124.997$ iterations

$124.997 / 2 = 62.498$ iterations \Rightarrow \$F422



Parallel vs. Serial Connection

- Before the development of high-speed serial technologies, the choice of parallel links over serial links was driven by these factors:
 - Speed
 - Cable length
 - Complexity
- The decreasing cost of integrated circuits, combined with greater consumer demand for speed and cable length, has led to parallel communication links becoming deprecated in favor of serial links; for example, IEEE 1284 printer ports vs. USB, Parallel ATA vs. Serial ATA, and SCSI vs. FireWire.